

HOW TO REPAIR CD DISCS

APRIL 1998

Electronics NOW®

Build the Data Monitor

Gather data in the lab, on the workbench, or around the house, without tying up your computer

Experience the Fechner Phenomenon

Astound your friends and family with a workbench experiment that explores how we perceive colors



Using Technology to Fight Crime

New advances are helping law-enforcement agencies find criminals, stop terrorists, and gather evidence

Restoring a

"Reel" Recorder

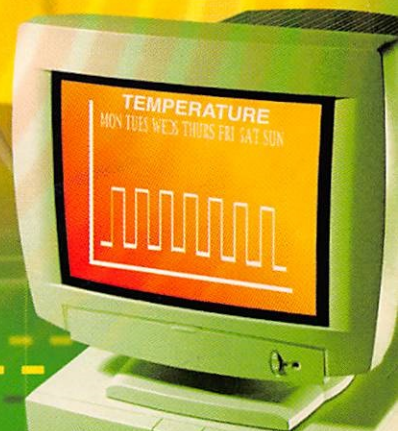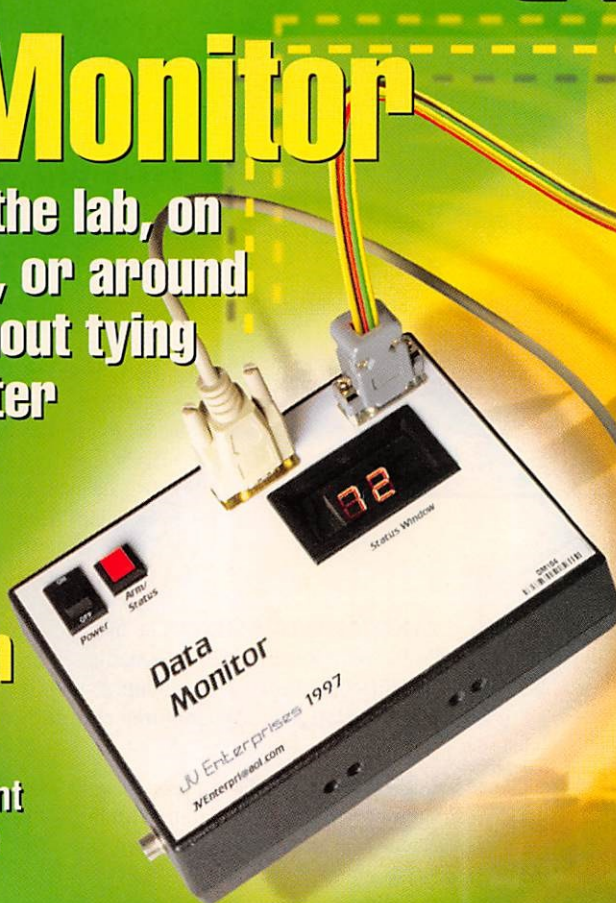Return your treasure to its original glory




A GERNSBACK
PUBLICATION

\$4.50 U.S.

\$4.99 CAN.


Professional Power

at a hobbyist price.

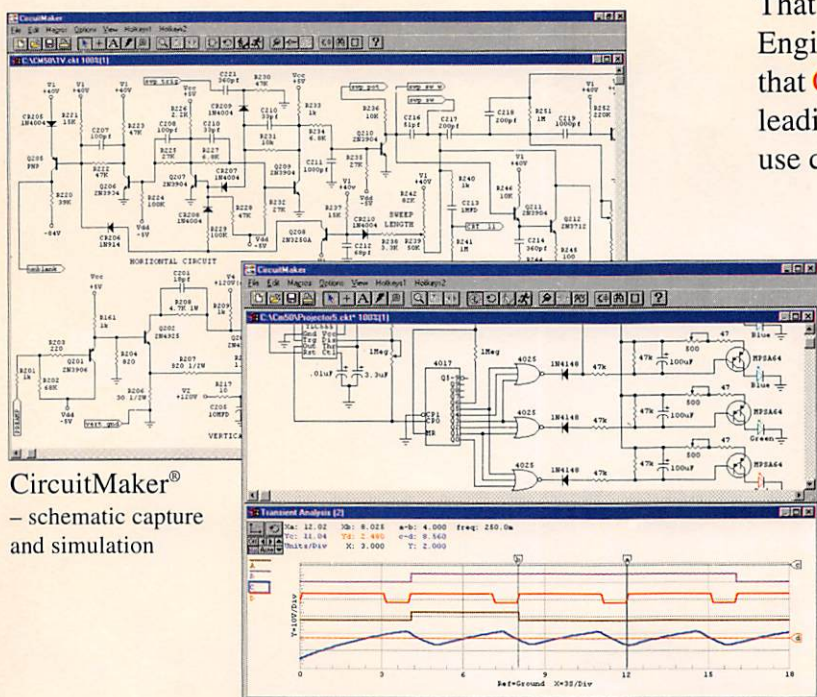

CircuitMaker®
— schematic capture
and simulation

TraxMaker® — PCB layout and autorouting

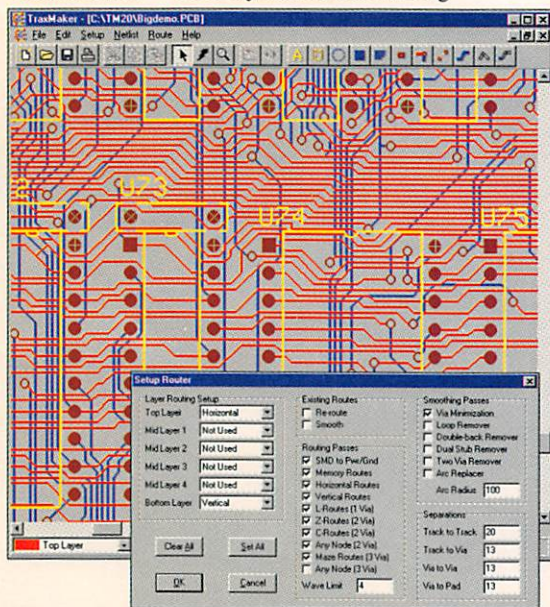

**Call 800-419-4242 for more
information and free demos**

(or download from www.microcode.com)

CIRCLE 171 ON FREE INFORMATION CARD

That has been our philosophy at MicroCode Engineering since 1987. So it's no surprise that **CircuitMaker** and **TraxMaker** are the leading software tools for affordable, easy-to-use circuit design, simulation and PCB layout.

QUICKLY DESIGN analog, digital or mixed analog/digital circuits with CircuitMaker's advanced schematic features. You fully control the wiring, device placement, annotation and colors. And the Symbol Editor and macro features let you create unlimited custom devices and symbols.

SIMULATE and ANALYZE what you create — try all the "what if" scenarios with:

- Fast, proven 32-bit SPICE 3f5/XSpice simulator
- True mixed analog/digital simulation
- Fully interactive digital logic simulation
- 4,000-device library
- AC Frequency Analysis
- DC Operating Point Analysis
- DC Transfer Function
- Transient Analysis
- Step Function — step component values and sources over a user-definable range

TAKE MEASUREMENTS at any point in the circuit with a click of the Probe tool. Results appear immediately on virtual instruments like the Digital Oscilloscope, Curve Tracer, Digital Multimeter and Bode Plotter. No other simulator lets you take measurements as quickly and easily as CircuitMaker.

COMPLETE the design process with TraxMaker, a professional printed circuit board layout program with built-in autorouter. Import netlists from CircuitMaker and other schematic programs, or design boards from scratch.

- Includes autorouter, auto component placement and Design Rules Check
- Supports up to 8 copper layers, board sizes up to 32 x 32 inches
- Surface mount and through-hole components from a customizable library
- Outputs your PCB as a Gerber file, Excellon N/C drill file, and prints to any Windows-selectable printer or plotter

RELY ON free technical support from qualified engineers. And every MicroCode product is backed by our **30-day Money-Back Guarantee** if it does not live up to your expectations.

CircuitMaker Version 5	\$299
TraxMaker Version 2	\$299
CircuitMaker Design Suite™	\$549
(CircuitMaker and TraxMaker)	

CONTENTS

APRIL 1998

ON THE COVER

33 BUILD THE DATA MONITOR

In the lab, on the workbench, or around the house, there are many instances where we need to gather information over a period of time. The traditional approach is to use a computer to first collect that information, and later to analyze it. But is it really a good idea to tie up an expensive piece of hardware like a computer for hours, days, weeks, or even longer? Of course not, and thanks to the Data Monitor there is now a better, lower-cost way to perform the information-gathering part of the task. What's more, through the use of simple plug-in modules, it can be configured to handle virtually any data-collecting application.

— Jon Varteresian




TECHNOLOGY

13 PROTOTYPE

Using technology to fight crime and terrorism, a camera on a chip, geothermal heating, and more.



49 EXPERIENCE THE FECHNER PHENOMENON

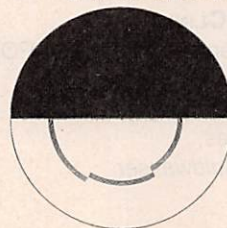

Astound your friends and family when you conduct this simple workbench experiment that explores


how we perceive colors.

— Dave Sweeney

52 RESTORING A "REEL" RECORDER

This month we show you how to return your treasure to its original glory

— Phil Van Praag

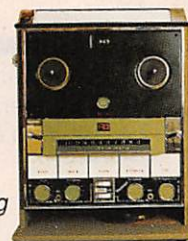

As a service to readers, ELECTRONICS NOW publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, ELECTRONICS NOW disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

Since some of the equipment and circuitry in ELECTRONICS NOW may relate to or be covered by U.S. patents, ELECTRONICS NOW disclaims any liability for the infringement of such patents by the making, using, or selling of any such equipment or circuitry, and suggests that anyone interested in such projects consult a patent attorney.

ELECTRONICS NOW, (ISSN 1067-9294) April 1998. Published monthly by Gernsback Publications, Inc., 500 Bi-County Boulevard, Farmingdale, NY 11735-3931. Periodicals Postage paid at Farmingdale, NY and additional mailing offices. Canada Post IPM Agreement No. 334103, authorized at Mississauga, Canada. One-year subscription rate U.S.A. and possessions \$19.97. Canada \$27.79 (includes G.S.T. Canadian Goods and Services Tax, Registration No. R125166280), all other countries \$28.97. All subscription orders payable in U.S.A. funds only, via international postal money order or check drawn on a U.S.A. bank. Single copies \$4.50. © 1998 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.


POSTMASTER: Please send address changes to ELECTRONICS NOW, Subscription Dept., Box 55115, Boulder, CO 80328-5115.

A stamped self-address envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

BUILD THIS

44 BUILD THIS PERSONALITY MODULE FOR YOUR DATA MONITOR

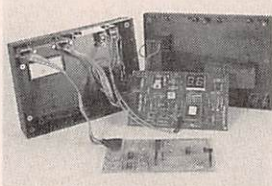
Put your Data Monitor to work with this general-purpose I/O module that can accept both analog and digital data, and includes a temperature sensor. — *Jon Varteresian*



DEPARTMENTS

12 EQUIPMENT REPORT

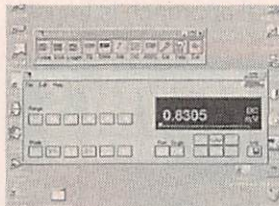
National Instruments virtual digital multimeter.



17 SERVICE CLINIC

How to "repair" CD and CD-ROM discs, and an introduction to repairing CD players and CD-ROM drives.

— *Sam Goldwasser*

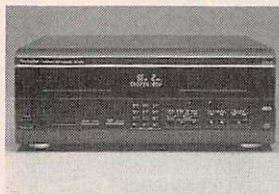


22 COMPUTER CONNECTIONS

Stayin' Alive: The great Pilot Plot. — *Jeff Holtzman*

66 TECH MUSINGS

All about quadrature, a new scanner, and more.

— *Don Lancaster*

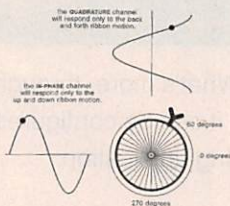

AND MORE

4 EDITORIAL

5 LETTERS

6 Q&A

24 NEW PRODUCTS

28 NEW LITERATURE

106 ADVERTISING INDEX

106 ADVERTISING SALES OFFICE

Electronics NOW®

Hugo Gernsback (1884-1967) founder

LARRY STECKLER, EHF, CET,
Editor-in-chief and publisher

ADRIA COREN, Vice-President

KEN COREN, Vice-President

EDITORIAL DEPARTMENT

CARL LARON, editor

JOSEPH J. SUDA, technical editor

JULIAN S. MARTIN, associate editor

EVELYN ROSE, assistant editor

TERI SCADUTO, assistant editor

MICHAEL A. COVINGTON, N4TMI

contributing editor

SAM GOLDWASSER, service editor

JEFFREY K. HOLTZMAN,

computer editor

FRANKLIN J. MILLER,

audio editor

DON LANCASTER,

contributing editor

DEBBIE CYBULA, editorial assistant

ART DEPARTMENT

ANDRE DUZANT, art director

RUSSELL C. TRUELSON, illustrator

PRODUCTION DEPARTMENT

RUBY M. YEE, production director

KATHRYN R. CAMPBELL,

production assistant

KEN COREN,

desktop production director

LISA BAYNON, desktop production

MELISSA GIORDANO, desktop production

CIRCULATION DEPARTMENT

THERESA LOMBARDO,

circulation manager

GINA GALLO,

circulation assistant

REPRINT DEPARTMENT

CHRISTINA M. ESTRADA, reprint bookstore

Typography by Mates Graphics

Electronics Now is indexed in *Applied Science & Technology Index*, and *Readers Guide to Periodical Literature*, *Academic Abstracts*, and *Magazine Article Summaries*.

Microfilm & Microfiche editions are available. Contact reprint bookstore for details.

Advertising Sales Offices listed on page 106.

Electronics Now Executive and Administrative Offices
1-516-293-3000.

Subscriber Customer Service:
1-800-999-7139.

7:00 AM-6:00 PM Monday-Friday MST

VISIT US ON THE INTERNET AT:
www.gernsback.com



Audit Bureau
of Circulations
Member

JAMECO's 25th Year of Serving You

Special Prices for Electronics Now Readers. Please mention VIP #4R8!

JAMECO 75MHz Barebones Pentium® System



Monitor, video card and hard drive not included

- 16MB of RAM upgradeable to 128MB
- 256KB cache RAM, upgradeable to 512KB
- Hard disk and floppy I/O controller card
- Four exposed bays (two 5.25", two 3.5"); one internal 3.5" bay
- Includes keyboard, mouse and cables
- 3.5" floppy drive
- Four PCI slots and three ISA slots

Part No.	Description	Price
146499	75MHz Pentium® Sys. Special	\$299.95

Embedded CPU Card for Intel Pentium® Processor



Industry wide compatibility.

- Microprocessor: Intel Pentium® 75/90/100/133/166MHz—not included
- System memory: 8-128MB
- Cache size: pipelined burst sync/asynch cache module slot, up to 512KB
- 128KB Award licensed BIOS
- Two serial ports, one multi-mode parallel
- Two PCI IDE ports, up to 4 IDE drives
- Watchdog timer: 0.5/1/2/4 sec time-out period selectable

Part No.	Description	Price
149286	Pentium® embedded MB	\$329.95

PCI I/O Cards

- PCI bus
- PnP ready
- Software support for DOS, Windows® 95, NT 4.0
- One-year warranty



Part No.	Description	Price
146675	1 parallel, 2 serial ports	\$139.95
146659	1 serial port	99.95
146667	2 serial ports	129.95
146691	1 parallel port	99.95
146683	2 parallel ports	129.95

Component Cabinet Kits

Kits include the most popular components with extra space for your customized expansion. Each kit includes a 20 drawer component cabinet.



More kits available - call for details!

Part No.	Description	Price
84953	330 pc. 7400 series IC kit	\$159.95
84961	420 pc. 74LS series IC kit	119.95
84970	300 pc. CD4000 series IC kit	84.95
84988	385 pc. Linear series IC kit	159.95
108329	540 pc. 1/8 watt Resistor kit	29.95
81832	540 pc. 1/4 watt Resistor kit	28.95
107879	540 pc. 1/2 watt Resistor kit	32.95
108433	2200 pc. Electr. Hardware kit	39.95
81867	110 pc. Radial Capacitor kit	34.95
81859	320 pc. Ceramic Capacitor kit	29.95
81883	160 pc. Mylar Capacitor kit	34.95
81841	129 pc. Tantalum Capac. kit	49.95
82587	270 pc. Diode kit	39.95
82595	180 pc. Transistor kit	49.95

METEX 3 1/2-Digit Digital Multimeter

- 3 1/2-digit LCD (5" high digits)
- AC voltage: 200mV, 2V, 20V, 200V, 700V
- DC voltage: 200mV, 2V, 20V, 200V, 1000V
- AC & DC current: 20µA, 200µA, 2mA, 20mA, 200mA, 2A, 20A
- Resistance: 200Ω, 2KΩ, 20KΩ, 200KΩ, 2MΩ, 20MΩ
- Input impedance: 10MΩ
- Auto zeroing • One-year warranty



Part No.	Product No.	1-4	5-9
27115	M3800	\$39.95	\$35.95


Muscle Wires Project Book & Deluxe Kit

Get the facts behind the unusual properties of Muscle Wires. Study their uses in heat engines, industrial, medical and aerospace applications, electronic and mechanical devices, prosthetic limbs, robotics, virtual reality systems, and more!



Part No.	Description	1-4	5-9
141348	Muscle Wires kit	\$59.95	\$53.95

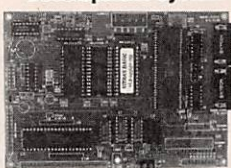VITRAX Programmable Controller Control, Measurement, Data Collection Self-Contained Development System



Kit or Fully Assembled

- 24 digital I/O lines
- Two serial channels to 19.2K baud: DE9 interface
- Four external interrupts for instant response
- 8KB RAM (expand to 32KB)
- 16KB EPROM space for application code
- Built-in EPROM programmer
- Optimized BASIC language in ROM—fast!
- -80 commands
- -sup. float point, strings, integers, arrays
- -interrupt service commands
- -serial channel data manager and buffer
- Power: 5VDC regulated; 250mA
- Size: 4.5" L x 6.5" W • One-year warranty

Part No.	Description	Price
148700	VITRAX controller kit	\$129.95
148697	VITRAX - assembled	159.95
148734	A/D converter module, 10-bit, 8-ch	39.95
148726	RealTime calendar clock module	39.95
148718	LCD interface port: 2 x 7 pin mod.	19.95
134658	Novation power supply	6.95

JAMECO ELECTRONIC COMPONENTS COMPUTER PRODUCTS

© 1998 Jameco 4/98
Order Toll Free 24-Hours 7-Days a Week!



Call 1-800-831-4242 day or night!

mission technology PC-Multiscope 2

- 20MHz sampling rate; 10MHz analog bandwidth; built in external trigger
- 1mV/div to 10V/div; built in adjustable DC power supply output
- Frequency analyzer (FFT) and transient signal modes



Part No.	Description	Price
142834	PC-Multiscope 2	\$399.95

Hand-held EPROM Programmer/Emulator

- 512Kbits of RAM
- Supports EPROMs, EEPROMs and Flash memories up to 8Mbits
- Self-powered and completely portable - ideal for field service work
- Maximum pins: 32



Part No.	Description	Price
124003	EPROM programmer	\$749.95

AXIOM 48-Bit Digital I/O Card

- Low cost IBM PC/XT/AT compatible DVO card
- 48 TTL/DTL compatible digital I/O lines arranged into 8-bit ports
- Software programmable for inputs/outputs
- Emulates 8255 PPI mode 0



Part No.	Description	Price
136784	48-bit digital I/O card	\$99.95

PARALLAX Basic Stamps



- Basic Stamps are small computers using a variation of Basic, called PBASIC to control execution of many applications. The BS1-IC has 8 I/O lines, while the BS2-IC has 16 I/O lines which can be connected directly to buttons, LEDs, registers, and many other TTL level devices.
- One-year warranty

Part No.	Description	Price
127693	Basic stamp BS1-IC	\$34.95
130892	Basic stamp BS2-IC	49.95

Easy Photo Reader Scanner

- 133 dpi color optical resolution
- Up to 1200 dpi color enhanced resolution
- 24-bit true color
- TWAIN compliant
- Single pass scanning
- Photo reader with feeder 5.5" x 6" x 3", feeds up to a 5" x 7" photo
- Easily plugs into a parallel port



Part No.	Description	Price
147264	Photo scanner	Special \$69.95

Call for your FREE catalog!

1355 Shoreway Road
Belmont, CA 94002-4100
FAX: 1-800-237-6948 (Domestic)
FAX: 650-592-2503 (International)
E-mail: info@jameco.com
http://www.jameco.com



Mention V.I.P. # 4R8

Hyper Peppy Robot Kit

- Changes course when it comes in contact with an object or hears a loud sound



Part No.	Description	Price
140863	Robot kit	Special \$19.95

Jameco Solderless Breadboards

- Low static plastic body - CMOS safe
- Nickel plated clips designed to withstand up to 5,000 insertion cycles



Part Number	Contact Points	Size L x W	1-9	10-49
94457	100	6.5 x 0.4	\$2.49	\$2.25
20600	400	3.5 x 2.1	4.95	4.49
136901	1,600	5.5 x 2.3	Sale 19.95	
20669	630	6.5 x 1.4	5.49	4.95
20722	830	6.5 x 2.1	7.95	6.95
20757	1,360	6.5 x 3.1	11.95	10.95
20773	1,660	6.5 x 4.3	17.95	15.95
20790	2,390	6.9 x 5.8	22.95	20.49
20811	3,220	7.3 x 7.5	30.95	27.95

EDWin NC (CAD/CAE) Software

The first truly seamlessly integrated suite of software running in all Windows® formats... simulation, schematics, and PCB design. Large start-up libraries.



Part No.	Description	1-4	5-9
141680	EDWin NC	\$149.95	\$134.95

Weller 40-Watt Electronic Soldering Station

- 40 watts, 120V @ 60Hz
- Lighted on/off switch
- Adjustable power from 5 watts - 40 watts
- Temperature is electronically controlled from 350°F to 850°F • UL listed
- Includes ST3 1/8" screwdriver tip, soldering station, soldering handle and manual



Part No.	Description	Price
146595	40 watt soldering station	\$44.95

BUKIN Power Authority II

- Master power switch and 5 auxiliary switch for each outlet
- Heavy duty 8' cord with 3 line AC protection
- Ground indicator • EMI/RFI filtering
- Static discharge plate (will eliminate static charge once touched)
- UL approved telephone line protection
- Maximum spike current @ 96,000 amps
- UL1499 clamping voltage: 330 volts
- \$15,000 connected equipment manufacturer's warranty



Part No.	Description	Price
147011	Power base	Special \$24.95

SHARP Camera Board

- EIA system 512(H) x 492(V)
- Composite output - 380 lines resolution
- 1/50 to 1/1000 sec. shutter speed
- 2.1mm female center positive



Part No.	Description	1-4	5-9
127263	Camera board	\$129.95	\$116.95

Accredited B.S. Degree in Computers or Electronics

by studying at Home

Grantham College of Engineering
offers 3 distance education programs:

- B.S.E.T. emphasis in Electronics
- B.S.E.T. emphasis in Computers
- B.S. in Computer Science

NEW Electronics Workbench Professional 5.0
included in our B.S.E.T. curriculums
-Approved by more than 200 Companies,
VA and Dantes, (tuition assistance avail.)

For your free catalog of our programs dial

1-800-955-2527

<http://www.grantham.edu>

GCE


Your first step
to help yourself
better your future!



Grantham College of Engineering
34641 Grantham College Road
Slidell, LA 70460-6815

ANTIQUE RADIO CLASSIFIED Free Sample!

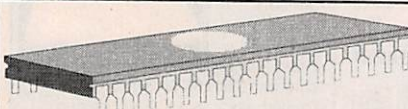Antique Radio's
Largest Circulation Monthly.
Articles, Ads & Classifieds.
6-Month Trial: \$19.95. 1-Yr: \$38.95 (\$55.95-1st Class).
A.R.C., P.O. Box 802-L19, Carlisle, MA 01741
Phone: (508) 371-0512 VISA/MC Fax: (508) 371-7129



CABLE CONVERTER DIAGNOSTIC TEST CHIP

LOAD FULL ACTIVATION OF CABLE CONVERTER

WE STOCK A COMPLETE LINE OF CHIPS, TOOLS,
WIRELESS QUICK INSTALL TEST BOARDS AND
DIAGNOSTIC CUBES FOR ALL CONVERTERS!

ANYONE IMPLYING ILLEGAL USE WILL BE

DENIED SALE. WE SELL PRODUCTS ONLY!! TO
TECHNICIANS OR CABLE REPAIR FACILITIES!!

#1 IN CUSTOMER SERVICE & TECH. SUPPORT!

*ALL ORDERS SHIP WITHIN 24HRS, UPS/ FED-X.

*PRIORITY NEXT DAY SHIPPING AVAILABLE!

*SALE= BUY 5 TEST BOARDS AND GET 1 FREE.

*MON-FRI - 8AM-7PM - SAT 10AM-2PM EST.

*WEB PAGE [HTTP://WWW.800-GO-CABLE.COM](http://WWW.800-GO-CABLE.COM)

VISA MasterCard

VISUAL

COMMUNICATIONS INC.

ORDERS/CATALOG 1-800-GO-CABLE

TOLL FREE TECH. DEPT. 1-888-519-TECH EST. 1976

EDITORIAL

Alphabet Soup

Last time we met, I spoke about the confusion the impending switch from NTSC TV broadcasting to digital TV (DTV) was causing broadcasters and manufacturers. Well, if these industry insiders are confused, how are ordinary consumers, even technically savvy ones, supposed to make sense out of the alphabet soup and multiple standards that the change is engendering?

Recognizing that, CEMA (the Consumer Electronics Manufacturers Association) announced at the just-concluded Winter Consumer Electronics Show (look for more coverage of that show in our next issue) an industry-standard set of definitions, and a logo that manufacturers can use to certify that a TV set or other device is capable of receiving and displaying all of the ATSC (Advanced Television Systems Committee) video formats. Here are the definitions:



Digital Television (DTV)—DTV is the umbrella term used to describe the new digital-television system adopted by the FCC in December 1996.

High-Definition Television (HDTV)—HDTV refers to a complete system or product with the following performance attributes:

- Resolution: A vertical display resolution of 720P (720 lines, progressive scan), 1080I (1080 lines, interlaced scan), or higher.
- Aspect Ratio: Capable of displaying a 16:9 image at the minimum resolution level.
- Audio: Receives, reproduces, and/or outputs Dolby digital audio.
- Receiver: Receives all ATSC Table-3 (digital) formats.

Standard-Definition Television (SDTV)—SDTV refers to a complete system or product with the following performance attributes:

- Resolution: A vertical display resolution lower than that of HDTV.
- Aspect Ratio: None specified.
- Audio: Produces useable audio.
- Receiver: Receives all ATSC Table-3 formats and produces a useable picture.

The road to digital TV has lots of bumps, twists, and turns. These standardized definitions and the certification program will certainly help make the trip over it at least a little smoother. But there is still so much more that needs to be done to minimize what's sure to be a period of great confusion among consumers.

Carl Laron

Carl Laron
Editor



LETTERS

SEND YOUR COMMENTS TO THE EDITORS OF ELECTRONICS NOW MAGAZINE

Seeing Red Over "Green" Cars

I read with interest your article, "Neighborhood Electric Vehicles" (*Electronics Now*, January 1998). It was well researched as far as the different options for locally operated vehicles are concerned, but I have a problem with the term "Zero Emission." The more accurate term would be "Transferred Emission." The Laws of Thermodynamics do not allow "something for nothing" as we all know; however, as long as we cling to the fallacy that these vehicles do not produce any emission, this problem will only get bigger.

As far as electrical vehicles are concerned, they rank as some of the most energy-wasting devices in use. The con-

version of heat into electricity, at best, is 50% efficient at the plant. Assuming another 50% loss in transmission (some say 75%), this leaves only 25 units of energy out of 100 delivered to the charger. Given that at least 10–20% of the charger's energy is converted into heat

and other losses for the high-current charging, that reduces the amount of delivered power to the battery at 20–22.5 units. Battery technology is such that, at best, brand new cells only deliver 40% of the energy put in. That leaves us with only 8–9 units actually delivered. This is a whopping 8–9% efficiency. Electric vehicles do get some of this back by dynamic braking, but the returns are minuscule.

The implications are that until there is a significant change in the technology, the conversion to electric cars will cause more pollution—not less. It will only change *where* the pollution is generated.

Also the introduction of a charger in every home will boost demand for elec-

(Continued on page 26)

Write To:


Letters,
Electronics Now Magazine,
500 Bi-County Blvd.,
Farmingdale, NY 11735

Due to the volume of mail we receive, not all letters can be answered personally. All letters are subject to editing for clarity and length.

ProtoLab 4.0

Easy-to-use circuit simulation package from the leader in electronic prototyping.

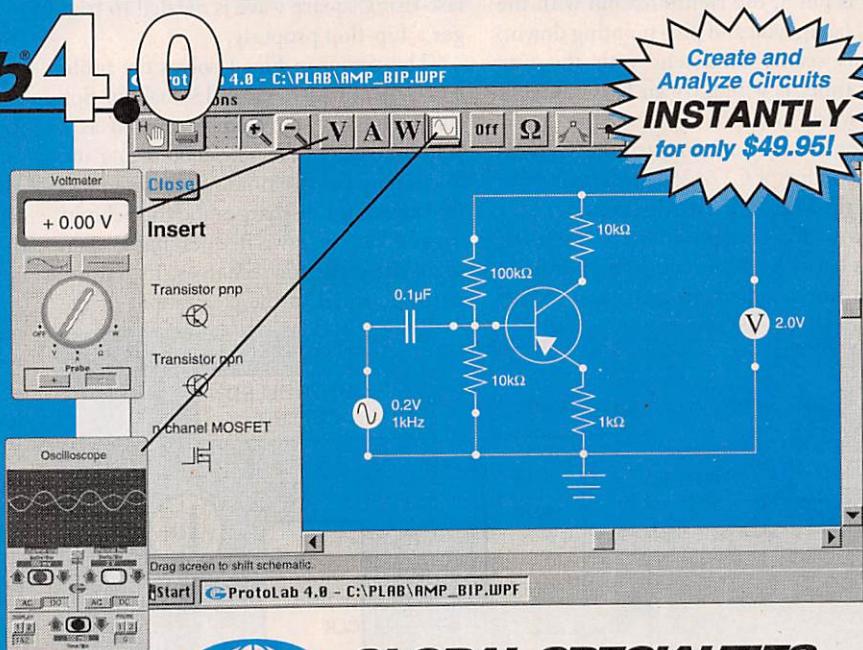- Designed for use with Windows® 95
- Low Cost - \$49.95
- Design circuits instantly while choosing from a complete list of active and passive components
- Analyze circuits using built-in test instruments.



Create and Analyze Circuits
INSTANTLY
for only \$49.95!



GLOBAL SPECIALTIES
SOFTWARE

INNOVATIVE PRODUCTS. UNSURPASSED QUALITY.
1-800-572-1028 • For a demonstration, visit:
www.globalspecialties.com

Windows® 95 is a U.S. registered trademark of Microsoft Corporation.



Q & A

READERS' QUESTIONS, EDITORS' ANSWERS

Push On, Push Off

Q I'm building a project that requires power to toggle on and off with one pushbutton, like the on-off button of a pocket calculator. Is there a simple circuit that will do this without relays, using a 6-volt battery?

Also, is there a single CMOS static-memory chip with 32K capacity in an SMT package? Last, I'm unable to locate a replacement part with imprints "Q576," "MEX," "H3," in a TO-220 case. I think it's a Triac. The tab is electrically isolated from all three pins. This is for a programmable digital timer I purchased from Canadian Tire.—
M. K., Willowdale, Ont., Canada

A Taking your questions in reverse order, the ECG 5638 is a 400-volt, 8-ampere Triac with the tab isolated from all of the pins; it may fill the bill. (The gate is pin 3, the rightmost pin with the label facing you and pins pointing down.) If this seems consistent with the way your timer is wired, try an ECG 5638; it may work.

For a static memory, try the Cypress Semiconductor CY62256; documentation is on the Web at www.cypress.com.

Now for the pushbutton question. Calculators and electronic toys usually use a microcontroller that has a "sleep

mode" in which it consumes very little power but can be awakened by a single pulse. Since your project apparently involves a microprocessor, you might go at it from that angle.

Otherwise, don't overlook the advantages of using a mechanical toggle switch; there are "push-on, push-off" switches that require no special circuitry.

But if you're stuck with a single SPST pushbutton, returned to ground, you can still use it as an on-off power control as shown in Fig. 1. Obviously, the switch operates a flip-flop. The catch is that before entering the flip-flop, the signal from the switch has to be debounced and then converted into a clean squarewave with a fast rise time. Debouncing is necessary because when you press a button, the switch "bounces" open and closed for a few milliseconds; a fast-rising square wave is needed to trigger a flip-flop properly.

The circuit in Fig. 1 solves the problem elegantly with one 4013 dual flip-flop chip. The first flip-flop is rewired as a Schmitt trigger to handle debouncing and to clean up the rise time. When you press the button, C1 discharges and the Schmitt trigger latches low; it goes high again when the capacitor recharges. Its output, at pin 2, is fed to the clock input of the

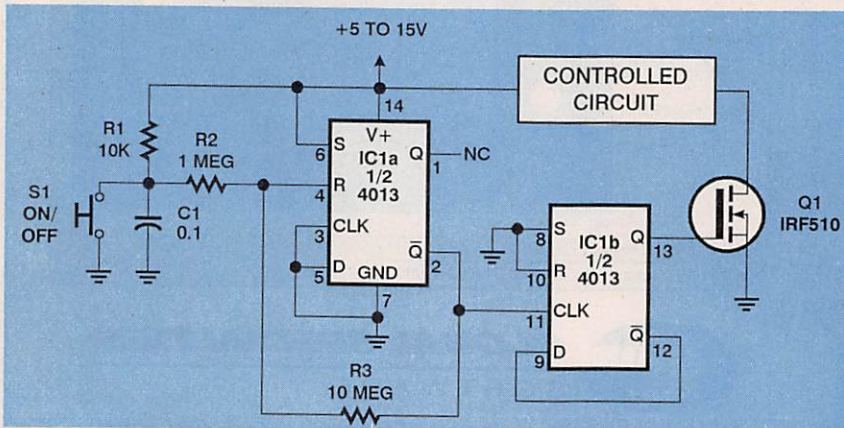


FIG. 1—A PUSH-ON, PUSH-OFF CIRCUIT. The first flip-flop is wired as a Schmitt trigger to debounce the signal from the button (S1); the second flip-flop receives a clean signal and toggles when the button is pushed.

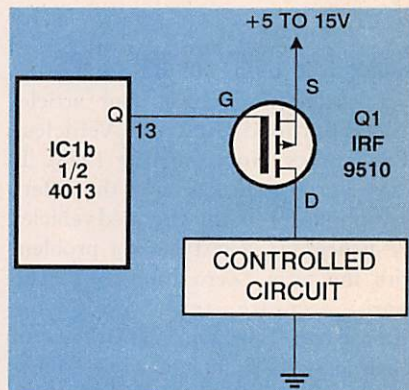


FIG. 2—IF THE CONTROLLED CIRCUIT and the controller must share the same ground, use "high-side switching" and a P-channel MOSFET.

second flip-flop, whose outputs swap states every time the button is pressed. The flip-flop operates an IRF510 switching MOSFET. Because the circuit is all MOS, it consumes less than 5 microamperes in the "off" state.

If the controlled circuit has to share its ground (negative) supply line with the controller, you can use a P-channel MOSFET as shown in Fig. 2. This is called "high-side switching." Note that the MOSFET is wired upside down (source positive, drain negative).

A disadvantage of this circuit is that you can't predict the state of the flip-flop when power is first applied. That is, when you first connect the battery, the device may be either on or off. At worst, you'll have to press the button once after installing the batteries.

Tektronix Oracle

Q In your December issue, a reader requested a manual for a Telequipment D53A oscilloscope. I've written to him and now I'll tell you what I have available. I supply manuals for all Tektronix and Telequipment products from 1945 to 1990, as well as for many older test instruments made by HP, Fluke, General Radio, DuMont, Hickock,

Ballantine, and others. I prefer to supply manuals to the owners of the equipment for their own use.

I worked for Tek for 41 years and collected manuals and parts, which were available through their company store. Now I spend hours on the phone helping people who come to me.—Deane Kidd, W7TYR, 27270 S.W. Ladd Hill Road, Sherwood, OR 97140.

A Thanks, Mr. Kidd. That reader (and his Tek 575 curve tracer) can personally attest to your helpfulness. Vintage Tektronix oscilloscopes are widely available at hamfests and are becoming collectors' items. Like Leica cameras or Zeiss microscopes, they're highly repairable, extraordinarily well-built, and capable of outstanding performance. If you can get tubes, they seem to last forever. Tektronix aficionados should also consult the book *Oscilloscopes: Selecting and Restoring a Classic* (which covers only Tek products), written and published by Stan Griffiths, W7NI, 18955 S.W. Blanton St., Aloha, OR 97007

Invisible Motorcycle?

Q As a motorcycle rider, I find myself invisible to many car drivers. The requirement for keeping headlights on during the day was supposed to make us more conspicuous, but now many cars also drive with their headlights on and motorcycles no longer stand out.

There is a headlight modulator legal in all 50 states that solves this problem; could you tell me how to build one? The requirement is to modulate the high beam (12–14 volts, 55 watts) 240 times a minute between full and 20% power.—R. A. H., Eugene, OR

A We'll have to take your word about the official specifications, but the circuit in Fig. 3 will probably do what you need. As Fig. 4 shows, it varies the brightness of the headlight by varying the duty cycle of a squarewave. That is, instead of consuming energy in a resistor, it switches the power on and off very fast. Since the power is always either on or off, little or no electricity is wasted, and because the switching rate is so high (5 kHz), the light-bulb filament remains at a constant temperature and doesn't suffer any extra wear.

You may have to experiment with component values to get the performance you need. Resistor R3 determines the brightness of the "dim" state; if you use a

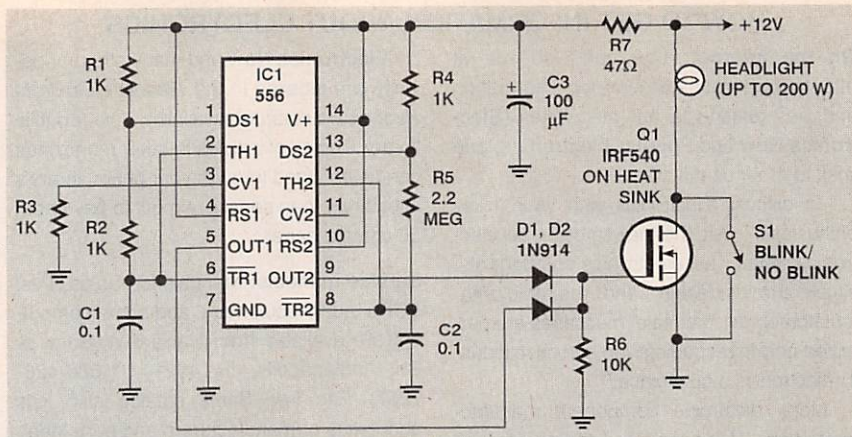


FIG. 3—THIS MODULATOR CIRCUIT makes a motorcycle headlight alternate between full and 20% power at a rate of four times a second.

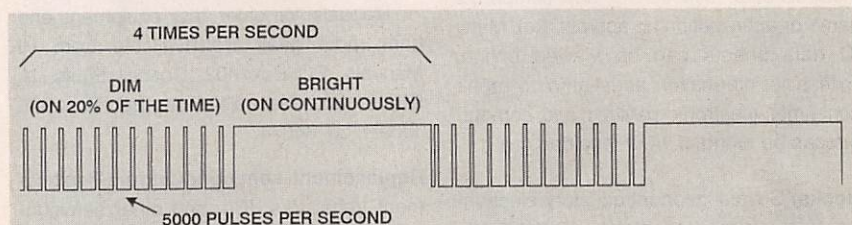


FIG. 4—THE MODULATOR IN FIG. 3 VARIES the brightness of the bulb by changing the duty cycle of a squarewave. The pulse rate in the dim state is so fast that the filament does not flicker.

CMOS 556 (such as 7556, TLC556, or LMC556), it will need to be much larger. The 4-Hz pulse rate is determined by R5 and C2. The purpose of R7 and C3 is to protect the 556 from voltage surges.

Darkroom Timer Wanted

Q I have done photographic lab work both professionally and as a hobby, and for a long time I have wanted to build my own darkroom timer to suit my own needs. Now that electronics is a new hobby of mine, I am excited about the prospect of finally doing this.

I would really like to build an LED timer including both minutes (up to 99) and seconds. I need it to count down from a pre-selected time and activate a relay to switch an AC load.

I'm aware of the "Time-Off" project in your sister magazine, *Popular Electronics*, September, 1997. I can use it in some lab work, but it is not usable in the darkroom because of the LCD display.—G. A. P., Ft. Myers, FL

A Red LEDs are indispensable in the darkroom because they're safe for black-and-white photographic paper and orthochromatic film. In fact, big arrays of LEDs make excellent safelights; there's

no filter that can fade, and for physical reasons, all their light is confined to a narrow band of wavelengths.

You might be able to add a red LED to illuminate the Time-Off, or position neon lamp NE1 so that it illuminates the display. In that case, use a red-filtered neon pilot light (available at appliance-part stores).

What you really want, though, is a timer that was published in *Popular Electronics* back in August, 1992, pp. 53–58 and 91. It uses thumbwheel switches so you can select 0 to 99.9 or 0 to 999 seconds, and the display consists of red LEDs. Admittedly, it doesn't go up to 99 minutes, but 999 seconds are more than 16 minutes, long enough for most if not all steps in photographic processing. All of the parts are still widely available.

Plated-Through Holes

Q How can I make plated-through holes on my two-sided printed-circuit boards so that I don't have to solder the same hole from both sides?—E. V., Toledo, OH

A As far as we know, there is no easy way. Plated-through holes involve electrolysis plating with special chemi-

HOW TO GET INFORMATION ABOUT ELECTRONICS

On the Internet: See our Web site at <http://www.gernsback.com> for information and files relating to our magazines (**Electronics Now** and **Popular Electronics**) and links to other useful sites.

To discuss electronics with your fellow enthusiasts, visit the newsgroups sci.electronics.repair, sci.electronics.components, sci.electronics.design, and rec.radio.amateur.homebrew. "For sale" messages are permitted only in rec.radio.swap and misc.industry.electronics.marketplace.

Many electronic component manufacturers have Web pages; see the directory at <http://www.hitex.com/chipdir/>, or try addresses such as <http://www.ti.com> and <http://www.motorola.com> (substituting any company's name or abbreviation as appropriate). Many IC data sheets can be viewed online. Extensive information about how to repair consumer electronic devices and computers can be found at www.repairfaq.org.

Books: Several good introductory electronics books are available at RadioShack, including one on building power supplies.

An excellent general electronics textbook is *The Art of Electronics*, by Paul Horowitz and Winfield Hill, available from the publisher (Cambridge University Press, 1-800-872-7423) or on special order through any bookstore. Its 1125 pages are full of information on how to build working circuits, with a minimum of mathematics.

Also indispensable is *The ARRL Handbook for Radio Amateurs*, comprising 1000 pages of theory, radio circuits, and ready-to-build projects, available from the American Radio Relay League, Newington, CT 06111, and from ham-radio equipment dealers.

Copies of past articles: Copies of past articles in **Electronics Now** and **Popular Electronics** (post 1993 only) are available from our Claggg, Inc., Reprint Department, P.O. Box 4099, Farmingdale, NY 11735; Tel: 516-293-3751.

cals and equipment, followed by electroplating, and even the professionals consider the process difficult. But if a reader discovers an inexpensive way to make plated-through holes, we'd be glad to hear about it.

Converting Car to 12 Volts

Q About your comments on converting a 6-volt positive-ground automobile to 12 volts, negative ground (Sept. 1997), I have a

Electronics Now and many other magazines are indexed in the *Reader's Guide to Periodical Literature*, available at your public library. Copies of articles in other magazines can be obtained through your public library's interlibrary loan service; expect to pay about 30 cents a page.

Service manuals: Manuals for radios, TVs, VCRs, audio equipment, and some computers are available from Howard W. Sams & Co., Indianapolis, IN 46214 (1-800-428-7267). The free Sams catalog also lists addresses of manufacturers and parts dealers. Even if an item isn't listed in the catalog, it pays to call Sams; they may have a schematic on file which they can copy for you.

Manuals for older test equipment and ham radio gear are available from Hi Manuals, PO Box 802, Council Bluffs, IA 51502, and Manuals Plus, PO Box 549 Tooele, UT 84074.

Replacement semiconductors: Replacement transistors, ICs, and other semiconductors, marketed by Philips ECG, NTE, and Thomson (SK), are available through most parts dealers (including RadioShack on special order). The ECG, NTE, and SK lines contain a few hundred parts that substitute for many thousands of others; a directory (supplied as a large book and on diskette) tells you which one to use. NTE numbers usually match ECG; SK numbers are different.

Remember that the "2S" in a Japanese type number is usually omitted; a transistor marked D945 is actually a 2SD945.

Hamfests (swap meets) and local organizations: These can be located by writing to the American Radio Relay League (Newington, CT 06111; <http://www.arrl.org>). A hamfest is an excellent place to pick up used test equipment, older parts, and other items at bargain prices, as well as to meet your fellow electronics enthusiasts—both amateur and professional.

1949 Ford truck on which I have done this. I removed the 6-volt generator and installed a 12-volt Delco alternator. The ammeter is a feed-through type and voltage doesn't matter. I installed dropping resistors in series with the gas, oil-pressure, and temperature gauges. I also installed resistors in series with the coils of the headlight and horn relays. I checked the accuracy of the oil-pressure gauge by temporarily connecting another pressure gauge.

Of course, I changed all the light bulbs to 12 volts. I still use the 6-volt starter; it draws more power on 12 volts but still works as long

as I don't crank too long at a time. I changed to a 12-volt ignition coil and installed a breaker-less ignition system. I'm almost 86 years old but still drive my truck every week.—R. E. Cook, Meridian, MS

A Thanks very much for sharing your results! The values of the dropping resistors will have to be determined experimentally, of course, but 10 ohms at 10 watts is a good starting point.

Emergency Alert System and SAME

Q Years ago, I read an article, "Build a Low-Cost Emergency Broadcast System Monitor." The monitor would detect the 853- and 960-Hz tones and turn on an alarm. I built one and verified that it responded to the weekly tests. It was great for bad-weather warnings.

Can you tell me about the new E.A.S. system? What frequency are the tones?—L. W. Mason, MI

A The Emergency Broadcast System (EBS) goes back to the 1950s and was originally intended to warn us of incoming nuclear bombs, but authorities have realized that it's also useful to warn people about tornadoes and the like, and that is now its main use. As you noted, EBS warnings are preceded by simultaneous 853- and 960-Hz tones. They're transmitted by ordinary radio and TV stations. Meanwhile, NOAA weather stations use a 1050-Hz tone to announce warnings, and you can buy radios that respond to the tone.


The new Emergency Alert System (EAS) has now replaced EBS, although the old tones are still transmitted for backward compatibility. NOAA's version of it is called SAME (Specific Area Message Encoding) because you can set your alarm to go off only when an announced warning pertains to your location.

EAS uses digital messages, not just analog tones. The audio encoding is similar to that used by modems, but the protocols are nonstandard (520.83 baud, 2083.3/1562.5-Hz FSK) to enhance security (the signals can't be faked with an ordinary modem). There is an elaborate code for the contents of the messages. To decode them, you need a computer (which can be built into a radio), not just a tone detector.


Designed To Serve All Your EE Reference Needs!

Take
3 Books
FOR ONLY
\$4.95


VALUES TO
\$316.25

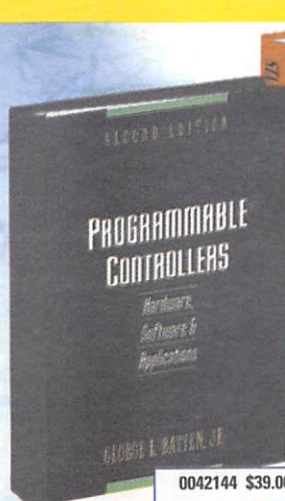

0042144 \$39.00

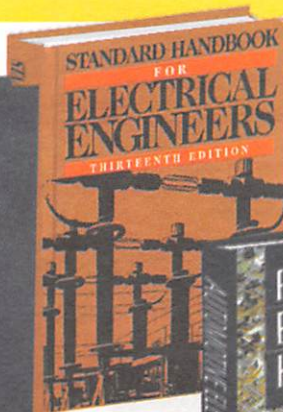


0209847 \$125.00

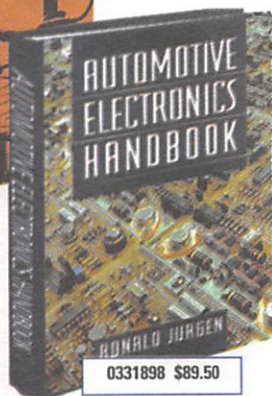


0331898 \$89.50

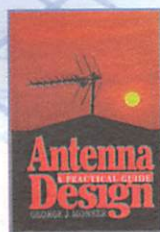When you join the
Electronics Engineers' Book Club®




0428433 \$60.00

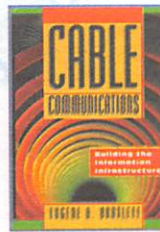

0053553 \$50.00




0704414 \$85.00

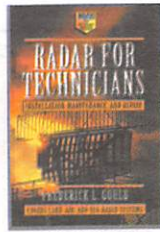

0240620 \$45.00




0280495 \$60.00

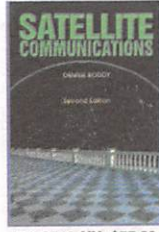


0523746-XX \$55.00
Counts as 2




0524157 \$65.00

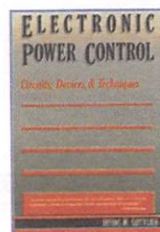


0239193 \$27.95

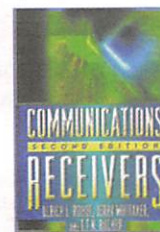


0536082 \$65.00

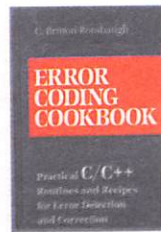


9117201 \$55.00

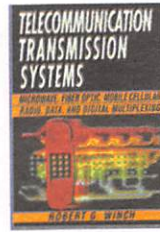

0709645 \$70.00

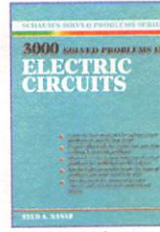


0459363 \$24.95

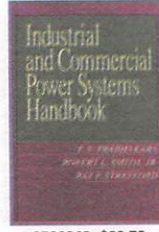

0506248 \$69.50




0520550 \$60.00

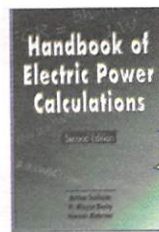

0570485 \$59.95

JOIN TODAY!

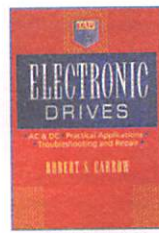

4603701 \$70.00

ELECTRONICS ENGINEERS'
BOOK CLUB®

A Division of The McGraw-Hill Companies
PO Box 549
Blacklick, OH 43004-0549

☐ **YES!** Please send me the books listed below, billing me just \$4.95, plus shipping/handling & tax. Enroll me as a member of the **Electronics Engineers' Book Club** according to the terms outlined in this ad. If not satisfied, I may return the books without obligation and have my membership cancelled. I agree to purchase just 2 more selections at regular Club prices during the next 12 months and may resign anytime thereafter.

Code #'s of my book(s) for \$4.95

--	--	--

If a book counts as two, write the book number in one box and XX in the next.

Name _____

Signature _____

Address/Apt. # _____

City/State _____ Zip _____ Phone _____




Valid for new members only, subject to acceptance by EEBC. Canada must remit in U.S. funds drawn on U.S. banks. Applicants outside the U.S. and Canada will receive special ordering instructions. A shipping/handling charge & sales tax will be added to all orders.

See other side
for more great
selections...


Save Time and Money With These Essential EE Resources...

Choose
3 Books
FOR ONLY
\$4.95

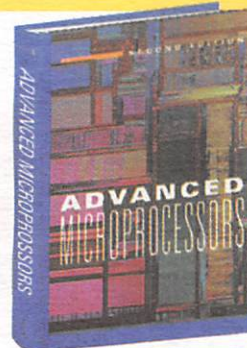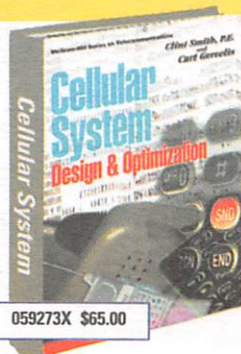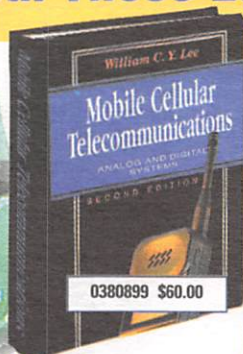
When you join the
Electronics Engineers' Book Club®



156490X \$22.95

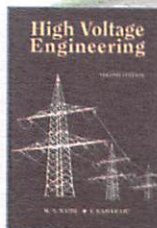

4622862 \$55.00

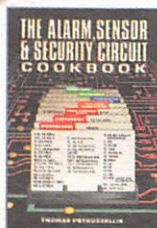


0497060 \$34.95



5875551-XX \$69.95
Counts as 2



9119018 \$32.95

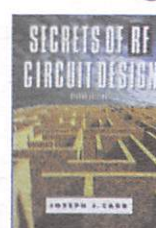


0116725 \$49.95

VALUES TO
\$316.25




0384762 \$55.00

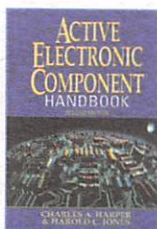


0266921 \$79.50



5879239 \$44.95

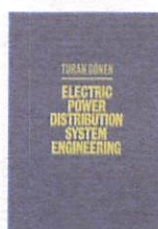


0237077 \$101.75

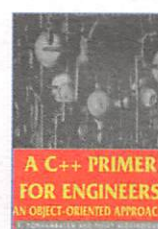


9131409 \$50.18




057278X \$60.00

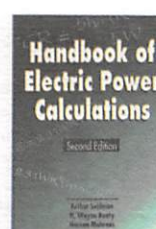


0570485 \$59.95

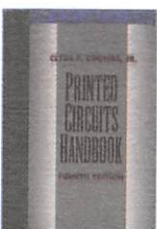

0127549 \$89.50

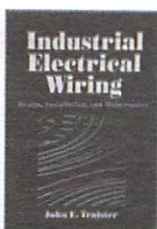

0653291 \$59.95

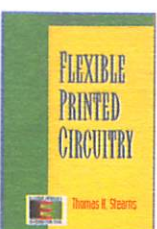

0610320 \$60.00



0717753 \$19.95



0109141-XX \$84.56
Counts as 2

As a member of the **ELECTRONICS ENGINEERS' BOOK CLUB...**

you'll enjoy receiving Club bulletins every 3-4 weeks containing exciting offers on the latest books in the field at savings of up to 50% off the regular publishers' prices. If you want the Main Selection, do nothing and it will be shipped automatically. If you want another book, or no book at all, simply return the reply form to us by the date specified. You'll have at least 10 days to decide. If you ever receive a book you don't want due to late delivery of the bulletin, you can return it at our expense. Your only obligation is to purchase 2 more books during the next 12 months, after which you may cancel your membership at any time. And you'll be eligible for FREE BOOKS through our Bonus Book Program.

A shipping/handling charge and sales tax will be added to all orders. All books are paperback unless otherwise noted. Publishers' prices shown. © 1997 EEBC

If card is missing, write to:
Electronics Engineers' Book Club®,
A Division of The McGraw-Hill Companies,
P.O. Box 549, Blacklick, OH 43004-0549

PHONE: 1-614-759-3666
(8:30 a.m. to 5:00 p.m. EST Monday-Friday)

FAX: 1-614-759-3749
(24 hours a day, 7 days a week)

Internet: www.bookclubs.mcgraw-hill.com

BUSINESS REPLY MAIL

FIRST-CLASS MAIL PERMIT NO. 4474 COLUMBUS, OH

POSTAGE WILL BE PAID BY ADDRESSEE

ELECTRONICS ENGINEERS' BOOK CLUB®

A Division of The McGraw-Hill Companies

P.O. Box 182601

Columbus, OH 43272-3028

NO POSTAGE
NECESSARY
IF MAILED
IN THE
UNITED STATES



More information about EAS can be obtained from an article in *QST*, November, 1997, pp. 50-51 (published by the American Radio Relay League, Newington, CT 06111); from EAS (FCC, MS 1500C Room 736, Washington, DC 20554); and on the Web at www.fcc.gov/cib/eas.

Headphone Jack for TV

Q I have a 13-inch color TV that has no headphone jack, and I want to put one in safely. How do I do it?—A. D. B., Pittsburgh, PA

Q I'm interested in taking the audio (mono) from my older TV and running it through my stereo amp and speaker system. Is there a way I can tap into the audio output stage of the TV, bypassing the speaker?—D. S. P., Sacramento, CA

A Forty years ago, when all TVs had power transformers and audio-output transformers, this would have been an easy question—just replace the speaker with an 8-ohm, 2-watt resistor and take the audio signal across that.

Today, though, if you do that you may be risking your life. Some TVs have a "hot chassis" in which even the speaker is not isolated from the AC line. Although small audio transformers exist, they are not necessarily safe enough to use in this application. We consulted our TV-service expert, Sam Goldwasser, who told us that if the manufacturer has not already provided an audio output, it probably can't be done easily and safely. In any case, analysis of the circuit of your particular TV is required.

We have also found that the audio quality in cheap TVs is often dreadful, with plenty of hum, and connecting to a larger audio system only magnifies the defects!

Electricity and Water

Speaking of safety, we get lots of questions about electrically controlled sprinkler and pump systems, which we're

usually reluctant to answer because water and electricity can be a dangerous combination, and also because we're not plumbers—water systems are outside our area of expertise.

Reader R. H. Hammett of Grandview, MO., writes to advise anyone experimenting with such systems to use low-voltage, line-isolated equipment for safety's sake. He recommends consulting the 400-page catalog of pumps, valves, and control components published by Aquatic Eco-Systems, Inc., 1767 Benbow Court, Apopka, FL 32703. As for us, we'll stick to electricity.

Writing to Q&A

That's all for this month. As always, we welcome your questions; please write to: "Q&A," *Electronics Now* Magazine, 500 Bi-County Blvd., Farmingdale, NY 11735. The most interesting ones are answered in print. Please be sure to include plenty of background information (we'll shorten your letter for publication). *If you are asking about a circuit, please include a complete diagram.* Due to the volume of mail, we regret that we cannot give personal replies.

EN

**DESIGNERS
HOBBYISTS
STUDENTS**

90% Off!

**PROFESSIONAL ELECTRONIC
DESIGN SOFTWARE**

**EDWin NC for Non Commercial Use. Now You Can
Benefit from 10 years development for industry in Europe.**

EDWin NC Basic* offers a 100 component database with Schematics, PCB Layout, 500 Device Library, Basic Autorouter & PostProcessing on CD Rom (Commercial Use Price \$590.00) **\$59.00***

DELUXE 1 Basic PLUS Professional Libraries and Unlimited Database \$99.00*

DELUXE 2 Basic PLUS Profess Libraries and Mixed Mode Simulation \$99.00*

DELUXE 3 all the above PLUS Arizona Autorouter ONLY \$149.00*

DELUXE 4 ADDS Thermal Analysis, ED SPICE Simulation and ED Co MX (SPICE Model development) ONLY \$280.00*

ADEPTX INC.

**Call 1-888-EDWinNC TOLL FREE
(339-4662)**

Features Include:
PCB Layout, Schematic Capture Autorouting, Full SMD support, PostProcessing Simulation Integrated Layout Database Comprehensive Start up Libraries, Easily Produced Customized Libraries, Full Pan/Zoom Redraw, Bill of Materials, Design Rule Checking from 1 to 32 Layer Boards, GERBER and NC Drill Outputs, Full Printer/Pen Plotting Help and Manuals on CD-ROM

Major Credit Cards Accepted
Fax: 1-561-393-2945 • E-mail: Edwinnc@aol.com
*add \$9.00 S&H plus tax




A public service of this magazine




EQUIPMENT REPORT

NATIONAL INSTRUMENTS DAQMETER 4050 VIRTUAL DMM

Turn your computer into a full-function, digital multimeter with storage capabilities.

CIRCLE 15 ON FREE INFORMATION CARD

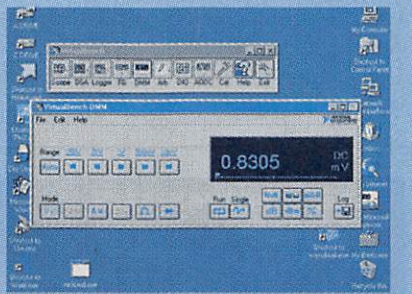

Notebook computers are becoming more powerful and more affordable almost every day. It seems likely that someday soon it'll be a coin toss as to whether you buy a portable TV set or just spend a few extra dollars to get a notebook computer that can not only act just like a portable TV, but also as a VCR, and much, much more.

That said, right now notebook computers are still a bit too expensive for most of us to purchase for such casual use. But for those who own or have access to a notebook computer, there are hardware and software applications available that can let you use that computer in a variety of ways you might not have thought possible. One such application that is sure to be of interest to readers of this magazine comes from National Instruments. It is the DAQMeter 4050 digital multimeter, which provides all the functions of a traditional DMM and adds the storage capacity and processing power of a computer.

The hardware part of the DAQMeter comes as a PC Card for notebook computers (it is also available as a PCI or ISA expansion card for desktop systems; while all three versions are said to function identically, only the PC-Card version is reviewed here). The system requirements are 16MB of memory and 20MB of free disk space. The DAQMeter package includes the PC-Card multimeter, test leads, "VirtualBench" software, drivers, documentation, and a nylon carrying bag; it sells for \$695. The software is provided in Windows 3.1, 95, and NT versions.

Specifications

The DAQMeter 4050 is a 5½-digit virtual multimeter, or VMM, that can measure voltage, current, and resistance. You also get the power of data logging, time stamping, and recallable settings. Power consumption is about 45 mA, so it's not too hard on notebook-computer batteries. The package is ideal for making and logging remote measurements.

The DAQMeter 4050 works with AC or DC coupling and can measure AC and DC voltage in five ranges from 20 millivolts to 250 volts, AC and DC current in five ranges from 20 milliamps to 10 amps, and resistance in five ranges from 200 ohms to 20 megohms. The DAQMeter is auto-ranging with 10-, 50-, or 60-readings per second. AC measurements are true rms from 20 Hz to 25 kHz. The unit can also measure the forward voltage drop on diodes. Current can only be measured with an optional current-shunt module that converts the current into a voltage that the DAQMeter can measure when in its voltage mode. Software then automatically does the math and displays the result directly as current.

Setup and Use

Setting up the DAQMeter is very easy, once you know how it is done; a bit of background knowledge about the DAQ-Card product line goes a long way to making the installation painless. For example, none of the DAQ Cards are recognized by a notebook computer in the traditional way—where the computer sees

the card and asks for a driver diskette. The cards will be recognized only after NI-DAQ, a comprehensive driver bundle, is installed from a CD-ROM. The single "driver" recognizes the entire line of DAQ Cards. Since we had already installed NI-DAQ when we reviewed the DAQScope (see *Electronics Now*, November 1997), no additional drivers needed to be loaded. In fact, no software at all had to be installed because VirtualBench was also already in place. A simple configuration utility informed VirtualBench about the capabilities of the card and DAQMeter hooked right up.

As you probably inferred from the above, VirtualBench can provide multiple functions other than the multimeter. The same software works with the oscilloscope card mentioned before and with many other products in the National lineup. However, only the multimeter function is "unlocked" by the serial number provided and when the DAQMeter card is installed. The VirtualBench-DMM software provides a "front-panel" display on your computer's screen that offers all of the controls found on a traditional DMM, but with hot-changing button labels and functions depending on operating mode.

Once set up, DAQMeter is easy to use. You simply insert the PC Card into a notebook-computer slot and connect the test leads. You then run VirtualBench and select the DMM function. A special cable that connects to the DMM card provides jacks for the test leads. The test probes are used with plastic covers placed over the ends to directly probe a circuit under test. With the covers off, the probes accept standard banana-jack accessories including spade lugs, alligator clips, and more.

For more information on the DAQMeter 4050, contact the manufacturer directly (National Instruments Corporation, 6504 Bridge Point Parkway, Austin, TX 78730, Tel: 512-794-0100; Fax: 512-794-8411), or circle 15 on the Free Information Card.

EN


Prototype

New Technology for Finding Felons, Terrorists, and Evidence

A convict tries to escape from prison by hiding in a secret compartment he built into a truck. He is quickly detected by guards using a device that detects his heartbeat. Airport security detains a terrorist bent on mayhem when he walks through a portal that detects explosives. Criminal investigators easily find all the evidence at the crime scene because it "blinks" when they wear special glasses. These very unique electronic technologies being developed for law enforcement could also find other applications.

Enclosed Space Detection System

The Enclosed Space Detection System (ESDS), developed by the Department of Energy's Oak Ridge National Laboratory (ORNL) and Lockheed Martin Energy Systems Inc., can "hear" the heartbeat of someone hiding in a car or truck. When the heart beats, it generates a small but measurable shock wave that travels through the body. That "ballistocardiac" wave is transferred to any surface or object in contact with the body. For instance, if somebody is hiding in a car trunk, the heart, being the strongest muscle in the body, actually moves the vehicle a few millionths of an inch at the same frequency as the

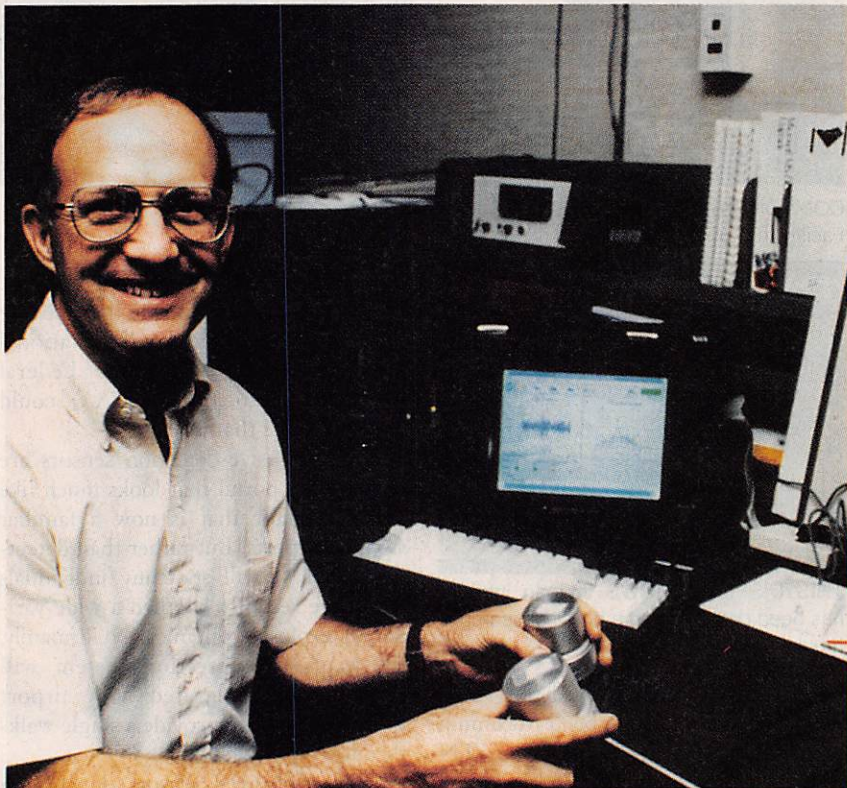

THE GEOPHONES AND PORTABLE COMPUTER used with the Enclosed Space Detection System (ESDS). (Oak Ridge National Laboratory)

heartbeat. That slight shockwave is quite detectable.

To detect a person hiding in a vehicle at a checkpoint, the engine is shut off, all legitimate occupants leave, and seismic geophones are placed at strategic locations on the vehicle. Computerized signal processing software filters out and discriminates between the unique beating of the human heart and other noise and vibration, such as fuel sloshing in the fuel tank or the contraction of the engine as it cools. The results of the "search" are displayed on the computer

screen. The process takes about two minutes and has been shown to be 100% reliable, provided the vehicle is protected from moderate to high winds.


Recently, the Oak Ridge researchers have developed a system that uses microwave detectors mounted to a rigid structure, eliminating the need for the geophones to be placed on the vehicle. As a result, the ESDS will be even less intrusive and easier to use. A prototype ESDS was tested at California's Centinella Prison. When prison officials tried to smuggle someone past the ESDS, they

FOR MORE INFORMATION


Oak Ridge National Laboratory
PO Box 2009, Bldg. 9113, MS 8206
Oak Ridge, TN 37831
Web: www.ornl.gov

Sandia National Laboratories
PO Box 5800
Albuquerque, NM 87185
Web: www.sandia.gov

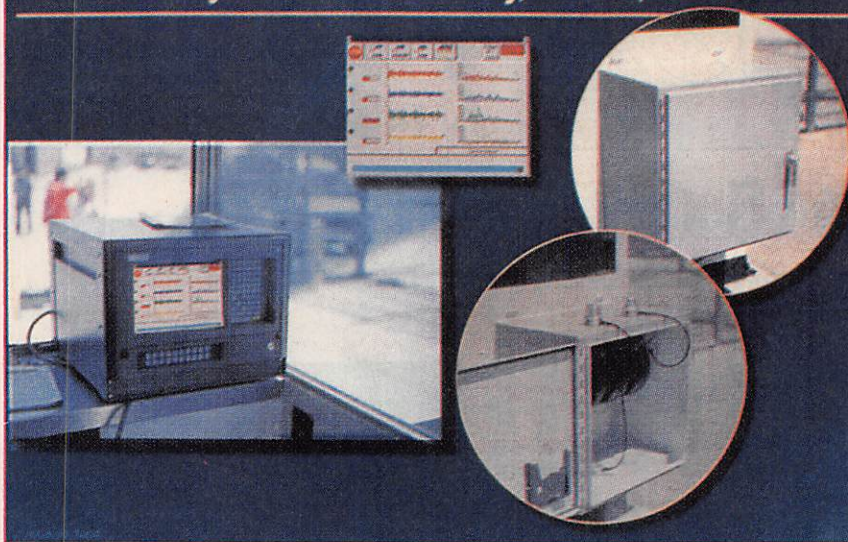AVIAN Security System Wabash Valley Correctional Facility, Carlisle, Indiana



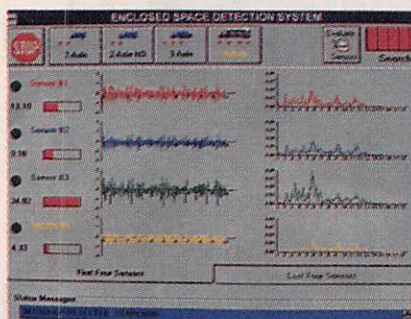COMPONENTS OF THE ESDS as installed on a system at the Wabash Valley Correctional Facility in Carlisle, IN. (ORNL)



THIS DISPLAY SHOWS that an intruder has been detected and a physical search is required. (ORNL)

were quickly discovered. Other systems are installed at the Riverbend Maximum Security Installation in Nashville, TN and the Wabash Valley Correctional Facility in Carlisle, IN. Geovox Security Systems of Houston, Texas is planning to market the ESDS commercially as the AVIAN for Advanced Vehicle Interrogation And Notification System.

Among other possible applications, the technology could be used to detect illegal immigrants being smuggled into the country or intruders trying to break into secured facilities. In the future, it could be used to search for vital signs of survivors after an earthquake or victims buried in an avalanche.

Explosives-Detection Portal

Terrorists carrying explosives have become an all too-real threat at air-

ports and in public buildings. A new explosives-detection system that is being developed by the Sandia National Laboratory for use by the Federal Aviation Administration (FAA) could greatly reduce that threat.

The explosive-detection sensors are located in a portal that looks much like metal detector that is now a familiar sight at airports. But rather than detecting metal, it will spot any individuals who have recently handled a wide variety of explosive chemicals. Ultimately, the explosives-detection system will probably be integrated with airport metal detectors to provide a single walk-through unit.

The explosives sensors depend on chemical preconcentrator technology developed as part of Sandia's mission to protect critical nuclear-weapons facilities from would-be saboteurs. The system is capable of detecting very small concentrations of all explosives of interest to the FAA.

The new portal sports vents and nozzles on its inside walls and ceiling. Persons being inspected stand inside the portal for a few seconds while the detector blows a quiet, gentle "puff" of air over them. An air sample is collected and passed through a commercial ion-mobility spectrometer. The system's software recognizes the chemical signatures of a variety of explosives.

If the system detects even a minute concentration of explosive residue on the skin or clothing, the quantity and type of chemical is displayed on an adjacent computer screen. People that show up positive for explosives would be further screened to see if there are any circumstances that might explain the reading. If suspicions remain after additional screening, airport security would be notified.

After three years of development, a prototype of the portal was recently installed at a main security checkpoint at the Albuquerque International Sunport. The portal is fully automated, providing instructions such as "enter the portal," "turn left," and "exit the portal"—in a friendly male voice.

Once the tests are complete, the FAA will use the results to determine the feasibility of licensing and manufacturing the explosives-detection portal technology for use at airports across the country, as well in public buildings such as government offices and courthouses. The basic technology could also be adapted to sniff for drugs.

Evidence Detector

"Dusting" for fingerprints and finding urine and other organic evidence at a crime scene is not easy even for experienced criminal investigators. Sandia National Laboratories is now developing an evidence-detection technique whereby organic material would actually blink before the eyes of crime-scene investigators so they can locate potential evidence quickly, even in a well-lighted room.

Sandia's evidence detector uses the fact that all organic substances give off weak fluorescent emissions that are usually invisible to the naked eye due to interference from brighter lights. The system is based on a heterodyning effect; that is, the periodic dissonance between two signals at slightly different frequencies plus the human eye's natural affinity to see anything that moves or blinks.

The flashing lamp used in system is modulated at 100-times-per-second, which is much too fast for the eye to see. The shutters on a pair of modified glasses from a 3-D video game open and close at a slightly different frequency—102 times per second. That turns the glasses on and off at a rate that is also too fast to




IN THE EXPLOSIVES-DETECTION PORTAL, a "puff" of air is blown over a person and an air sample is collected and analyzed by a spectrometer. (Sandia National Laboratories)

be detected by the human eye making the lenses appear transparent to the wearer. About twice a second, the glasses' shutter opens at the exact moment the lamp is on. Therefore, for a split second, most of the background light whose wavelengths are different than that of the lamp is drowned out. With the background light masked, the fluorescing organic evidence appears to flash so it is quite easily seen by the eye. Investigators wearing the special glasses see the room lighted normally, but more important, see any organic evidence flash a few times per second when illuminated by the lamp.

A prototype system will be tested by the Albuquerque Police Department's crime laboratory at actual crime scenes to work out any bugs in the technique. Testing will determine the type of evidence it can discover as well as verify that it can be practically used as a tool in criminal investigations. An important factor is that the system be affordable enough so it can be used by just about any law enforcement agency's criminal investigation unit.

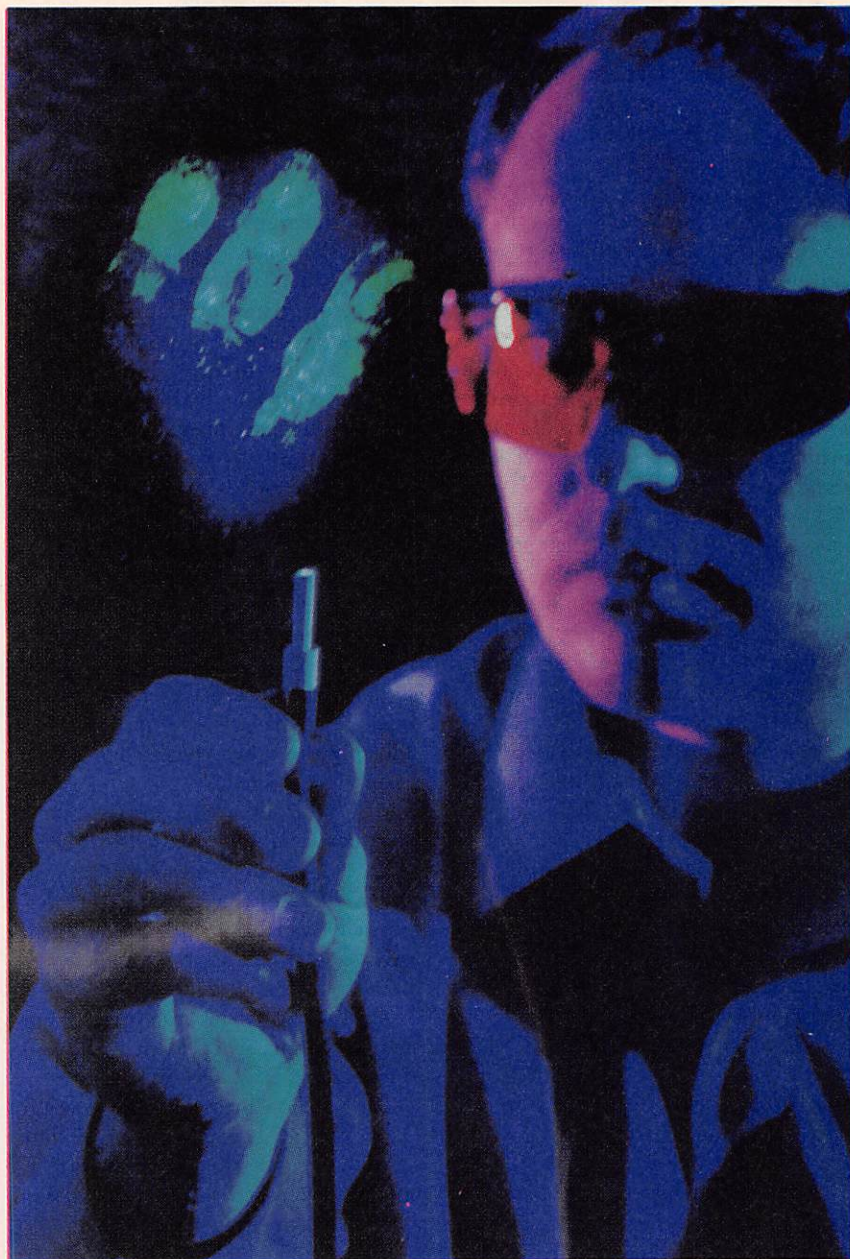The technique could be especially useful for finding semen after sexual



IN SANDIA'S EVIDENCE DETECTOR, fingerprints and other organic evidence blink when special glasses are worn. (Sandia National Laboratories)

assault crimes because semen fluoresces much more brightly than the oils from fingertips. Researchers also hope to find out if fresh fingerprints fluoresce more brightly than "stale" organic materials. If so, the system could be effective in screening out evidence that is not part of a crime.

The bad guys can cover their tracks and stay out of sight, but thanks to these new technologies, it is getting ever more difficult to hide.—**BILL SIURU and ANDREA STEWART**

Camera on a Chip

An image sensor based on a complementary metal oxide semiconductor (CMOS) technology that could make the digital camera as inexpensive and as common as a computer mouse was recently announced by Sarnoff Corporation. The CMOS Active Pixel Sensor (APS) delivers nearly 100× the dynamic range of a standard Charge-Coupled Device (CCD) sensor, at comparable resolutions, for better shadow

and highlight detail. It controls exposure without a mechanical iris, and its on-board electronics eliminate the need for external analog-to-digital converters and other circuitry required in CCD-based cameras.

"The CMOS APS is virtually a 'camera-on-a-chip,' and we believe it will revolutionize the way cameras are made and used," said Michael Ettenberg, Senior Vice President of Sarnoff's Solid State Division. "Not only can it replace CCDs in many current camera applications, it will create new applications. Its low cost allows engineers to add vision capability to products where it once would have been too expensive."

Sarnoff will license the technology to camera makers and provide engineering support. Two foundries to fabricate the chip have been approved, and the company will supply design tapes for manufacturers who wish to produce it in other foundries. Ettenberg foresees uses for the CMOS APS in such products as digital still cameras, PC-based video cameras, security and surveillance systems, videophones, even toys with built-in vision capabilities.

The Sarnoff design incorporates breakthrough technology that virtually eliminates the performance limitations associated with previous CMOS-based image sensors. Those sensors suffered from high levels of Fixed Pattern Noise (FPN), which gives an image a "dirty window" effect. In the Sarnoff design, internal circuitry reduces FPN to less than 0.01% of full signal, below the threshold of visibility.

Other features include full TV resolution, video output in both analog and 12-bit digital form, dynamic range over 110 dB to preserve image detail, low power consumption, and compatibility with color-filter technology. **PT**

Filtered Sunglasses

A modification in sunglass filters developed by NASA engineers may make our skies and roads safer by helping pilots and drivers see better. The filter—a low-cost, brownish, plastic material—was originally designed to help farmers identify diseased plants. The filter blocks much of the yellow and green light during daylight hours, enhancing

the ability of the human eye to detect other colors in the visible spectrum, according to its developer Dr. Leonard Haslim, of NASA's Ames Research Center at Moffett Field, CA. This filter was modified by Optical Sales Corp., Portland, OR, and used in a new sunglass product now being marketed.

Stress in plants tends to be camouflaged by the plant's natural chlorophyll. As a result, many plant diseases cause irreversible damage by the time they become evident to the eye. In the past, it was necessary that highly-trained professionals examine plants to detect early signs of stress. "Now farmers can use goggles equipped with the special filter to locate diseased or stressed plants," said Haslim. "Sick leaves that appear just a bit yellow in normal light show up a much brighter yellow when viewed through the filter. Conversely, healthy leaves appear as a vivid green. If we diminish or block a lot of the yellow-green light that the eye normally sees, suddenly the other colors stand out in much greater relief."

The filter, called the passive chlorophyll detector, was invented by Haslim in 1991. The sunglass adaptation with the modified filter was first made commercially available in 1997. Government inventions, like the NASA filter, are often commercialized by the industry. According to Michael Weingarten, manager for business development (NASA, Washington, DC), "NASA invests more than \$5 billion in technology development annually. It makes good economic sense to bring that state-of-the-art technology back to U.S. taxpayers when such a huge investment is being made." **PT**

Mother Earth Warms Up the Golden Arches

A McDonald's restaurant that opened in the Detroit area last December was one of the first in the chain to use the earth for its heating and cooling needs. A geothermal heat pump system, installed with the help of Detroit Edison and Electric Power Research Institute (EPRI), the science and technology organization of the electric power industry, will provide natural, environmentally safe energy at reduced cost. McDonald's will

be monitoring the energy usage of the 3600 square-foot restaurant, evaluating results, and examining the potential of geothermal heat pump technology to save money.

Geothermal technology can economically and efficiently use solar energy naturally stored in the earth to heat water and to heat or cool buildings year-round. Geothermal heat pumps (also called ground source heat pumps) take advantage of the earth's stable temperature to help keep indoor temperatures comfortable. The system circulates water or other liquids through pipes buried horizontally or vertically underground.

In cold weather, geothermal heat-pumps transfer the earth's heat through the buried pipes into a circulating liquid, which transfers it into the building. In hot weather, the continually circulating fluid in the system's pipes cools the building by "picking up the heat" and transferring it into the cool earth. In cold climates, heat pumps offer an energy-efficient alternative to furnaces and air conditioning.

EPRI is working with member utilities and their customers to incorporate geothermal technology in many different national projects, including Wendy's in New York, a Texaco gas station/minimart and a Hardee's in Oklahoma, office buildings in Pennsylvania, and a country club in Georgia. This technology is also being used in historic sites such as Colonial Williamsburg.

"EPRI's demonstration projects provide valuable opportunities to transfer science and technology into practical solutions where we can learn how well the system's work under many different conditions. In the process, we will develop more reliable and cost-effective applications," explained Mukesh Khattar, Team Leader in EPRI's Customer Systems Group.

Geothermal systems reduce carbon-dioxide emissions that contribute to global warming. Benefits over other heating/cooling systems include being much quieter, and, with the heat exchange units inside the building and the buried pipes, greater reliability since the system is not exposed to weather conditions nor susceptible to vandalism.

The EPRI can be found on the Internet at www.epri.com. **PT**

Cleaning a Disc, Repairing Scratched Discs, and More

WE'LL BEGIN THIS MONTH'S DISCUSSION OF CD-PLAYER/CD-ROM-DRIVE REPAIR BY LOOKING AT ONE OF THE MOST COMMON SOURCES OF PROBLEMS—THE DISCS THEMSELVES.

THEN WE'LL LAY SOME OF THE GROUNDWORK WE'LL NEED TO


get into the process of troubleshooting and repairing a defective player or drive.

Cleaning a CD is not a difficult chore, and you most certainly do not need a fancy CD-cleaning machine. Instead, just use a soft cloth, tissue, or paper towel moistened with water. Add a little mild detergent, if needed (Ivory soap works well). Wipe from the center of the disc out toward the edge—not in the circular motion usually recommended for a vinyl LP. *Never* use any strong solvents. Even stubborn spots will eventually yield to your persistence. Washing under running water is fine as well.

Once done, gently dry with a lint-free cloth. Do not use a dry cloth as any dirt particles may cause scratches. The polycarbonate the CD is made of is tough, but don't expect it to survive everything. Very fine scratches are not usually a problem, but why press your luck?

Something that not everyone is aware of is the multilevel error handling technology in a CD player. Therefore, a dirty CD may not instantly produce obvious audio problems, but can nevertheless result in less-than-optimal audio performance. Very severe errors—long bursts—will result in audible degradation, including noise and/or muting of the sound. Even that might not always be detectable, depending on the musical content. Shorter runs of errors can result in the player interpolating between what it thinks are good samples. That process isn't perfect, but any inaccuracies proba-

bly will not be detected during casual listening. Errors within the correcting capability of the Cross Interleave Reed Solomon Code (CIRC), which is used to encode the data on a CD, will not be noticed at all. In principle, it should be possible to drill a 2.5mm-diameter hole in the discs (in fact, some test discs have such a hole), but not all players implement all of the possible error-handling strategies.

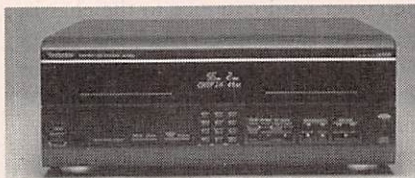

A DIRTY DISC OR LENS might cause even the best CD player to sound poor, but it is unlikely to cause damage to the unit itself.

Can Dirt Damage My Player?

One common thing you might hear from the man behind the counter in your local CD store is "Dirty CDs could do irreparable harm to your CD player, your stereo, your disposition, etc. Buy our \$19.95 Super-Laseriffic CD Cleaning Kit." One claim I heard at a store that was part of a major chain was that dirt or dust on the laser lens would cause heat buildup that would burn out the mechanism. What he was promoting here was not a disc cleaner, but a little brush attached to a CD that brushed off the lens as it played.

This kind of stuff is total rubbish. The power of a CD laser is less than 1 mW, and it is not concentrated at the lens. And, those cleaning CDs with the little brush are almost useless on anything but the smallest amount of dry dust. If the lens or disc is dirty, the worst that can happen is that the CD will not play properly. There could be audible noise, or the disc might fail to track properly, abort at random times, or not even be recognized. However, the electronics will not melt down because of dirt on the disc or the laser lens.


In short, it is just about impossible for a dirty CD to do any damage to the player, and a dirty lens will only result in disc recognition or play problems similar to those caused by a dirty CD; the laser will not catch on fire. About the only way damage could occur is if you loaded a cracked CD and the crack caught on the lens.

In any case, you do not need any fancy CD cleaners—soap or mild detergent, water, and a soft cloth will do the job. If the CD looks clean, it will probably be fine. If there are serious smudges or fingerprints, then cleaning could make a significant difference in performance.

Repairing a Scratched CD

So your favorite CD has turned up badly scratched (maybe your five-year-old decided that it would make a nice Frisbee), is there anything you can do? The answer is yes. There actually are three basic techniques for repairing scratches. They are: Mild Abrasives, Fillers, and Blowtorch.

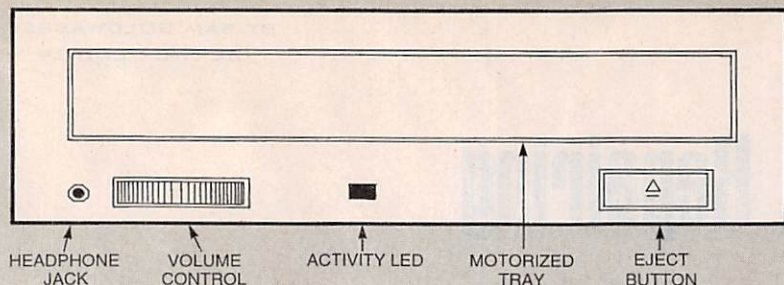- Mild abrasives: Use plastic or furniture polish, Brasso metal polish, or toothpaste to try and remove minor scratches. (Don't worry too much about causing damage; if the disc doesn't play, you can't



WHEN TROUBLESHOOTING A CD-ROM drive, the first step is to play an audio CD. If basic audio playback is fine, you can be reasonably certain that the optical pickup, the front-end electronics, and the servo systems are working correctly.

do any more harm.) When applying or rubbing any of these materials, wipe only from the center to the outside edge. A CD player can generally track across scratches that are perpendicular to its path reasonably well. It is the scratches that are parallel to the path that cause all the problems. If the scratch is minor, a mild abrasive may actually remove it completely. This is more effective when the surface has been scuffed or abraded rather than deeply scratched.

- **Fillers:** These include such typical items like car wax or furniture wax. Apply over the whole disc and buff out with a lint-free cloth. Filling larger scratches should be fairly effective, but be aware that the repaired disc will be more prone to damage in the future because of the soft wax filler. This technique works because the wax will fill in the space where the scratch is. Even deep scratches might give in to this approach.

- **Blowtorch:** A least one person who claims to have worked for several years in a used CD store swears by this technique. Supposedly, he uses a pencil-type pocket butane torch and with great dexterity fuses the surface layer of the readout side of the disc so that scratches and unsightly blemishes—well—melt away. Now there are obvious dangers in using fire on plastic and this is likely a last resort. I cannot tell you how many years of practice are required to get a CD-repair license. However, I am highly skeptical of this approach and suspect that destruction of the CD is the most likely outcome.

As an alternative to home repair, there are companies that actually specialize in fixing damaged discs. A couple of these are Aural Tech CD (www.nsynch.com/~auraltch) and CD Repairman (www.cdrepairman.com). I have no experience with any of these companies, so I can't comment on their effectiveness or

cost, but if you have an irreplaceable CD that has become damaged, they might be worth considering.

That concludes our discussion on the media itself. Assuming that cleaning of fixing a disc has not cleared up your problem, it will be necessary to deal with the CD player or CD-ROM drive itself. Let's begin that topic next with some preliminary information and tips.

Safety at All Times

While there are far fewer potential dangers involved in servicing a CD player compared to a TV, monitor, or microwave oven, some precautions are still required when working on a line-powered unit with its cover removed. There may be electrically live parts connected to the power line, usually around the power cord entrance to the chassis, the power transformer, and the on/off switch. If there are, tape them over or cover them somehow so you need not be concerned with a shock. Unless you are troubleshooting a primary-side power-supply problem, there should be no need for you to go near the AC line. For portable players, the internal voltages are all quite low, so shock is less of a concern than accidental damage to the equipment due to carelessness.

The laser in a CD player is infra-red. It usually operates at 780 nm—while that wavelength is at the edge of the visible range, for all intents and purposes, the beam is invisible. Note that the beam is very low power (under 1 mW), and coupled with the optics, presents very little danger. Nonetheless, don't go out of your way to look closely into the lens while the unit is on!

Note: With most CD-type lasers, if the lens is viewed from an oblique angle, you'll usually see a deep-red spot, about the size of a period. This emission

appears to be low intensity, and might be a spurious emission in the red part of the spectrum or just your eye's response to the near IR energy of the main beam. In any case, do not be misled into thinking that the laser beam is weak. The main beam is up to 10,000-times more intense! Take care. However, the red dot is an excellent indication that the laser is being powered and is probably functioning. To be sure, you need an IR detector to confirm the existence of the laser beam. A circuit for testing IR remote controls, like the one presented in the June 1997 installment of "Service Clinic," could also be used for this purpose.

Troubleshooting Tips

As in all electronics troubleshooting, many problems have simple solutions. Don't immediately assume that the problem you are looking at is some combination of esoteric, complex, convoluted failures. For a CD player, it may just be a bad belt or a dirty lens. Try to remember that the problems with the most catastrophic impact on operation (a CD player that will not play past track 6) usually have the simplest solutions (the gears that move the optical pickup need lubrication). The kinds of problems we would like to avoid at all costs are the ones that are intermittent or difficult to reproduce: the occasional audio noise or skipping, or a CD player that refused to play classical CDs of music composed between 1840 and 1910. (If you come across a player that won't play heavy-metal rock, send it to me—please.)

When attempting to diagnose problems with a computer's CD-ROM drive, start by trying to get it to play an audio CD. Data read-back is more critical since the error correction needs to be perfect. But if the audio playback works, you know that the optical pickup and most of the servo systems and front-end electronics must be working. A CD-ROM drive that won't play a music CD has no chance of loading Windows 95

If you get stuck, sleep on it. Sometimes, just letting the problem bounce around inside your head will lead to a different, more-successful approach or solution. Don't work when you are really tired—it is dangerous and mostly non-productive.

Whenever you work on precision equipment, make copious notes and diagrams. You will be eternally grateful that you did when the time comes to put the

(Continued on page 26)

GET HERE.

LEARN A SKILL YOU ENJOY... ...THEN FIND A JOB THAT HAS A FUTURE.

Everyone has to start somewhere.

As 150,000 CIE graduates have discovered, independent-study from The Cleveland Institute of Electronics can get you where you want to be. In a secure, financially rewarding, exciting career field of your choice.

Since 1934, CIE has been on the forefront of an ever expanding technological revolution




Industrial Robotics

ment. CIE's curriculum is unique from other independent-study schools in the respect that we not only provide hands-on training utilizing today's technology we also instill the knowledge and understanding of why technology works the way it does. This is the foundation upon which every CIE graduate can trace their success back to and in which CIE's reputation as a quality learning facility is based on.




Project Engineer

Independent study is not for everyone. But, if you have the desire, the basic intellect and the motivation to succeed, CIE can make it happen. Our learning program is patented and each lesson is designed for independent study while our instructors are available to assist you whenever you feel you need help. In fact, CIE's curriculum is so well respected many Fortune 1000 companies utilize it for their own employees.

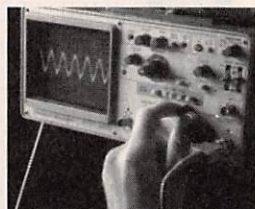

Telecommunications

START HERE...

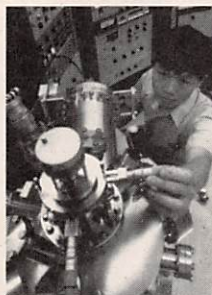

Electronics

Back then it was radio and TV, today it's computer technology, programming and the electronics that make it all possible. Today and yesterday's similarities are

uncanny... Employers are looking for qualified applicants to hire and having a hard time finding them.

Students at CIE receive the training and the education needed to get hired and to succeed in challenging fields such as computer programming, robotics, broadcast engineering, and information systems manage-

YES! Please send me more information on:

- ☐ CIE's Associate Degree Program
- ☐ CIE's Computer Programming Course
- ☐ CIE's 12 Career Courses
- ☐ World College's Bachelor Degree Program

AE118

Name

Address

City

State Zip

Phone:

Check for G.I. Bill Details

☐ Active Duty ☐ Veteran

successful career the same way you can...by sending for your free CIE course catalog and judging for yourself if CIE's for you.



Computer Programming

CIE

*It's More Than Just Training...
...It's an Education.*

1776 East 17th Street
Cleveland, OH 44114
(216) 781-9400 • 1-800-243-6446

New Web Site!
Visit our new web site at
www.cie-wc.edu
• Preview a sample from one of our lessons, detailed course descriptions, visit the bookstore, order a free catalog & much more!

Stayin' Alive: The Great Pilot Plot

SURPRISE, SURPRISE: READING CHARACTERS ONE AT A TIME FROM A SERIAL PORT IS A HIGH-OVERHEAD, SLOW PROCESS. READING CHARACTERS IN BLOCKS RUNS MUCH FASTER, ALMOST ACCEPTABLY SO.

To back up a step, we've been working the past few months on a chart-recorder application for the 3Com PalmPilot. The application is called HiLo. The purpose of HiLo is to read data in byte-sized chunks as it comes in an RS-232 serial port, maintain statistics about the data—minimum value, maximum value, and average (mean) value—and display the data in a scrolling format like a chart recorder. Our progress to date is shown in Fig. 1. This month's code is available at the Ingeniinc web site, www.ingeniinc.com. Look for a file named hilo2.zip.

Looking at Fig. 1, note that there is a new edit field, labeled *Scale*, on the screen. To its left is a field labeled *Last*. Last displays the actual value of the last item received. Scale displays the value scaled to fit the 90 × 100 plot area. The Scale value is approximately 35% of the received value (in pixels).

The central portion of the display functions as the chart recorder. Data points are displayed right to left in the order in which they are received. The display function is smart enough not to scroll the display point by point. Rather, when it receives a block of points (as many as 100 in the current implementation), it scrolls the chart recorder portion of the display by as many pixels (leftward) as points received. Then it draws the points one by one, right to left. The right-most point always represents the most recently received value.

Implementation Notes

The overall structure of HiLo remains the same. Four major changes have occurred:

1) I replaced the deadly slow AddPoint routine with a much faster AddPoints routine, shown in Listing 1.

2) The old AddPoint also performed the display function. Now there is a separate routine, DisplayChart, shown in Listing 2. As mentioned above, DisplayChart is not completely brain-dead, although there is certainly room for improvement.

3) I added a John Travolta "Stayin' Alive" call to the operating system so that the Pilot won't "go to sleep" (enter

a low-power mode in which it doesn't respond to serial-port activity) while HiLo is running.

4) Miscellaneous new and improved #defines and the like were added, as was a new debug routine for displaying a string and number in a dialog box at run-time.

Listing 1 shows the new multi-byte read routine, AddPoints. (AddPoints is called by SerIOReceive, discussed in an earlier article.) AddPoints is pretty simple, although there is one trick. The calling routine passes four things to AddPoints: a pointer to an input buffer (where the OS has stashed the data), a pointer to an output buffer (where we save the data), a count (number of bytes received), and a position (where in the output buffer the next byte is stored).

The output buffer is defined to be 100 bytes long. So what happens when we receive data byte 101? The output buffer is actually implemented as what is called a *ring buffer*. Imagine a ring with 100 slots. When the 100th slot is filled,

LISTING 1—ADDPPOINTS

```
static void AddPoints (UInt pos, ULong cnt, Byte *ib, Byte *ob) {
    SerIOCnt += cnt;
    while (cnt > 0) {
        // get input char, put in buffer
        SerIOCur = *ib;
        ob[pos] = SerIOCur;

        // update stats
        SerIOSum += SerIOCur;
        SerIOMin = (SerIOCur < SerIOMin) ? SerIOCur : SerIOMin;
        SerIOMax = (SerIOCur > SerIOMax) ? SerIOCur : SerIOMax;

        // update pointers, counters
        cnt--;
        ib++;
        pos = (pos + 1) % MAX_DATA_POINTS;
    }

    // update stats
    SerIOAvg = SerIOSum / SerIOCnt;
    SerIOSca = (int) (SerIOCur * VERT_SCALE);
}
```


the next byte “wraps around” and is stored in the first slot, overwriting the original contents. The slots are actually numbered 0 to 99. The wrapping behavior is obtained using C’s modulus function using the following line of code.

```
pos = (pos + 1) % MAX_DATA_POINTS;
```

Listing 2 shows the display routine, DisplayChart. It gets a pointer to the display buffer, a count of bytes to be displayed, and the position of the ring pointer. First DisplayChart scrolls the display rectangle left by the number of pixels specified by the count parameter. Then the area where the new points are to be plotted is erased. Last, points are extracted from the data buffer, scaled to fit the display, and plotted one by one.

For plotting, I used the WinDrawGrayLine function. The name is some-

thing of a misnomer, as the Palm OS supports only 1-bit (monochrome) graphics. It simulates gray by drawing every other pixel. The routine is somewhat intelligent, but has some bugs. For example, if you send it a series of bytes of equal value, you expect to see stripes—alternating bands of black and white. It turns out that if you send data slowly, a byte at a time, such as by pressing a key on a keyboard about once per second, you get stripes. However, if you hold the key down, you get an alternating pattern, in which the blacks and whites are offset by 1 pixel.

Either way, though, the display is not always consistent; sometimes it switches modes, seemingly arbitrarily. Also, line length may be off by one, because in the process of eliminating pixels to simulate the gray effect, the end may be eliminated. Those are not major issues, but they are limitations that need to be under-

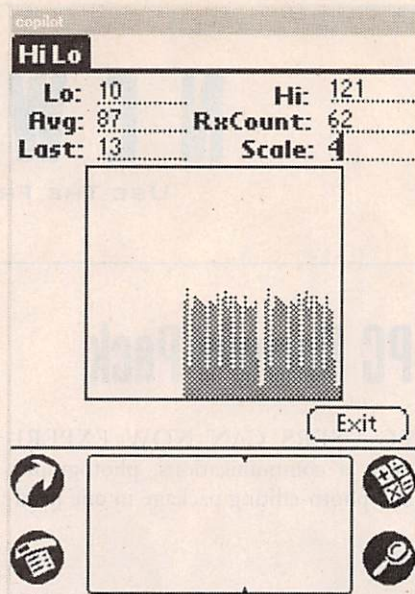


FIG. 1—THIS MONTH we implement a real scrolling chart-recorder display.

LISTING 2—DISPLAYCHART

```
static void DisplayChart(Byte *buf, UInt buffHd, UInt cnt) {
    Short xPos;
    RectangleType r;
    Short ScrollSize = 0;

    // scroll the window, erase any leavings
    cnt = (cnt > MAX_DATA_POINTS) ? MAX_DATA_POINTS : cnt;
    if (cnt < MAX_DATA_POINTS) {
        WinScrollRectangle(&ChartRecRect, left, cnt, &r);
        WinEraseRectangle(&r, 0);
    }
    else
        WinEraseRectangle(&ChartRecRect, 0);

    // draw the last point received, right-most, and work backward
    xPos = POS_X;
    while (cnt > 0) {
        buffHd--;
        buffHd = (buffHd >= MAX_DATA_POINTS) ? MAX_DATA_POINTS - 1 : buffHd;

        SerIOCur = buf[buffHd];
        SerIOSca = (int) (SerIOCur * VERT_SCALE);

        WinDrawGrayLine(xPos, POS_Y, xPos, POS_Y - SerIOSca);
        //WinDrawLine(xPos, POS_Y, xPos, POS_Y - SerIOSca);

        xPos--;
        cnt--;
    }
}
```

LISTING 3—MAIN FORM EVENT LOOP

```
...
else if (event->eType == nilEvent) {
    RcvCount = 0;
    SerIOReceive();
    if (RcvCount > 0)
        DisplayChart(Data, BufHead, RcvCount);

    handled = true;
}
...

```

stood. For comparison purposes, the code also has a “commented-out” line to draw solid lines, using WinDrawLine.

Listing 3 shows another point of interest. As discussed in preceding articles, the Palm OS is event driven. In the absence of “real” events, the OS pumps nil events through the system to give various processes a chance to do something. HiLo watches for nil events, and when it receives one, checks the serial port for data. If any is pending, it is retrieved, and then displayed. Note that DisplayChart is only called if the Receive Count is greater than zero.

At the top of that routine, but not shown here, is the following call:

```
EvtResetAutoOffTimer();
```

That forces the Pilot to stay alive as long as HiLo is running.

Limitations, Optimizations, and Improvements

This version of HiLo is *much* better than the previous one. However, it still has some problems. For example, although it’s much more responsive now, you can still swamp it by sending too much data too fast. If that happens, a dialog pops up, warning you of an error. You must click OK to dismiss that dialog, and you may have to click in one of the edit fields or the system will block (not receive any more characters).

The main problem there is the lack of intelligence in the Display routine, the

(Continued on page 26)




NEW PRODUCTS

USE THE FREE INFORMATION CARD FOR FAST RESPONSE

PC Camera Pack

PC USERS CAN NOW EXPERIENCE a communications, photography, and photo-editing package in one prod-

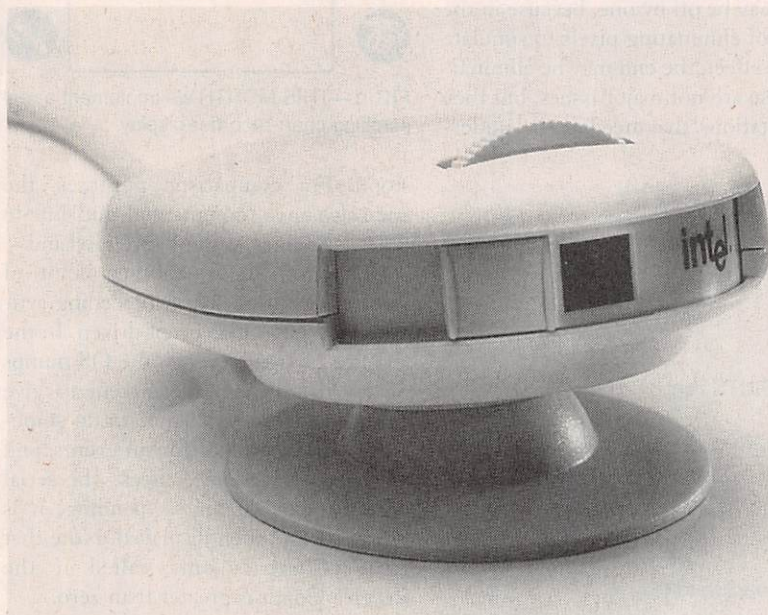videos made with the camera pack and to subsequently drag and drop those images into editing applications. The Scene



CIRCLE 20 ON FREE INFORMATION CARD

uct that plugs into Pentium processor-based PCs. The easy-to-use Create & Share Camera Pack includes an Intel PC camera, hardware, and an integrated suite of communications and image-editing software. The software suite enables consumers to make, enhance, and organize snapshots and videos that can be passed along to others in print, on screen, and on the Web. The camera pack also includes the necessary ingredients for making video phone calls over the web as well as over regular phone lines. An Intel PC camera sits on top of the PC's monitor and serves as the center of the Create & Share software suite.

The software suite includes all of the following applications: The Guided Tour introduces the capabilities of the camera pack. The Launcher and The Gallery make it easy to organize snapshots and

Recorder is an easy way to record a short video or take an instant snapshot with just a few mouse clicks—snapshots that can personalize Christmas cards or calendars. PhotoEnhancer quickly and easily enhances images captured from the PC camera. NetCard enables postcards with pictures and sound to be e-mailed. Other applications permit morphing, stretching, and shrinking images.

The Intel Camera Packs are available for systems with a Pentium-processor-based PC running at 90 MHz and higher; Windows 95; 16 MB RAM; an 800 × 600 display; 16-bit color; 16-bit SoundBlaster-compatible sound system with microphone and speakers; a 4× CD-ROM drive; approximately 75MB free hard disk space; an Internet service Provider that supports TCP/IP; and a 28.8 K (or faster) modem.

Three versions of the camera pack are available: The USB version retails for \$199; the PCI version sells for \$299; and the PCI Modem version retails for \$399.

Intel Corporation

2200 Mission College Blvd.


P.O. Box 58119

Santa Clara, CA 95052-8119

Web: www.intel.com

Automotive Tester

ADVANCED FUNCTIONS AND features in demand for diagnosing and troubleshooting auto and truck problems are available in the Model 488 Digital Multimeter. The handheld meter (measuring $8\frac{1}{2} \times 4\frac{1}{4} \times 2$ inches and weighing under 21 ounces) tests and measures AC/DC volts, amps, and ohms under the hood or under the dash. With the inductive pick-up probe attached, it performs rpm/tach readings for both vehicles with or without distributors. In addition, the frequency function tests engine sensors, ABS, and other automotive systems. The temperature reading function gives readings in Celsius and Fahrenheit, making

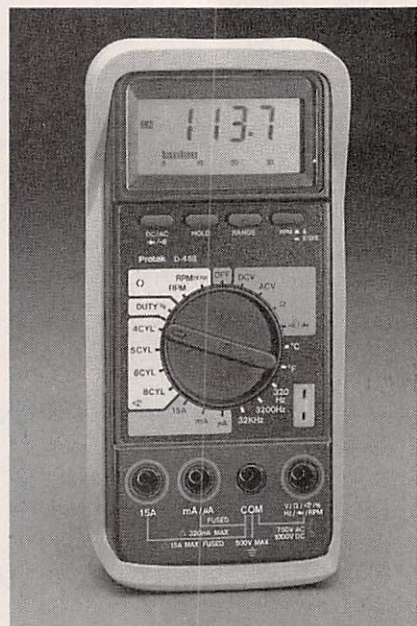

CIRCLE 21 ON FREE INFORMATION CARD

conversion charts unnecessary when servicing foreign autos.

The easy-to-read LCD display provides a 3 $\frac{3}{4}$ -digit, 3200-count readout, and the Data-Hold function freezes readings for future reference. Continuity, diode test, duty cycle, and dwell measurements are standard features. The D-488 also tests and measures ignition and engine systems; sensors, solenoids, and components; coils, diodes, and alternators; charging systems; and cooling, heating, and lighting systems. An "auto-power-off" feature extends battery life.

The Model D-488 digital multimeter comes complete with test leads, alligator clips, temperature probe, rpm pick-up, battery, manual, rubber holster, and carrying case. It retails for \$179.

HC Protek

154 Veterans Drive
Northvale, NJ 07647
Tel: 201-767-7242
Fax: 201-767-7343

Data Radio

THE MFJ-8631 IS A DEDICATED data transceiver for the 220-MHz band that operates on a factory-installed frequency 223.700 MHz. It has all the features of the 2-meter version and provides up to 3-watts output. This transceiver allows users to get away from the crowded 2-meter band and opens up the 220-MHz band for high-performance packet use. All data rates from 1200 to 9600 baud can be run directly out of the box.



CIRCLE 22 ON FREE INFORMATION CARD

Compatible with all TNCs having hardware DCDs as well as with most that have software DCDs, the MFJ-8631 is ready to use as soon as an appropriate TNC cable and 12-VDC is plugged in, and the antenna is set up. Its five-watt output covers your operating area without disrupting distant nodes.

Features include ultra-fast PIN-diode switching, instantaneous change-over between transmit and receive, a dual-conversion receiver, 0.25 μ V low-noise preamp, and a double-tuned front-

end. The narrow 10.7 MHz IF filter and special full data-bandwidth IF filter provides an optimum passband and steep skirts for error-free data reception. Unquenched audio feeds directly to the TNC for lightning-fast DCD response. Plug-in crystals for other frequencies and pre-wired cables are available as add-ons.


The tiny MFJ-8631 (5- \times 5- \times 1 $\frac{1}{2}$ -inches) draws just 15 mA on receive and less than 1 amp on transmit on 12-VDC, and it retails for \$139.95.

MFJ Enterprises, Inc.

300 Industrial Park Road
Starkville, MS 39759
Tel: 800-647-1800 or 601-323-5869
Fax: 601-323-6551

Embedded Controller Board

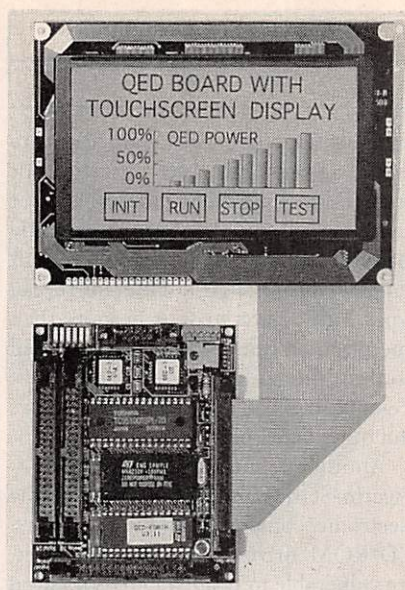PACKING DATA ACQUISITION, control, and a touch-screen-user interface on a palm-sized surface-mount board, the QED board is easily programmable in C, Forth, or Assembly using any PC. Built-in programming tools include an interactive debugger, multi-tasking, executive and comprehensive libraries of device-driver functions—including drawing and plotting functions



CIRCLE 23 ON FREE INFORMATION CARD

for the 128 \times 240 pixel touch-screen/graphics display with which the board directly interfaces.

The QED board is ideal for a wide range of applications, including machine automation, data acquisition, industrial control, robotics, and scientific instrumentation. Because of its small size,

(Continued on page 31)

One Touch Auto Set-Up

100MHz and 200MHz Analog Oscilloscopes

$\pm 2\%$ Accuracy
Save & Recall
Up To 32
Panel Settings



3 Year Product Warranty

Model SS-7821, 200 MHz Bandwidth - \$2,995.
Model SS-7811, 100 MHz Bandwidth - \$1,795.

Featuring... 3-CH, 8 Traces • 2m V/div Sensitivity • Full TV Trigger with Field and Line Select
• 5 Digit Frequency Counter • Cursor Measurements with CRT Readouts • Fine Adjustment Modes
• Auto Probe Readout, CH-2 Output • Z-Axis Input • Bright, Sharp, 6" Meshless CRT • Built-in Diagnostics.

Also available: 400 MHz & 470 MHz models. Send for Complete Catalog

IWATSU AMERICA, Inc.

TEST & MEASUREMENT EQUIPMENT DIVISION

430 Commerce Blvd., Carlstadt, NJ 07072 • Tel: (201) 935-8486 • Fax: (201) 935-8533

WebSite: <http://www.iwatsu.com> • e-mail: iwatsu@access.digex.net

CIRCLE 134 ON FREE INFORMATION CARD

SERVICE CLINIC

continued from page 18

unit back together. Most connectors are keyed against incorrect insertion or unintentional interchange of cables, but that's not always the case. Apparently identical screws might have different lengths or have slightly different thread types. Little parts may fit in more than one place or orientation. Try using pill bottles, 35mm film canisters, and plastic ice-cube trays to sort and store screws and other small parts.

Another consideration is ESD—Electro-Static Discharge. Some of the electronic components in CD players, CD-ROM drives, and similar devices, are vulnerable to ESD. There is no need to go overboard, but taking reasonable precautions like not wearing clothing made of wool, which tends to generate static, is a good idea. When working on component CD and laserdisc players, get into the habit of touching a ground, like the metal chassis, before touching any circuit components. An anti-static wrist strap is another good idea.

A basic set of precision hand tools should be all that you will need to disassemble a CD player and perform most adjustments. Needed tools include a selection of Philips and straight-blade screwdrivers, needle-nose pliers, wire cutters, tweezers, and dental picks. A jeweler's screwdriver set is a must, especially if you plan to work on a portable unit. For adjustments, a miniature ($1/16$ -inch blade) screwdriver with a non-metallic tip is desirable (the non-metallic tip prevents the screwdriver from detuning the circuit as you make your adjustments).

Unless you get into optical alignment of the laser assembly, no special tools will be needed, and the service manual will indicate what you do need if you are faced with that kind of repair. A low-wattage fine-tip soldering iron and fine rosin-core solder will handle any soldering or desoldering that needs to be done along the way.

For thermal or warm-up problems, a can of "cold spray" or "circuit chiller," and a heat gun or blow drier can come in handy. Use them to locate thermally sensitive parts that are causing problems. Use the extension tube of the spray can and make a cardboard nozzle for the heat source to provide precise control of which components you are affecting.

That wraps it up for this time. Until next month, if you have any specific problems or questions, you can reach me by e-mail at sam@stdavids.picker.com. For general information on electronics troubleshooting and repair visit my Web site at www.repairfaq.org. **EN**

LETTERS

continued from page 5

tricity beyond the abilities of the grid, and power-plant construction will have to mushroom to keep up. I know there are other ways to generate electricity that are non-, or at least not as polluting, but they are dwindling and not expanding. No new nuclear reactors have been commissioned for over a decade, the hydroelectric situation is even worse, solar is not an option due to poor efficiency, and geothermal cannot supply enough to handle even a fraction of the added load.

The one solution to this problem is the Hybrid Vehicle, in which the size of the internal combustion engine is reduced and attached to a generator. The batteries are used for acceleration and hill-climbing assistance. The emissions of this type of vehicle are greatly reduced by increasing efficiency and not overpowering the power plant to accelerate the car. Most charging would be handled by the motor/generator combination, thus only using the grid for light charging and not for a deep charge. The battery weight could also be reduced, since it is in a supporting role only.

Thanks for your time and your ear, and by the way, I do like your magazine very much!

RICHARD PERCIFIELD
Tonganoxie, KS

Editorial Approval

Regarding the recent dialog between yourself and your readers, I thought you might want to know that, in my opinion, your editorials about the Internet are right on target. While I agree that the signal-to-noise problem on the Net/Web is a bad one, my entire research agenda is being immeasurably helped by data and contacts that I have been able to make using that valuable resource.

Keep up the good work.
FOREST M. MIMS III
via e-mail **EN**

COMPUTER CONNECTIONS

continued from page 23

PILOT DEVELOPER RESOURCES

www.wademan.com/Pilot/Program/FAQ.htm
www.massena.com/darrin/pilot/index.html
www.sis.lcs.mit.edu/raylau/pilot/
www.usr.com/palm/pilotlinks.html
www.roadcoders.com/pilot/index.html
www.shoppersmart.com/lehett/gccwin32.html
www.usr.com/palm/dresources.html
www.metroworks.com (general info)
www.metroworks.com/db/updates.qry?function=list&sw=CWPP3 (patches)
www.ingeninc.com

Newsgroups

alt.comp.sys.palmtops.pilot
comp.sys.palmtops.pilot
news.massena.com/pilot.programmer
news.massena.com/pilot.programmer.codewarrior
news.massena.com/pilot.programmer.gcc
news.massena.com/pilot.programmer.jump
news.massena.com/pilot.programmer.pila

routine that calls it, or both. The way it works now, if lots of data is streaming in, we get 100 bytes, and display 100 bytes. A more sensible solution would decrease the amount of display processing when there is lots of activity.

Related is the fact that the current routine simply copies input data from one buffer (the system's) to another (ours). If we set the system buffer to be our buffer, we could eliminate that overhead. I have resisted doing so, because I don't think there will be that much performance gain, and because we're going to end up copying data anyway to deal with the next item.

HiLo currently has no ability to store data for subsequent retrieval, analysis, and display. Dealing with the operating system's concept of databases brings a whole new layer of complexity to the application, and will undoubtedly have significant performance ramifications as well. With persistent storage in place, it might be interesting to implement live scrolling.

A limitation (that purposely hasn't been dealt with yet) is that there is no user interface for the serial port settings; 9600, 8N1 is hard-coded into the program. Not critical, but interesting is the concept of responding to serial I/O from sleep mode. There is no documented, simple way to do so. Hmmm . . .

That's all for now. Stay in touch
via e-mail; (jeff@ingeninc.com) **EN**



NEW LITERATURE

USE THE FREE INFORMATION CARD FOR FAST RESPONSE

Master Catalog—1997/1998

Jensen Tools Inc.

7815 S. 46th Street

Phoenix, AZ 85044-5399

Tel: 800-426-1194 or 602-968-6231

Fax: 800-366-9662 or 602-438-1690

Web: www.jensentools.com

Free



CIRCLE 338 ON FREE INFORMATION CARD

Featuring 300 pages of items essential to electronics and other related industries, this latest catalog is filled with tool kits for the installation, maintenance and repair of electronic equipment. Several

newly developed kits, including the JTK-3100 Aircraft Pre-Flight/Preventive Maintenance Kit, the JTK-2001 PC Workstation Plus Kit, and the JTK-2900 Network Support Kit, are introduced. Products offered for the first time are a number of test instruments, specialty tools, testers, and probes, among which are Fluke's DSP-2000 Cable Analyzer, an insulation-piercing electronics probe, a mini-flip circuit-board holding fixture

from FIL, and B&K Precision's NTSC TV generator.

A special 8-page section is devoted to Hewlett-Packard products, such as state-of-the-art electronic measuring devices, including an assortment of oscilloscopes, logic analyzers, function generators, and universal counters.

Practical RF Design Manual

by Doug DeMarw W1FB

MFJ Publishing

300 Industrial Park Road

Starkville, MS 39759

Tel: 800-647-1800 or 601-323-5869

Fax: 601-323-6551

Web: <http://mfjenterprises.com>

\$19.95

BooksNow To order books in this magazine or, any book in print. Please call anytime day or night: (800) BOOKS-NOW (266-5766) or (702) 258-3338 ask for ext. 1456 or visit on the web at <http://www.BooksNow.com/electronicsnow.htm>.

POPTRONIX®

Online
Edition

We're on the web

FREE

We are starting up,
but you can watch us grow!

Projects for beginners to experts!

New Product information!

Bookstore—discover what's new!

<http://www.poptronix.com>

WE'RE WITH YOU EVERY DAY

24 HOURS A DAY! DROP IN!

WE'D LOVE TO HAVE YOU VISIT!

MATELECTRONICS®

Over 20 years of dependable service to the industry



Call now
for FREE
116 PAGE
CATALOG!

TV/VCR PARTS · CHEMICALS
· SURVEILLANCE EQUIPMENT
· AUDIO/VIDEO
ACCESSORIES · MATV, CATV
& DSS PRODUCTS ·
MICROWAVE OVEN PARTS ·
TOOLS AND SERVICE AIDS
· BATTERIES · ANTENNAS ·
TELEPHONE ACCESSORIES ·
VIDEO GAME ACCESSORIES
· COMPUTER PARTS &
ACCESSORIES



"The On Time Electronics Distributor"



CALL TOLL-FREE
1-800-628-1118

FAX: 1-800-628-1005


MATELECTRONICS
400 Pike Road
Huntingdon Valley, PA 19006

WEB SITE: www.matelectronics.com

EMAIL: 74271.645@compuserve.com



PRACTICAL RF DESIGN MANUAL

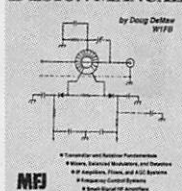

CIRCLE 339 ON FREE INFORMATION CARD

Engineers, designers, technicians, amateur radio operators, and students will find a wealth of information here about transmitter and receiver fundamentals, mixers, balanced modulators, detectors, IF amplifiers, filters, AGC

systems, frequency-control systems, small-signal RF amplifiers, large-signal amplifiers, and frequency multipliers.

The scores of useful circuit diagrams in this book are founded on practical laboratory experience. Although these circuits are not intended for exact duplication, they will function well if they are built. Many of them can be used as building blocks for composite systems in the RF-communications industry.

The reader will find no theoretical circuit examples, and there is little reference to circuits that have appeared in trade journals and manufacturer's application notes. This book is written in easy-to-understand language, without "talking down" to the reader. Equations are used only where necessary to demonstrate a particular design approach. Approximations are used where acceptable, owing to the non-uniformity found in semiconductors that are not graded for a tight set of parameters. Usually the designer has to do some finalizing of a circuit to compensate for the differences in performance of ICs or transistors that have the same part number.

QuickCross 6.0

NTE Electronics, Inc.

44 Farrand Street

Bloomfield, NJ 07003

Tel: 800-631-1250 or 201-748-5089

Fax: 800-683-3338

Web: www.ntelinc.com

Free



CIRCLE 340 ON FREE INFORMATION CARD

QuickCross is a software cross-reference to the NTE line of industry-standard replacement components and is available in Windows and DOS formats. In

addition to containing replacements for over 260,000 semiconductors, 41,000 relays, and 1386 flyback transformers, this

edition includes surface-mount resistor and capacitor selector guides.

Version 6.0 provides users with one of the most comprehensive and easy-to-use cross references of electronics components. It allows distributors, technicians, and hobbyists to easily access NTE's full line of products. To use QuickCross, the searcher simply keys in any industry device number—U.S., Japanese, or European—and in less than a second, the NTE equivalent is displayed.

QuickCross can be downloaded free from their Web site; it also can be purchased from NTE distributors for \$12.

rugged surface-mount construction, and low power requirement, it is extremely useful in many handheld applications as well.

The embedded controller provides up to 512K on-board memory and 60 I/O lines including keypad and graphic-display interfaces, time-controlled I/O, 16 analog inputs, 8 analog outputs, quad high-current drivers, and dual serial ports. Battery-backed write-protectable RAM eliminates the need for PROM burning. It is priced at \$495 in single quantities.

Mosaic Industries, Inc.

5437 Central Avenue #1

Newark, CA 94560

Tel: 510-790-1255

Fax: 510-790-0925

E-mail: info@mosaic-industries.com

Web: www.mosaic-industries.com

1998 Publications Catalog

Prompt Publications

Howard W. Sams & Company

2647 Waterfront Parkway, East Drive

Indianapolis, IN 46214-2041

Tel: 800-428-7267 or 317-298-5400

Fax: 317-298-5604

Web: www.hwsams.com

Free



CIRCLE 341 ON FREE INFORMATION CARD

Aimed at hobbyists, students, and professional technicians, the catalog presents hundreds of best-selling titles from Prompt Publications, Butterworth-Heinemann, Macmillan Computer Publishing, and UCANDO Educational Videos. Along with many new books, there are updated editions—second editions of *Real-World Interfacing with Your PC*

and of *Power Supplies*, as well as the sixth edition of *Modern Dictionary of Electronics*.

Concentrating on technical books for both the novice and the experienced electronics technician, Prompt has published more than 100 books in its first seven years, and has another 30 scheduled for 1998. Prompt's Web site provides complete book summaries, new release dates, and other information.

Some of the new publications coming out in 1998 are *Complete Guide to Audio* from Prompt; *Laser Technology*, an educational video from UCANDO; *Surface Mount Technology Terms & Concepts* from Butterworth-Heinemann; and the eighth edition of Macmillan's *Upgrading and Repairing PCs*.

Electronic Inventions and Discoveries: Electronics From Its Earliest Beginnings to the Present Day

by G.W.A. Dummer

Institute of Physics Publishing

The Public Ledger Building (U.S. Office)


Suite 1035

150 South Independence Mall West

Philadelphia, PA 19016

Web: www.iop.org

\$40

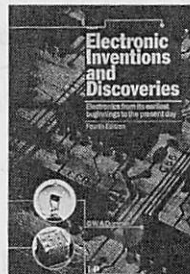

CIRCLE 342 ON FREE INFORMATION CARD

In a remarkably short time, electronics has penetrated almost every aspect of modern life. The pace shows no sign of slackening. Spanning two and a half centuries, this book traces electronics from its earliest be-

ginnings to the present day. It is a mini-encyclopedia full of valuable information on practically all inventions in electronics, as well as an up-to-date systematic review of the major developments in the field.

BooksNow

To order books in this magazine or, any book in print. Please call anytime day or night: (800) BOOKS-NOW (266-5766) or (702) 258-3338 ask for ext. 1456 or visit on the web at <http://www.BooksNow.com/electronicsnow.htm>.

EXPAND

your world with NRI

CHOOSE HANDS-ON TRAINING IN:

- PC Servicing
- Computer Programming
- Game Programming
- Multimedia Programming, and more!

NRI has new products and services we just know you won't be able to pass up — a powerful Pentium® MMX PC that you train with and keep, a new course in

Game Programming Fundamentals, great diagnostic and interactive software in our newly updated PC

Servicing course, and an all-new Computer Programming course featuring in-depth coverage of your choice of popular languages.

PC Servicing

In NRI's PC Servicing course, you'll become acquainted with the Internet, perform actual experiments with today's most sophisticated diagnostic tools, and experiment with NRI's exclusive labs: computer-aided electronics demonstrations, 8085 Microprocessor, and NRI Discovery Lab, a complete breadboarding system. With the active support of helpful

The Computer Programming and PC Servicing courses feature the Pentium® 200 MMX PC, Norton Interactive CD-ROM, and a guaranteed Windows 98 upgrade.

NRI instructors, this course will also help you prepare for the A+ certification exam, with updated lessons and interactive tutorial.

Computer Programming

Whatever your previous experience, NRI's Computer Programming course gives you the hands-on training you need to compete in today's high-tech marketplace. Step by step, you acquire basic skills and master more complex programming design concepts and techniques, ultimately focusing in depth on your choice of languages: Visual Basic, C++, or Java.

The Pentium® 200 MHz PC

- MMX™ technology
- 16 meg RAM
- 1.6 gigabyte hard drive
- VGA color monitor
- 8X CD-ROM drive
- 16-bit sound card
- 33,600 baud fax/modem



Game Programming Fundamentals

Learn programming the easy way in this new course featuring graphic simulations, animation, and sound effects. Not only will you learn the fundamentals of game programming, but you'll also gain an in-depth understanding of your choice of programming languages: Visual Basic, C++, or Java. An exploding field in programming, computer gaming has a strong and growing market among the MTV-generation. This course teaches you how a popular computer game was written, from storyboarding to coding. In addition to covering game design, performance, and debugging, you'll gain hands-on experience as you make direct modifications to the game itself.

Please note: You must own a PC and be computer literate in order to take this program. A personal computer is not included.

SEND TODAY FOR YOUR FREE CATALOG!

NRI Schools

4401 Connecticut Avenue, NW • Washington, DC 20008

☒ Check for a free catalog.

- ☐ PC Servicing
- ☐ Computer Programming Fundamentals
- ☐ Game Programming
- ☐ Networking with Windows NT
- ☐ Desktop Publishing with PageMaker
- ☐ Multimedia Programming
- ☐ Mastering Microsoft Office
- ☐ PC Applications Specialist
- ☐ Electronic Music Technology
- ☐ Bookkeeping and Accounting

Or call
1-800-321-4634

Ext. 3001

OR GET YOUR AAS DEGREE!

- ☐ Accounting
- ☐ Business Management
- ☐ Computer Science
- ☐ General Studies

Name (please print)

Age

Address

City

State

Zip

A Division of The McGraw-Hill Companies



Accredited Member, Distance Education and Training Council

4702-0498

Watch your job prospects rise with NRI's innovative PC training

Businesses everywhere promise solid employment prospects for people with the skills to create software for a Windows environment, program multimedia applications, or set up office networking systems. Now, you can prepare for success in today's hottest PC careers with your choice of NRI's innovative new courses:

Networking with Windows NT

Networking has revolutionized the workplace. Now you can make it your specialty! NRI's Networking with Windows NT course enables you to earn top dollar setting up network foundations with Windows NT 4.0, the leading server in terms of power, usability, and integration. This comprehensive course gives you the skills to install, maintain, troubleshoot, and adapt the kind of networks today's businesses need to operate efficiently.

Desktop Publishing with PageMaker™

Today, businesses of every kind need skilled desktop publishers to create eye-catching, result-



getting publications. And now, NRI has just updated its popular desktop publishing course to feature today's most sought-after software, Adobe PageMaker 5.0. NRI's course moves from the basics of design to the intricacies of electronic publishing and the Internet, giving you the complete know-how you need to succeed in a new career or an exciting home-based business.

Multimedia Programming

You can create the kinds of contemporary multimedia programs that make everything — from shopping to educa-

tion to business presentations — easier and more exciting. NRI's newest programming course helps you bring text and graphics to life with sound, animation, and photo-quality images. As you become skilled with the professional-level Asymetrix ToolBook authoring software included in your course, you'll be able to add drama and impact to all your computer applications, ultimately creating the kinds of dynamic programs that will put you at the forefront of multimedia technology.



SEND POSTAGE-PAID CARD FOR YOUR FREE CATALOG!



NO POSTAGE
NECESSARY
IF MAILED
IN THE
UNITED STATES

BUSINESS REPLY MAIL

FIRST CLASS MAIL PERMIT NO. 10008 WASHINGTON, D.C.

POSTAGE WILL BE PAID BY ADDRESSEE

NRI Schools

4401 CONNECTICUT AVENUE NW
WASHINGTON DC 20078-3543



Mastering Microsoft Office

Learn the ins and outs of Microsoft Office Pro, today's most popular software suite. This comprehensive course, which includes a Pentium® 166 multimedia PC, features an innovative combination of easy-to-follow lessons, online tutorials, and hands-on projects so that you can use Office's word processing spreadsheet, database management, and other applications like a pro!

NEW!

PC Options Plan — Keep up with late-breaking advances in technology by upgrading your computer system at special student rates. It's NRI's state-of-the-art guarantee!

This book is an essential reference for engineers wishing to broaden their knowledge, and provides a sound background for students, hobbyists, and general science readers. The first section presents concise but comprehensive histories of developments in the major areas of electronics: transistors, audio and sound, radio, television, computers, robotics, and in business applications. Inventions are categorized both by subject and chronologically, with concise descriptions of over 1000 key inventions.


Acronyms and abbreviations are explained, and there are complete bibliographies of books on inventors and inventions.

Analog Dialogue: Volume 31-1

Analog Devices, Inc.
Ray Stata Technology Center
804 Woburn Street
Wilmington, MA 01887
Tel: 800-ANALOGD or 617-937-1428
Fax: 617-821-4273
Web: <http://www.analog.com/publications/magazines/Dialogue/dialog.html>

Free

Analog Dialogue

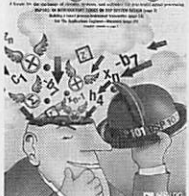

CIRCLE 343 ON FREE INFORMATION CARD

Analog Dialogue is a forum for the exchange of information on circuits, systems, and software for real-world signal processing. Feature articles include "DSP101"—Part One of a multi-part introductory series

on DSP system design, "Selecting Mixed-Signal Components in Digital Communication Systems," and "Build a Smart Analog Process-Instrument Transmitter."

In other articles, recently-released amplifiers, buffered switches and multiplexers, A/D and D/A converters, and power-management supervisory circuits are described; and sources of information for further information are suggested, such as data sheets, newsletters, and application notes.

EN

BooksNow

To order books in this magazine or, any book in print. Please call anytime day or night: (800) BOOKS-NOW (266-5766) or (702) 258-3338 ask for ext. 1456 or visit on the web at <http://www.BooksNow.com/electronicsnow.htm>.

NEW PRODUCTS

continued from page 25

rugged surface-mount construction, and low power requirement, it is extremely useful in many handheld applications as well.


The embedded controller provides up to 512K on-board memory and 60 I/O lines including keypad and graphic-display interfaces, time-controlled I/O, 16 analog inputs, 8 analog outputs, quad high-current drivers, and dual serial ports. Battery-backed write-protectable RAM eliminates the need for PROM burning. It is priced at \$495 in single quantities.

Mosaic Industries, Inc.

5437 Central Avenue #1
Newark, CA 94560
Tel: 510-790-1255
Fax: 510-790-0925
E-mail: info@mosaic-industries.com
Web: www.mosaic-industries.com

Speech Recognition Kits

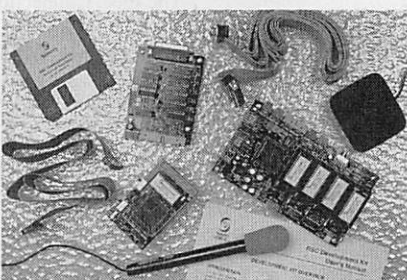TWO SPEECH RECOGNITION kits from Sensory, the RSC Development Kit 2.2 and the Interactive Speech Demonstration Unit, allow designers to integrate speech recognition into consumer telephony and electronic applications.



CIRCLE 24 ON FREE INFORMATION CARD

The RSC Development Kit 2.2 contains a complete package of hardware and software tools, including a development board, an in-circuit emulator, and a memory board. It gives designers unlimited access to Sensory's speech and audio-technology libraries so they can develop custom programs using the company's RSC-164 and RSC-164i Interactive Speech Chips.

The Interactive Speech Demonstration Unit is intended to showcase Sensory's speech recognition and audio capabilities through a series of interactive demonstrations. The unit comes complete with all necessary hardware components and pre-programmed ROMs to

provide real-life demonstrations of low-cost speech recognition, including voice dialing, voice password, and speaker-dependent and speaker-independent applications.

The development and demonstration kits have several new speech-technology capabilities, including higher accuracy and enhanced filtering software. The continuous listening feature allows compete hands-free and eyes-free product operation. A product will continuously listen for pre-programmed command words and carry out the associated tasks upon recognition. The kits also feature consecutive-digit speech recognition for speaker-dependent and speaker-independent technologies. Enhanced noise-filtering software improves recognition rates by over 97%.

The RSC Development Kit sells for \$3200, and includes all the necessary hardware and software to integrate an RSC chip into a product or project. The Interactive Speech Demonstration Unit sells for \$300. Current owners of earlier versions of the kits can purchase upgrades for \$50 and \$30 respectively.

Sensory, Inc.

521 East Weddell Drive
Sunnyvale, CA 94089
Tel: 408-744-9000
Fax: 408-744-1299
Web: www.SensoryInc.com

EN

MULTIMEDIA on the PC!



What is Multimedia? What can it do for you? It can do lots of nice things! This 184-page book helps you create your own multimedia presentation.

Multimedia applications by people like you can revolutionize educational and business applications as well as bring more FUN, FUN, FUN into your leisure computer activities.

Mail coupon to:

Electronics Technology Today, Inc.
P.O. Box 240
Massapequa Park, NY 11762-0240

Please send me my copy of *Multimedia on the PC* (PCP120). I enclose a check or money order for \$18.95 to cover the book's cost and shipping-and-handling expenses. NY state resident must add local sales tax.

Name

Address

City State Zip

All orders must be paid in U.S. funds only. Sorry, no orders accepted outside of USA and Canada. Please allow 6-8 weeks for delivery.

MA02

RETAILERS THAT SELL OUR MAGAZINE MONTHLY

California

California Electronics
221 N. Johnson Ave.
El Cajon, CA 90202

Ford Electronics
8431 Commonwealth Avenue
Buena Park, CA 90621

All Electronics
14928 Oxnard Street
Van Nuys, CA 91411

Gateway Electronics of CA
9222 Chesapeake Drive
San Diego, CA 92123

Mac's Electronics
191 South "E" Street
San Bernardino, CA 92401

Electronics Warehouse
2691 Main Street
Riverside, CA 92501

Orvac Electronics
1645 E Orangethorpe Ave.
Fullerton, CA 92631

Sav-On Electronics
13225 Harbor Blvd.
Garden Grove, CA 92643

JK Electronics
6395 Westminster Blvd.
Westminster, CA 92683

Kandarian Electronics
1101 19th Street
Bakersfield, CA 93301

Whitcomm Electronics
105 W. Dakota #106
Clovis, CA 93612

Minuteman Electronics
37111 Post St., Suite 1
Fremont, CA 94536

HCS Electronics
6819 S. Redwood Drive
Cotati, CA 94931

Halted Specialties Co.
3500 Ryder Street
Santa Clara, CA 95051

Metro Electronics
1831 J Street
Sacramento, CA 95814

HSC Electronics
4837 Amber Lane
Sacramento, CA 95841

Colorado

Gateway Electronics of CO
2525 Federal Blvd.
Denver, CO 80211

Centennial Electronics
2324 E. Bijou
Colorado Sps., CO 80909

Connecticut

Cables & Connectors
2198 Berlin Turnpike
Newington, CT 06111

Electronic Service Prod.
437 Washington Avenue
North Haven, CT 06473

Georgia

Norman's Electronics, Inc.
3653 Clairmont Road
Chamblee, GA 30341

Illinois

Tri State Elex
200 W. Northwest Hwy.
Mt. Prospect, IL 60056

Kansas

Electronic Hobby Shop
309 E. McKay
Frontenac, KS 66763

Maryland

Mark Elec. Supply Inc.
5015 Herzel Place
Beltsville, MD 20705

Amateur Radio Center
1117 West 36th Street
Baltimore, MD 21211

Massachusetts

U-Do-It Electronics
40 Franklin Street
Needham, MA 02194

Michigan

Purchase Radio Supply
327 East Hoover Avenue
Ann Arbor, MI 48104

Norwest Electronics
33760 Plymouth Road
Livonia, MI 48150

The Elec. Connection
37387 Ford Road
Westland, MI 48185

Elec. Parts Specialists
711 Kelso Street
Flint, MI 48506

Minnesota

Acme Electronics
224 Washington Avenue N.
Minneapolis, MN 55401

Missouri

Gateway Electronics Of MO
8123-25 Page Blvd.
St. Louis, MO 63130

New Jersey

Lashen Electronics Inc.
21 Broadway
Denville, NJ 07834

New York

R&E Electronics
4991 Rt. 209
Accord, NY 12404

Unicorn Electronics
Valley Plaza
Johnson City, NY 13790

Ohio

Philcap Electronic Suppliers
275 E. Market Street
Akron, OH 44308

Oregon

Norvac Electronics
7940 SW Nimbus Avenue
Beaverton, OR 97005

Taztronics
257 N. Wasson St.
Coos Bay, OR 97420

Pennsylvania

Business & Computer Bookstore
213 N. Easton Road
Willow Grove, PA 19090

Texas

Mouser Electronics
958 N. Main Street
Mansfield, TX 76063

Tanner Electronics
1301 W Beltline
Carrollton, TX 75006

Electronic Parts Outlet
3753 B Fondren
Houston, TX 77063


Electronic Parts Outlet
17318 Highway 3
Webster, TX 77598

Washington

Amateur Radio Supply Co.
5963 Corson Ave., Ste 140
Seattle, WA 98108

**If you'd like to sell our magazine in your store,
please circle 210 on Free Information Card.**

BUILD THE DATA MONITOR

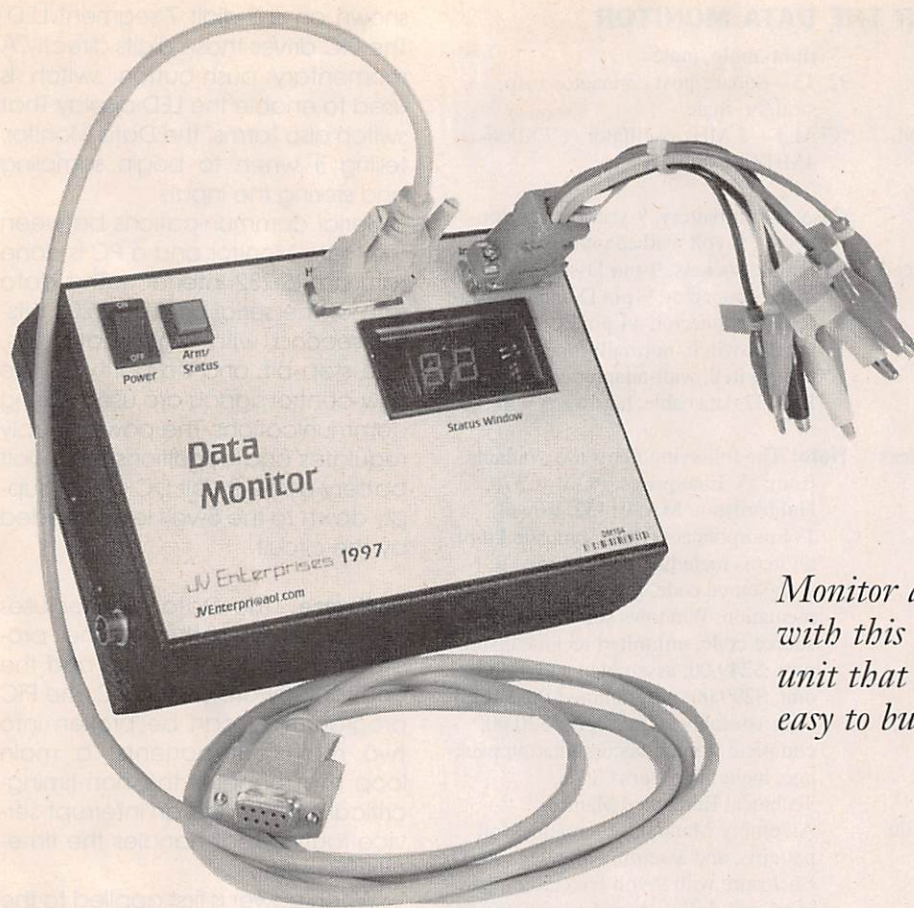

*Monitor and record events
with this sophisticated
unit that is both
easy to build and use.*

JON VARTERESIAN

Imagine how useful it would be to be able to monitor and record information about your environment for extended periods of time without having to be physically there. With a variety of input sensors, you could analyze the temperature of your attic to see if you really needed those ridge vents. You could count the number of people that came in and out of your store, and when each one entered and left, for weeks at a time. You could monitor the relative humidity or pressure of your lab or home. You could monitor the voltage and current output of your latest solar-cell project. You could even count the squirrels opening your squirrel feeder. The uses for such a monitoring device are only limited by the imagination. Now imagine how useful such a device would be if it could be run from either battery or AC power and didn't need to be tied to a PC to store information.

The Data Monitor described in this article is just such an instrument.

It is highly configurable, low in cost, and easy to use. It can monitor and store up to four analog and four digital inputs at the same time. The sampling rate can be set anywhere from 30 milliseconds to more than 49 days. There is also an eight-term complex trigger that can include up to four digital and four analog inputs. All of the information is recorded in an electrically-erasable programmable read-only memory module (EEPROM) that has a capacity of 2048 words. The EEPROM is extremely error tolerant and can hold onto any data that has been stored in it even if the power is turned off or lost. Each sample has a time and date stamp included in order to protect the integrity of the data. That makes it easy to analyze any data that has been stored over a long period of time.

The Data Monitor is set up using an easy-to-use Windows-based program. Once it has been set up, the Data Monitor runs by itself. When the sample and store process

is complete, the same program is then used to retrieve all of the data that has been collected. The only computer requirements for using the Data Monitor is a PC that is running either Windows 3.1 or Windows 95 and has an available COM1 or COM2 serial port.

The Data Monitor's hardware can monitor and record almost any electronic or electrical circuit through the use of plug-in personality modules. An accompanying article details the building of a general-purpose personality module that includes four digital and three analog inputs. Also included is a temperature sensor that uses the Data Monitor's fourth analog input. Although not needed to test the Data Monitor, building that personality module is a good idea and is very handy for testing the various functions of the Data Monitor.

How it Works. The heart of the Data Monitor is a PIC16C74 microcontroller, which controls all of the functions of the unit. That particular

PARTS LIST FOR THE DATA MONITOR

SEMICONDUCTORS

IC1—PIC16C74 microcontroller, programmed (Microchip)
 IC2—24LC16B/P 16K serial EEPROM, integrated circuit (Microchip)
 IC3—MAX232CPE RS-232 converter, integrated circuit (Maxim)
 IC4, IC5—Not used
 IC6—LM340T 5-volt regulator, integrated circuit
 D1, D2—1N4001 silicon diode
 Q1, Q2—FMMT3904 NPN transistor, SOT-23 package

RESISTORS

(All resistors are 1/4-watt, 5% units unless otherwise noted.)
 R1, R3, R17—R20, R25, R26—10,000-ohm
 R2—10-ohm
 R4—not used
 R5—12,100-ohm, 1%, metal-film
 R6—4020-ohm, 1%, metal-film
 R7, R8—not used
 R9—16—91-ohm
 R21—R24—not used

CAPACITORS

C1, C2—15-pF, axial ceramic
 C3, C6, C7, C10—0.1-μF, axial ceramic
 C4, C5, C8, C9—1-μF, 63-WVDC, electrolytic
 C11—0.22-μF, axial ceramic
 C12—10-μF, 25-WVDC, electrolytic

ADDITIONAL PARTS AND MATERIALS

DISP1—LN524 2-digit 7-segment light-emitting diode display, common cathode (Digi-Key P355-ND or similar)
 J1, J4, J5—Square-post connector strip,

right-angle, male

J2, J3—Square-post connector strip, straight, male

XTAL1—4-MHz oscillator (CTX006-4MHZ or similar)

Case, 9-volt battery, 9-volt battery connector, 9-volt wall adapter, square-post female sockets, 9-pin D-subminiature male, connector, 9-pin D-subminiature female connector, 44-pin PLCC socket, toggle switch, normally-open momentary switch, wall-adapter connector, RS-232 data cable, hardware, wire, etc.

Note: The following items are available from: JV Enterprises, PO Box 370, Hubbardston, MA, 01452. E-mail: JVEnterpri@aol.com: Complete kit of all items including programmed IC1 with source code, manuals and documentation, Windows software with source code, unlimited technical support, \$249.00; assembled and tested unit, \$299.00; programmed PIC16C74 with assembly source code, \$20.00; complete printed documentation package, including Users Guide, Technical Reference Manual, Assembly Manual, schematics, foil patterns, and assembly drawing, \$9.00; Enclosure with 9-volt battery compartment and drilling template, \$20.00; PC board with silk-screen, plated holes, and solder mask, \$13.50; Windows software with source code, \$29.00. Please add \$7.00 shipping and handling for complete kit and assembled unit; \$5.00 for all other orders. Massachusetts residents must add 5% sales tax. Check or money order only.

Electronics Now describes a general-purpose personality module that will get you started with the Data Monitor. That add-on device will provide four digital inputs, three analog inputs, and one temperature-measurement input.

Data is stored and retrieved from the EEPROM using a two-wire technique called the Inter-I²C (or IIC) protocol. That method was developed by Philips and Signetics. Although an "enhanced" specification that allows data transfers at a rate of 400,000 bits per second is supported by the EEPROM, the Data Monitor follows the 100,000 bits-per-second rate that was established by the original specification. See the sidebar for a technical overview of the IIC protocol.

Status for the Data Monitor is

shown on a 2-digit 7-segment LED. The PIC drives those digits directly. A momentary push-button switch is used to enable the LED display. That switch also "arms" the Data Monitor, telling it when to begin sampling and storing the inputs.

Serial communications between the Data Monitor and a PC is done with an RS-232 interface. The data rate of the serial port is 19,200 bits-per-second with eight data bits, one stop bit, and no parity bit. No flow-control signals are used during communications. The power supply regulates and conditions the 9-volt battery or the 9-volt DC power supply down to the 5-volt level needed by the circuit.

Software. The Data Monitor uses two types of software: the programming in the PIC chip and the control software on the PC. The PIC programming can be broken into two main components: a main loop that handles the non-timing-critical events, and an interrupt-service routine that handles the time-critical events.

When power is first applied to the Data Monitor, the PIC program initializes all of its internal variables and waits for configuration information to be sent through the RS-232 port from the PC. While waiting, the Data Monitor's system voltage is monitored. That lets the battery voltage be checked at any time. Once the configuration data is sent to the Data Monitor, it is written to the EEPROM. When the arm switch is pressed, the Data Monitor begins sampling and storing data based on the user-supplied parameters. Once sampling has begun, the percentage that the EEPROM is full is also calculated. Any information that needs to be sent over the RS-232 link to the PC is also done.

The interrupt-service routine does two functions. The first function is to run the PIC's internal clock. Each "tick" of the clock is one millisecond. That means that anything that the interrupt-service routine is doing must be finished in less than one millisecond, or the next tick will be missed, messing up the Data Monitor's real-time clock. The other section services the RS-232's receive interrupt. That section takes care of all of the


member of the PIC microcontroller family has several features built into it that make it particularly attractive for use in the Data Monitor. Two of the features that help reduce the number of components in the circuit are a serial-interface controller and an 8-channel 8-bit analog-to-digital converter.

As mentioned above, analog and digital inputs are supplied to the unit through a plug-in "personality module." That module contains circuitry that can interface, buffer, or modify any input signals before they are passed to the Data Monitor itself. Although the design and construction of a personality module will not be discussed here, the article "Build this I/O-Temperature Personality Module" found elsewhere in this issue of

The Data Monitor is controlled by a Microsoft Windows program. With it, the Data Monitor is prepared for sampling, and the stored information is retrieved. When configuring the Data Monitor, you can say what combination of analog and digital inputs are to be stored, whether to average the analog samples or not, how many samples to include in any averaging, set the rate that the Data Monitor takes samples,

Most of the controls are self-explanatory. However, the trigger equation can become complex so some explanation is in order. Depending on your needs, the trigger equation can be used to set up any type of triggering condition from the very simple to the extremely complex. The format of the trigger equation is as follows:

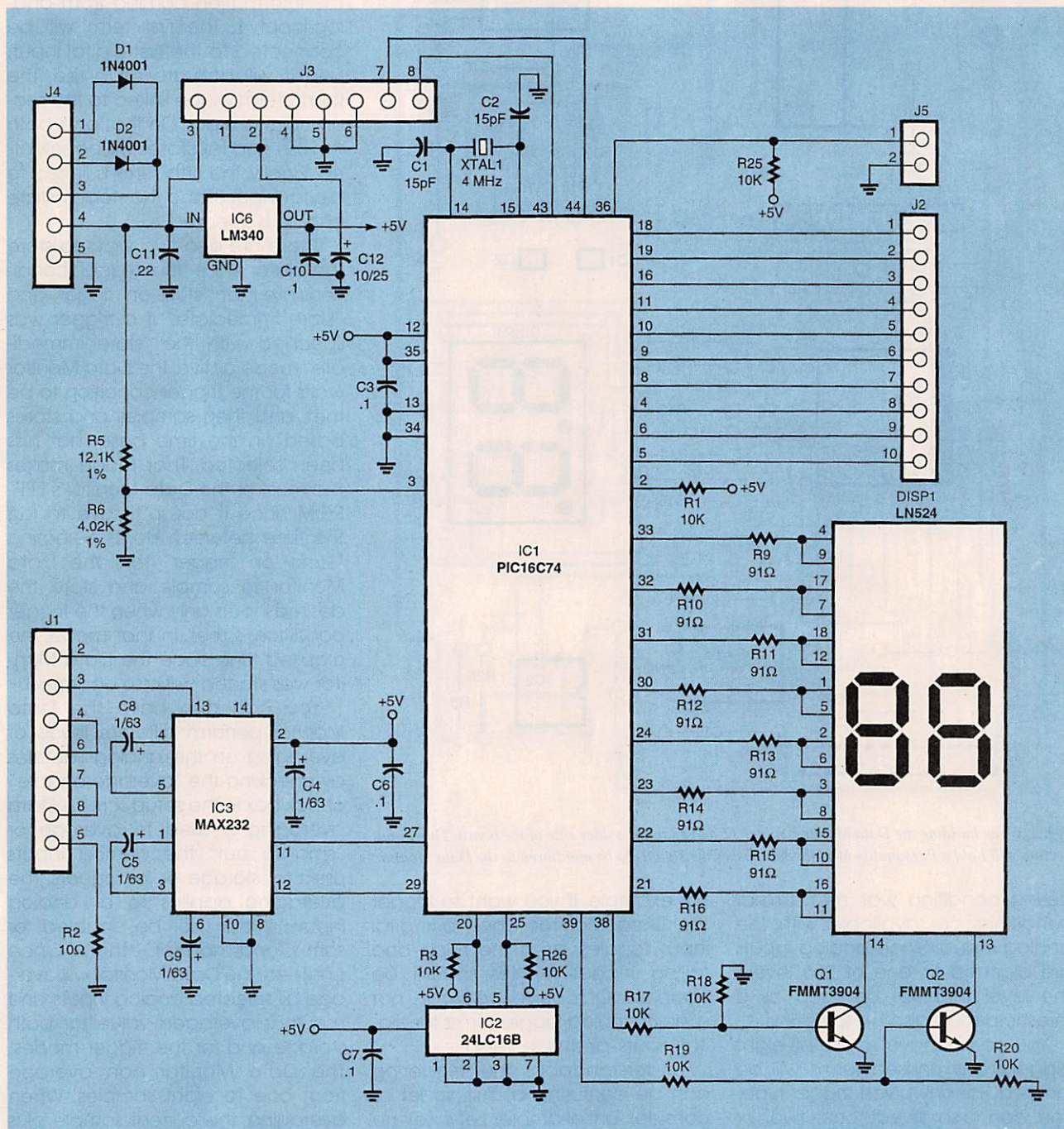The "&" is a logical AND and the "#" is a logical OR. Each of the eight trigger terms can be linked to any one of the analog or digital inputs, along with one or more trigger modes. With a digital input, the trigger can become active when the input is rising, falling, or at the same level it was before the overall tri-



April 1998, Electronics Now

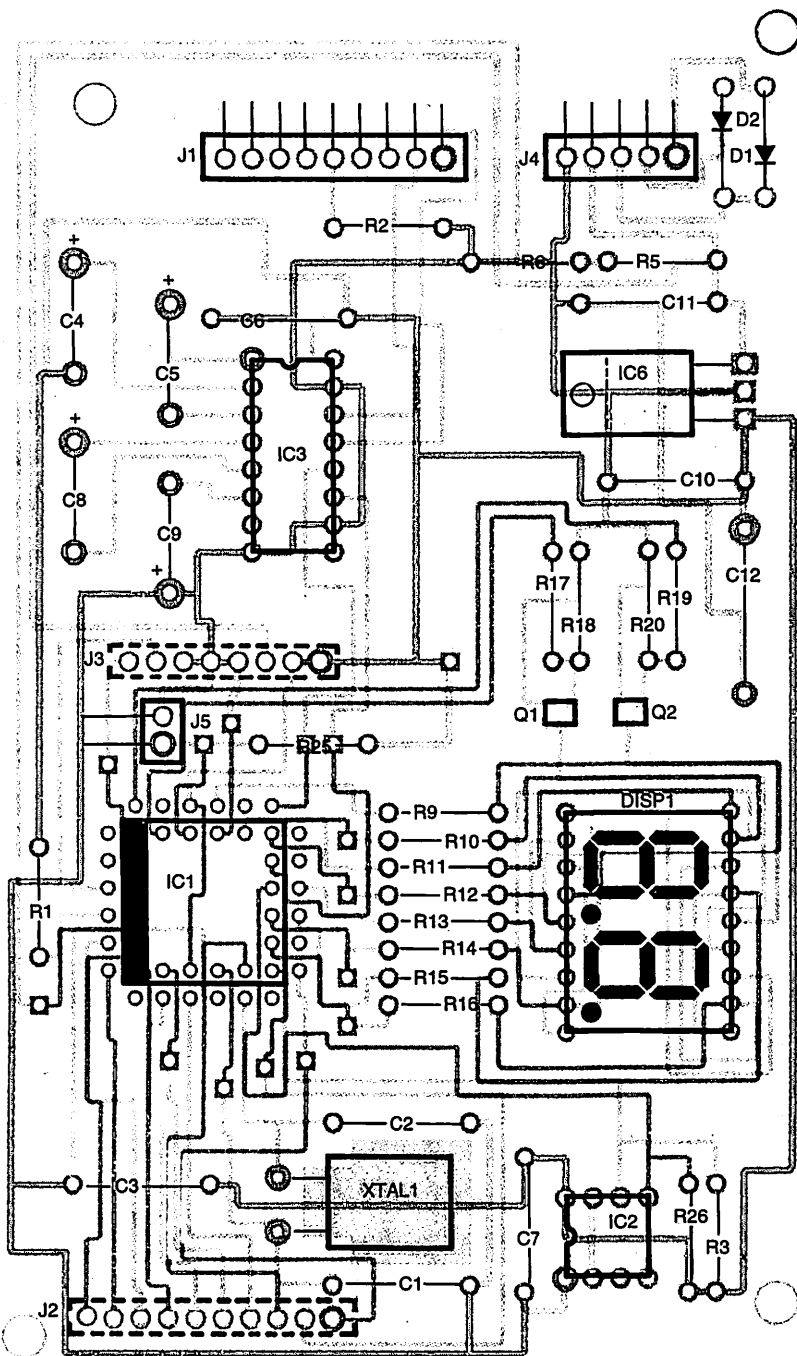


Fig. 2. When building the Data Monitor, solder J2 and J3 to the solder side of the board. Those connectors will hold a Personality Module that passes the signals to be monitored to the Data Monitor.

gering condition was met. Similar conditions are available with the analog inputs. Since analog inputs are digitized to one of 256 levels, the level that will be used as a threshold must also be specified.

You do not have to use all eight triggers; any unused terms will be ignored. For any given trigger type, you can also select one, two, or even all three of the trigger modes that are linked to a particular input.

For example, if you want to trigger the Data Monitor when a digital input toggles, both the rising and falling trigger modes should be enabled. Of course, you can not specify analog trigger terms for digital inputs, and *vice versa*.

Understandably, the triggering can be confusing at first, so let us consider an example. Let's set up the Data Monitor to store the ambient temperature from a sensor con-

nected to analog-input 1 whenever any of the following conditions are met: digital-input 1 rises or digital-input 2 toggles while digital-input 3 is high. We'll use trigger terms 1, 4, and 5. Remember, terms 1, 2, and 3 are linked together according to the logic formula given above. Similarly, terms 4, 5, and 6 are also linked together. Note that all other trigger terms are left unused so that they will be ignored.

The Data Monitor will only store the information coming from analog-input 1. The first term will be connected to the first digital input, and it will activate on a rise. The fourth term will be linked to the second digital input. On that one, both the rise and fall states will be selected. Finally, the fifth term is linked to digital-input 3, and the steady-state choice is selected.

There are also two ways to store the data once the trigger conditions are met: "store on trigger" and "store immediate." If a trigger was specified with the "store immediate" mode active, the Data Monitor waits for the trigger condition to be met, and then samples and stores based on the time base that has been selected. That mode makes the most of the Data Monitor's EEPROM since it doesn't have to log the time between stores. Selecting "store on trigger" tells the Data Monitor to sample and store the desired inputs only when the trigger condition is met. In that mode, the elapsed time since the Data Monitor was started will also be stored.

You can also have the Data Monitor perform different levels of averaging on the analog samples by checking the "average enable" check box in the setup screen. Data averaging is used to average or "smooth out" the analog inputs used for storage or for triggers. The averaging applies to all analog inputs; it can not be enabled for some and not for others. Once enabled, the Data Monitor will average all selected analog inputs and use that averaged value for both storage and for the trigger modes. The Data Monitor can average from one to eight samples. When averaging, the current sample plus the last several samples are used. For example, if eight samples are to

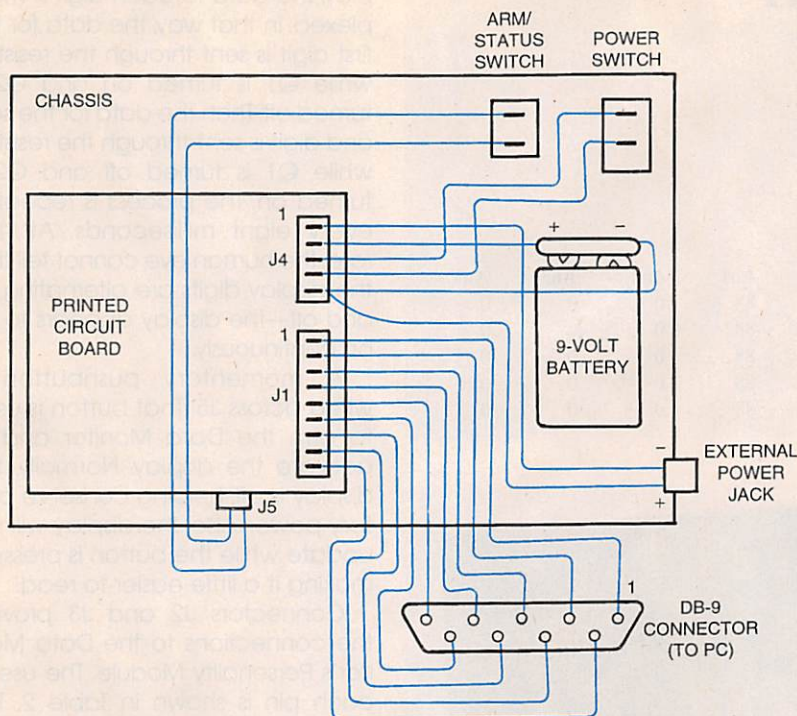


Fig. 3. Use extra care when wiring the Data Monitor's power connector. A mistake here can destroy the unit when power is applied.

TABLE 1

Sample No.	Input Value	Output (Averaging=2)	Output (No Averaging)
1	0	$([0]+0) \div 2=0$	0
2	130	$(0+130) \div 2=65$	130
3	128	$(65+128) \div 2=96$	128
4	133	$(96+133) \div 2=114$	133
5	130	$(114+130) \div 2=122$	130
6	128	$(122+128) \div 2=125$	128
7	128	$(125+128) \div 2=126$	128
8	128	$(126+128) \div 2=127$	128
9	128	$(127+128) \div 2=127$	128
10	128	$(127+128) \div 2=127$	128
11	128	$(127+128) \div 2=127$	128

be averaged, the current sample plus the last seven samples are used. An example of the effects of averaging is shown in Table 1. In that example, an averaging of 2 is used to show the difference between averaging the data and storing the straight values.

Once all of the configuration information has been entered, the data is then sent to the Data Monitor over the RS-232 cable. Once that is done, the Data Monitor is then ready to be armed. It can be disconnected from the PC at this

time and placed wherever it needs to be. Pressing the Arm/Status switch will arm the Data Monitor, and begin the sample and store process. You will see two three-bar characters on the display, showing that the sample and store process has begun. Pressing the Arm/Status switch will display the percentage that the EEPROM is full.

When the EEPROM is full, or you have collected enough data, you can download the information recorded in the Data Monitor to the PC for analysis. The same pro-

gram is used to download the stored information. Type in the name of the file that you wish to save the data in and select a directory in which to store it. Press the OK button, and the software will download the collected data and place it in an ASCII text file with the name that you gave. The download process can take up to 5 seconds. The downloaded file can be opened by any standard text editor or word processor. You can also use a spreadsheet in order to analyze and chart the information from the Data Monitor.

Circuit Description. The schematic diagram in Fig. 1 shows that the Data Monitor is built around IC1, a PIC microcontroller. The circuit needs a DC power source between 7 and 12 volts that can supply 200 milliamperes. That power is fed through J4. Both a 9-volt battery and a wall-mounted 9- to 12-volt DC adapter are connected through pins 1 and 2 of J4, with pin 5 serving as the ground. Each power source is isolated from each other by D1 and D2. The power is then routed through an on-off switch that is connected between pins 3 and 4 of J4. The power is regulated down to 5 volts by IC6 and filtered by C10-C12.

The rest of the circuitry supports IC1. Translating IC1's serial transmit and receive lines between TTL and RS-232 voltage levels is done by IC3. Through that chip and J1, the Data Monitor connects to a PC. The pinout on J1 is designed to match the pinout used on the 9-pin serial ports commonly found on PCs. An unusual feature of the serial-interface circuit is R2, which gives a small measure of short-circuit current protection for the RS-232 connection. Any power-supply noise that might disturb the operation of IC3 is decoupled by C6.

The Data Monitor's status is displayed on DISP1, a 2-digit 7-segment LED display. The display is a common-cathode type—all of the cathodes in each individual LED are tied together, with the anodes separated. The anodes of each digit are driven from IC1 directly through current-limiting resistors R9-R16. In order to minimize the number of pins needed for IC1 to control the dis-

LISTING 1

Data Monitor Download Data (V1.0) -- JV Enterprises

Storage Mode :: Immediate
Trigger Mode :: None
Average Off ::---
Time Stamp :: 20:50:22.070
Date Stamp :: 01/02/97
User Time Scale :: 30 MilliSeconds

Time	Dg1	Dg2	Dg3	Dg4	An1	An2	An3	An4
20:50:25.297	0	0	0	0	88	0	0	0
20:50:25.327	0	0	0	0	88	0	0	0
20:50:25.357	0	0	0	0	88	0	0	0
20:50:25.387	0	0	0	0	88	0	0	0
20:50:25.417	0	0	0	0	88	0	0	0

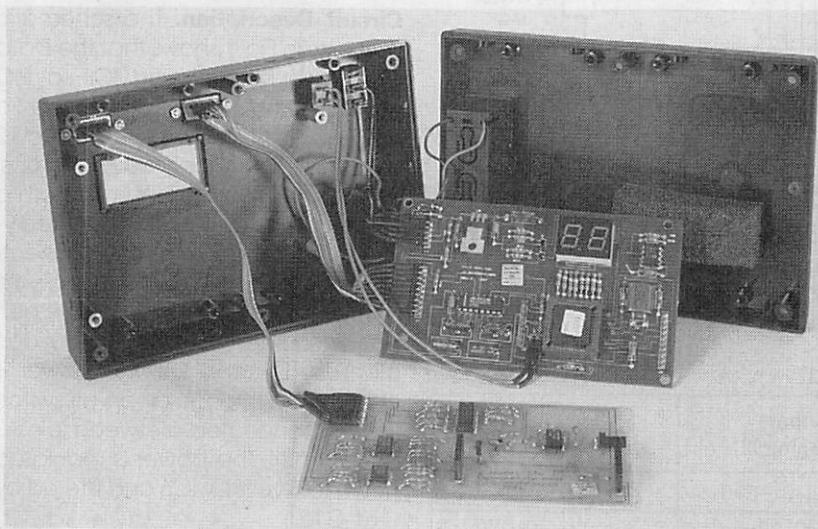


Fig. 4. When your Data Monitor is ready to be closed up, it should look something like this. The additional PC board in the foreground is a general-purpose I/O-temperature sensor Personality Module that is described in an accompanying article in this issue. You will need some type of Personality Module to use the Data Monitor. You can design your own if you want.

play, the data to each digit is multiplexed. In that way, the data for the first digit is sent through the resistors while Q1 is turned on and Q2 is turned off. Then the data for the second digit is sent through the resistors while Q1 is turned off and Q2 is turned on. The process is repeated every eight milliseconds. At that rate, the human eye cannot tell that the display digits are alternating on and off—the display appears to be on continuously.

A momentary pushbutton is wired across J5. That button is used to arm the Data Monitor and to activate the display. Normally, the display is off, helping conserve battery power. Also, the display will not update while the button is pressed, making it a little easier to read.

Connectors J2 and J3 provide the connections to the Data Monitor's Personality Module. The use of each pin is shown in Table 2. The analog- and digital-input signals are applied to those pins. The analog inputs are connected to the PIC's A/D converter. Two additional pins are used to let the Data Monitor know what type of Personality Module is connected to it. The voltage from a voltage divider made up of R5 and R6 is applied to one of the unused analog inputs of IC1. That way, the Data Monitor can also watch the unregulated voltage level of its own power supply, and take appropriate action if the batteries (if used) get too weak.

Data Monitor

Storage Inputs

☒ Digital 1
☒ Digital 2
☒ Digital 3
☒ Digital 4
☒ Analog 1
☒ Analog 2
☒ Analog 3
☒ Analog 4
☐ Average Enable
Average Depth

User Time Base

☐ Day
☐ Hour
☐ Minute
☐ Second
☒ Millisecond

Trigger Definition

[T1 and T2 and T3] or [T4 and T5 and T6] or [T7 and T8]

	Source	Digital	Analog	Data
		Rise	Fall	State
Term 1	<None>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Term 2	<None>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Term 3	<None>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Term 4	<None>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Term 5	<None>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Term 6	<None>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Term 7	<None>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Term 8	<None>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>

☐ Store On Trigger
☒ Store Immediate

OK

Fig. 5. Programming the Data Monitor is a snap with this Windows-based program. Selecting the various features and options is as easy as pointing and clicking with a mouse.

Building the Data Monitor. Although the Data Monitor is a sophisticated information-gathering device, its construction is quite straightforward. If you decide to etch and drill your own board, foil patterns are provided. As an alternative, an etched and drilled PC board can be purchased from the source given in the Parts List. Since the Data Monitor PC board is double-sided, you should make sure that all connections on both sides of the board are properly soldered if you make your own board. A purchased board will have all of the component and via holes plated, making assembly much easier.

Microcontroller IC1 must also be programmed with the instructions needed to run the Data Monitor.

The Four-Year Electronics Degree Program That Really Hits Home!

Bring The Technology Home With A Bachelor Of Electronics Engineering Degree. No Hassles. No High Cost!



Now's the time to prepare for a profitable career.

We've lowered the cost of higher education.

It's true! You can earn a four-year Bachelor of Electronics Engineering Technology degree today ... and prepare yourself for a high-paying electronics career ... without quitting your job or ever leaving your home. Because World College, an affiliate of the Cleveland Institute of Electronics, offers you the total flexibility of independent study programs proven effective for people like you who truly want to succeed! World College independent study lessons help you build valuable skills

**Mail/Fax Today
or Call
1-800-696-7532**

step-by-step, and expert instructors are personally available to you with a toll-free call. What a way to earn an education!

A world of opportunity.

Where is your career headed? With a four-year bachelor's degree from World College, you call the shots, choosing from incredible, high-paying opportunities in electronics, telecommunications, computer, electrical power, and many other growing fields.

World College gives you the skills, the knowledge, the power to take advantage of your best opportunity in electronics. And you can do it all at your own pace!

Without leaving home.

World College continually works to provide its students with the most advanced education tools. From the latest equipment and reference books to breakthrough computer-simulated experiments, students are exposed to the latest technological advancements.

All the equipment, parts, and software you need are included in your affordable tuition, including more than 300 hands-on lab experiments you can complete in your home.

Choose your own pace.

Earn your bachelor's degree on your time — and at your pace — because you pay tuition to World College only as you complete the upper-level semesters close to graduation. The faster you make it through, the less you pay. So you have an incentive to make your future happen quickly — yet the freedom to choose your own pace!

Send today for your FREE course catalog — and give yourself that future you've always wanted — with an electronics degree education from World College.



Take charge of your future in electronics.

Four Powerful Reasons To Connect With World College Today:

- 1. Earn your four-year degree!**
- 2. Self-paced training!**
- 3. Independent study in your home!**
- 4. Expert instruction!**

Give Me The Power!

Send me a FREE World College course catalog today!



(Please Print Neatly)

Name _____

Address _____

City _____

State, Zip _____

Phone () _____

Age _____

**For faster service, call
1-800-696-7532,
or call
1-804-464-4600.**

**Or fax this coupon to
1-804-464-3687.**



Lake Shores Plaza
5193 Drive, Suite 113
Virginia Beach, VA 23455-2500



Affiliated with
Cleveland Institute of Electronics

WAE64

Again, a pre-programmed part is available from the source given in the Parts List. Blank chips can also be programmed. The programming information, along with the computer-interface program, is available at the Gernsback FTP site (<ftp://ftp.gernsback.com/pub/EN/datamon.zip>).

Once you buy or etch your board, use the parts-placement diagram in Fig. 2 for the proper location of the components. Pay particular attention to the orientation of any polarized components. If a part is soldered onto the board backwards, removing it will be much more difficult due to the double-sided traces.

Start assembly by mounting all of the resistors and capacitors. A socket will also be needed for IC1. Sockets may also be used for the other ICs, but that is not necessary.

Doing so, however, will make troubleshooting and repair of the Data Monitor much easier. Connectors J1-J5 should also be mounted. Note that J2 and J3 are mounted on the *solder* side of the board. The other connectors are right-angle types; their pins should point to the closest edge of the board.


The first semiconductor to be mounted is IC6. It should be mounted flat to the board with the metal tab facing away from the PC board and the plastic front *against* the board—opposite from the normal way to mount such a component. Before going any further, the board should be tested to see that the proper voltages appear at the various locations of the other semiconductors. If there is a problem or mistake in the board, it is easier (and less expensive) to correct the problem now rather than destroying sev-

eral ICs. Set up a bench-type power supply for 9 volts DC. If you do not have a bench supply, a 9-volt battery can be used instead. Connect the positive terminal of the supply to pin 1 of J4 and the negative (ground) terminal of the supply to pin 5. The output voltage of IC6 should be 5 volts. That voltage should also appear at the several power-supply pins on the rest of the IC locations. Use the schematic diagram in Fig. 1 as a guide as to which pins should be checked. As a final test, pin 3 of IC1 should be about 3 volts. Once the board checks out, the rest of the semiconductors and DISP1 can be mounted. Double-check the orientation of the devices against Fig. 2, as you mount them.


Prepare a suitably-sized enclosure by drilling and cutting holes for the power switch, status switch, and power connector. Four holes will be needed for mounting the PC board to the front panel. A cutout for viewing DISP1 is also needed in the front panel. In addition, two 9-pin connectors will be used for both the serial interface to the computer and to connect the monitored circuits to the Data Monitor's personality module.

The various connectors and switches are wired as shown in Fig. 3. Use suitable connectors for attaching the wires to J1, J4, and J5. The status switch simply connects across J5. The computer interface is wired to J1 connecting pin 1 to pin 1, pin 2 to pin 2, and so on. Pay special attention to the wiring of J4. That connector brings the 9-volt battery, the external DC wall adapter, and the Data Monitor's power switch together. Do not miswire J4, or the unit will be destroyed the first time power is applied. Wiring the input connector to the Personality Module will depend upon what type of connector and Personality Module you will be using.

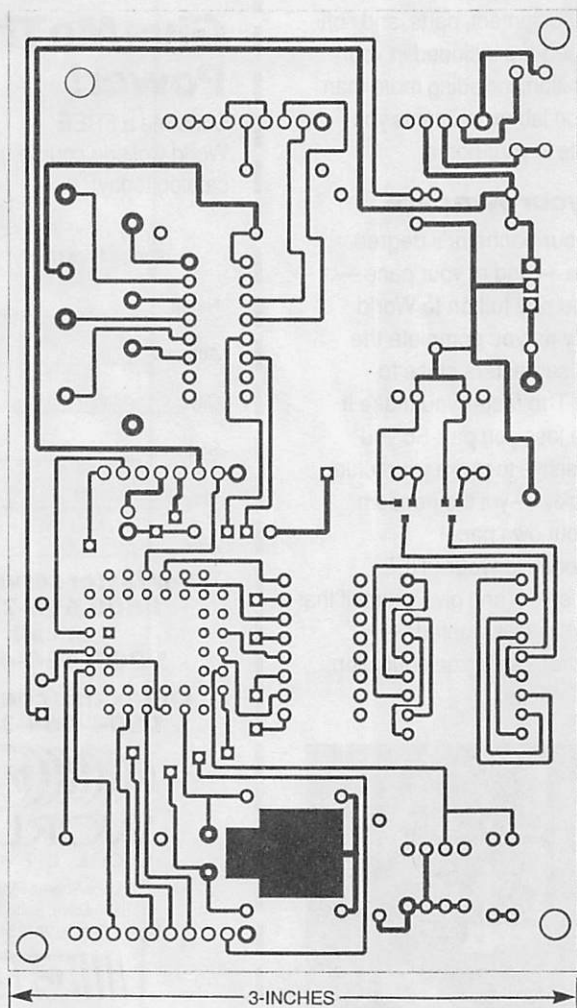Once all of the wires are attached to the various connectors, mount the connectors and switches to the enclosure. Attach the connectors at the other ends of the wires to J1, J4, and J5. If you are using the Personality Module described in the accompanying article, the unit should look similar to Fig. 4. Simply



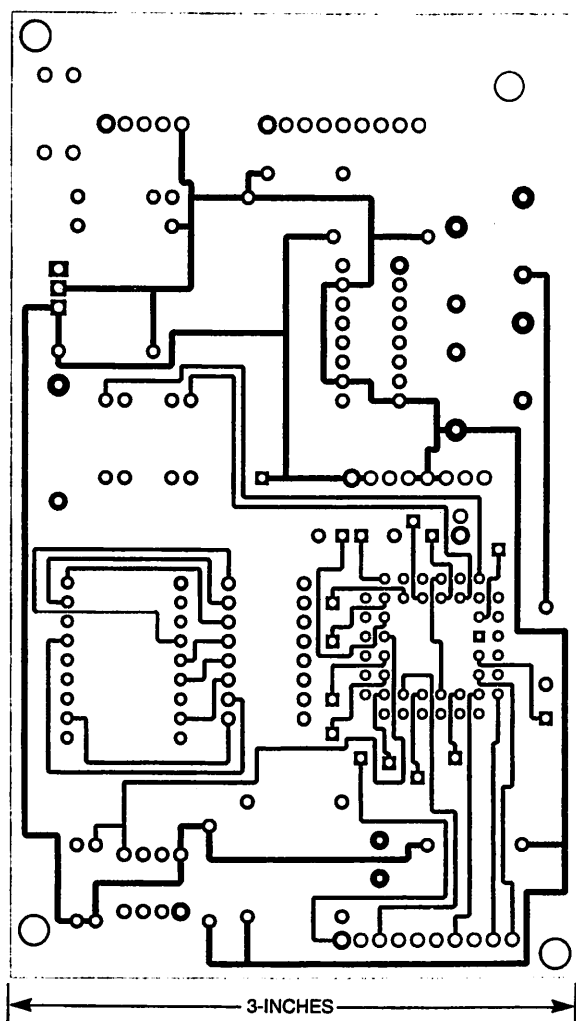Here is the foil pattern for the component side of the Data Monitor PC board.



Here is the foil pattern for the solder side of the Data Monitor PC board. If you etch and drill your own board, don't forget to connect any foil connections that pass from one side of the board to the other.

screw the PC board onto the spacers mounted on the front panel, mount the Personality Module onto J2 and J3, and close up the case. The Data Monitor is now ready for testing.

Testing. Now that you have fully completed assembling the Data Monitor, you must test it to make sure it is fully functional. Insert a fresh 9-volt battery or attach a 9-volt DC wall adapter to the Data Monitor. Turn on the power switch and press the Arm/Status button. Two single bars should be seen in DISP1. That means that the Data Monitor is ready for communications with the host computer.

Connect the serial cable from the Data Monitor to the PC and run the Data Monitor software. Click on the "Configure" pull-down menu

and select "Comport." Choose the serial port that the Data Monitor is attached to. Now select "Setup" from the "Configure" pull-down menu and set the Data Monitor's options to record all of the digital and analog inputs. You can leave all other options at their defaults. With the Data Monitor storing information at 30-millisecond intervals, the setup screen should look like the example shown in Fig. 5.

Send the setup information to the Data Monitor by selecting "Initialize" from the "Configure" pull-down menu. You should see a "Data Monitor initialized" information box if everything went OK. If not, check both the internal and external cables and connections. Make sure that you haven't plugged some of the internal cables on backwards.

Now press and hold the Arm/

TABLE 2	
PINOUT FOR J2	
Pin No.	Signal
1	Digital Input 1
2	Digital Input 2
3	Power On/Off Control
4	Personality ID 2
5	Personality ID1
6	Personality 0
7	Analog Input 4
8	Analog Input 3
9	Analog Input 2
10	Analog Input 1
PINOUT FOR J3	
Pin No.	Signal
1	5-volt regulated supply
2	5-volt regulated supply
3	9-volt unregulated supply
4	Ground
5	Ground
6	Ground
7	Digital Input 4
8	Digital Input 3

Status button. You should see two three-bar characters on DISP1. Release the button. The Data Monitor is now sampling and storing the data from the analog and digital inputs. The complete cycle should take less than a minute. Let the Data Monitor run until it is full. You can check on the progress of the cycle by pressing the Arm/Status button. When pressed, DISP1 will display how full the EEPROM is as a percentage. The status will not update while you hold the button. To update the display, let go of the button and press it again. When the status window shows "00.," the Data Monitor is finished and ready for downloading to the host. The dot to the right of the zeros shows that the Data Monitor is full. You do not need to wait for the EEPROM to fill completely before downloading; you can download at any time.

Select the "Download" pull-down menu and pick "Download." A pop-up menu will appear. Choose a directory and filename for the downloaded data. Press the "OK" button, and the software will download the Data Monitor and place the data in a text format in the loca-

(Continued on page 48)

BUILD THIS PERSONALITY MODULE FOR YOUR DATA MONITOR

JON VARTERESIAN


A Personality Module for the Data Monitor will get you started with monitoring digital and analog inputs. You can even track the temperature at the same time!

By now, you've probably studied the Data Monitor described elsewhere in this issue. You probably have some ideas as to where such a useful device can be used. You're ready to roll up your sleeves and dive right into the construction, but that article says that you need a Personality Module to connect the Data Monitor to the outside world. You might not have the patience or expertise to design your own, but you'd still like to use the Data Monitor. It seems like you'll never be able to use the Data Monitor.

Enter the General-Purpose I/O-Temperature Personality Module! This add-in circuit board for the Data Monitor will let you get started with using the Data Monitor, and just might be all that you need for all of your data sampling and event recording.

How it Works. In order to use different sensors for unique monitoring applications as well as to protect the internal circuitry from surges and possible electrical damage, the Data Monitor is designed to use what is called a Personality Module. A Personality Module connects to the Data Monitor's main circuit board through a 10-pin and an 8-pin connector.

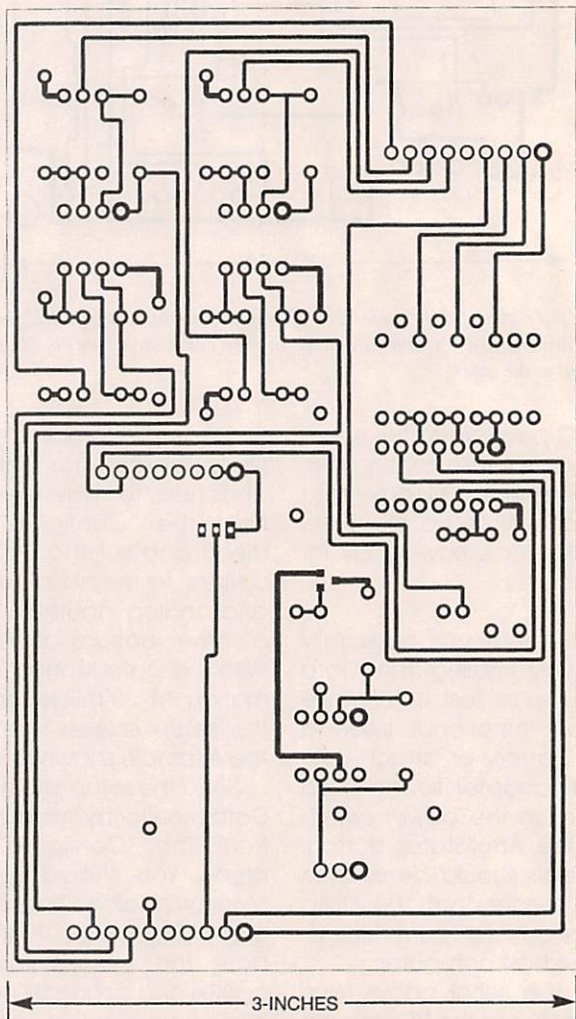This Personality Module is a very simple design. It has buffer circuits



Here is the foil pattern for the component side of the Personality Module.

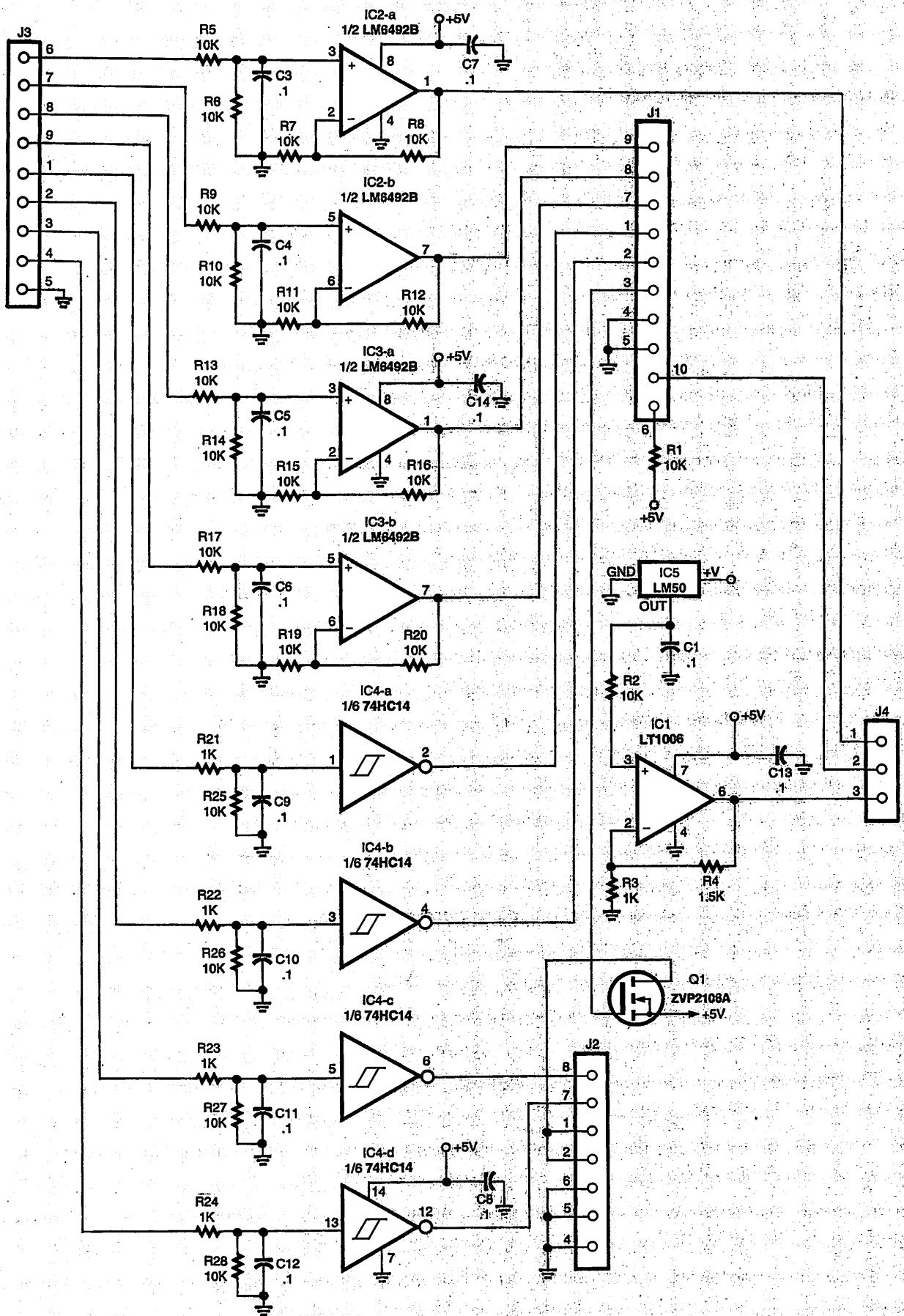


Fig. 1. The Personality Module is a set of simple analog and digital buffers that protect the Data Monitor's sensitive circuitry. Analog-input 1 can also be used to measure temperature.

for both the digital and analog inputs, as well as an on-board temperature sensor. The temperature sensor is designed to connect to the Data Monitor through analog input 1. If you need all four analog inputs, or you just need to use the first analog input for whatever reason, a movable jumper block on the Personality Module lets you bypass the output of the temperature sensor. That way, the first analog input has the same buffering circuit that the other analog inputs have.

Power for the Personality Module comes from the Data Monitor itself. An on-off control transistor is included for future compatibility; future versions of the Data Monitor software will let the Data Monitor power down the Personality Module circuitry in order to conserve battery power if the Data Monitor is going to be used in the field where a wall adapter cannot be used for extended periods of time.

Circuit Description. The schematic diagram for the General-Purpose I/O-Temperature Personality Module is shown in Fig. 1. The buffering circuits for the digital and analog inputs are the same buffer circuit duplicated for each channel. Only one of each type of channel will be described. The other three channels of each type will work the same way.

In the analog channel, the input signal is buffered by IC2-a, an LM6492 CMOS rail-to-rail op-amp. Resistors R5 and R6 form a voltage divider on the input signal. With a value of 10,000 ohms, the input signal is attenuated by a factor of 2 for a gain of $\frac{1}{2}$. Those values also present an input impedance of about 20,000 ohms to the source of the signal. The op-amp is used as a non-inverting voltage follower. The gain of IC2-a is set by R7 and R8. With those resistors at 10,000 ohms, IC2-a has a gain of 2. Capacitor C3 along with R5 and R6 form a low-pass filter that has a cutoff frequency of about 500 Hz with the values shown. A gain of $\frac{1}{2}$ followed by a gain of 2 will have an effective gain of 1 for the analog buffer circuit.

The digital buffer is built around IC4, a 74HC14 inverting Schmitt trig-

ger. Using a Schmitt trigger helps clean up any slow-rising digital signals and prevents any jitters if the input does not change cleanly from one state to the other. A low-pass filter is formed by R21, R25, and C9. With the values shown, the cutoff frequency is about 910 Hz. Resistor R25 does extra duty by holding a valid logic level on the inputs of IC4-a if the input is not being used. Without it, the input of IC4-a will act like an antenna, picking up stray noise that will cause problems with the other gates in IC4. The input impedance

that the external digital signals will see from the input buffer is about 11,000 ohms.

Temperature sensing is done by IC5, a National Semiconductor LM50. That sensor is capable of detecting temperatures between -10 and $+50^{\circ}\text{C}$. It has a very linear output over the full range of temperatures. The output voltage of the LM50 for any particular temperature can be found by using the formula:

$$\text{Output Voltage} = 0.5 \text{ volts} + (0.01 \text{ volts} \times ^{\circ}\text{C})$$


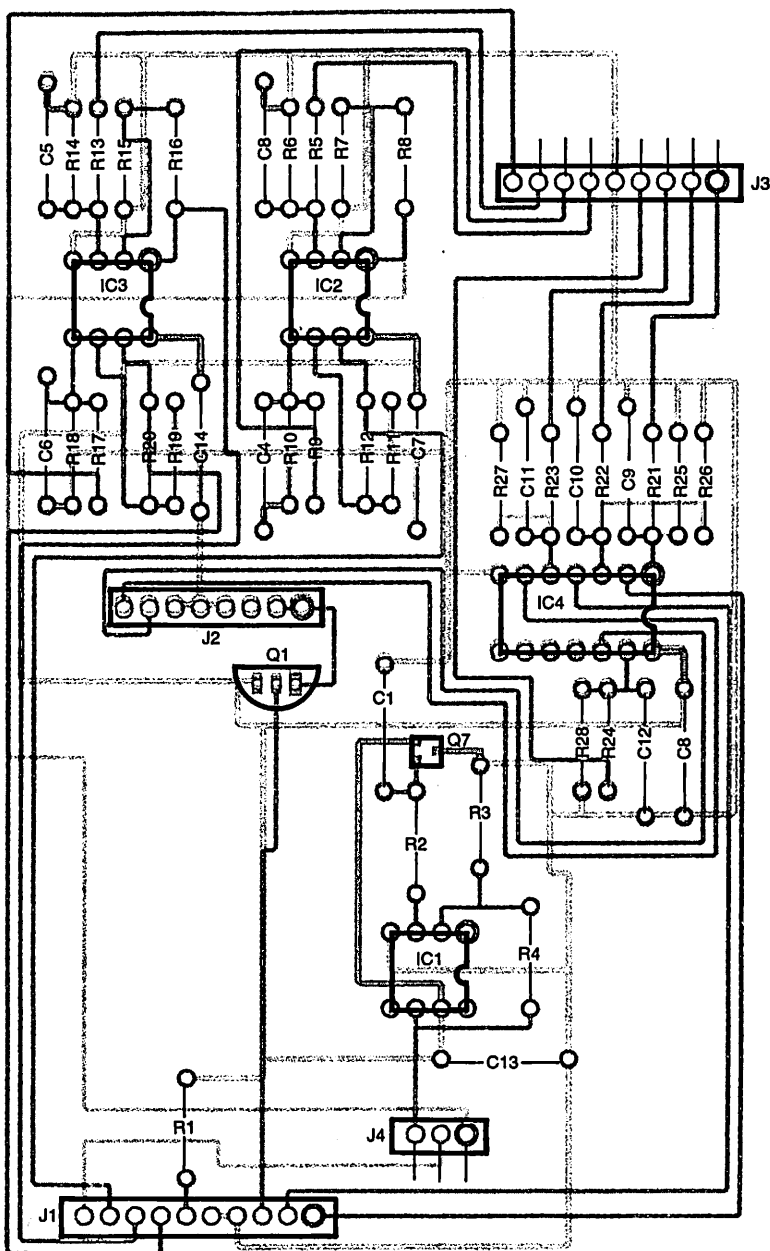


Fig. 2. When building the Personality Module, be careful of the orientation of the polarized parts. Some of the semiconductors are sensitive to ESD, especially Q1.

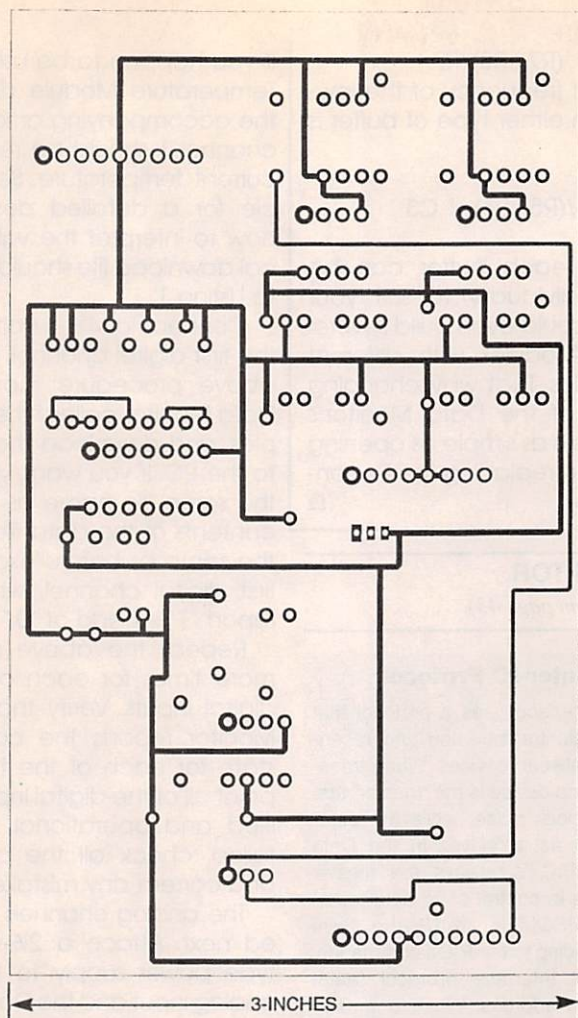

Here is the foil pattern for the solder side of the Personality Module.

For example, a temperature of 20° C would yield an output voltage of $0.5 + (.01 \times 20)$, or 0.7 volts.

The output of the temperature sensor is then amplified by IC1, a non-inverting op-amp with a gain of 2.5. That gain increases the voltage range of IC5 so that it will cover the full range of the Data Monitor's analog-to-digital converter. The reference voltage for the A/D converter inside the Data Monitor is 5.0 volts. Since the converter is an 8-bit device, the digital value reported by the Data Monitor is represented by the following formula:

$$\text{Reported value} = (\text{Input voltage} / 5) \times 255$$

A temperature of 20° C produces an output of 0.7×2.5 , or 1.75 volts. The Data Monitor's A/D converter would output a value of 89.

The input to the first analog input can be switched between the

temperature sensor and the usual analog input voltage by shorting the appropriate pins on J4 with a jumper block. With the jumper in place between pins 1 and 2, analog input will be routed to the Data Monitor. If you want to read the temperature sensor, place the jumper on pins 2 and 3.

The Personality Module also contains Q1, a P-channel MOSFET, in order to control the power consumed by the Personality Module. The current version of the Data Monitor PIC program leaves Q1 always on, so that the Personality Module is always powered up. As previously mentioned, future versions of the Data Monitor software will be able to turn the Personality Module on only when data sampling is to take place. That technique will help conserve power when the unit is operating from a 9-volt battery.

Connections for the digital and

analog inputs are made through J3, with J1 and J2 being used to mount the Personality Module onto the back of the Data Monitor's main board.

Building the Personality Module.

The Personality Module is a simple double-sided PC board. Foil patterns are included if you wish to etch and drill your own board. As an alternative, you can purchase one from the source given in the Parts List. In either case, the parts-placement diagram in Fig. 2 shows where the various components are to be located.

All of the components are located on the component side of the board. If you are using a board that you etched yourself, keep in mind that you will have to solder connections on both sides of the board if you did not plate the holes beforehand. It is easiest to begin by mounting the smallest parts first. Start with the resistors and capacitors. Follow them with the connectors. Once all of the passive components have been soldered to the board, install the ICs. The temperature sensor, IC5, should be the second-to-last component installed. Finish the board by installing Q1. Be careful when installing Q1, as it is very sensitive to electrostatic discharge. The jumper on J4 should be installed depending on whether you want to use the Personality Module's temperature-sensing capability. Placing the jumper on pins 2 and 3 of J4 will select the on-board temperature sensor.

When the Personality Module is finished, inspect it carefully for poor solder joints, solder bridges, incorrectly-installed components, and other similar errors in workmanship. Once you are satisfied with your work, the Personality Module can be installed in the Data Monitor by simply inserting J2 and J3 into the connectors on the back of the Data Monitor's main board.

If you want, you can mount an additional 9-pin connector onto the Data Monitor's case and connect it to J3 of the Personality Module. That way, you will have a convenient way to connect the Data Monitor to whatever devices you wish to monitor. You may use any pin numbers

PARTS LIST FOR THE GENERAL I/O - TEMPERATURE MODULE

SEMICONDUCTORS

IC1—LT1006CN8 op-amp, integrated circuit (Linear Technologies)
IC2, IC3—LM6492BEN op-amp, rail-to-rail, integrated circuit
IC4—74HC14 hex Schmitt trigger, integrated circuit
IC5—LM50 temperature sensor, integrated circuit (National Semiconductor)
Q1—ZVP2106A P-channel MOSFET transistor (Zetex)

RESISTORS

(All resistors are 1/4-watt, 5% units.)
R1, R2, R5—R20, R25—R28—10,000-ohm
R3, R21—R24—1000-ohm
R4—1500-ohm

ADDITIONAL PARTS AND MATERIALS

C1, C3—C14—0.1-mF, axial-ceramic capacitor
C2—Not used
J1, J2—Square-post connector, straight, female
J3, J4—Square-post connector, right angle, male
Jumper block, hardware, etc.

Note: The following item is available from: JV Enterprises, PO Box 370, Hubbardston, MA, 01452. E-mail: JVEnterpri@aol.com: PC board with silk-screen, plated holes, and solder mask, \$13.50. Please add \$5.00 shipping and handling. Massachusetts residents must add 5% sales tax. Check or money order only.

you wish for the 9-pin connector; just make a careful note of which pins are connected to which input channels. If you are going to use the temperature sensor, you should drill several holes in the Data Monitor's case so that the air around the Data Monitor will be able to reach IC5.

Circuit Modifications. You can change the values of the resistors on the input-buffer circuits if you need different levels of amplification or attenuation. On the analog input circuit, the gain of the input resistors is:

$$R5/(R5+R6)$$

The overall gain of the buffer is the resistor gain times the op-amp gain. To adjust the op-amp gain, use the following formula:

$$(R7+R8)/R7$$

The cutoff frequency of the low-pass filter on either type of buffer is found by:

$$1/(R5+R6) \times C3$$

Naturally, each buffer can be modified individually to suit your needs. You could even build several Personality Modules with different characteristics. That way, changing the design of the Data Monitor's input circuits is as simple as opening the case and replacing the Personality Module. Ω

DATA MONITOR

(continued from page 43)

The Inter-IC Protocol

The IIC interface uses a protocol that ensures reliable transmission and reception of data between devices. When transmitting data, one device is the "master" that generates a clock pulse, while the other device(s) acts as a "slave." In the Data Monitor, the PIC is always the master device, always in control of all data transfers. The EEPROM is always the slave device, responding to the PIC's commands.

In the IIC interface protocol, each device has an address. When a master wishes to start a data transfer, it first transmits the address of the device that it wants to "talk" to. All of the devices on the IIC bus listen to see if the address being sent is their address; only the target device responds. Within the address field, one bit specifies whether the master wishes to read or write to the target device. In the Data Monitor, IC2 (the EEPROM) has a fixed constant in the address field because it is the only slave device on the IIC interface bus, so it does not need an address. In any case, the master device generates the clock for the data transfer. In the Data Monitor, the clock is transmitted on pin 20 of IC1, and the data is transmitted and received on pin 25. For more detailed information, Microchip's databooks are excellent sources for their devices (the PIC and the EEPROM). The original specification from Philips and Signetics, "The IIC Bus and How to Use It" is also an excellent source of information.

tion and under the name that you chose.

Open the download file with any text-viewing program. Because all of the Data Monitor's inputs were left unconnected, all of the digital and analog inputs should report "0."

If you happen to be using the I/O-Temperature Module described in the accompanying article, analog-channel 1 should be reporting the current temperature. See that article for a detailed description of how to interpret the values. A typical download file should look similar to Listing 1.

Connect a 4½-5-volt source to the first digital channel. Repeat the above procedure: configure the Data Monitor, collect the data samples, and download the new data to the PC. If you want, you can use the same file name as before. The contents of the data file should be the same as before except for the first digital channel, which should report "1" instead of "0."

Repeat the above steps three more times for each of the other digital inputs. Verify that the Data Monitor reports the correct logic state for each of the tests. At this point all of the digital inputs are verified and operational. If any test failed, check all the connections and correct any mistakes.

The analog channels will be tested next. Attach a 2½-volt bench-type power supply to the second analog input and the Data Monitor's ground. Configure, initialize, arm, and download information from the Data Monitor as before. You should see that the second analog channel has a value of about 128 ± 1 . As with the digital channels, test each analog channel in the same way.

The Data Monitor is now fully operational and needs only the addition of a personality module to be ready for use. Details on a suitable module can be found beginning on page 44. Congratulations and happy monitoring! Ω



Explore the mysteries of human perception, or just impress your friends with a piece of workbench "magic."

DAVE SWEENEY

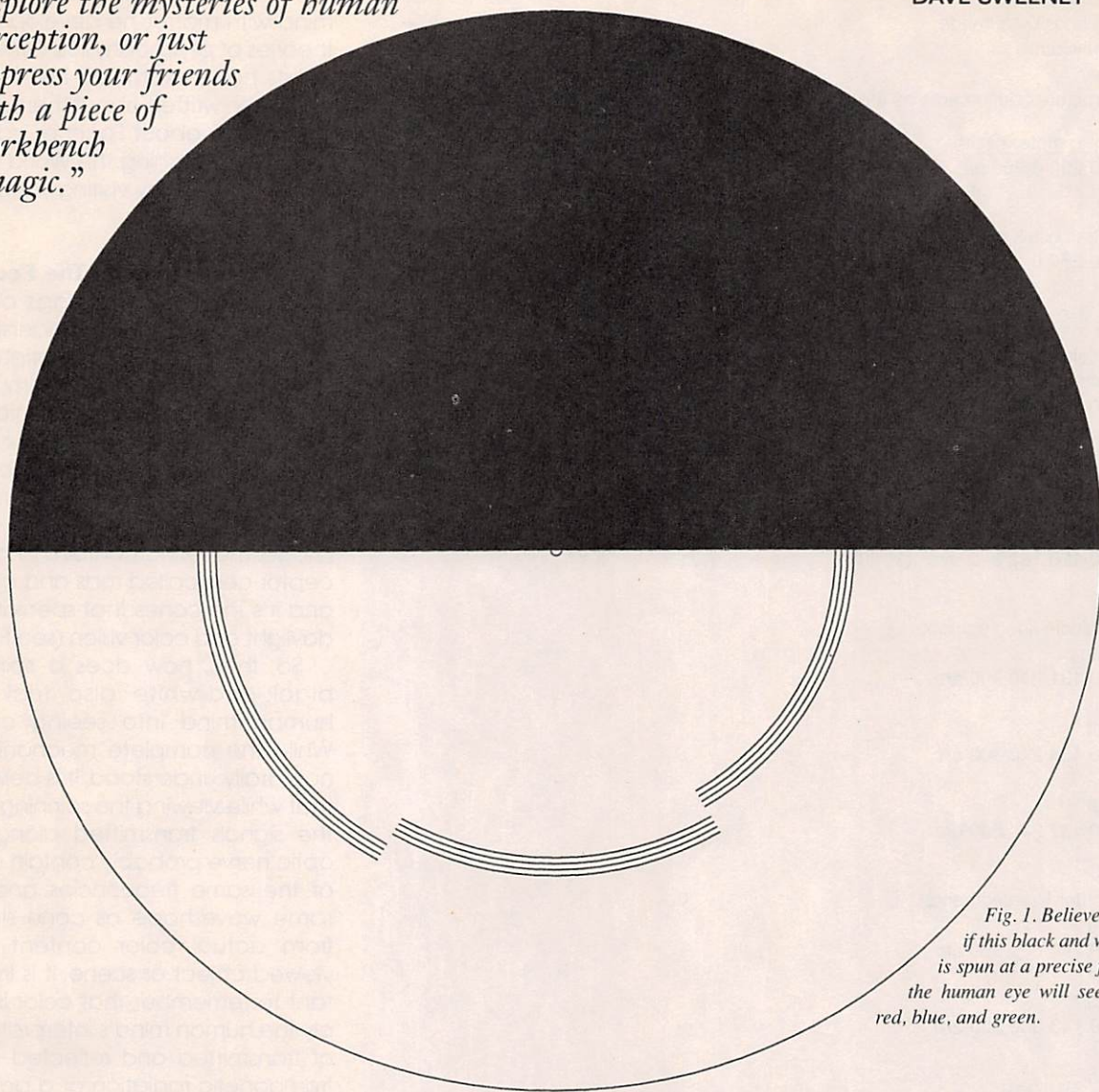


Fig. 1. Believe it or not, if this black and white disc is spun at a precise four rpm, the human eye will see lines of red, blue, and green.

EXPERIENCE THE **FECHNER** PHENOMENON

How would you like to enjoy some workbench entertainment, and, at the same time, explore the basics of human perception? You can do that by creating a "Fechner" Disc, which, for those unfamiliar with it, is simply a piece of paper containing a circular black and white pattern. When you spin the disc at a precise four rotations-per-second, the black lines in the pattern suddenly take on vivid colors. Spin the disc clockwise and the outer lines become red, the middle lines green, and the inner

lines blue. Reverse the spin direction, and the color order reverses.

Setting up the demonstration is easily done using the disc presented in Fig. 1 and parts that are found around most electronics workbenches. First, cut out the disc pattern and mount it on a matching piece of light cardboard to give it

strength. Next, attach the disc to the shaft end of an electric motor mounted in a vise. Power the motor through a speed-control circuit and get the disc spinning at just the right speed. When you see the colors, invite friends and family for a demonstration of something important. Ask them to observe the colors.

LISTING 1

```
%IPS-Adobe-1.0
%%Fechner Disc Image
.5 setlinewidth
0 setgray
%All structures define arcs as follows: center x, center y, radius, start angle, end angle

% The perimeter circle
270 350 250 0 360 arc
stroke

% The half black circle
270 350 250 0 180 arc
fill
stroke

%The inside line segments
newpath
270 350 122 180 240 arc
stroke
newpath
270 350 125 180 240 arc
stroke
newpath
270 350 128 180 240 arc
stroke

%The middle line segments
newpath
270 350 131 240 300 arc
stroke
newpath
270 350 134 240 300 arc
stroke
newpath
270 350 137 240 300 arc
stroke

%The outer line segments
newpath
270 350 140 300 360 arc
stroke
newpath
270 350 143 300 360 arc
stroke
newpath
270 350 147 300 360 arc
stroke

showpage

%%Trailer
%%Pages: 1
%%EOF
```

Mention the rings and point out the locations of the red, green, and blue. When they agree that they see the colors, have them focus on the disc as you cut power to the motor. The disc stops rotating and, presto, there's no more color. Your astounded subjects will stand in awe and might be heard to mutter: "Cool."

Gustav Fechner. The optical effect discussed above is called the Fechner Phenomenon and is

named after Gustav Fechner (1801-1887), who studied mental perception and developed early theories of psychophysics. Born in Gross-Sachsen, Prussia, Fechner received a medical degree at the University of Leipzig, then studied physics and mathematics. In 1834, he was appointed Professor of Physics at Leipzig.

Although he was essentially a physicist, he turned to the problems of philosophy and concentrated on

the entire spectrum of perception. Considering the interaction of the mind with matter, he developed his theories of psychophysics. Other scientists have examined his theories and have written about them. More information about Fechner can be found by searching the World Wide Web, as well as by visiting your local library.

Color Perception and The Fechner Disc.

The basic workings of the human eye are well understood: Focused by the lens with brightness limited by the pupil, light stimulates the retina and sends visual information along the optic nerve. Our brain detects that information, and based upon signals from different elements within the retina, defines a visual image. The retina contains photoreceptor cells called rods and cones, and it's the cones that specialize in daylight and color vision (see Fig. 2).

So, then, how does a spinning black-and-white disc trick the human mind into seeing color? While the complete mechanism is not totally understood, it is believed that while viewing the spinning disc, the signals transmitted along the optic nerve probably contain some of the same frequencies and the same waveshape as cone signals from actual color content in a viewed object or scene. It is important to remember that color is simply the human mind's interpretation of transmitted and reflected electromagnetic radiation of a particular frequency, that color perception can vary among individuals, and that image perception can depend greatly on the surrounding background. Interestingly, a monochrome videotape of a Fechner Disc image played back on a raster scan, monochrome television generates the same color effect as a "live" Fechner-Disc demonstration.

Speed Controller for the DC Motor.

While there are many educational and philosophical aspects to the Fechner Disc demonstration, you'll probably want to do it just for the fun factor. The good news is that you'll not have to spend a lot of time or money on building the setup.

The most important component is, of course, the motor. An inexpen-

PARTS LIST FOR THE MOTOR-SPEED CONTROLLER

SEMICONDUCTORS

IC1—555 timer IC, integrated circuit
IC2—LM317T voltage regulator, integrated circuit
Q1—2N3904 NPN transistor

RESISTORS

(All resistors are 1/4-watt, 5% units unless otherwise noted.)

R1—4700-ohm
R2—10,000-ohm, potentiometer
R3, R8—270-ohm
R4—R6—1000-ohm
R7—4700-ohm
R9—10-ohm, 5-watt

CAPACITORS

C1—20- μ F, 15-WVDC, electrolytic
C2—0.02- μ F, 15-WVDC, electrolytic
C3—10- μ F, 15-WVDC, electrolytic

ADDITIONAL PARTS AND MATERIALS

MOT1—Hobby motor, RadioShack 273-231 or similar
Fechner Disc (see text), perf board, wire, solder, etc.

sive hobby motor will work fine as long as it is reversible, but there is another important requirement: It must be capable of turning at a relatively low rate of four to five rotations-per-second. Since that rate is very slow for your typical hobby motor (most spin at thousands of rpm at their rated operating voltage), we need some way to reduce that speed. One approach is to place a potentiometer in series with the motor. Unfortunately, that won't work well with most motors. That's because most motors will simply stop once the applied voltage is significantly below the rated operating voltage. Besides, we need a way to precisely control the rate of revolution, and it is nearly impossible to achieve the needed precision using just a potentiometer.

Instead, we will use the approach shown in Fig. 3, which illustrates a concept for using a variable voltage regulator to run a small motor. In its normal configuration, pin 3 of the voltage regulator connects to a potentiometer, which controls the output voltage. However, for our motor-control circuit the potentiometer is replaced by a pulse generator, which means that the output

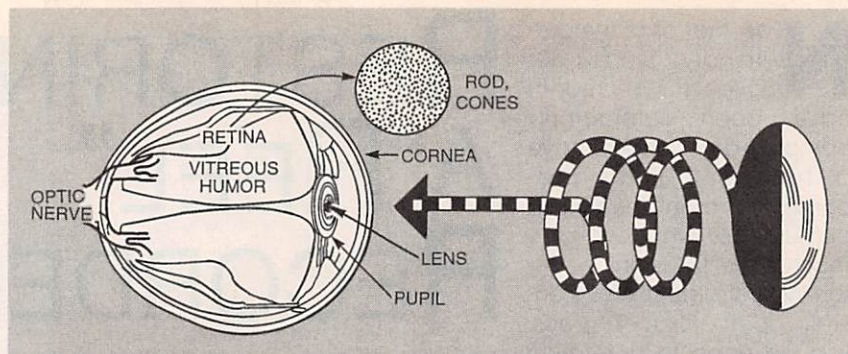


Fig. 2. Light from the spinning Fechner disc enters the eye through the pupil, stimulates the rods and cones of the retina, and is passed by the optic nerve to the brain.

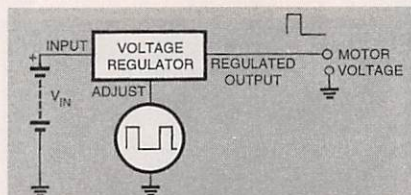


Fig. 3. In its normal configuration, the output of a motor-control circuit like this one is varied using a potentiometer connected to the regulator's ADJUST pin, but in our circuit the potentiometer will be replaced with a pulse generator.

Figure 4 provides the circuit details for our controller. The speed of motor MOT1 varies with the output frequency of IC1, a 555 timer wired as a pulse generator. Pulses applied to the base of Q1 turn it on, which in turn modulate the ADJ pin (pin 3) of the LM317T regulator, IC2. The resulting pulsed power to the hobby motor provides a voltage that is sufficient for starting the motor, yet provides a low average

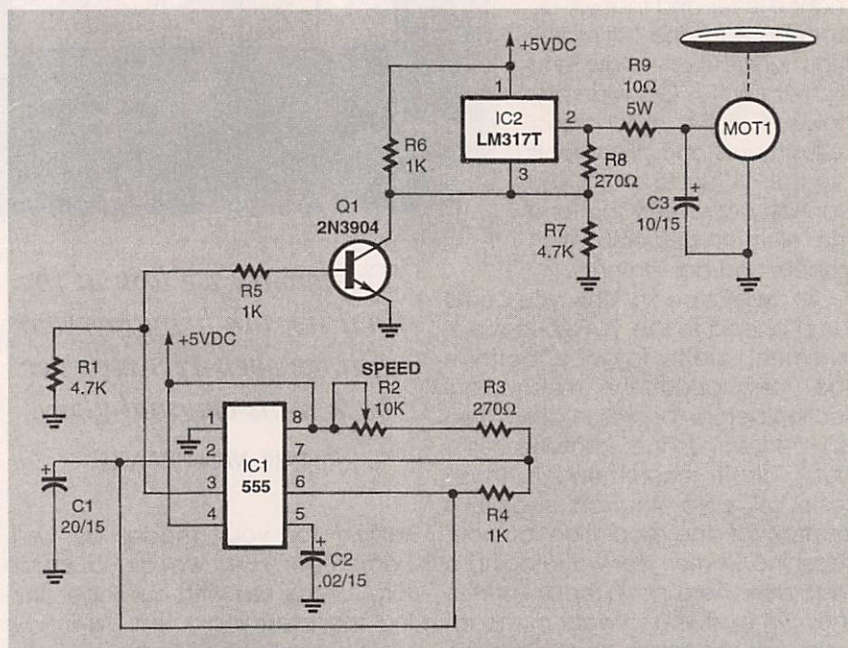


Fig. 4. Here's the schematic diagram for our motor-control circuit. It allows a standard hobby motor to turn at a precise four rpm.

to the motor takes the form of a train of pulses. The amplitude of the pulses is sufficient to move the rotor; however, the average power varies with pulse frequency and the motor speed varies with the average power. As a result, controlling the pulse frequency provides the motor-speed control we need.

power, and thus low speed. In the circuit shown, resistor R2 and capacitor C1 determine the pulse rate. By adjusting R2, you control the pulse frequency applied to the base of Q1, and thus the running speed of the motor.

There is one drawback to the use
(Continued on page 64)

Now that all of the preliminary steps described last month have been satisfactorily completed, you should have a "functioning" tape recorder. This month, we'll find out just how well your tape recorder is functioning. Assuming you find it is not entirely up to factory specs, you will need to determine whether the reasons for this are simply a matter of adjustment, or require component replacement. Finally, we'll describe critical alignment steps needed to bring out the best possible performance from your vintage audio recorder.

We're going to start with the tape recorder's mechanical section. We already know the basic electronic functions are at least working at some minimum performance level, and that will be adequate for the "ultimate" mechanical test—wow and flutter (W/F). Conversely, however, if the mechanical adjustments and alignments are not all "up to snuff", you cannot accurately perform the electronic specification checks and adjustments.

Okay, let's begin. Now you could jump ahead to the W/F spec measurement and try to get a "bottom-line" idea about the mechanical section before (or presumably in lieu of) performing the following tests, but I don't recommend it. These tests will give you an excellent portrait of the condition of your machine. Remember we're doing a restoration here, not a repair. Further, they will alert you to wear or misadjustment conditions that may be masked during the W/F test, but nonetheless are crying for attention.

Tensions. First, let's check the take-up and supply reel tensions. Please recognize that we can only provide general guidelines here, with "ballpark" specs. The actual specs are those originally provided by the manufacturer of your machine. Regarding those tensions, however, the ballpark numbers will probably

RESTORING A "REEL" RECORDER



This month we look at the final steps in bringing your vintage open-reel recorder back to its original glory.

PHIL VAN PRAAG

suffice for your model as well. Remember how we did a crude form of this test with our finger during the preliminary test. Well, now we'll actually measure the tensions.

To do this, you will need an empty reel, some string, and a spring tension gauge capable of reading up to 10 or 15 ounces. Fasten one end of the string to the hub of the reel and place it on the take-up turntable. Now manually wind the string onto the reel clockwise a couple of revolutions. Fasten the other end of the string to the gauge. Now, with the recorder in play mode, and with the motor

shutoff defeated (as in the preliminary test), allow the string to continue winding onto the reel while ensuring that the string is not binding against either reel flange and that the spring gauge is held parallel to the string. Read the tension as the string is slowly winding; it should be about three to five ounces.

If it's much less than three ounces, it could cause the tape to wind too "loosely" onto the reel; that could cause "bunching up" on the reel when it is subjected to the high tension encountered during the start of rewind mode. It can also result in a sudden jerking of the tape a second or two after the start of play mode if tape slack is formed as play is initiated. On the other hand, if the take-up tension exceeds about seven or eight ounces, that could cause the tape to be "yanked" (how's that for a technical term!) through the capstan/pinch-roller area, resulting in uneven tape speed, high W/F, and perhaps even tape stretching.

A similar test should be performed on the supply side (except, of course, winding the string counter-clockwise instead of clockwise). Supply-reel play-mode tension is often somewhat less than on the take-up side, with normal readings at about two to four ounces.

The adjustment for play-mode reel tension is either rather easy, or rather difficult, depending on whether this is a three-motor or a single-motor machine. If it's a three-motor machine, an adjustment can usually be made via slide rings on large power resistors connected to the supply and take-up motors. Hopefully, you have located a schematic diagram of your recorder, or at least an adjustment pictorial, to help find the appropriate resistor(s). If not, you might be able to visually (or through the use of an ohmmeter) trace down to the proper component.

If you have a single-motor ma-

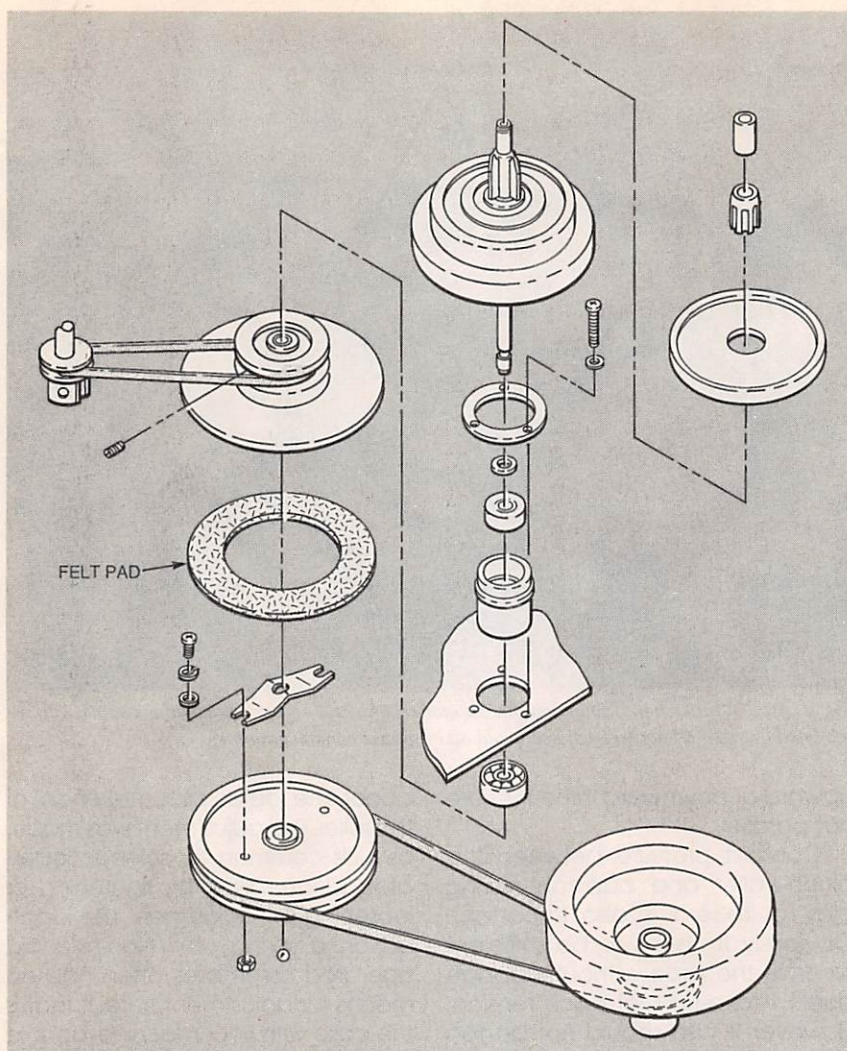


Fig. 1. A typical take-up turntable-clutch assembly from a single-motor recorder. The felt pad is used as a "slip clutch," transferring rotational force on an as-needed basis to ensure smooth winding of tape onto the take-up reel. Great care must be used to avoid oil or grease contamination of either the felt or its mating surface.

chine, chances are the supply and take-up tensions are created through the use of a "slip/clutch" contraption, usually formed by a cotton/felt pad slipping on a smooth nylon plate or plastic film washer. Figure 1 shows a typical take-up turntable clutch assembly. Driving force is transferred to this assembly from the motor via a belt or rubber idler. Therefore, the cause of tension problems can be from any or all of the above items. Belts should be soft and supple, and still possess sufficient tension to adequately drive all associated pulleys. If cloth belts were used, check for excessive fraying, or general decomposition, as well as tensioning and free rolling of the spring-tensioning pulley. Idler rubber must be

soft enough, and free of flat spots or gouges, to evenly and reliably drive their associated pulleys.

Perhaps the most likely culprit in single-motor tensioning problems, however, is the slip clutches themselves. Occasionally, reconditioning is possible; but the majority of cases require the replacement of both the felt material and the nylon/plastic surface. In any event, the entire turntable assembly must be disassembled to gain access to those parts. That is often a difficult task for the uninitiated; so, if you don't feel up to it, this may be the time to call for professional help. If you do attempt this repair, be sure to take careful note of all the little washers, clips, and other hardware that will need to be removed along the way.

Also note the sequence of removal, as that will need to be precisely reversed when re-assembling.

Once you have gotten to the slip clutch, inspect it for obvious damage. Usually, you will find that the felt has compressed somewhat because of the tension against it for many years. If it is not shiny, however, and if the compression has not resulted in a loss of reel height (as would be evidenced by the tape scraping on the upper reel flange), then it may still be serviceable. Now look at the nylon/plastic surface. It must not have any abrasions, deposits, or any other surface roughness of any kind. If it does, ordinarily it should be immediately replaced. Unfortunately, that is often not possible; in that case your next line of attack is to attempt refinishing via very light scraping and/or polishing of the surface. That will sometimes work; unfortunately, the only way to find out is to completely re-assemble the turntable assembly and see what happens. That can be one of the more frustrating aspects of the restoration process; but hang in there, eventually you will get it right!

Though of somewhat less concern, the other reel tensions to consider are the brake tensions. We can't get as specific here because of the wide variance in the brake methods used over the years, as well as the means of measurement and adjustment. The good news is that as long as the tape is not being unduly stressed or slackened, after the brakes are applied, and as long as you are satisfied with the amount of time it takes for the reels to stop (once again, specs vary widely here), then you are okay. After all, the brakes are totally out of the picture during play or record (actually, even here there are a few exceptions).

If you have access to the original factory specs, or if tape damage could occur if something isn't done, go ahead and check out and/or make some adjustments. If you have a three-motor machine, the most common adjustment is at one end of the brake band. A typical brake band configuration for three-motor designs is shown in Fig. 2. Sometimes the adjustment takes the form of moving to a different

spring stop along a tab at the end of the band; other times it's a matter of bending the tab slightly, relative to a stop post. In single-motor machines, perhaps it's a heavier tension applied to the same slip clutch used to create play-mode back tension. If that is the case, the repair you performed to correct play-mode problems might also take care of the brake issue.

Note that there are two different brake specs for each turntable; one for each direction of travel. The tension spec for one direction will be perhaps as much as double that of the other direction. To give you at least some point of reference, the three-motor Ampex Model 350 has specs of 7 and 14 ounces at each turntable, using the string measurement method described above (this time with the transport in stop mode), but based on a 10 $\frac{1}{2}$ -inch reel instead of a 7-inch reel. It's important to note the type of reel used in conjunction with the specification, since different reel sizes will have different hub diameters.

Pinch Roller. Let's spend a few moments discussing the pinch roller and its contact with the capstan shaft. First, having gone through all the preliminary cleaning and lubrication, the pinch roller should spin free, exhibiting no sluggishness. If it is sluggish, remove it from its shaft and clean both the shaft and the inside of the pinch-roller wheel again. Then apply a couple drops of oil and re-assemble. Now, with the recorder power off, push the roller very lightly against the capstan shaft (depending on the mechanics, you might have to move the operating lever into play mode in order to do this—as is the case with the Tandberg 3000X shown in Fig. 3). With your head at capstan level and one eye closed, sight down the area at which the pinch roller is making contact with the capstan. With just very light pressure, ensure that the edge of the pinch roller is perfectly parallel to the capstan. As you ease the pressure on the pinch roller, check that the amount of clearance between the two as the pinch roller is moved away is identical top and bottom. That is important as the tape will tend to skew

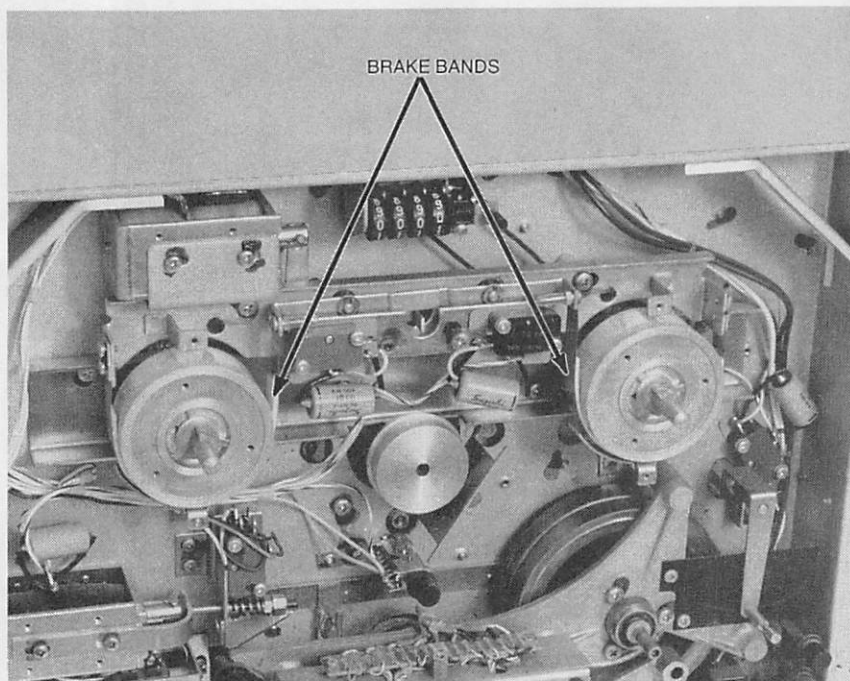


Fig. 2. Typical brake bands found on three motor recorders. The same precautions apply with the felt band linings—do not moisten and avoid oil or grease contamination.

upward or downward if the two are not parallel.

Contact pressure between the pinch roller and capstan during play or record is also important. Obviously, it needs to be sufficient to drive the tape without slippage due to take-up-reel back tension. However, it also should not be too great, otherwise it could exert undue strain on the upper capstan bearing. Unfortunately, most manufacturers do not have a spec on this; so you are left to your own judgment as to whether the force you observe and feel is sufficient, but not excessive. Another factor in the amount of contact pressure required is whether the pinch roller has hardened, or whether the capstan shaft has become too smooth as a result of wear. (You will note that the capstan shaft usually has a satiny finish when it comes from the factory. I have seen capstan shafts with lots of wear that have mirror finishes over the $\frac{1}{4}$ -inch tape-contact area.)

Just to provide a ballpark number here, the Crown SX822 (a three-motor machine with a solenoid-actuated pinch roller) calls for a 10- to 12-pound pressure, measured by pulling straight down on the bar to which the pinch roller is mounted. The end of the bar is located at

about the outer circumference of the roller. The adjustment was made, as was common for solenoid-operated pinch rollers, by tightening or loosening an adjustment nut located on a spring arm. Non-solenoid operated assemblies often had no means for adjustment here. If that is the case with your machine, double check all of the other possible causes of slippage mentioned above; if that still doesn't do it, then consider replacing the spring that holds the pinch roller against the capstan.

Before proceeding with the W/F measurement, take a final look at any roller-style tape guides. Those rollers (many of which have ball-bearing race assemblies) should spin freely, with no visible signs of embedded dirt still lurking in the corners or edges. It's a good idea to just disassemble these roller guides, clean them thoroughly, and lubricate as you put it all back together.

Wow/Flutter Measurement. Finally, let's go ahead and perform the W/F measurement. By this time, you should have taken care of all major mechanical subsystems, so I would expect decent results. However, don't be surprised if it doesn't quite meet spec the first time. While there are many factors that we have already checked, there are proba-

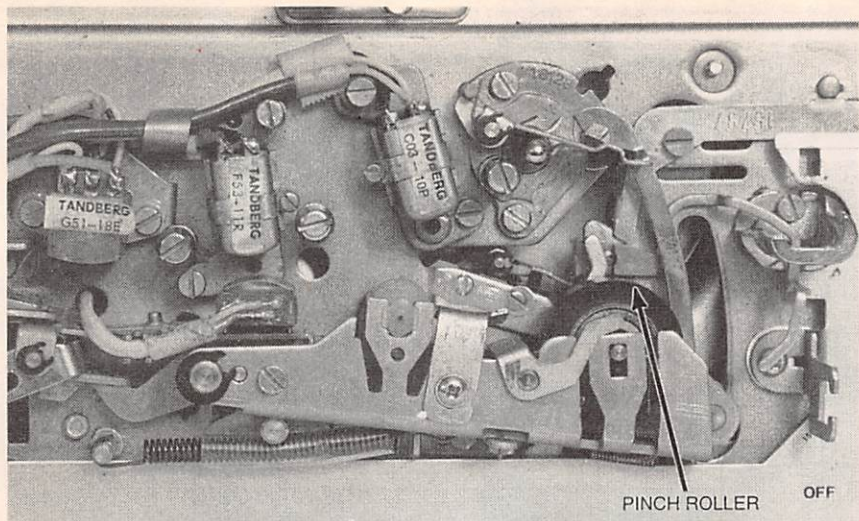


Fig. 3. On some machines, such as this Tandberg Model 3000X, the transport function lever must be moved toward the play position in order to check that the tape-contact surface of the pinch roller is perfectly parallel to the capstan shaft.

bly as many others that we haven't; many of which really can't be checked, from a practical standpoint, without replacing suspected components and comparing the results.

If you have a pre-recorded W/F tape, thread it up, set the appropriate tape speed, connect the recorder's playback pre-amp output to your W/F meter, and "let 'er rip." If you don't have a prerecorded W/F tape, don't worry about it. You can record the flutter test frequency directly onto the machine you're restoring (unless, of course, it's a "play-only" machine) and then simply play it back. The latter method does, technically, allow errors to creep in due to alternate reinforcement and canceling of the flutter components upon subsequent playback. However, the results obtained using this technique will be close enough.

Just take the time to record a sufficient length of tape, and then study the meter when playing back. Look at the dips and peaks for about a minute. This should allow you to observe the "usual" peak and average levels, as opposed to the "occasional" peaks and averages. The reading of W/F is always somewhat subjective; not using a prerecorded tape simply makes it a bit more subjective. Some W/F-meter manufacturers recommend making several test recordings, and use the "average of the peaks" as the "official" W/F number.

Several methods have been used by manufacturers to express their W/F specs. Sometimes they will not state whether the published number is "peak" or "rms;" other times they will state "average peak" or "average rms;" still other times they will not stipulate whether the number is "weighted" or "unweighted". But, at least by now you will know the W/F of your machine; and, if you happen to own more than one, it can be a point of relative comparison between them.

If your reading is obviously out of spec, then I would recommend the following sequence: First, double check all of the mechanical work you have done thus far. Next, review your log of this machine, looking back to the very first cleaning-related observations. Are there any clues there that might lead to a cause for this condition? If neither of those steps help, then you will need to explore new ground.

It is always possible that a bad bearing somewhere is causing the problem. Listen very carefully to the sounds emanating from the mechanics as you play a tape. Are there any grinding, or raspy sounds? Sometimes, with the W/F meter still connected, you can simultaneously see and hear abnormal fluctuations in sight and sound, synchronized so as to point out the source. You might try replacing the capstan-motor capacitor (often somewhere between 2 and 4 mF, at about 350 volts).

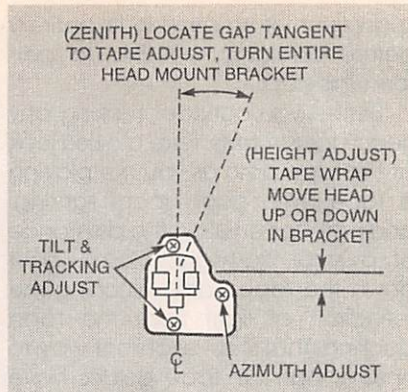


Fig. 4. The various adjustments needed to bring tape heads into proper alignment.

If any of the above doesn't resolve the problem, at this point tracking down its source becomes more difficult. At the factory, or at a field service center, the technician would most likely start swapping out major parts, like capstan motors, to try to isolate the source. Obviously, that is even more difficult today, owing to a lack of replacement parts. If you happen to own two identical machines, then this is the time to drag out the other one and swap parts, one at a time. It's not pretty, but eventually you will find the problem this way; unless, of course, the second machine has the same problem. This does happen, when you consider that high wear items—or really any weaknesses—can easily be the same for identical model machines.

Now that we've gotten the mechanics "beaten into shape," let's move on to the electronics.

Tape Path Alignment. First, we're going to tackle tape-path and head alignment. If things here are not perfectly aligned, the electronic performance of your recorder will suffer. During a restoration, proper alignment should be assured before making any other electronic adjustments. That alignment includes vertical height, wrap, tilt, zenith, and azimuth.

A primary issue here might be wear: if the tape path is well worn (e.g., substantial grooves worn into the head faces), then it might be best not to attempt any tape-path alignments. If that is the situation with your machine, then be especially careful to read the following

alignment information in its entirety before deciding whether to perform this step.

Before you consider making any head adjustments, take a close look at the tape path as you are playing a tape. With good room lighting, and perhaps enlisting the assistance of a small flashlight, closely sight down the tape path, watching the reflection of light from the tape backing. That is an excellent way to ensure that the tape guides have not become bent or misadjusted. If, for example, you see one edge of the tape crimped against a particular guide, that could be an indication of trouble. However, be extremely careful before adjusting anything. Take careful notes of all abnormalities; and, if you do make any adjustments, be sure to note the extent of the adjustment. It might subsequently turn out that that was not the source of the problem. If so, you will want to return the adjustment to its original setting.

Make sure that alignment tools to be used in the head area are all demagnetized or non-metallic before you begin. Also, take a look at Fig. 4, which will familiarize you with the various head-adjustment parameters along with the common adjustment-screw locations. Note that these adjustments may or may not be located just as shown; and in some cases, not all of these adjustments may be present.

Figure 5 shows the proper track spacing for most 1/4-inch open-reel tape standards. While track spacing relative to the tape edge is obviously very important, it's not something you can do much about during a restoration process, unless, of course, you need to replace a head. The reason is that many "used" machines have developed a wear groove across their front face as a result of tape friction. If, for some reason, vertical head positioning has gotten out of alignment (it's unlikely this happened at the factory), the odds are that the wear groove reflects that condition. If so, and if you were to readjust the vertical position to conform with Fig. 5, it would create an "overlap" condition over one edge of the groove. That would most likely mean the creation of an air gap between the

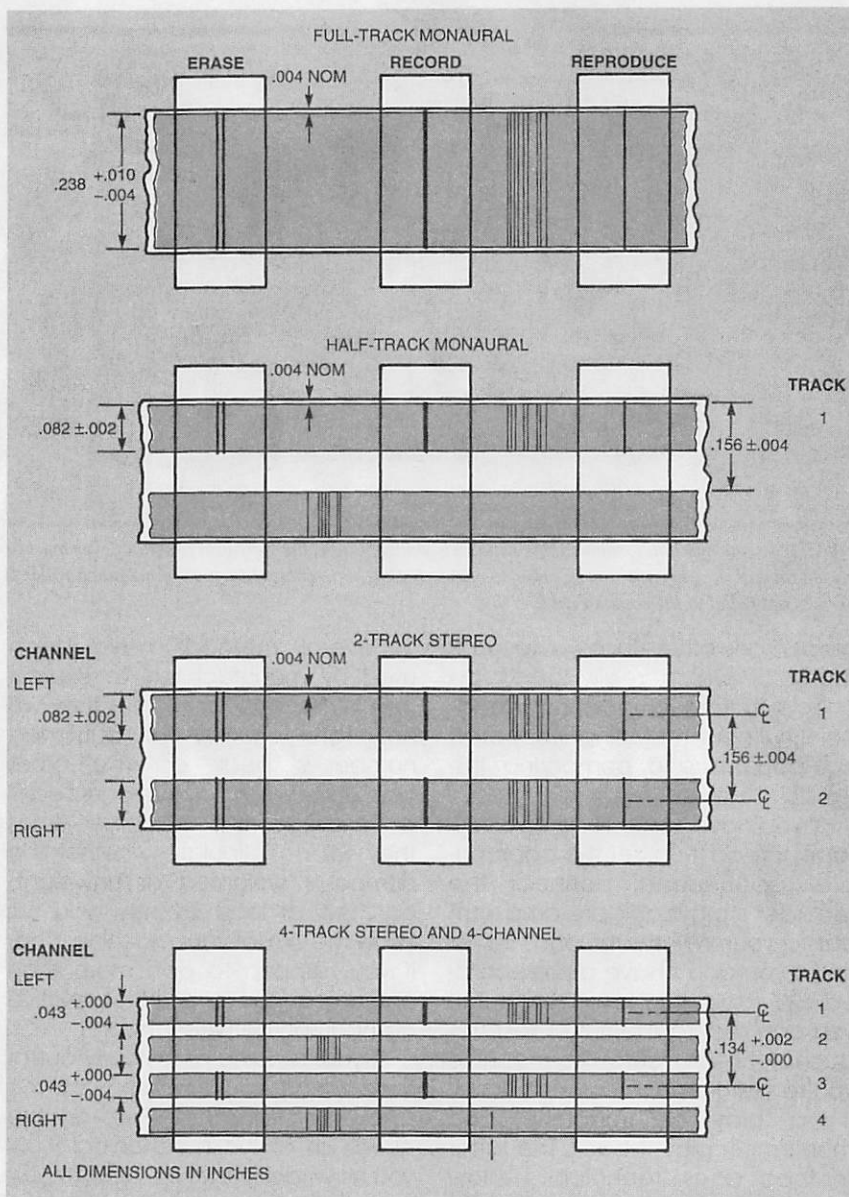


Fig. 5. Track spacing standards for popular 1/4-inch tape audio recorders.

head and the tape at one side. The result of this could be vertical tape skew, increased tape wear, poor high-frequency response, and reduced S/N on the track(s) closest to the air gap. The bottom line here is that it's not a good idea to mess with the vertical head alignment on used machines whenever a wear groove is present.

If you have a four-track machine, and do not hear any crosstalk (from alternate tracks) when playing commercial prerecorded tapes, then the odds are that your play head is in proper vertical alignment. With a two-track machine, you will have to rely on careful visual observation.

The erase-head gap is typically slightly longer than that of the record head, so erase-head height is usually not an issue. However, that can be easily verified, and you don't even need instruments to read the result. Simply record a 1-kHz peak signal; then rewind and place the machine in record again, this time with no input signal, and while monitoring the output by ear. If you don't hear any trace of the 1-kHz tone, the erase-head height is okay. Note, however, that even if you do still hear the tone faintly, it doesn't necessarily mean that erase-head height is to blame. It could also be inadequate current flowing to the erase head, perhaps due to weak

ELECTRIFY Your Library

when you join EBC

GET **5** Books
FOR ONLY
\$4.95

Values to
\$257.85

BUILD YOUR OWN
TEST EQUIPMENT




0155593 \$22.95



0707618 \$21.95



0239193 \$27.95
Hardcover

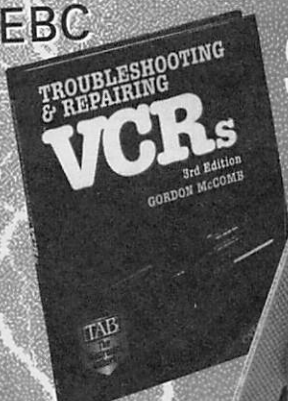

1550178 \$22.95



0317917 \$80.00



0497060 \$34.95
Hardcover




0304068 \$17.95



073092X \$19.95



0650780 \$24.95

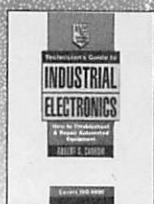

0112738 \$47.95



0157537 \$44.95



0236143 \$24.95



0242054 \$24.95




0350787 \$44.95



1577564 \$24.95




0380767 \$39.95

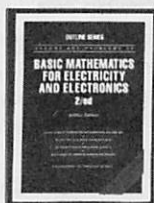

0044392 \$14.95




1575472 \$29.95

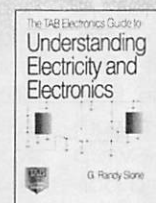


0582165 \$19.95



0331898-XX \$89.50
Hardcover/Counts as 2

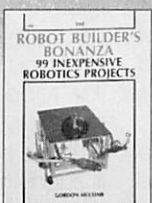

1571469 \$18.95

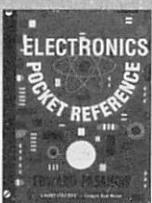

0487375 \$24.95



0428433 \$60.00
Hardcover

As a member of the ELECTRONICS BOOK CLUB...

you'll enjoy receiving Club bulletins every 3-4 weeks containing exciting offers on the latest books in the field at savings of up to 50% off the regular publishers' prices. If you want the Main selection, do nothing and it will be shipped automatically. If you want another book, or no book at all, simply return the reply form to us by the date specified. You'll have at least 10 days to decide. If you ever receive a book you don't want due to late delivery of the bulletin, you can return it at our expense. Your only obligation is to purchase 2 more books during the next 12 months, after which you may cancel your membership at any time. And you'll be eligible for FREE BOOKS through our Bonus Book Program.

A shipping/handling charge and sales tax will be added to all orders. All books are paperback unless otherwise noted. Publishers' Prices Shown © 1998 EBC

If coupon is missing, write to:
Electronics Book Club®

A Division of The McGraw-Hill Companies
P.O. Box 549, Blacklick, OH 43004-0549

PHONE: 1-614-759-3666 (8:30 a.m. to 5:00 p.m. EST Monday-Friday)

FAX: 1-614-759-3749 (24 hours a day, 7 days a week)

INTERNET: www.bookclubs.mcgraw-hill.com

RPIE498

Electronics Book Club®

A Division of The McGraw-Hill Companies
P.O. Box 549, Blacklick, OH 43004-9918

☐ **YES!** Please send me the books listed below, billing me just \$4.95 plus shipping/handling & tax. Enroll me as a member of the **Electronics Book Club®** according to the terms outlined in this ad. If not satisfied, I may return the books within 10 days without obligation and my membership will be cancelled. I agree to purchase just 2 more selections at regular Club prices during the next 12 months and may resign anytime thereafter.

Code numbers of my books for \$4.95

--	--	--	--

If you select a book that counts as 2 choices, write the book number in one box and XX in the next.

Name _____

Signature _____

Address/Apt.# _____

City _____ State _____ Zip _____ Phone _____

Valid for new members only, subject to acceptance by EBC. Canada must remit in U.S. funds drawn on U.S. banks. Applicants outside the U.S. and Canada will receive special ordering instructions. A shipping/handling charge & sales tax will be added to all orders. ©1998 EBC

RPIE498

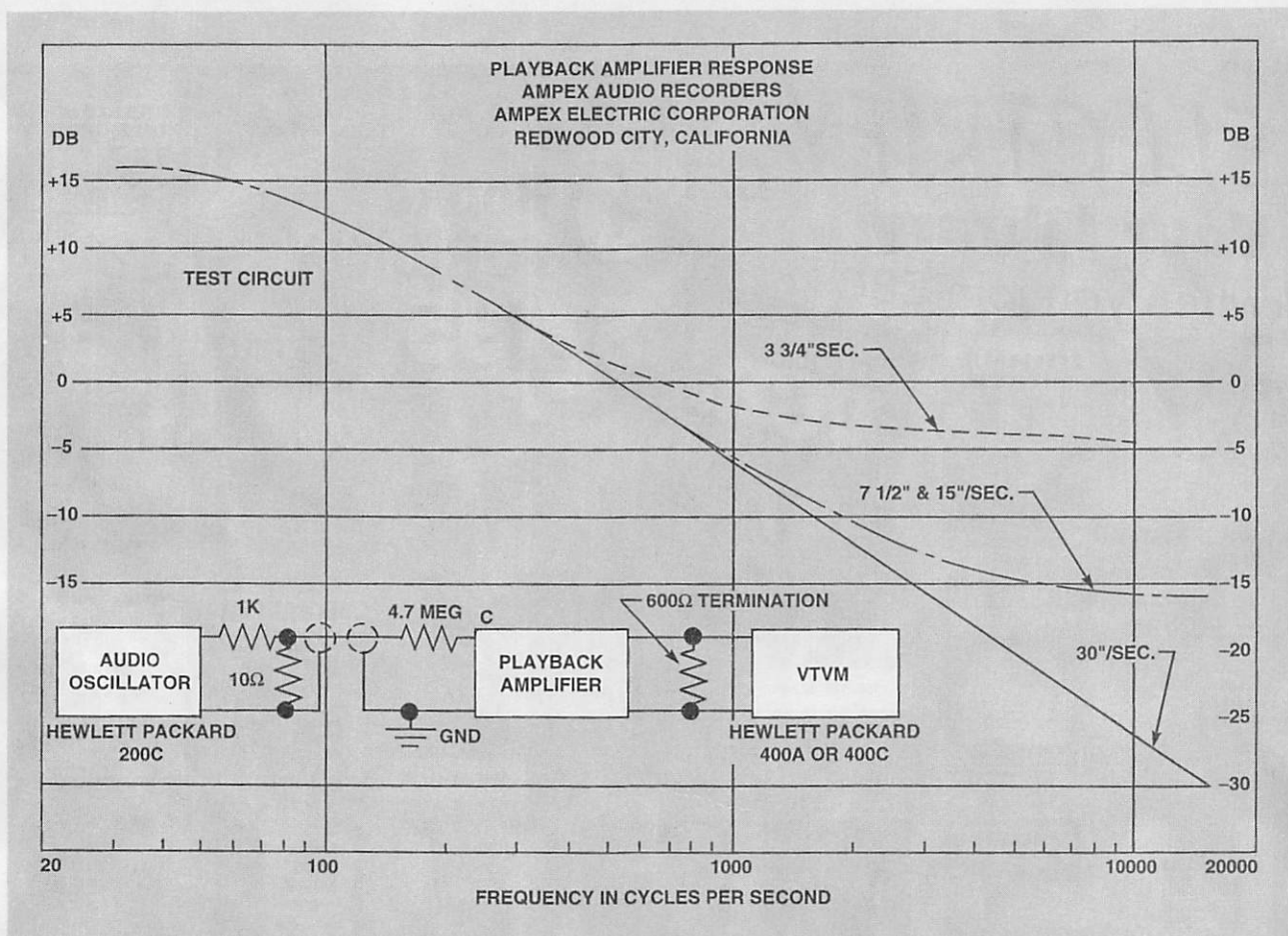


Fig. 6. Typical playback-amplifier equalization curves.

emission of the bias/erase oscillator tube, or a leaky oscillator capacitor. If you have a schematic diagram of the electronics, check to see if a current or voltage specification is given for the erase signal.

Tape wrap has to do with the extent of tape contact across the head, and is a function both of the shape of the front of the head (which, obviously, you can't control—but remember this if you replace a head with a non-identical substitute), and the "penetration" the head makes into the line of the tape path. Penetration is sometimes adjustable, usually by moving the platform onto which the head is mounted forward or backward. Excessive penetration might be, for example, where the head pushes the tape far enough forward to where it is lifted from the adjacent guides, or another head. Insufficient penetration would be where the head barely touches the tape. There's no mathematical precision here; just look at how the heads are

situated relative to the penetration issue. For example, often the record and play heads have similar geometry, and so one might expect a similar tape wrap. Another clue is to look very closely at the groove worn into the head face. If the tape wrap is such that it's not covering a portion of the wear area, that could be an indication that tape wrap is now insufficient.

A related adjustment (called "zenith") ensures that the head gap is centered within the portion of the tape that is in contact with the head. If a significant wear groove is present, however, it might be better to leave this adjustment alone.

The "tilt" alignment ensures that the "front-to-back" angle of the heads is correct with respect to the tape. If it is off, the tape will have more head contact on one side than on the other. One way to observe that is to look at the wear pattern on the head. If it is in the shape of a trapezoid instead of a rectangle, you likely have a poor tilt

adjustment. As with head height, it's not a real good idea to go making changes if this situation has been around long enough to create a significant trapezoidal groove. However, if the tape wrap is fairly extensive, it might be okay to make a small correction here. You might be best off to just note the problem, and then see how successful the rest of the electrical spec checks and adjustments are before changing the tilt settings. If all else comes back to spec, and the "dropout" level (instability in playback level) is tolerable, then leave it alone.

Next, we'll tackle azimuth adjustments, which will ensure that the record- and play-head gaps are perpendicular to the length of the tape. The first check should be made on the play head, and you will need a standard alignment tape to accomplish this. Typically these tapes will have a number of recorded passages, often with a voice lead-in to identify the next passage. (If you have need for an

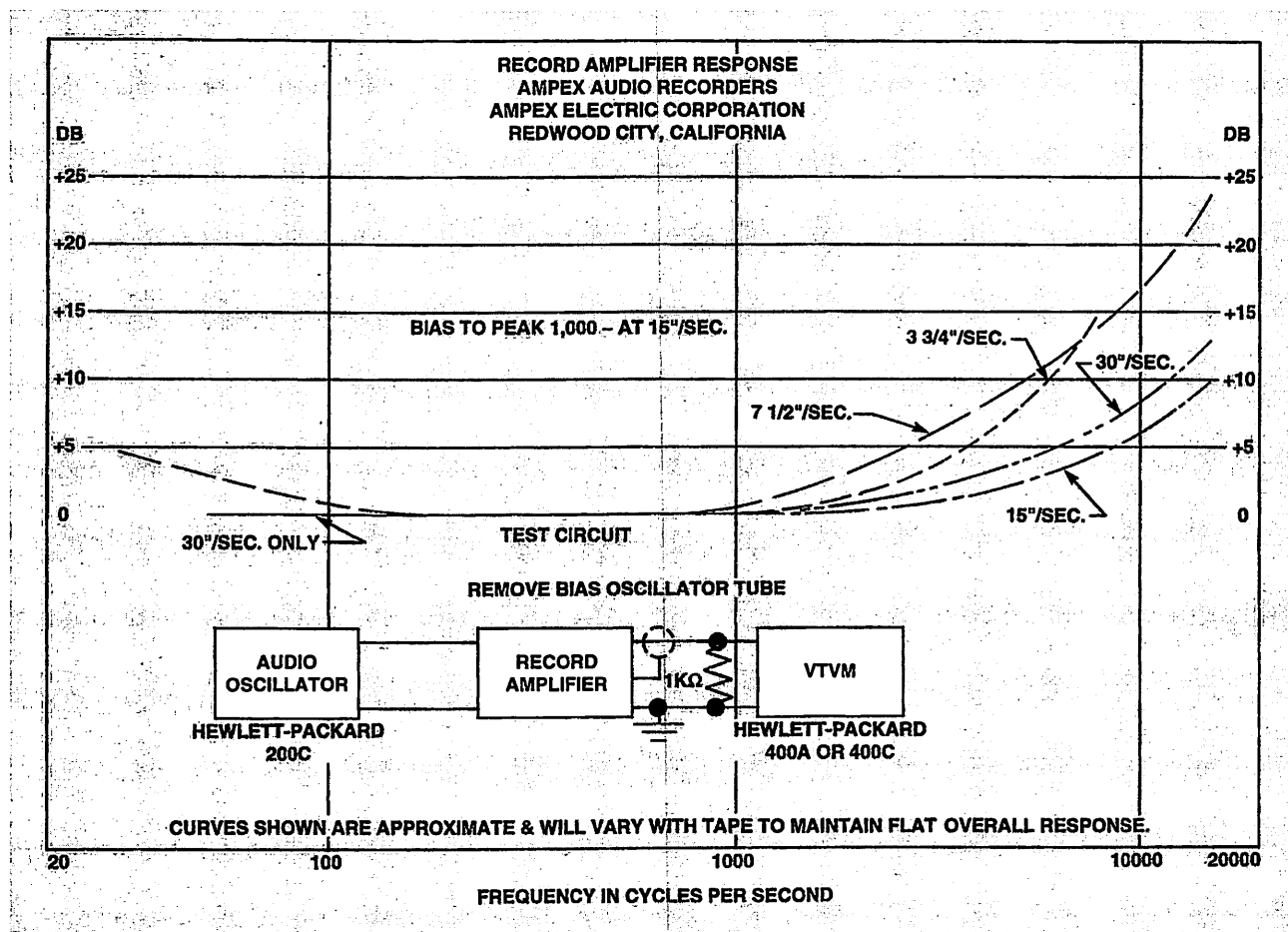


Fig. 7. Typical record-amplifier equalization curves.

alignment tape, you may contact the author c/o EC Designs at the address given in the "For More Information" box for suggestions.) The passage of interest here is a high frequency tone (often 10 kHz). Before playing it, identify which screw on the play-head platform influences the azimuth angle, and clean off any locking paint as necessary. Adjust for a peak level while watching an output meter, then take careful note of the extent of adjustment (just in case you need to reset it later).

Now let's align the record-head azimuth. (If your machine has a combination record/play head, you're done; just go to the next adjustment.) Set up the machine to record a 10-kHz tone onto a blank tape, at a level of about -15 dB. While watching the simultaneous play-head output on a meter, adjust the record-head azimuth very slowly for a peak reading (note that there is a delay between the time you make the adjustment and the

time that portion of the passage reaches the play head). Again, write down the amount of adjustment needed.

That completes the head-alignment process. Before we leave the subject of heads, and get into frequency response, it's probably worthwhile to spend a moment on head wear. While all tape heads wear out eventually, they do last a long time. Typical head life from an early 1970s machine, using premium tapes, could be 4,000 hours or more. There's no sudden, magic point where the heads become useless. Rather, the wear process is gradual, eventually affecting the electrical specifications. Further, different model heads have different head-gap depths and are composed of different materials with still different wear characteristics. What I'm saying here is to not rule out a set of heads just on the basis of the size of the wear groove. Check the electrical specs first. See what effect bias and level adjustments might have.

You might discover that there are still hundreds of hours of life remaining!

On the other hand, improper cleaning of the tape path very often spells premature doom for the tape heads—if not in the form of poor frequency response, then perhaps in the form of excessive dropouts (maybe as a result of "craters" formed on a head face due to a glob of oxide stuck there for a long time). While it certainly pays to carefully note those issues when evaluating a machine for potential purchase, once again don't categorically rule it out on the basis of improper wear; just be cautious.

General Adjustments. Now that we've gotten the mechanics back to spec, and we're confident that the tape heads are aligned properly, what's left is a number of general electronic checks and adjustments. Please note that the following procedure is very general in nature. Tape recorder electronic designs vary widely; and, as such, you are

always better off if you have the manufacturer's alignment instructions. If you do, then follow those instructions in lieu of the following. If you do not, then proceed with the following instructions, but bear in mind that this might not be the optimum way to set up your machine. While this procedure will work, a few things might get overlooked, and other things may have to be done twice due to interacting controls.

The approach we're going to take is to first make a few assumptions. If true, we can streamline the remaining electronics alignment. (If they are not true, we'll find that out anyway, in the process of the tests we perform.) These assumptions are based on the electronic alignment controls still appearing to be at (or near) their original factory settings, and on the overall condition of the electronics appearing to be excellent (and/or you have already replaced any "suspect" components—leaky wax/paper capacitors, weak tubes, etc.). If these assumptions are correct, then it's a good bet that the equalization and approximate record- and play-level calibrations are close to spec.

Frequency-Response/Bias Adjustment.

Let's take a look at the frequency response. To do this, connect your audio oscillator and THD analyzer (assuming that it also houses an audio voltmeter), and thread a blank tape of the formulation you will be using on this recorder. If the machine has separate record and play heads, this process will proceed much faster as that will allow simultaneous playback monitoring as you adjust the bias. (We'll assume this configuration for the following adjustments. If you do not have playback capability during record, you will have to alternately record, then play back several times to find the optimum settings.)

Initially, set the oscillator to 1 kHz and a level of 0 VU on the recorder meter. Now, reduce the oscillator level by 20 dB, and, while monitoring the source with the external voltmeter, set the voltmeter pointer (achievable if your instrument has a "set level" mode) to a 0 VU meter reading. Now place the machine into record mode (let's start at the

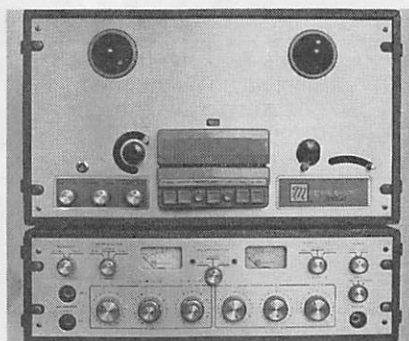


Fig. 8. Magnecord Model 1024 deck. Another "big iron" machine from the 1960s.

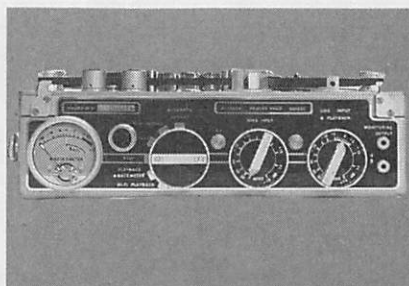


Fig. 9. Nagra Model III recorder. This was a professional portable machine, popular with the motion-picture industry.

fastest tape speed on your recorder), and switch the output to "playback" monitoring. The tape output level at this point might, or might not, be at 0 VU. Don't worry about that right now; just note the level relative to the 0 VU setting you had when looking at the record preamp.

Now switch the oscillator to 10 kHz (while maintaining the same oscillator level). Ideally, the 10-kHz output level should be at 0 VU, but a level within +3 dB or so is often still within factory spec. If it's much higher than that, try increasing the bias-level control to bring the 10-kHz response into that range. Now, increase the oscillator frequency, and note the point where the response trails off to -3 dB. If the frequency is less than the high-frequency-response spec, and if the 10-kHz response was identical to that at 1 kHz, then you might try going back to 10 kHz, decreasing the bias a bit to increase the 10-kHz level to, say +2 dB, and then check the 3 dB drop-off point again.

If you are unable to achieve the factory frequency-response specs, something is obviously wrong. This could be due to worn heads,

improper equalization (either record or play), or a faulty preamp component (again either record or play). The frequency-response portion of a standard alignment tape could be used to rule out the play head and play-preamp/equalization circuitry. If that's okay, then the record circuitry should be considered suspect. If you have an oscilloscope, and are adept at such things, you might find a faulty component in a preamp section.

Total Harmonic Distortion (THD). If, on the other hand, the machine now meets the high-frequency spec, the next step is to measure the THD at 0 VU. Simply make a 1-kHz recording at 0 VU (on the recorder meter) for a couple of minutes; then, while playing it back, "set level" at 0 VU on the THD meter, then switch to "distortion" mode, and adjust frequency and balance for a null. If the THD is what you want it to be for a 0-VU recording level, then proceed to the S/N test, coming up next. If the distortion is greater than what you want it to be at 0 VU, then you can try to go back and increase the bias a bit more. While that will bring down the distortion, it will also decrease the high frequency response. So, if that is not to your liking, you can try the THD test again, this time at, say -3 dB.

If the THD is to your liking, the next step is to re-calibrate the record preamp "VU meter record level" to read 0 VU for that signal level going to the head. (This is another area where you must be careful if you do not have a schematic. Some recorder designs do not have a separate VU-meter calibration pot. Therefore, the only record-level adjust is sometimes an overall record level, acting on both the VU meter and the signal going to the head. If that is the case, it will be apparent when you try to adjust it; just be sure to watch for it.)

If your machine has separate bias controls for each speed, go ahead at this point and complete the bias adjustments, along with THD checks.

Signal-to-Noise Ratio (S/N). Assuming frequency response and THD is now acceptable, the next

step is to measure S/N. If you wish to measure S/N relative to 0 VU, simply make another recording at 0 VU for about 20 seconds (otherwise, if measuring relative to 3 % THD, first determine the "head room," then set the VU level for that peak reading. You may need to use an external meter for this if the recorder meter is above full scale); then, while still in record, turn off the oscillator—or turn the record level control down to zero—and continue recording for another 30 seconds. Play back that same section of tape, quickly "setting level" on the audio meter to 0 VU and then, when the level drops, measure the decade drops and residual meter reading to determine the S/N. If it meets spec, congratulations! If it doesn't, then—once again—you've got some work to do.

Some common causes for poor S/N, beyond what we've already covered, are noisy transistors or tubes, faulty capacitors, and sometimes (although much less often) even resistors. This can be a very time-consuming investigative process. An oscilloscope may be very helpful here to spot the "corrupt creature."

It's worth mentioning again that we have really simplified the alignment process described above. It may, or may not, be totally adequate for your machine. If you have a "professional" machine, for example, then you should pay more attention to "standard" levels. Use the alignment tapes, along with the manufacturer's instructions, to set up your recorder.

Equalization. Finally, let's cover equalization. So far, we've been assuming that record and play equalization is probably okay. If you need to check it out, however (or, are simply curious), let's take a look at what's involved.

Figure 6 shows the playback equalization published by Ampex for their recorders back in 1953. These curves are similar to those for many other recorders, representing an approximate doubling in signal amplitude with a doubling of frequency (an increase of 6 dB per octave). This has to do with the physics of magnetic recording,



Fig. 10. Acme Model 1500 recorder. A modest 3-inch reel machine, using "rim drive" and a swing-out permanent magnet to erase previous recordings when in the record mode.

and, in theory at least, will be the same for all machines. This curve "levels off" at the higher frequencies due to natural losses.

If you have a standard alignment tape for this purpose, that would be the quickest means to check conformance with the curves at each speed on your recorder. If not, then a setup similar to the one shown in Fig. 6 can be used to directly inject the test frequencies. One frequency representing each of the low-, mid-, and high-frequency points should be adequate (e.g., 30 Hz, 1 kHz, 10 kHz). Recorders differ as to the adjustments available: from none at all (fixed equalization), to a single control (usually influencing the high-end response), to multiple controls (high- and low-frequency adjustments, sometimes with one set for each machine speed).

Figure 7 shows some record-equalization curves, published for the early Ampex professional machines. Before checking or adjusting record equalization, be sure that play equalization has been set properly, as the measuring of record equalization uses the play preamp as well to ensure overall flat response. Unlike play equalization, record equalization may have to be reset for significantly different tape formulations; particularly, for example, if converting from a typical 1950s formulation (such as Scotch 150) to a premium 1970s low noise tape (such as Maxell UD35).

Note the test circuit shown in Fig. 7, which is to be used if you want to measure the actual signal being applied to the head. Also note the recommendation that the bias oscillator tube be removed during the measurements; that's done to

eliminate any bias component from influencing the readings. If your recorder is transistorized, you would need to carefully select a test point at which to insert the VTVM; it should be after the equalization boost and before mixing with the bias signal (just before delivery to the record head). Then, make sure to check for presence of the bias signal, after you have set up your audio oscillator, by temporarily removing the audio frequency and ensuring that any bias component is minimal.

Perhaps a simpler method, however, is just to read the overall response throughout the recorder, exploiting the fact that we now know that the play equalization is correctly adjusted. We also know that the bias has already been optimized for the desired tape formulation. Therefore, if we simply connect an audio oscillator to the record input jacks, thread the desired tape, enter record mode, set the input level to -20 dB, and then monitor tape output with our trusty audio meter, we should be able to sweep through the frequency range and see a reasonably flat response (depending on the manufacturer's frequency response spec).

If the response is not flat, then carefully adjust the record equalization. Note, however, that you will then have to go back and reset bias, and also re-check THD. It shouldn't take more than two "equalization-bias" adjustment cycles to get a feel for the capabilities of your machine and thus choose an optimum setting. If the response will not smooth out, and you have confirmed proper operation in all of the previous steps, then you must suspect the equalization circuit components.

Believe it or not, if you have successfully made it through to this point, you should now have a tape recorder capable of virtually the same performance as when new. As a matter of fact, the existence of modern premium tapes could mean even better specs than when new if your machine is more than 25 years old.

Completing the Restoration Process. What remains in the restoration process is all the cosmetic stuff;

FOR MORE INFORMATION

This article is based on the new book, *Evolution of the Audio Recorder* by the author, Phil Van Praag. It contains over 500 pages of history, evolution, restoration, photos, and a price guide. It's available at \$39.95 postpaid, from EC Designs, P.O. Box 33, Genesee Depot, WI 53127.

everything from re-gluing and pinning cracked or broken cabinet joints, to buffing front panels, to restoring worn lettering, to replacing hardened rubber feet, and on and on. The list is long, but the additional work is necessary if the restoration is to be complete.

I sincerely wish you the best of luck in these pursuits. Whether your machine is a "big iron" Magnecord 1024 (Fig. 8), a professional Nagra III (Fig. 9), or a modest Acme 1500 (Fig. 10), it will be well worth the effort. If you "stick it out" to a successful completion, I'm sure you'll derive much more satisfaction and enjoyment from the subsequent use of your "like new" tape recorder. Ω

FECHNER PHENOMENON

(continued from page 51)

of pulse-width modulation to control a DC motor: It tends to make them run hotter than they would if you simply cut off the voltage. Inexpensive motors could easily burn out if run continuously for prolonged periods of time. In short, don't run the demonstration for hours on end without some type of heatsink or another cooling arrangement, or, at the very least, shut things down and let the motor's insides cool off at regular, reasonable intervals.

PostScript for the Fechner Disc.

As stated earlier, the image shown in Fig. 1 can be photocopied and attached to a motor shaft for a quick look at the Fechner Phenomenon. However, you may want to explore the way that perceived colors vary with arc segment length and with changes to the black field. To do that you could try to re-create the disc in a graphics application, but due to the pattern's need for precisely positioned, perfectly

circular arcs as well as the pattern's lack of symmetry, you will benefit greatly if you write PostScript code instead. Then, by editing the PostScript text, you could create a disc of any size as well as explore the relationship between image segments and color effects.

If you read this magazine often, especially Don Lancaster's "Tech Musings" column, you are no doubt aware of PostScript, which is an object-oriented page-description language. The page-description programs are generated by software applications, transferred to a PostScript printer, and interpreted to produce a printed page. The language has an extensive array of commands and operators to facilitate the creation and placement of precise and often complex figures and graphics. Compared to PostScript's capability, our Fechner Disc is quite simple. To get you started, Listing 1 contains the PostScript code that generated the Fechner Disc in Fig. 1. Note that the image comprises a set of arc segments. An outer circle is defined as an arc segment from 0 to 360 degrees. The half black segment is defined as an arc from 0 to 180 degrees; the "fill" statement defines it as a black area.

All of the arcs have the same center coordinates, (270, 350) and various start and end angles. The remarks in the listing identify the function of each of the code statements, and show the parameter values for the image generation. To produce the image, you need to store the PostScript code as a text file and send it to a PostScript printer under an operating system command that tells the printer to process the image, not print the text. Under DOS, for example, use the COPY command with the PostScript text file as the file to be copied and the PostScript printer as the destination. Ω

TIPS FOR MAIL ORDER PURCHASE

It is impossible for us to verify the claims of advertisers, including but not limited to product availability, credibility, reliability and existence of warranties. The following information is provided as a service for your protection. It is not intended to constitute legal advice and readers are advised to obtain independent advice on how to best protect their own interests based upon their individual circumstances and jurisdictions.

1. **Confirm price and merchandise information** with the seller, including brand, model, color or finish, accessories and rebates included in the price.

2. **Understand the seller's return and/or refund policy**, including the allowable return period, who pays the postage for returned merchandise and whether there is any "restocking" or "return" charge.

3. **Understand the product's warranty.** Is there a manufacturer's warranty, and if so, is it for a U.S. or foreign manufacturer? Note that many manufacturers assert that, even if the product comes with a U.S. manufacturer's warranty, if you purchase from an unauthorized dealer, you are not covered by the manufacturer's warranty. If in doubt, contact the manufacturer directly. In addition to, or instead of the manufacturer's warranty, the seller may offer its own warranty. In either case, what is covered by warranty, how long is the warranty period, where will the product be serviced, is there a charge for service, what do you have to do to obtain service and will the product be repaired or replaced? You may want to receive a copy of the written warranty before placing your order.

4. **Keep a copy of all transactions**, including but not limited to cancelled check, receipt and correspondence. For phone orders, make a note of the order including merchandise ordered, price, order date, expected delivery date and salesperson's name.

5. **If the merchandise is not shipped within the promised time**, or if no time was promised, within 30 days of receipt of the order, you generally have the right to cancel the order and get a refund.

6. **Merchandise substitution without your express prior consent is generally not allowed.**

7. **If you have a problem with your order or the merchandise**, write a letter to the seller with all the pertinent information and keep a copy.

8. **If you are unable to obtain satisfaction from the seller**, contact the consumer protection agency in the seller's state and your local Post Office.

If, after following the guidelines, you experience a problem with a mail order advertiser that you are unable to resolve, please let us know. Write to Advertising Department, Gernsback Publications Inc., 5008 BI-County Blvd. Farmingdale, NY 11735.

Be sure to include copies of all correspondence.

**Support
The College Fund.
Call 1-800-332-UNCF.**

The College Fund/UNCF
A mind is a terrible thing to waste.



All About Quadrature, and More

MOST SCIENCE STUDENTS AND ENGINEERS SHOULD LEARN AND APPLY THIS ESSENTIAL RULE: AN HOUR SPENT IN THE LIBRARY IS WORTH A MONTH IN THE LAB. SAME GOES FOR ENGINEERS. THAT'S BECAUSE THERE'S NOT MUCH POINT

in doing any personal lab work or any product development when someone else has long ago clearly created something much better, or has found all of the hidden insider "gotchas" that are flat out going to prevent you from getting where you think you are headed. Let's begin this month with a topic that starts off with a lot more library than lab time.

Understanding Quadrature

I've often been accused of heading off at right angles to everyone else. It turns out that there often is a darn good reason for doing so.

Take a bicycle wheel. Tie a ribbon on its rim. Spin it on a north-south axis as illustrated in Fig. 1. When viewed "axle-on" from the south, you will see the ribbon going round and round, spending time east, west, up, and down from the axle.

When viewed from the west, you should see a ribbon bouncing up and down. Rapidly changing in mid-path, but spending "dwell time" near its upper and lower travel limits. The west-view waveform traced out by the ribbon is often called a sinusoid or simply a sinewave.

Now view the wheel from the top. You'll again see the ribbon bouncing back and forth, but this is different somehow. It is still sort of a sinewave, although this particular "sinewave" responds to the east and west ribbon motion rather than the up and down motions of the previous

one. By itself, the shape does seem sinusoidal. But compared to the up and down viewing, we have a cosine. Such a cosine wave will be phase shifted by precisely 90 degrees from its sinewave counterpart.

Note particularly that the side view ignores any and all back and forth ribbon motion, while your top view will ignore any and all up and down ribbon motion. The information content on the one channel is invisible to that of the other!

The two waveforms are said to be either orthogonal or in quadrature. Quadrature waveforms do occur over and over again in electronics.

For instance, your ribbon position could define a vector from your axle, expressed in polar coordinates. Our vector has a length and a direction. In a math space, your angle will be in degrees counterclockwise from east. Alternately, in a geographical space, the degrees are clockwise from north. Obviously, you should pick one or the other and stick with it.

Electronic stuff almost always uses math-space degrees. The west-view sinewave and the top-view cosine wave instead define your ribbon position with two scalar quantities, or a pair of single values. Often, quadrature measurements or waveforms can be used to convert between a vector and its two scalar components. Such separated parts are said to be in rectangular or Cartesian coordinates.

For example, say you have a 20-inch bike wheel with a 10-inch radius, and say the ribbon happens to slant +60 degrees in math space. The top viewed east to west, or the cosine component, should be +5.0 inches, because the trigonometric cosine of 60 degrees is 0.5000. The side viewed up-down or sine component will be +8.660 inches, because the trigonometric sine of 60 degrees is calculated as 0.8660.

Such trig values are easily found in math tables, in scientific calculators, and even slide rules. They also could be created by a series approximation algorithm or whatever.

The side or sine view is sometimes called the real or the I (in-phase) component; the top or cosine view is sometimes called the imaginary or the Q or (quadrature) component. The letter *j* is often used to denote an electronic imaginary axis (it seems that current had first dibs on the more obvious *i* variable).

Neat Quadrature Tricks

One remarkable property is that all quadrature channels of information can be independent of each other. If you try multiplying any sine times a cosine over precisely one cycle, you will get a zero result.

That happens because your cross products change for each quadrant.

NEED HELP?

Phone or write all your US Tech Musings questions to:

Don Lancaster
Synergetics
Box 809-EN
Thatcher, AZ 85552
Tel: 520-428-4073

US e-mail: don@tinaja.com
Web page: www.tinaja.com

new from DON LANCASTER

ACTIVE FILTER COOKBOOK

The sixteenth (!) printing of Don's bible on analog op-amp lowpass, bandpass, and highpass active filters. De-mystified instant designs. **\$28.50**

RESEARCH INFOPACKS

Don's instant cash-and-carry flat rate consulting service. Ask any reasonable technical question for a detailed analysis and complete report. See www.tinaja.com/info01 for specifics. **\$75.00**

CMOS AND TTL COOKBOOKS

Millions of copies in print worldwide. THE two books for digital integrated circuit fundamentals. About as hands-on as you can get. **\$28.50** each.

INCREDIBLE SECRET MONEY MACHINE II

Updated 2nd edition of Don's classic on setting up your own technical or craft venture. **\$18.50**

LANCASTER CLASSICS LIBRARY

Don's best early stuff at a bargain price. Includes the CMOS Cookbook, The TTL Cookbook, Active Filter Cookbook, PostScript video, Case Against Patents, Incredible Secret Money Machine II, and Hardware Hacker II reprints. **\$119.50**

LOTS OF OTHER GOODIES

Tech Musings V or VI	\$24.50
Ask the Guru I or II or III	\$24.50
Hardware Hacker II, III or IV	\$24.50
Micro Cookbook I	\$19.50
PostScript Beginner Stuff	\$29.50
PostScript Show and Tell	\$29.50
PostScript Video & secrets	\$29.50
PostScript Reference II	\$34.50
PostScript Tutorial/Cookbook	\$22.50
PostScript by Example	\$32.50
Understanding PS Programming	\$7.50
PostScript: A Visual Approach	\$22.50
PostScript Program Design	\$24.50
Thinking in PostScript	\$22.50
LaserWriter Reference	\$19.50
Type 1 Font Format	\$16.50
Acrobat Reference	\$24.50
Whole works (all PostScript)	\$380.00
Technical Insider Secrets	FREE

BOOK-ON-DEMAND PUB KIT

Ongoing details on Book-on-demand publishing, a new method of producing books only when and as ordered. Reprints, sources, samples. **\$39.50**

THE CASE AGAINST PATENTS

For most individuals, patents are virtually certain to result in a net loss of sanity, energy, time, and money. This reprint set shows you Don's tested and proven real-world alternatives. **\$28.50**

BLATANT OPPORTUNIST I

The reprints from all Don's Midnight Engineering columns. Includes a broad range of real world, proven coverage on small scale technical startup ventures. Stuff you can use right now. **\$24.50**

RESOURCE BIN I

A complete collection of all Don's Nuts & Volts columns to date, including a new index and his master names and numbers list. **\$24.50**

FREE SAMPLES

Check Don's Guru's Lair at <http://www.tinaja.com> for interactive catalogs and online samples of Don's unique products. Searchable reprints and reference resources, too. Tech help, hot links to cool sites, consultants. email: don@tinaja.com
FREE US VOICE HELPLINE VISA/MC

SYNERGETICS
Box 809-EN
Thatcher, AZ 85552
(520) 428-4073

FREE catalog: <http://www.tinaja.com>

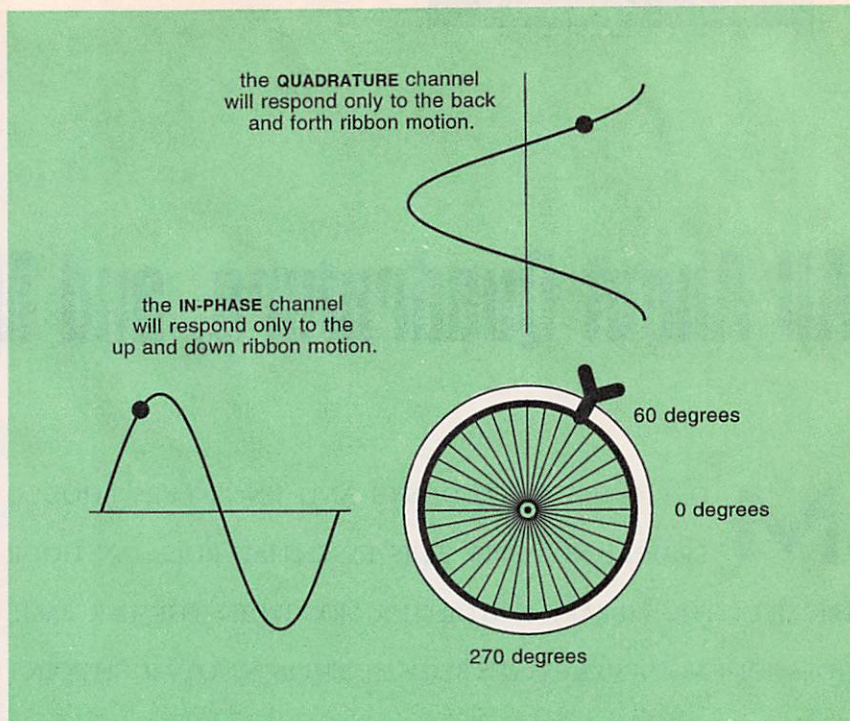


FIG. 1—QUADRATURE WAVEFORMS are mechanically or electrically shifted by precisely 90 degrees from each other. They have many uses.

Algebraic signs are both positive in quadrant I and are both negative in quadrant III. But they are opposites in quadrants II and IV.

Yet another group of remarkable properties is that the slope for any cosine is a quadrature sine wave! And the slope of a sine wave is a negative quadrature cosine wave. A different name for "slope" is the derivative.

Further, the accumulated area under any sine wave is a quadrature cosine wave. And the accumulated area under the cosine wave is a negative quadrature sine wave. Another name for "accumulated area" or any "area under the curve" is the mathematical integral.

As with trig values, integrals and derivatives are found in books of math tables, or can be generated by finding slopes or by adding up cumulative areas. See any introductory calculus book for all the gory details.

In fact, you could build a dandy oscillator simply by cascading two integrators and a sign changer. That circuit "solves" the fundamental differential equation relating sines and cosines, and thus simply has to create them. Such an oscillator can simultaneously provide you with a pair of quadrature sine and cosine wave outputs.

A lossy variation on cascaded sine and cosine integrators is known as a state-variable active filter, which can offer you a stable high Q. One obscure use for

such a circuit is quadrature art where psychedelic audio color patterns are displayed on an oscilloscope or a computer screen. More details on state variable filters and quadrature art applications can be found in my *Active Filter Cookbook*.

Although the sine values and the cosine values can end up completely independent of each other, together they should define a unique ribbon position or phase on the wheel. That suggests that we can place two totally different channels of information on a rotating vector or a similar carrier, which lets us put twice as much stuff in a given bandwidth than we might have thought we could.

Those channels might be called an "I" (for in phase) and the "Q" (for quadrature) channel. They become quite important in cellular communications and wireless modems. One older example of I and Q channel use is color TV where the chroma information is set by a pair of color difference values.

Generating Quadrature Signals

One really big use for quadrature signals can involve single-sideband communications. Figure 2 shows how a broadband quadrature phase-shift network can be used to create SSB transmissions. For those unfamiliar with it, SSB gives us compelling advantages over earlier AM or amplitude modulation in that only half the bandwidth is needed and no raw

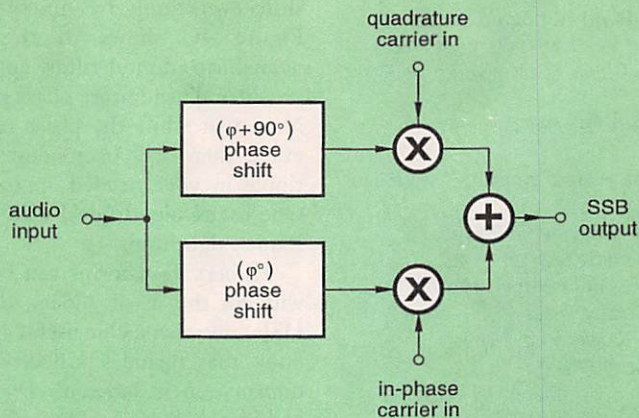


FIG. 2—ONE POPULAR METHOD of single-sideband generation uses a broadband audio quadrature phase shifter.

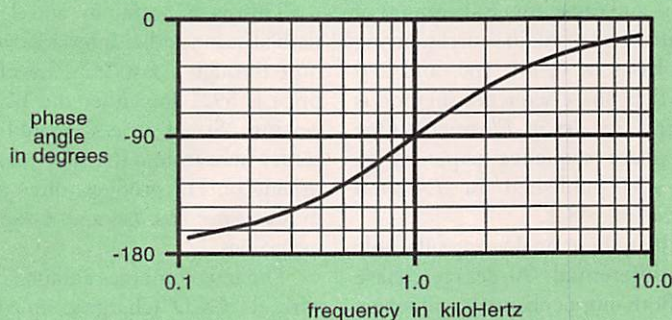
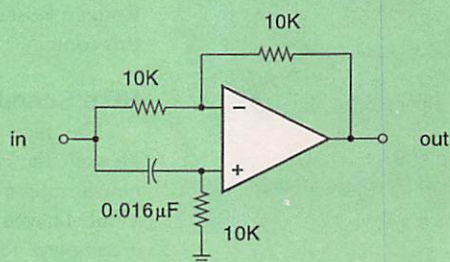


FIG. 3—A FIRST-ORDER ALL-PASS active filter can be used as an equalizer, cranking out phase as fast as some other circuit cranks it in.

carrier power needs to be transmitted or otherwise wasted.

Generating a quadrature signal at a single frequency is no big deal. We have seen that changing a physical point of view by 90 degrees does it. You also can simply stall or delay for a quarter cycle.

For instance, a 1-kHz audio sine wave has a time period of one millisecond. To generate a quadrature signal, any fixed delay of a quarter millisecond should suffice. At 100 MHz, a quarter wavelength or 90 degrees will be slightly over two feet. Thus, the time delay from any short piece of coax or other line can be used as

a single-frequency quadrature phase shifter. There even used to be trombone lines found in VHF phase-shifting lab work just for this.

For useful SSB or modem communication, though, you will need to quadrature delay a band of frequencies. Sadly, what was your 90-degree fixed delay phase shift at 1000 Hz becomes a 135-degree phase shift at 1500 Hz and a 180 degree phase shift up at 2000 Hz. Instead, what you will want is a linear phase system that advances phase exactly by 90 degrees as you advance your frequency.

Nearly any analog low-pass circuit

using either capacitors or inductors inherently has to provide more delay than a linear phase for the simple reason that capacitors and inductors are causal, meaning that they can "remember" what went on in the past but have no means of foretelling the future. Thus, higher-frequency parts of waveforms tend to get further and further behind. That is known as the group-delay problem, and is it ever a problem.

For example, if the ones of an older modem were at one frequency and the zeros were at another, with bad group delay in a filter, you will get times when you have a one, a zero, neither, or both at the output! Obviously "neither" or "both" are not very good.

So, you'll have to get real fancy if you decide to build up a wideband quadrature network. In fact, it turns out there is no perfect way known to do so. Amplitude or phase lumps are certain to crop up, as is limited bandwidth. But there might be some useful approaches you could try. However, we are getting ahead of ourselves; first we need to pick up some details on a circuit we might find useful.

An All-Pass Equalizer

To work around all of the inherent excess phase shifting problems with traditional inductors and capacitors, an equalizer can sometimes be used. An equalizer is simply a circuit that tries to crank out excess phase as fast as the problem circuit cranks it in.

A simple first-order all-pass section and its response appears in Fig. 3. That circuit has the property that all reasonable frequencies will be passed with unity gain.

To analyze the circuit, note that the gain of the op-amp will be -1 to an input on the left side of the left resistor on the inverting (-) input; and +2 to a signal applied directly to the non-inverting (+) input. At the lowest of frequencies, the capacitor will seem to be nearly an open circuit, and the gain will be -1 for a phase advance of 180 degrees. At very high frequencies, the capacitor will be nearly a short circuit, and the gain will be -1 + 2 = +1 for a phase shift of 0 degrees. Whenever your capacitive reactance matches your resistance, the combined phase shifts and gains on the op-amp inputs will still give you a unity gain output, but at a phase advance of 90 degrees.

Thus, unlike any typical low-pass filter circuit, phase is retarded as frequency increases. That retardation can be used to

BROADBAND QUADRATURE RESOURCES

- Albersheim and Shirley, "Computation Methods for Broad-Band 90 degree Phase Difference Networks," *IEEE Transactions on Circuit Theory*, May 1969, page 180.
- Bedrosian, S.D., "Normalized Design of 90 Degree Phase-Difference Networks," *IRE Transactions on Circuit Theory*, June 1960, page 128.
- Darlington, Sidney, "Realization of a Constant Phase Difference," *Bell System Technical Journal*, January 1950, page 94.
- Diethelm, Kai, "A Method for the Practical Evaluation of the Hilbert Transform," www.informatik.uni-hildesheim.de
- Gingell, M. J., "Single Sideband Modulation using Sequence Asymmetric Polyphase Networks," *Electrical Communication*, 1973 volume 48, nos 1 & 2, pp 21-25.
- Hawker, Pat, *Technical Topics Scrapbook*, Radio Society of Great Britain, 1993.
- Horowitz and Hill, *The Art of Electronics*, Cambridge University Press, 1989, page 5.16.
- Jackson, Leland B., *Digital Filters and Signal Processing*, Kluwer Pub, 1989.
- Lancaster, Don, *Active Filter Cookbook*, Synergetics Press, 1995.
- Mikhael, Wasfy B, "Sequence Discriminators and their use in Frequency Division Multiplex," *IEEE Transactions on Circuits and Systems*, February, 1979.
- O'Meara, T.R., "The Synthesis of 'Bandpass' All-Pass Time Delay Networks with Graphical Approximation Techniques," *Hughes Research Laboratories Technical Reports #114 and #159*, September 1960.
- Orchard, "Synthesis of Wideband Two-Phase Networks," *Wireless Engineer*, March 1950, page 72.
- Saraga, W., "Design of Wideband Phase-Splitting Networks," *Proceedings of the IRE*, July 1950 page 754.
- Schmidt, "Phase-Shift Network Analysis and Optimization," *QEX*, April 1994.
- Sekey, Andrew, *Digital Signal Processing*, IEEE Press, 1975.
- Snyder, Richard V, "A New Broad-Band Multiport Differential Phase-Shift Network," *Proceedings of the IEEE*, Aug 1971.
- Winder, Steve, *Filter Design*, Newnes Publishing, 1997, Chapter 9.
- Yoshida, Tetsuo, "Polyphase Network Calculation Using a Vector-Analysis Method," *QEX*, June 1995.

offset excess phase in whatever your new all-pass equalizer is trying to equalize.

You can also have fancier second-order equalizer circuits that let you crank phase in and out faster with more control. Higher order all-pass networks are also possible, but they are usually implemented using cascades of first-order and second-order all-pass sections grouped together.

Broadband Quadrature Networks

How can you generate a broadband quadrature phase shift? Three schemes are shown in Fig. 4. Our first scheme (Fig. 4A) is called the phase-difference method. In it, you set up two cascaded chains of first-order all pass circuits; one for I, one for Q.

By carefully specifying the phase advance of each circuit, you can get a 90-degree differential delay between the two channels over a chosen wide bandwidth. Those differential delays typically can be +45 degrees and -45 degrees with respect to the input. The amplitude is reasonably smooth, but there will be lumps in the phase. An original phase-difference paper by Bedrosian appears in the June 1960 *IRE Transactions on Circuit Theory*.

The second route (Fig. 4B) uses the

phase-sequence network. The fixed array of resistors and capacitors is driven off of a differential pair of audio sources, giving relative phases of 0, 90, 180, and 270 degrees. This phase sequence method is covered in *The Art of Electronics*. One original phase sequence paper is by Gingell and published in *Electrical Communication*, v48-1.

Note that these analog circuits only provide differential 90-degree phase shifting. Both output channels will inherently be "behind" the real world in-phase channel, because a capacitor can causally react only to events that have already happened.

Digital filters, however, have a stunningly interesting property. They can look "forward" as well as "backward" in time simply by checking earlier or later taps in a time storage history. Thus, digital filters can be non-causal and hence "distortionless." It's quite easy to build a linear-phase, sharp-cutoff, digital filter. We looked at these techniques a while back (see MUSE105.PDF through MUSE107.PDF on my www.tinaja.com Web site.)

In fact, digital filters can easily do all sorts of things that are difficult or impossible with analog. There is a piece of black magic math known as a Hilbert

Transform that simply tells us "phase shift everything by ninety degrees." Figure 4C shows us the Hilbert-Transform digital-filter approach to broadband quadrature phase generation. Note that while the phase can end up exact, there will be modest amplitude ripple in your needed approximations. One useful ploy to deal with that is the Ramez algorithm.

Hilbert Transforms can be built up with all the usual adders, delays, and DSP multipliers. One useful digital filter book that includes Hilbert-Transform information is Jackson's *Digital Filters and Signal Processing*. I've gathered more detailed information on the above-mentioned and other references on broadband quadrature networks together for you as this month's "Resource Sidebar." Loads of thanks to Winfield Hill and Rodger Rosenbaum for their inputs on this topic.

HP's ScanJet 6100C


The nice developer people over at Hewlett Packard loaned me one of their new ScanJet 6100C scanners to play with. While I haven't had it long enough yet for a complete review, I am very impressed with what this beast can really do.

This is a premium and legal-sized flatbed scanner that interfaces with a PC host through a fast SCSI interface. List price is \$921 for either the PC or Mac version. Street prices should end up somewhere around the \$620 range. Good pricing on HP products often shows up in *Computer Reseller* and *Comp-U-Mart* magazines.


The unit combines a fluorescent light with its CCD (charge-coupled device) sensor. Optical resolution is 600 DPI, with software deliverable resolutions ranging from 12 to 2550 DPI. Cropping is a snap and scaling can go from 3 to 400 percent.

Color or black and white is done in a wide variety of formats, including a self-optimizing 10-bit gray and 24-bit full color. Fancy image processing options include dithering, filtering, thresholding, interpolation, a gamma adjustment, inversion, scaling, color correction, and mirroring. There is even an optional 35 MM slide scanner accessory.

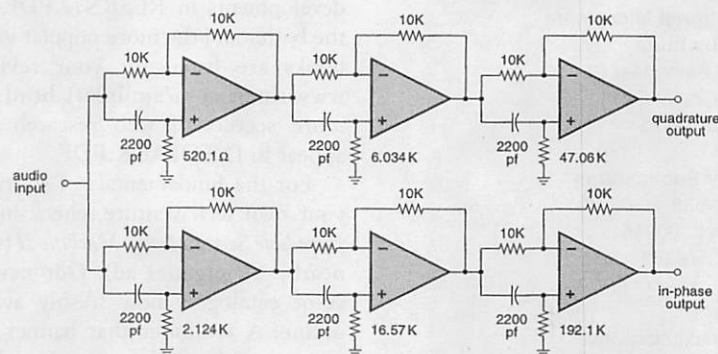
My main interest in a scanner is to capture all of my older books for my Web site and CD-ROM publishing ventures. The HP scanner interfaces beautifully with Acrobat Capture for extraction of both the text and the layout. Bee is



(A) Analog phase difference method.

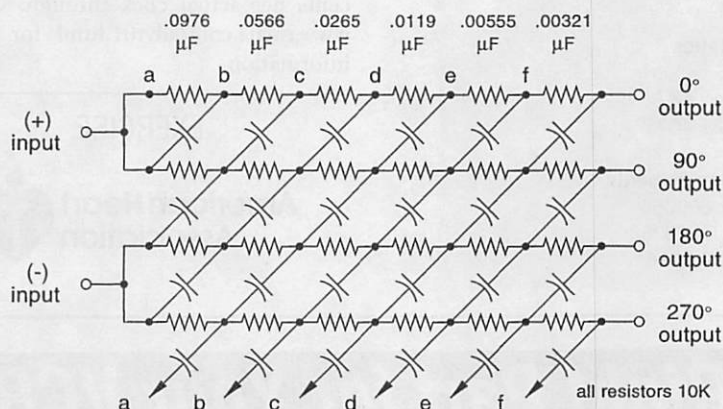

(B) Analog asymmetric polyphase method.

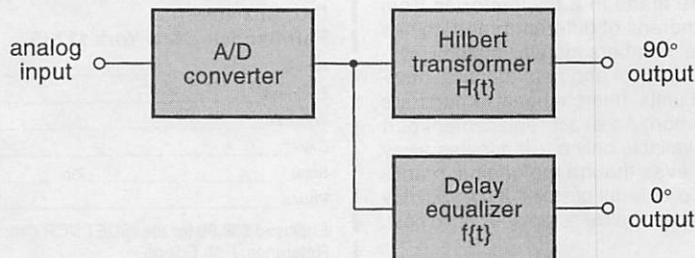

(C) Digital using Hilbert transform.

FIG. 4—THREE APPROACHES to broadband quadrature phase shifting.

going bonkers over this machine, scanning all sorts of stuff for textile teaching, crafts, and her co-op food newsletters.

There's also a copier mode that sure is handy. It works with your laser print-

er and gives you all sorts of size, quantity, quality, shading, and enlargement options. Compared to a "real" copier, the 6100C ends up somewhat slower using its highest quality mode, but nor-

mally produces much-better looking results. This is a really great machine.

New Tech Lit

From Texas Instruments comes CD-ROMs on Logic and 1394 Solutions. From AKM Semiconductor, there's a new *Audio & Multimedia Data Book*. And from Raychem, there's the revised *Circuit Protection Databook*.

From Atmel, comes a *AVR Risc Microcontroller* data book. For those unfamiliar with it, the AVR seems to me to be cheaper and faster than a PIC, but a lot less elegant. Their instruction set is very much 6502 like, (yea, team), but typically should execute in single machine cycles. Even their smallest units include a fast multiplier and an analog comparator. Both external and internal interrupts are supported.

Landsat MSS image data is newly available on CD ROM by way of Tom Oliver. His prices start at \$13 per CD. Broad coverage in several spectral bands is available. Amazingly cheap aerial photos with surprisingly high resolution are separately offered by several advertisers in *Earth Observer Monthly* (EOM). Information on microwave and RF heating ideas can be found at the International Microwave Power Institute at www.impiweb.org.

We have bunches of worthwhile books this month. Let's start with *Inside Intel*, which is an unflattering look at this industry giant. I don't care for either the title or the really awful fonts in *Web Psychos*, *Stalkers*, & *Pranksters*, but the book nicely reveals solid information on hiding and un-hiding web addresses and steps you can take towards your own web security. For guidance on where the web seems to be taking us, read *Growing Up Digital: The Rise of the Net Generation*. Check out my www.tinaja.com/amlink01.html for more details on these titles.

From Lindsay, his latest new-old book is *Popular Mechanics 1919 Shop Notes*. The hydraulic ram on page 2971 sure is a cute and "free" way to pump water uphill.

A great and free master industry-wide electronic search service is now up at www.questlink.com.

While not obvious, PostScript can elegantly (though not instantly) get tricked into painting with translucent ink! It can also be used to create "alpha" channel overlay effects and even blue screens. Further details can be found in ALPHA DEM.PDF on my www.tinaja.com. Also

NAMES AND NUMBERS

AKM Semiconductor
2001 Gateway Pl. 650 W
San Jose, CA 95110
(888) 256-7364

Atmel
2325 Orchard Pkwy.
San Jose, CA 95131
(408) 441-0311

Compu-Mart
899 Presidential #110
Richardson, TX 75081
(972) 238-1133

Computer Reseller
600 Community Dr.
Manhasset, NY 11030
(516) 562-5000

Earth Observer Monthly
13741 E Rice Place #200
Aurora, CO 80015
(303) 690-2242

Hewlett-Packard
PO Box 10301
Palo Alto, CA 94303
(415) 857-1501

International Microwave Power Institute
10210 Leatherleaf Ct.
Manassas, VA 22111
(703) 257-1415

Lindsay Publications
PO Box 538
Bradley, IL 60915
(815) 935-5353

Raychem
300 Constitution Drive
Menlo Park, CA 94025
(800) 227-7040

Tom Oliver & Associates
PO Box 999
Dewey, AZ 86327
(520) 632-8774

Synergetics
Box 809
Thatcher, AZ 85552
(520) 428-4073

Texas Instruments
PO Box 809066
Dallas, TX 75380
(800) 336-5236

look for information on new wireless developments in RESBN72.PDF, while the better and the more popular wireless books are listed for your review at www.tinaja.com/amlink01.html. And more secrets of web research newly appear in INFOPACK.PDF.

For the fundamentals of starting up your own tech venture, check into my *Incredible Secret Money Machine II* (see my nearby Synergetics ad). Our new full-color catalog is now freshly available online. A reminder that banner sponsors are welcomed for my Guru's Lair Web site. We've now "exceeded the speed of light" with way over 186,384 hits per month, and are fast sneaking up on "going to the moon" at 240,000. Total costs might end up under two cents per actual click through. Check www.tinaja.com/advt01.html for more information.


EN

EXERCISE.

American Heart Association



NOW Find the Right Part for Your VCR!

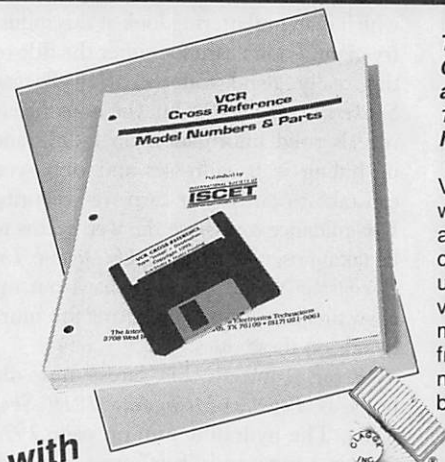

The 119-page Fifth Edition of the VCR Cross Reference contains both model and part number cross references. Over 1300 new parts and 360 new models have been added.

VCR's are made in a few factories from which hundreds of different brand names and model numbers identify cosmetically-changed identical and near-identical manufactured units. Interchangeable parts are very common. An exact replacement part may be available only a few minutes away from you even though the original brand-name supplier is out of stock. Also, you may be able to cannibalize scrap units at no cost.

with the ISCET VCR CROSS REFERENCE

NEW! The Fifth Edition is contained on a diskette for IBM PC AT/XT compatibles, DOS 2.1 or higher. The disk software allows technicians to search by manufacturer for model numbers and description of part numbers. A parts editing sequence gives an on-screen view of all substitutes for parts entered. With the diskette, the technician can update files by adding model and parts

crosses of future models. The Fifth Edition can be printed on pages completely from the diskette.

The ISCET VCR Cross Reference, Fifth Edition, is on 8 1/2 x 11-in., pre-punched pages and sell for \$38.00. The 3 1/2 inch diskette sells for \$69.95 and you can view listings from a monitor or printed page.

**Only \$38.00 for pages
\$69.95 diskette**

Clagck Inc.
VCR CROSS REFERENCE OFFER
P.O. Box 4099
Farmingdale, New York 11735

Name _____
Business _____
Address _____
City _____
State _____ Zip _____
Phone _____

Enclosed \$38.00 for the ISCET VCR Cross Reference, Fifth Edition.

Enclosed \$69.95 for the diskette containing the ISCET VCR Cross Reference, Ver. 6.0. Please specify:

5 1/2 Diskettes (2) 3 1/2 Diskette (1)

Include \$3.00 for shipping each Cross Reference (Pages or Diskette)

The total amount of my order is \$ _____

Check enclosed—do not send cash.

☐ Visa ☐ MasterCard Exp. Date ____/____/____

Signature _____

New York State residents must add applicable local sales tax to total.

CB03

Electronic SHOPPER[®]

TEST EQUIPMENT SALES

customer
satisfaction
#1 priority!

WE BUY
SURPLUS
EQUIPMENT

MC & VISA
ACCEPTED

NEW SCOPES
IN STOCK

TEK SG504.....1 GHz SINE WAVE GENERATOR.....\$2695	TEK 7L18.....18 GHz SPEC. ANALYZER.....\$1995
HP 8111A.....PULSE/FUNCTION GENERATOR.....\$1795	BMI 2400.....POWER LINE MONITOR.....\$995
TEK 2465A.....350 MHz 4 CH. SCOPE.....\$3795	HP 8656A.....SIGNAL GENERATOR.....\$1895
TEK 2445A.....200 MHz 4CH. SCOPE.....\$2395	HP 8640B.....SIGNAL GENERATOR.....\$995
HP 8902A w/ opts.....MEASURING RECEIVER.....\$25795	TEK 11A34.....4 CHANNEL PLUG-IN.....\$1795
TEK 465.....100 MHz 2 CH. SCOPE.....\$495	HP 5314A.....UNIVERSAL COUNTER.....\$395
TEK SG503.....LEVELED SINE GENERATOR.....\$695	WAV 801.....50 MHz PULSE GENERATOR.....\$795
HP 3325A.....SYNTH./FUNC. GENERATOR.....\$1995	HP 6002A.....50V 10A POWER SUPPLY.....\$795
TEK 7L5.....SPECTRUM ANALYZER P/1.....\$1295 (INCLUDES L3 MODULE)	FLUKE PM2811.....30V 10 POWER SUPPLY.....\$1195.

P.O. BOX 986
LONDONDERRY, NH 03053

PHONE (800) 684-4651
FAX (603) 425-2945

ASK ABOUT OUR NEW
TEKTRONIX & FLUKE
PRODUCTS

MICRO SIZE CCD VIDEO CAMERAS

MB-750U
Video Camera
\$99.95

MB-705UX
C-Mount Camera
with Lens Included;
8 or 12mm Lens
your choice!

LP-850i Lipstick
Camera

LP-850i Excellent
monitoring Camera,
and ideal for CU-SeeMe.
\$249.95

Cost Effective Color
Board Cameras
MB-1282 **\$199.95**
with Built-In Audio out

Polaris Industries
<http://www.polarisusa.com>

800.752.3571

Free Catalog

470 Armour Drive NE • Atlanta GA 30324 • Tech Info: 404-872-0722 • FAX 404-872-1038

Pinhole Versions
Available

See More Products @

**Same Day
Shipping**

C & S SALES
Your one stop source for
all your electronic needs!

CALL OR WRITE FOR OUR
**NEW FREE 64 PAGE
CATALOG!**
(800) 445-3201

Fluke Scopemeters



123...NEW.....\$950
92B.....\$1445
96B.....\$1695
99B...NEW.....\$2095
105B.....\$2495

**ALL FLUKE
PRODUCTS
ON SALE**

B & K PRECISION SCOPES

100MHz THREE-TRACE

Model 2190A

- 1mV/division sensitivity
- Sweeps to 5ns/division
- Dual time base
- Signal delay line
- 15KV accelerating voltage

\$1295.00



60MHz DUAL-TRACE

Model 2160

- 1mV/division sensitivity
- Sweeps to 5ns/division
- Dual time base
- Signal delay line
- V mode-displays two signals unrelated in frequency
- Component tester

\$895.00



40MHz DUAL-TRACE

Model 1541C

- 1mV/division sensitivity
- Video sync separators
- Z-axis input
- Single Sweep
- V mode displays two signals unrelated in frequency
- Component tester

\$695



60MHz, CURSORS & READOUTS, DUAL TIME BASE

Model 2260

- Cursors and readouts
- 1mV/div sensitivity
- 23 calibrated ranges - main time base
- 19 calibrated ranges - delayed time base
- Signal delay time
- V-mode - displays 2 signals unrelated in frequency
- Component tester
- Z-axis input
- Single sweep

\$1225



20MHz DUAL-TRACE

Model 2120B - 2 Year Warranty

Special \$375

Model 2125A with delayed sweep

\$539.95



- 1mV/division sensitivity
- AUTONORM triggered sweep operation
- AC, TVH, TVV and line coupling
- Calibrated 19 step time-base with x10 magnifier
- Compact low-profile design

Affordable Spectrum Analyzers by B&K

500MHz Series

Model 2615 - \$1595
Model 2620 w/ tracking generator - \$1895


1.05GHz Series

Model 2625 - \$2395
Model 2630 w/ tracking generator - \$2995



Quality Scopes by Elenco

Lowest Prices of the Year!

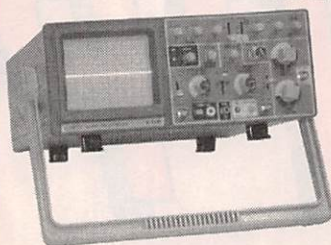

60MHz

DS-603 \$1350

- Analog / Digital Storage
- 20MS/s Sampling Rate

S-1360 \$749


- Analog with Delayed Sweep

100MHz

S-1390 \$995

- Analog

**Includes
Free Dust
Cover and
Probes**

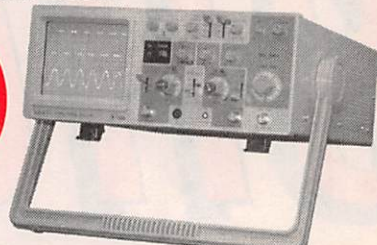

25/30MHz

DS-303 30MHz \$1095

DS-203 20MHz \$725

- Analog / Digital Storage

S-1330 \$439

- 25MHz Analog
- Delayed Sweep

S-1325 \$325

- 25MHz Analog

**2 Year
Warranty**

SIMM MODULE TESTER

B & K 898

\$625

- Tests 72 and 30-pin SIMMs to 36 bits.
- Stand alone and portable. No other equipment required.
- Automatically identifies width, depth and speed of SIMMs.
- 10 built-in tests identify most memory defects. Preheat cycle prior to test.



PORTABLE SEMICONDUCTOR TESTER

B&K 510

- In or out-of-order circuit tests for transistor, FETs, SCR's and darlington's.

\$199.00



Fluke Multimeters

Model 70III	\$85	Model 83	\$235
Model 73III	\$115	Model 85	\$269
Model 75III	\$139	Model 87	\$289
Model 77III	\$154	Model 863E	\$475
Model 79III	\$175	Model 867BE	\$650

B&K Precision Multimeters

Model 391	\$143	Model 388A	\$99
Model 390	\$127	Model 2707	\$75
Model 389	\$109	Model 2860A	\$79
Model 5390	\$295	Model 5370	\$219
Model 5380	\$265	Model 5360	\$195

MX-9300

Four Functions in One Instrument

Features:

- One instrument with four test and measuring systems:
 - 1.3GHz Frequency Counter
 - 2MHz Sweep Function Generator
 - Digital Multimeter
 - Digital Triple Power Supply
- 0-30V @ 3A, 15V @ 1A, 5V @ 2A



\$459⁹⁵

GUARANTEED LOWEST PRICES

C&S SALES, INC.

150 W. CARPENTER AVENUE
WHEELING, IL 60090

FAX: (847) 541-9904 (847) 541-0710

http://www.elenco.com/cs_sales/



**15 DAY MONEY BACK
GUARANTEE**

FULL FACTORY WARRANTY

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

CIRCLE 322 ON FREE INFORMATION CARD

CALL TOLL FREE
(800) 292-7711 orders only
Se Habla Español

C&S SALES

EXCELLENCE IN SERVICE

LOOK FOR OTHER
MONTHLY SPECIALS
ON OUR WEBSITE

NEW XK-700 Digital / Analog Trainer
Elenco's newest advanced designed Digital / Analog Trainer is specially designed for school projects. It is built on a single PC board for maximum reliability. It includes 5 built-in power supplies, a function generator with continuously sine, triangular and square waveforms and a 1560 tie point breadboard area. Tools and meter shown optional. (Mounted in a professional tool case made of reinforced metal).

XK-700
Assembled and Tested
\$189.95

XK-700 - SEMI KIT
w/ Fully Assembled PC Board
\$174.95

XK-700K - Kit
\$159.95



Made in the USA

Volt Alert™ By FLUKE

Volt Alert™ is the new pocket-sized AC line voltage detector from Fluke. Easy to use - just touch the tip to an outlet or cord. When it glows red, you know there's voltage in the line. Electrician's, maintenance, service, and safety personnel can quickly test for energized circuits and defective grounds on the factory floor, in the shop, or at home.

- Fits in shirt pocket for convenience.
- All outer surfaces are uncondutic for safety.
- Detects voltage metallic contact.

#1AC **\$19.50**



DIGITAL LCR METER

Model LCR-1810 **NEW**



\$99.95

- Capacitance .1pF to 20µF
- Inductance 1µH to 20H
- Resistance .01Ω to 2000MΩ
- Temperature -20°C to 750°C
- DC Volts 0 - 20V
- Frequency up to 15MHz
- Diode/Audible Continuity Test
- Signal Output Function
- 3 1/2 Digit Display

20MHz Sweep / Function Generator with Freq Counter

B&K 4040

- 0.2Hz to 20MHz
- AM & FM modulation
- Burst Operation
- External Frequency counter to 30MHz
- Linear and Log sweep

10MHz B&K 4017 **\$309**
5MHz B&K 4011 **\$239**



\$399



Model M-6100

The M-6100 is Elenco's most sophisticated meter with almost every possible feature available. The M-6100 even has a computer interface for viewing and storing data on a personal computer. It comes complete with software, RS-232 cable, test leads and manual.

\$125

Model XP-581

4 Fully Regulated DC Power Supplies in One Unit
4 DC voltages: 3 fixed - +5V @ 3A, +12V @ 1A, -12V @ 1A
1 Variable - 2.5 - 20V @ 2A

\$89.95



SATELLITE FINDER

Model SF-100A

- Aligns Satellite Dishes
- Range 950-2050MHz
- Audio Tone
- Compact Size
- Self Power Check



\$39.95

Digital Multimeter

Model M-1700

\$39.95

11 functions including freq to 20MHz, cap to 20µF. Meets UL-1244 safety specs.



Technician Tool Kit

TK-1500

28 tools plus a DMM contained in a large flexible tool case with handles ideal for everyone on the go.

\$49.95



Kit Corner

over 100 kits available

AK-700

\$14.95

Phone kit with training course.



RADIO CONTROL CAR KIT

MODEL AK-870

- 7 functions
- Remote control included

\$24.95

No Soldering Required



Model AM/FM-108K

Transistor Radio Kit

with training course

\$29.95



35mm Camera Kit

Learn all about photography

AK-540

\$14.95



No Soldering Required

The New DMM900 Series Handheld Digital Multimeters

For high-performance digital multimeters that are accurate, reliable, and rugged, the DMM900 Series extends the Tektronix line of already affordable DMMs. Twice the accuracy. Up to 10 times the resolution. And a full range of capability that spans voltage, current, digital multimeters features a dual numeric display, 3-year warranty, and autoranging capability. All backed by the reliability of the Tektronix brand.

Features

DMM912, DMM914, DMM916

- 40,000 Count Display
- 0.06% Basic DC Volts Accuracy (DMM916)
- DC Voltage Ranges from 400mV to 1,000V
- AC Voltage Ranges from 4V to 750V (True RMS)
- AC and DC Current Ranges from 10,000µA to 10A
- Resistance Ranges from 400Ω to 40MΩ
- Capacitance Ranges from 4nF to 40µF
- Frequency Ranges from 400Hz to 2MHz
- Temperature Measurements from -50°C to +980°C (DMM916, DMM914)
- 3 Year Warranty
- CE Marking



DMM 912
\$189



DMM 914
\$235



DMM 916
\$275

GUARANTEED LOWEST PRICES ON TEK DMMs

WE WILL NOT BE UNDERSOLD C&S SALES, INC.

150 W. CARPENTER AVENUE
WHEELING, IL 60090

FAX: (847) 541-9904 (847) 541-0710

http://www.elenco.com/cs_sales/

UPS SHIPPING: 48 STATES 5%
OTHERS CALL FOR DETAILS
IL Residents add 8.25% Sales Tax



15 DAY MONEY BACK GUARANTEE

FULL FACTORY WARRANTY

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

BLOWOUT! TIMELINE INC. BLOWOUT!

Over 11 years and 29,000 customers and still growing

LIQUID CRYSTAL DISPLAYS

240x64 dot LCD with built-in controller.
AND 4021ST-EO. Unit is EL back-lit. \$59.00 or 2 for \$109.00 or
OPTREX DMF5005 (non back-lit) \$49.00 or 2 for \$89.00
20 character x 8 line 7xL x 2xH The built-in controller allows you to do text and graphics.

Alphanumeric—parallel interface

16x1.....\$7.00	20x2.....\$10.00	32x2.....\$8.00
16x1 (lg. char.).....\$10.00	20x4.....\$15.00	40x1.....\$8.00
16x2.....\$7.00	20x4 (lg. char.).....\$10.00	40x2.....2 for \$20.00
16x2 (lg. char.).....\$10.00	24x2.....\$10.00	40x4.....\$20.00
16x4.....\$15.00	32x4.....\$10.00	4x2.....\$5.00

5V power required • Built-in C-MOS LCD driver & controller • Easy "microprocessor" interface • 98 ASCII character generator • Certain models are backlit, call for more info.

Graphics and alphanumeric—serial interface

size	Mfr.	price	size	Mfr.	price
640x480 (backlit)	Epson	\$25.00	480x128	Hitachi	\$10.00
640x400 (backlit)	Panasonic	\$20.00	256x128	Epson	\$20.00
640x200	Toshiba	\$15.00	240x128 (backlit)	Optrex	\$20.00
480x128 (backlit)	ALPS	\$10.00	240x64	Epson	\$15.00
			160x128	Optrex	\$15.00

6" VGA LCD 640X480, Sanyo LMDK55-22 \$25.00

LASER PRODUCTS

HeNe Laser Head (10mW max. output) TEMOO, 15.5" long MFG: NEC \$89.00

Laser Power Supply (for HeNe tube) \$79.00

LASER SCANNER ASSEMBLY \$19.00

Assembly intended for a laser printer. Includes laser diode, polygon motor (6 sided) and misc. optics and lenses.

LASER DIODE (5mW) with collimator \$20.00

VISIBLE LASER DIODE: 5mw at 670nm \$15.00

Index guided. Threshold current 40 ma typical.

3 and 4mW, 1,300nm LASER DIODES, 5.6mm package, \$15.00

Mitsubishi Electric part number ML701BIR-E21A, General specs are:

1. Vop=1.25, Beam Divergence 25.6° x 28.6°; 2. Tc=24°C, Iop=19 to 20mA, ITH=10.7mA; 3. Wavelength range between 1,280nm and 1,330 nm

POLYGON MOTOR UNIT & DRIVER \$69.00

Ten-sided first surface mirror mounted on an armature that spins at 125 revolutions per second yielding a beam sweep rate of 1250 sweeps per second. The driver for the polygon unit requires 24 volts and plus and minus 12 volts to operate. There is also an f-theta lens in front of the polygon scanning mechanism with a three inch diameter. Great for optical experiments, etc. Very high quality units. (MFR: JAPAN ELECTRONICS)

POS & BAR CODE

MAGNETIC CARD READER \$25.00

Includes: • 20 character dot matrix display with full alpha-numeric capability • keypad with full alpha-numeric entry • separate 7.5 VDC/0.5 Amp power supply • standard telephone interface extension cord • lithium battery and flat-cone speaker.

HP bar code wand (HBCS 2300).....\$25.00

POWER SUPPLIES

SWITCHING POWER SUPPLIES \$12.00 or 2 for \$20.00 115/230 Volts

73 WATT (2) 4 pin power connectors attached • Dim: 8.5" L x 4.5" W x 2" H

Output: +5V @ 2.975 A, +12V @ 0.15 A, -5V @ 0.04 A, -12V @ 0.05 A

60 WATT Dim: 8 1/2 x 4 1/2 x 3 • Output: 5V @ 6A + 12V @ 1A - 5V @ 1A - 12V @ 1A

CHARGE COUPLED DEVICES



"The Spy In The Sky" \$29.00

MATRIX TYPE

Thomson 576X550 pixel CCD

400-1,100nm resolution and responsivity. \$500.00 Original cost device

Sony CCD Imager - designed for black and white composite video cameras. Picture elements: 384 (H) x 491 (V) \$29.00

Chip size 10.7 (H) x 9.3 (V) mm² • Unit cell size 23.0 (H) x 13.4 (V) μm²

Ceramic 24 pin DIP package • Mfr: Sony, Part# 016AL

4096 element CCD \$15.00

1024 element CCD \$10.00

2048 element CCD \$10.00 • 1728 element CCD \$10.00

MISCELLANEOUS

ADAPTEC 4070A (RL) OR 4000A (MFM), SCSI Controller, your choice \$25.00

IBM 370 option XT and AT emulation boards \$25.00

2539 W. 237th Street, Bldg. F, Torrance, CA 90505

Order desk only: **USA: (800) 872-8878 CA: (800) 223-9977**

L.A. & Technical Info: (310) 784-5488 Fax: (310) 784-7590

OEM INQUIRIES WELCOME

MONITORS

Non-Enclosed TTL

Comes with pinout. 12V at 1.4 Amp input • Horizontal frequency 15KHz. • Ability to do 40 and 80 column.

5 inch Amber \$25.00 • 7 inch Amber \$25.00

9 inch Amber or Green \$25.00

5" COLOR MONITOR \$39.00

• Flat Faceplate • 320 x 200 Dot Resolution • CGA & Hercules Compatible

• 12 VDC Operation • 15.75 KHz Horiz. Freq. • 60 Hz Vert. Sync. Freq.

• Open Frame Construction • Standard Interface Connector • Degaussing Coil included • Mfr. Samtron

2 for \$69.00

9" COLOR SVGA MONITOR \$249.00

Fully Enclosed - Tilt and swivel type.

HACKER CORNER

EMBEDDED 486 COMPUTER \$99.00

Complete enhanced Intel 486SX-33 based computer in ultra small (9-7/8L x 6-5/8W x 3-1/8H) case. Ideal for embedded operations or as a second computer. Features include: • One 16 bit ISA slot • 3 serial ports plus dedicated printer port • Parallel optical coupled adapter port • Built in IBM PC/AT keyboard port • On board VGA video and port • Uses standard SIMM up to 32 MB • BIOS is PC/AT compatible

Unit has a backup Ni-Cd battery system in case of power failure (5 min. backup time) and lockable front cover to prevent floppy drive access. Mounting / interface provisions for standard 3.5" laptop floppy and 2.5 inch hard drives. Comes with very comprehensive manual.

Encased Spread Spectrum RF Modem \$199.00

The ProxLink Radio Module is a small communication device which replaces cables between RS-232 devices with wireless RF (Radio Frequency) technology. Attaching a pair of ProxLinks to any two devices with three wire asynchronous RS-232 ports allows wireless data transmission at rates up to 19.2 Kbaud (full duplex) over a range of 500 - 800 feet. Modules use 900 MZ spread spectrum radio for communication which does not require an FCC site license. A variety of configuration information (radio channel, baud rate, serial port configuration, etc.) can be programmed into module's non-volatile memory by host PC to provide compatibility and avoid overlapping systems. Configuration changes are supported by menu driven, on-board software. Commonly used Terminal Emulation software and transfer protocols can be used for configuring modules and transferring data between computers. ProxLinks require only 6-9 VDC (350 mA), RS-232 (9 pin sub - D) interface, and small (~ 4") whip antenna for operation. Unit size is 4.0" x 6.5" x 0.75". Installation schematics and application details available.

US made Micronics 486 VLB All in One \$39.00 or 2 for \$69.00

motherboard, supports 3.4 or 5V CPU, at either 25 or 33 mhz basic dock. Can use AMD or Intel from 486SX25 thru 486DX4-100 to HOT new AMD 5X86-133 cpu. On board SVGA video. On board 1 meg video ram expandable to 2 meg with ATI Mach 2 chip set. On board 2 high speed serial ports, 1 printer port, floppy and IDE hard drive controller. On board 256K cache. Uses 72 pin simm memory. Landmark speed rating of 479 with AMD chip.

Board will not fit standard All in One case because of non standard location of riser board. VLB riser board is included with motherboard.

COLOR CCD CAMERA \$149.00

• 12 VDC • 1/3-inch, CCD area image sensor • 514 (horizontal) x 491 (vertical) • 2:1 interlaced • 15.734 kHz (horizontal), 59.94 Hz (vertical) • 330 horizontal and 350 vertical lines • 10 Ix • IV, NTSC signal format • Lens: 1/3-inch, fixed focus (F:2.8 f5.6) • Dimensions: (W) 67 (2.63) x (H) 34 (1.45) x (D) 112.6 (4.43)

SONY Miniature Color LCD Display (LCX005BKB) \$29.00

• 1.4 CM (0.55 inch) Diagonal Full Color Display • Built In Horizontal and Vertical Drivers • Delta Dot Pattern for High Picture Quality • 537 dots (H) x 222 dots (V) • Compatible with NTSC & PAL Format and Sync Inputs • 12 VDC Operation with -1 to +17 V RGB Signal and Driver Input Voltage • Excellent Display for Virtual Reality Projects, Viewfinders, and Miniature Test Equipment Displays • Pin Out and Specification Included • Unit Requires Clock, Synchronization and Video

CELL SITE TRANSCEIVER \$49.00 2 for \$89.00

These transceivers were designed for operation in an AMPS (Advanced Mobile Phone Service) cell site. The 20 MHz bandwidth of the transceiver allows it to operate on all 666 channels allocated. The transmit channels are 870.030-880.030 MHz with the receive channels 45 MHz below those frequencies. A digital synthesizer is utilized to generate the selected frequency. Each unit contains two independent receivers to demodulate voice and data with a Receive Signal Strength Indicator (RSSI) circuit to select the one with the best signal strength. The transmitter provides a 1.5 watt modulated signal to drive an external power amplifier. Channel selection is accomplished with a 10 bit binary input via a connector on the back panel. Other interface requirements for operation are 26 VDC (unregulated) and an 18.990 MHz reference frequency for the digital synthesizer. The units contain independent boards for receivers, exciter, synthesizer, tunable front end, and interface assembly (which includes power supplies and voltage-controlled oscillator). Service manual, schematics and circuit descriptions included.

Encased Black & White Composite CCD Camera with Adapter

IR viewing to 1000 nm 7 1/2 L x 2 1/4 W x 1 1/4 H

Comes complete with CCD camera, mounting nut on bottom of casing.


12VDC power supply. Excellent low light capability, standard RCA NTSC video out. \$89.00

Great for: entryway security/remote monitoring, video conferencing/desktop video conferencing 2 for \$159.00

This miniature camera is perfect for multimedia computer applications as well as security and surveillance. NTSC output allows use with all popular video digitizing boards for Apple Macintosh and Microsoft video for Windows. Connects directly to any composite monitor or VCR with "video" input. Its razor-sharp wide-angle lens focuses from two inches to infinity and its state-of-the-art CCD technology accurately captures 16 level grayscale images for Quick Time movies and still pictures. Records at 30 frames per second and 260 lines resolution with excellent low light capability. Uses 12VDC (adapter supplied) and standard RCA cable.

Minimum Order: \$20.00. Minimum shipping and handling charge \$5.00. We accept cashiers checks, MC or VISA. No personal checks or COD's. CA residents add 8.25% sales tax. We are not responsible for typographical errors. All merchandise subject to prior sale. Phone orders welcome. Foreign orders require special handling. Prices subject to change without notice. 20% restocking fee for returned orders.

Synthesized FM Stereo Transmitter

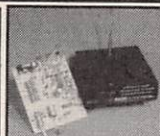

Microprocessor controlled for easy frequency programming using DIP switches, no drift, your signal is rock solid all the time - just like the commercial stations. Audio quality is excellent, connect to the line output of any CD player, tape deck or mike mixer and you're on-the-air. Foreign buyers will appreciate the high power output capability of the FM-25; many Caribbean folks use a single FM-25 to cover the whole island! New, improved, clean and hum-free runs on either 12 VDC or 120 VAC. Kit comes complete with case set, whip antenna, 120 VAC power adapter - easy one evening assembly.

FM-25, Synthesized FM Stereo Transmitter Kit \$129.95



Tunable FM Stereo Transmitter

A lower cost alternative to our high performance transmitters. Offers great value, tunable over the 88-108 MHz FM broadcast band, plenty of power and our manual goes into great detail outlining aspects of antennas, transmitting range and the FCC rules and regulations. Connects to any cassette deck, CD player or mixer and you're on-the-air, you'll be amazed at the exceptional audio quality! Runs on internal 9V battery or external power from 5 to 15 VDC, or optional 120 VAC adapter. Add our matching case and whip antenna set for a nice finished look.

FM-10A, Tunable FM Stereo Transmitter Kit \$34.95
CFM, Matching Case and Antenna Set \$14.95

RF Power Booster Amplifier



Add some serious muscle to your signal, boost power up to 1 watt over a frequency range of 100 KHz to over 1000 MHz! Use as a lab amp for signal generators, plus many foreign users employ the LPA-1 to boost the power of their FM Stereo transmitters, providing radio service through an entire town. Power required: 12 to 15 volts DC at 250mA, gain of 380dB at 10 MHz, 10 dB at 1000 MHz. For a neat, professionally finished look, add the optional matching case set.

LPA-1, Power Booster Amplifier Kit \$39.95
CLPA, Matching Case Set for LPA-1 Kit \$14.95
LPA-1WT, Fully Wired LPA-1 with Case \$99.95



Micro FM Wireless Mike

World's smallest FM transmitter. Size of a sugar cube! Uses SMT (Surface Mount Technology) devices and mini electret condenser microphone, even the battery is included. We give you two complete sets of SMT parts to allow for any errors or mishaps-build it carefully and you've got extra SMT parts to build another! Audio quality and pick-up is unbelievable, transmission range up to 300 feet, tunable to anywhere in standard FM band 88 to 108 MHz. 7/8" w x 3/8" h x 3/4" t.

FM-5 Micro FM Wireless Mike Kit \$19.95

Crystal Controlled Wireless Mike




Super stable, drift free, not affected by temperature, metal or your body! Frequency is set by a crystal in the 2 meter Ham band of 146.535 MHz, easily picked up on any scanner radio or 2 meter rig. Changing the crystal to put frequency anywhere in the 140 to 160 MHz range-crystals cost only five or six dollars. Sensitive electret condenser mike picks up whispers anywhere in a room and transmit up to 1/4 mile. Powered by 3 volt Lithium or pair of watch batteries which are included. Uses the latest in SMT surface mount parts and we even include a few extras in case you sneeze and lose a part!

FM-6, Crystal Controlled FM Wireless Mike Kit \$39.95
FM-SWT Fully Wired FM-6 \$69.95

RAMSEY

Super Pro FM Stereo Radio Transmitter

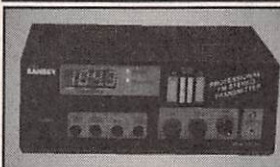

A truly professional frequency synthesized FM Stereo transmitter station in one easy to use, handsome cabinet. Most radio stations require a whole equipment

rack to hold all the features we've packed into the FM-100. Set frequency easily with the Up/Down freq buttons and the big LED digital display. Plus there's input low pass filtering that gives great sound no matter what the source (no more squeals or swishing sounds from cheap CD player inputs!) Peak limiters for maximum 'punch' in your audio - without over modulation, LED bargraph meters for easy setting of audio levels and a built-in mixer with mike and line level inputs. Churches, drive-ins, schools and colleges find the FM-100 to be the answer to their transmitting needs, you will too. No one offers all these features at this price! Kit includes cabinet, whip antenna and 120 VAC supply.

We also offer a high power export version of the FM-100 that's fully assembled with one watt of RF power, for miles of program coverage. The export version can only be shipped outside the USA, or within the US if accompanied by a signed statement that the unit will be exported.

FM-100, Professional FM Stereo Transmitter Kit \$299.95
FM-100WT, Fully Wired High Power FM-100 \$429.95

AM Band Radio Transmitter



Ramsey AM radio transmitters operate in the standard AM broadcast band and are easy to set to any clear channel in your area. Our AM-25, 'pro' version, fully synthesized transmitter features easy frequency setting DIP switches for stable, no-drift frequency control, while being jumper settable for higher power output where regulations allow. The entry-level AM-1 uses a tunable transmit oscillator and runs the maximum 100 milliwatts of power. No FCC license is required, expected range is up to 1/4 mile depending upon antenna and conditions. Transmitters accept standard line-level inputs from tape decks, CD players or mike mixers, and run on 12 volts DC. The Pro AM-25 comes complete with AC power adapter, matching case set and bottom loaded wire antenna. Our entry-level AM-1 has an available matching case and knob set for a finished, professional look.

AM-25 Professional AM Transmitter Kit \$129.95
AM-1 Entry level AM Radio Transmitter Kit \$29.95
Cam Matching Case Set for AM-1 \$14.95

Tone-Grabber Touch Tone Decoder / Reader



Dialled phone numbers, repeater codes, control codes, anywhere touch-tones are used, your TG-1 will decode and store any number it hears. A simple hook-up to any radio speaker or phone line is all that is required, and since the TG-1 uses a central office quality decoder and microprocessor, it will decode digits at virtually any speed! A 256 digit non-volatile memory stores numbers for 100 years - even with the power turned off, and an 8 digit LED display allows you to scroll through anywhere in memory. To make it easy to pick out numbers and codes, a dash is inserted between any group or set of numbers that were decoded more than 2 seconds apart. The TG-1 runs from any 7 to 15 volt DC power source and is both voltage regulated and crystal controlled for the ultimate in stability. For stand-alone use add our matching case set for a clean, professionally finished project. We have a TG-1 connected up here at the Ramsey factory on the FM radio. It's fun to see the phone numbers that are dialed on the morning radio show! Although the TG-1 requires less than an evening to assemble (and is fun to build, too), we offer the TG-1 fully wired and tested in matching case for a special price.

TG-1, Tone Grabber Kit \$99.95
CTG, Matching Case Set for TG-1 Kit \$14.95
TG-1WT, Fully Wired Tone Grabber with Case \$149.95
AC12-5, 12 Volt DC Wall Plug Adapter \$9.95



The Cube World's Smallest TV Transmitter

Perfect video transmission from a transmitter you can hide under a quarter and only as thick as a stack of four pennies - that's a nickel in the picture! Transmits color or B&W up to 150' to any TV



tuned to cable channel 59 with a solid 20 mW of power. Crystal controlled for no frequency drift with performance that equals law enforcement models that cost hundreds more! Deluxe model includes sound using a sensitive built-in mike that will hear a whisper 15 feet away! Units run on 9 volts and hook-up to most any CCD camera. Our cameras shown below have been tested to mate perfectly with The Cube and work great. Fully assembled.

C-2000 Video Transmitter Cube \$89.95
C-3000 Video and Audio Transmitter Cube \$149.95



CCD Video Cameras

If you're looking for a good quality CCD board camera, stop right here! Our cameras use top quality Japanese Canon

'A' CCD arrays, not the off-spec arrays that are found on many other cameras. You see, the Japanese suppliers grade the CCDs at manufacture and some manufacturers end up with the off-grade chips due to either cost constraints or lack of buying 'clout'. These cameras have nice clean fields and excellent light sensitivity, you'll really see the difference, and if you want to see in the dark, these are super IR (Infra-Red) sensitive! Available with Wide-angle (80°) or super slim Pin-hole style lens. Both run on 9 VDC and produce standard 1 volt p-p video. Add one of our transmitter units for wireless transmission to any TV set, or add our Interface board (below) for Audio sound pick-up and direct wire connection to any Video monitor or TV video/audio input jacks. Fully assembled.

CCDWA-2 CCD Camera, wide-angle lens \$99.95
CCDPH-2 CCD Camera, slim fit pin-hole lens \$99.95
IR-1 IR Illuminator Kit \$24.95



CCD Camera Interface Board

Here's a nifty little kit that eases hook-up of your CCD camera module to any video monitor, VCR or video input TV set. The board provides a voltage regulated and filtered source to power the camera (CCD Cameras require a stable source of power for best operation), sensitive electret condenser mike for great sound pick-up and RCA Phono jacks for both audio and video outputs. Runs on 11 - 20 VDC.


IB-1 Interface Board Kit \$14.95

Call for our Free Catalog !

RAMSEY ELECTRONICS, INC.
793 Canning Parkway
Victor, NY 14564

Order Toll-free: 1-800-446-2295
Sorry, no tech info or order status at this number

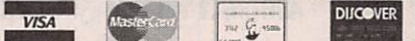Technical Info, Order Status
Call Factory direct: (716) 924-4560
www.ramseyelectronics.com




ORDERING INFO: Satisfaction Guaranteed. Examine for 10 days, if not pleased, return in original form for refund. Add \$6.95 for shipping, handling and insurance. Orders under \$20, add \$3.00. NY residents add 7% sales tax. Sorry, no CODs. Foreign orders, add 20% for surface mail or use credit card and specify shipping method.

DIGITAL STORAGE OSCILLOSCOPES

WITH
SPECTRUM
ANALYZER,
DVM, FREQ.
COUNTER,
AND DATA
LOGGER.

from
\$189.

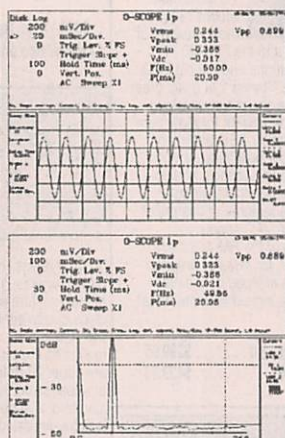PORTABLE
MODULES
CONVERT PC'S
INTO
MULTIPURPOSE
TEST AND
MEASURING
INSTRUMENTS.



Why lug a scope around? Toss one of our modules into your laptop case or tool kit. For a multi-purpose test device, plug to a PC parallel port and use the PC screen. Continuous, delayed, or triggered sweeps can be frozen on the screen, printed out, or saved to disk. Frequency Spectrums DC to 25 MHz.

Allison now provides PICO TECHNOLOGY Ltd. portable test equipment, including high-speed scopes, and multi channel data loggers. Pico and O-Scope modules accept standard probes and work with 286 or faster PC's.

FEATURES:

- ♦ PORTABLE UNITS TO 25 MHz
- ♦ USES PRINTER PORT
- ♦ USES STD. PROBES

OPTIONS:

- ♦ PROBE SETS
- ♦ AUTOMOTIVE PROBES
- ♦ BATTERY PACKS
- ♦ SOFT & HARD CASES

O-Scopes Made in U.S.A. Picos Made in U.K.
Same Day Shipping
Includes Cable, Software & Manuals

O-Scope I (DC-50KHz, single trace)\$189.
O-Scope II (DC-500KHz, dual trace)\$349.
PICO (ADC 200/20) (DC-10MHz, dual trace)CALL
PICO (ADC 200/50) (DC-25MHz, dual trace)CALL
PICO pc based data loggers from \$99.

Shipping within U.S. UPS Ground \$7.50(Second day \$11.50)

SEND CREDIT CARD INFO., M.O., or CHECK, OR CALL

1-800-980-9806

Allison Technology Corporation


8343 CARVEL, HOUSTON, TX. 77036 U.S.A.

PHONE: 713-777-0401 FAX: 713-777-4746 BBS: 713-777-4753

<http://www.atcweb.com>

World Passing You By?

Are you interested in Microprocessors & Embedded Control Systems? If not you should be! Look around, just about everything these days has an embedded microprocessor in it. TVs, cars, radios, traffic lights & even toys have embedded computers controlling their actions. The Primer Trainer is the tool that can not only teach you how these devices operate but give you the opportunity to program these types of systems yourself. Examples & exercises in the Self Instruction manual take you from writing simple programs to controlling motors. Start out in Machine language, then move on to Assembler, & then continue on with optional C, Basic, or Forth Compilers. So don't be left behind; this is information you need to know!

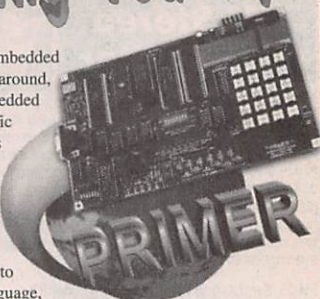

Examples Include:

- Measuring Temperature
- Using a Photocell to Detect Light Levels
- Making a Waveform Generator
- Constructing a Capacitance Meter
- Motor Speed Control Using Back EMF
- Interfacing and Controlling Stepper Motors
- Scanning Keypads and Writing to LCD/LED Displays
- Bus Interfacing an 8255 PPI
- Using the Primer as an EPROM Programmer
- DTMF Autodialer & Remote Controller (New!)

The PRIMER is only \$119.95 in kit form. The PRIMER Assembled & Tested is \$169.95. This trainer can be used stand alone via the keypad and display or connected to a PC with the optional upgrade (\$49.95). The upgrade includes: an RS232 serial port & cable, 32K of battery backed RAM, & Assembler/Terminal software. Please add \$5.00 for shipping within the U.S. Picture shown with upgrade option and optional heavy-duty keypad (\$29.95) installed. Satisfaction guaranteed.

EMAC, inc.

11 EMAC WAY, CARBONDALE, IL 62901
618-529-4525 Fax 457-0110 BBS 529-5708
World Wide Web: <http://www.emacinc.com>

1985 - 1998
OVER
12
YEARS
OF SERVICE

WHITE-STAR ELECTRONICS

TEL: 405-631-5153 FAX: 405-631-4788

CONVERTERS:	20	50	100+
Regal CR-83	45	39	35
* New, Panasonic TZPC 145	75	69	65
DQN-5 (2 or 3) (unmodified)	45	39	35
DRZ-3 PJ (unmodified) 70 Channel Plain	35	32	29
DRX-3 PJ (unmodified) 60 Channel Plain	32	30	27

Call for FREE catalog.
405-631-5153




REMOTE CONTROL

HAND UNITS:	20	50	100+
Jerrold Replaces: 400/450/550	4.95	4.50	4.25
Scientific Atlanta: 075/175/475	4.95	4.50	4.25
8600: On screen display	7.50	7.00	6.50
Pioneer: BR 81, 82	4.95	4.50	4.25
Panasonic: Call for model #	7.50	7.00	6.50
Zenith: All	4.95	4.50	4.25
Tocom: 5503-VIP, 5503-A	7.00	6.50	6.25
Universal: 4 in 1 R/M	7.50	7.00	6.50

Call for Oak, Hamlin, Regal-83, Regency, Texscan, and all others.

Tamper-Bit tools: (10-lot)

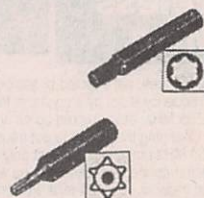Jerrold compatible bits:
1/4" Stacom Bit\$8.00
Oval Round D.....\$20.00
Torx Bit:
Tocom T-8\$8.00
Zenith T-10, T-15\$8.00
Pioneer T-20\$8.00
Scientific Atlanta T-20\$8.00
Pio 63XX Oval\$20.00
Bit Driver Handle\$4.00



We carry most remote hand units. If you don't find the one you're looking for, we can locate for you.

Specializing in large quantities.

HOURS: Monday thru Friday 9 am to 5 pm Central Time.

Call for FREE catalog.

Email: wse405@aol.com

CIRCLE 314 ON FREE INFORMATION CARD

Our Complete
Catalog is
now
online

www.cir.com

**Circuit
Specialists
Inc.**

**SINCE
1971**

**Check Out
What
We
Have
To Offer:**

Fantastic DMM Offer!!!

Don't let the price fool you. This meter is a digital multimeter designed for engineers and hobbyists. Equipped with 5 functions and 19 ranges. Each test position is quickly and easily selected with a simple turn of the FUNCTION/RANGE selector rotary switch.

General Rubber Boot Included

Display: 3-1/2 Digit LCD, 21mm Figure Height

with Automatic Polarity
Overrange Indication: 3 Least Significant Digits Blank

Temperature for Guaranteed Accuracy:

23 C 5 RH<75%

Temperature Ranges:

Operating: 0 C to 40 C (32 F to 104 F)

Storage: -10 C to 50 C (14 F to 122 F)

Power: 9V Alkaline or Carbon-Zinc

Battery (NEDA1604)

Low Battery Indication: BAT on Left of

LCD Display

Dimensions: 188mm long x 87mm wide x

33mm thick

Net Weight: 400g

DC Voltage (DCV)

Range: Resolution: Accuracy:

200mV 10V (1%rdg+2dgt)

2000mV 1mV (1%rdg+2dgt)

20V 10mV

200V 100mV

1000V 1V

Maximum Allowable Input: 1000V DC

or Peak AC

DC Current (DCA)

Range: Resolution: Accuracy:

200 A 100mA

2000 A 1 A (1.2%rdg+2dgt)

20mA 10 A

200mA 100 A (1.2%rdg+2dgt)

10A 10mA

Overload Protection: mA Input, 2A/250V

fuse.

CAT NO DESCRIPTION PRICE

9300G Rugged High Quality DMM with Rubber Boot \$19.00

20 AMP Switching Power Supply

A very special Circuit Specialists offer. This 20 amp

continuous switching power supply is available at

this fantastic low price!

Specifications

Input Voltage: AC 110V +/- 15%, 50Hz/60Hz

Output Voltage: DC9V 15V variable

Polarity: Negative ground

Current (13.8V): 25A peak, 20A continuous

Overvoltage Protection

Cooling fan inside chassis

CAT NO DESCRIPTION PRICE

SPS-1020G 20 Amp Switching Power Supply \$99.00

Developer This product is used as the developer

on our positive photo-resist printed circuit boards.

Includes instructions. 50 gram package, mixes with

water, makes 1 quart.

PRICE EACH

CAT NO DESCRIPTION 1 10 25

POSDEV Positive Developer \$.95 \$.80 \$.50

Etching Chemicals/Ferric Chloride

A dry concentrate that mixes with water to make 1 pint

of etchant, enough to etch 400 sq.

inches of 1oz board.

PRICE EACH

CAT NO DESCRIPTION 1 5

ER-3 Makes 1 pint \$3.50 \$2.75



Our
Best
Offer
Ever
on a

High
Quality
Full Sized
DMM

\$19.00
any qty

Resistance (Ω)

Range: Resolution: Accuracy:

200Ω 100mΩ

2000Ω 1Ω

20KΩ 10Ω (1.2%rdg+2dgt)

200KΩ 100Ω

2000KΩ 1KΩ

20MΩ 10KΩ (2%rdg+10dgt)

Maximum Open Circuit Voltage: 2.8V

Diode Test

Measures forward voltage drop of a

semiconductor junction in mV test cur-

rent of 1.5mA Max.

ohFE Test

Measures transistor hFE.

Frequency Range: 45Hz-450Hz

Maximum Allowable Input: 750V rms

Response: Average Responding. Cal-

ibrated in rms of a Sine Wave.

AC Voltage (ACV)

Range: Resolution: Accuracy:

200V 100mV (1.2%rdg+10dgt)

750V 1V

Positive Photo Resist Pre-Sensitized Printed Circuit Boards

These pre-sensitized printed circuit boards are ideal for small production runs. They provide high resolution and excellent line width control. High sensitive positive resist coated on 1oz. copper foil allows you to go direct from your computer plot or art work layout. No need to reverse art.

Single-Sided, 1oz. Copper Foil on Paper Phenolic Substrate

CAT NO	DESCRIPTION	1	10	50
PP101	100mm x 150mm/3.91" x 5.91"	\$2.55	\$1.90	\$1.70
PP114	114mm x 165mm/4.6" x 6.6"	2.98	2.45	1.98
PP152	150mm x 250mm/5.91" x 9.84"	5.40	3.98	3.60
PP153	150mm x 300mm/5.91" x 11.81"	6.15	4.48	4.10
PP1212	305mm x 305mm/12" x 12"	12.78	10.65	8.52

Single-Sided, 1oz. Copper Foil on Fiberglass Substrate

CAT NO	DESCRIPTION	1	10	50
GS101	100mm x 150mm/3.91" x 5.91"	\$ 3.90	\$2.98	\$2.60
GS114	114mm x 165mm/4.6" x 6.6"	4.80	3.49	3.20
GS152	150mm x 250mm/5.91" x 9.84"	8.69	5.98	5.78
GS153	150mm x 300mm/5.91" x 11.81"	10.20	7.20	6.80
GS1212	305mm x 305mm/12" x 12"	18.88	15.73	12.59

Double-Sided, 1oz. Copper Foil on Fiberglass Substrate

CAT NO	DESCRIPTION	1	10	50
GD101	100mm x 150mm/3.91" x 5.91"	\$ 5.07	\$3.68	\$3.38
GD114	114mm x 165mm/4.6" x 6.6"	5.95	4.29	3.99
GD152	150mm x 250mm/5.91" x 9.84"	10.47	7.39	6.98
GD153	150mm x 300mm/5.91" x 11.81"	11.95	8.69	8.30
GD1212	305mm x 305mm/12" x 12"	22.09	18.35	14.68



Etching Tank

This handy etching system will handle PC boards up to 8" x 9", two at a time. Ideal for etching your PCB's! System includes an air pump for etchant agitation, a thermostatically controlled heater for keeping etchant at optimum temperature and a tank that holds 1.35 gallons of etchant. A tight fitting lid is also supplied to prevent evaporation when system is not being used. Typical etching time is reduced to 4 minutes on 1oz. copper board!

REDUCES ETCHING TIME!	CAT NO	DESCRIPTION	PRICE
	12-700	Etch Tank System	\$37.95

1/3" CCD Board Cameras

Available with PINHOLE LENS with AUDIO; STANDARD LENS with AUDIO; and STANDARD LENS with INFRA-RED. These are the world's smallest commercially available CCD board cameras!

World's Smallest B&W Board Cameras

Specifications

Image Pick-Up Device	1/3" CCD area Sensor
Picture Elements	EIA-512(H) x 492(V)
Pixel Pitch	EIA-9.6UM (H) x 7.5UM (V)
Scanning System	2:1 Interlace
Scanning Frequency	EIA-525 lines, 60 field/sec (II) 15.750 KHz x 60.HK

Resolution	430 Lines
Minimum Illumination	0.03 LUX
S/N Ratio	45dB
Lens Mounting	4.3mm standard, 5mm pinhole
Video Output	1.0 VP-P/750OHM composite signal
Power Requirement	8-12 VDC (9VDC standard)
Power Consumption	100mA
Operating Temperature	-20C + 70 C RH 95% Max
Storage Temperature	-40C - 85 C RH 95% Max
Audio Pick-Up Sensitivity	-60 DB (ODB = 18/UBAR. 1KNZ)
Audio Frequency Range	20 Hz to 20KHz
Audio S/N Ratio	More than 35DB
Audio Output Level	1VP-P/600 OHM

Dimensions	WDP-2000	WDS-2005	WDI-4000
	30mm (H) x 30mm (W)	30mm (H) x 30mm (W)	44mm (H) x 30mm (W)

CAT NO	DESCRIPTION	1	5
WDP-2000	1/3" B&W Pinhole Lens with Audio	\$89.00	\$77.00
WDS-2005	1/3" B&W Standard Lens with Audio	89.00	77.00
WDI-4000	1/3" B&W Infra-RED (no audio)	89.00	77.00
WDPH-55BW	Plastic Housing Option for B&W Board Cameras (WDP-2000 & WDS-2005 ONLY)	13.00	12.00



WDP-2000



WDS-2005



WDI-4000

CIRCUIT SPECIALISTS, INC.

SINCE 1971
800-811-5203
602-464-2485
602-464-5824(FAX)

WE ACCEPT:



RECEIVE OUR LATEST 132 PAGE CATALOG!

It's chock full of all types of electronic equipment and supplies. We've got I.C.'s, capacitors, resistors, pots, inductors, test equipment, breadboarding supplies, PC supplies, industrial computers, data acquisition products, personal computers and computer parts, plus much, much more. FAX us your name and address or call 800-811-5203, ext. 5, to leave a message on our catalog request line.



EPROM Emulator

Sockit Rockit



\$99.00*
Emulates:
27C256
27C128
27C64

The SR256 EPROM Emulator can emulate 8K x 8 to 32K x 8 120 ns EPROMs, with features that provide embedded code developers increased productivity. Advantages include: software selectable device size and target address; download verify; Hex, S-Record and binary file support; status LED; dual polarity reset outputs and single device bus loading.

INCLUDES

- PC Software and Quick Start Manual
- Table Assembler supporting common 8-bit micros
- PC Parallel Port Adapter and 7 ft. Interface Cable
- Reset Jumper Wire

*Shipping and handling not included.
VISA, MasterCard, Discover and AmEx accepted.


Wisch Communications

2550 Trinity Mills Road
Suite 132B
Carrollton, TX 75006

Ph: (972) 417-3533
Fax: (972) 417-3821
wischcom@cyberramp.net

RF Data Modules

Transmitters

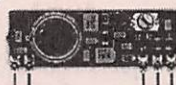

TXM-4XX-A..... \$24.50
TXM-4XX-F..... \$25.80

- ERP 0.25mW into 50Ω
- 3V(F), 5V(F) or 6-12V(A)
- 418 or 433.9MHz FM
- simply add antenna, data, power
- Range up to 200m
- Analog or digital data i/p
- SAW controlled - stability

Receivers



SILRX-4XX-A..... \$39.38
SILRX-4XX-F..... \$41.92

- Only 21 x 47 x 5mm
- 13mA; 130uA on power save (100:1)
- Carrier detect o/p
- 418 or 433.9MHz FM Superhet
- SAW controlled - stability
- Analog or digital o/p
- Wide supply range 4.5-9V (A/F ver.)
- Fast enable time <3ms

Transceivers



BIM-4XX-F..... \$87.36

- Only 23 x 33 x 11mm
- Up to 40,000bps of balanced code
- Up to 170m range.
- 5v operation
- 418 or 433MHz FM
- Direct interface to 5V CMOS logic
- Fast 1ms enable from power saving

RS232 Transceiver



CYPHERNET-RS232..... \$139.30

- 3 wire RS232 interface
- Up to 38400 bps
- 418 or 433MHz FM, 7.5-15Vdc
- TX/RX LED indication
- Up to 150m range



ABACOM
TECHNOLOGIES

Volume Discounts
Free Catalog Available
MasterCard / Visa

Tel: 416-242-3120
Fax: 416-242-2697
FaxBack: 416-242-3082

67 Hamptonbrook Dr • Weston • ON • M9P 1A2 • Canada

AUTOMATIC TELLER MACHINES

ATM crimes, abuses, vulnerabilities and defeats exposed! 100+ methods detailed, includes: Physical, Reg. E, cipher, PIN compromise, card counterfeiting, magnetic stripe, false front, TEMPEST, tapping, spoofing, inside job, vibration, pulse, high voltage - others, con jobs. Histories, law, security checklist, internal photos, figures. *Much more!* \$39.

CELLPHONE PHREAKING GUIDE

How cellphones operate and are modified. Vulnerabilities to hack attack and countermeasures. Details on programming NAMS, ESNs, etc (cloning), control data formats, computing encoded MINs, ESNs, SIDHs, operating systems, PROM programming, forcing ACK, test mode and resets, cable diagrams, scanning, tracking, scanner restorations, freq allocations, roaming. Step-by-steps to keypad-reprogram 100+ popular cellphones. *More!* \$59

PAGER / BEEPER MANUAL

How Pagers work, different types and uses, freqs, advantages over and uses with cellphones, and tips and tricks. How Pagers are hacked/countermeasures. And plans for a **Personal Pocket Paging System** (xmitter and receiver). *More!* \$29

PHREAKING CALLER ID & ANI

How they work and dozens of ways of defeating Caller ID, ANI, *69, *57, Call Blocking, *67 etc. Describes ESS, SS7, CNA, CAMA, DNR, Diverters, Centrex - *more!* \$19.

BEYOND VAN ECK PHREAKING

Eavesdropping on TV and computer video signals using an ordinary TV described in detail. Includes security industry reports. Range up to 1 KM. Plans include both the ours and the original Top Secret Van Eck designs! \$29.

HACKING THE INTERNET

The latest tricks and methods being used on the Net to pirate software (warez) and the newest hacking websites. *Updated every two months.* Includes examples, countermeasures, password defeats, UNIX, Sprintnet, brute force methods, lots of tips, and *more!* \$25.

COMPUTER PHREAKING

Describes in detail how computers penetrate each other, and how VIRUSES, TROJAN HORSES, WORMS are implemented. Dozens of computer crime and abuse methods and countermeasures. Includes disk filled with hacker text files and utilities, and the legendary FLUSHOT+ protection system. Internet advice, password defeats, glossary - *much more!* Manual + PC Disk! \$39.

OTHER EXCITING TITLES

Call For Descriptions

- Hacking Fax Machines - \$29
- PBX Hacking - \$19
- Voice Mail Hacking - \$29
- Beyond Phone Color Boxes - \$29
- Hacking Answering Machines - \$19
- By an Order of the Magnitude - \$49
- Ultimate Success Manual - \$15
- Internet Cons & Scams - \$19
- Internet Tracking & Tracing - \$29
- Cookie Terminator - \$19
- Casino Hacking - \$18
- Credit Card Scams - \$29
- Radionics Manual - \$29
- Heal Thyself - \$19
- Stealth Technology - \$24
- High Voltage Devices - \$29
- The Hacker Files - \$39
- Cons & Scams - \$29
- Cryptanalysis Techniques - \$29
- Secret & Survival Radio - \$24
- Secret & Alternate IDs - \$15
- Rocket's Red Glare - \$29
- Mind Control - \$29
- EM Brainblaster - \$29

SPECIAL PROJECTS SERVICES

We will build just about anything.
Ask about our application form!

STOPPING POWER METERS

As reported on "60 MINUTES"! All-new 6th Edition!! Over 45 pages jam-packed with how devices can slow down (even stop) watt-hour meters - while loads draw full power! Device plugs into one outlet and normal loads into other outlets. Describes meter creep, overload droop, etc. Plans only! \$29.

THE I.G. MANUAL: External magnetic ways (applied to meter) to slow down and stop power meters while drawing full loads. Plans \$25.

KW-HR METERS: How watt-hour meters work, calibration, error modes (many), ANSI Standards, etc. Demand and Polyphase Meters. Experimental results to slow and stop meters by others. \$25.

All 3 (above), Only \$59! (Add \$20 for Video)



MAIL \$3 FOR OUR LATEST CATALOG TO: (free w/order)

CONSUMERTRONICS

P.O. Box 23097 ABQ, NM 87192-1097

ORDER TODAY! 505-237-2073

Fax: 505-292-4078 Web Adventure: www.tsc-global.com

Established in 1971. Featured on CBS "60 Minutes," Forbes, New York Times. Add \$5 total S/H (US, Canada). Sold for educational purposes only. Postal M.O. is fastest. VISA, MC OK. COD (\$49-\$999), add \$7.

NEW S.P.M. THE VIDEO!! \$39



Now its easier to learn about KW-HR Power Meters than ever before! This educational video shows you how they work and their anatomy. Demonstrates SPM device and external magnetic methods used to slow and stop meters! Hosted by a top expert in the field. From the novice to the pro, an excellent source of info on these exciting devices! Great in combo with our SPM related manuals!

Only \$49 for SPM video + SPM manual!!

Any waveform you want!




Starting at

\$795

Quantity 1

Money back
guarantee


Telulex Inc. model SG-100

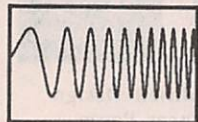


DC to 20 MHz linear
and log sweeps




Int/Ext AM, SSB,
Dualtone Gen.

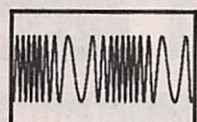


Int/Ext FM, PM,
BPSK, Burst

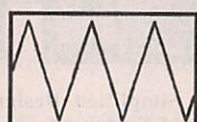


Ramps, Triangles,
Exponentials

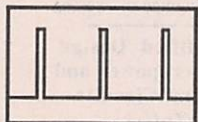


Pulse Generator

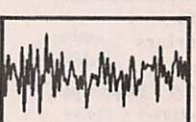

Noise

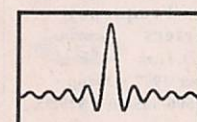

Arbitrary Waveforms

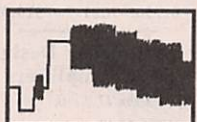

Unlimited Possibilities!

● Synthesized Signal Generator

Clean sinewaves DC-20 MHz with .001% accuracy!
.1 Hz steps. DC Offset. RS232 remote control.

● Arbitrary Waveform Generator

40 Megasamples/Second. 32,768 points. 12 bit DAC

● Function Generator

Ramps, Triangles, Exponentials & more to 2 MHz!

● Pulse Generator

Digital waveforms with adjustable duty cycle

Telulex Inc.

2455 Old Middlefield Way S Tel (415) 938-0240 <http://www.Telulex.com>

Mountain View, CA 94043 Fax (415) 938-0241 Email: sales@Telulex.com

CIRCLE 324 ON FREE INFORMATION CARD

WORLD'S SMALLEST UHF X-tal Locked Video Transmitters \$99.00

So small the transmitter, camera and battery will fit into a cigarette pack!!!

Used by hundreds in covert CCTV, R/C models, movie Special Effects, and Law Enforcement. "I've utilized your transmitters in covert video installations for about one year... previously, I used costly wireless units from Pelco, MVP, and Supercircuits. Nothing approaches the VidLinks in terms of power, picture quality, size, and value. Thank you." R. Leslie, CCTV Installer, NY.
"Incredible color, resolution... easy to use, convenient. Very cool." P. Davis, Props, CA.
"... like having a TV station in your pocket." J. Ramsay, Electronic Hobbyist, FL.

**LIVE REMOTE
VIDEO FROM: \$99.00**

**ACTUAL
SIZE!!!**

VidLink 100: 100mW Power- upto 1/4 Mile
\$199.00 New! High-Power!

VidLink 15: 15mW Power- upto 150 Feet
\$99.00 New! Low Price- Same Size!

Covert Camera: 1 1/4" sq. Pinhole Lens
\$169.00 Pro Grade Japanese Quality!

*** Audio Module Now Available. Call. ***

Check/MO, COD +\$5.00, S&H \$5.50



**AEGIS
RESEARCH**

#671-1225 E. Sunset Dr.
Bellingham, WA
98226-3529 USA

1-604-224-0416

Visit our virtual catalog on the INTERNET at:
<http://www.lynx.bc.ca/virtualspy>

PIC'n Books

LEARN ABOUT PIC16/17 MICROCONTROLLERS

EASY PIC'n Beginner

- Programming techniques
- Instruction set
- Addressing modes
- Bit manipulation
- Subroutines
- Sequencing
- Lookup tables
- Interrupts
- Using a text editor - source code
- Using an assembler
- Timing and counting
- Interfacing - I/O conversion
- Lots of examples

\$29.95

PIC'n Up The Pace Intermediate

- Serial communication
- PIC16 to peripheral chips
- PIC16 to PIC16
- Serial EEPROMS
- LCD interface
- Scanning keypads
- D/A conversion
- Sensors - analog voltage output
- A/D conversion
- Math routines
- Decimal interface
- PIC16C84 EEPROM data memory
- Lots of circuits and code

\$34.95

+ \$4 s/h in US for one book, \$6 both books
VISA, MC, AMEX, MO, Check
CA residents please add 7.25% CA sales tax
PIC is a trademark of Microchip Technology Inc.

SQUARE 1 ELECTRONICS

P.O. Box 501, Kelseyville, CA 95451
Voice (707) 279-8881 FAX (707) 279-8883
<http://www.sq-1.com>

Key Titles from...



Newnes

An imprint of Butterworth-Heinemann

Buy more
than 1 book
and take 15%
off total order

JOHN D. LENK
SIMPLIFIED
DESIGN OF
VOLTAGE-
FREQUENCY
CONVERTERS



JOHN D. LENK
SIMPLIFIED
DESIGN OF
DATA
CONVERTERS



JOHN D. LENK
SIMPLIFIED
DESIGN
OF
IC AMPLIFIERS



JOHN D. LENK
SIMPLIFIED
DESIGN OF
MICROPOWER
AND BATTERY
CIRCUITS



JOHN D. LENK
SIMPLIFIED
DESIGN OF
SWITCHING
POWER
SUPPLIES



JOHN D. LENK
SIMPLIFIED
DESIGN OF
LINEAR
POWER
SUPPLIES



Simplified Design of Switching Power Supplies

by John D. Lenk
1996 • 225pp • pa •
0-7506-9821-7 • \$29.95

Simplified Design of IC Amplifiers

by John D. Lenk
1996 • 240pp • pa •
0-7506-9508-0 • \$29.95

Lenk Series

Simplified Design of Voltage-Frequency Converters

by John D. Lenk **NEW**
September 1997 • 304pp •
pa • 0-7506-9654-0 • \$29.95

Simplified Design of Data Converters

by John D. Lenk **NEW**
April 1997 • 242pp • pa •
0-7506-9509-9 • \$29.95

Simplified Design of Linear Power Supplies

by John D. Lenk
1996 • 246pp • pa •
0-7506-9820-9 • \$29.95

Simplified Design of Micropower and Battery Circuits

by John D. Lenk
1996 • 240pp • pa •
0-7506-9510-2 • \$29.95

**Audio Power
Amplifier Design
Handbook**
DOUGLAS SELF



PCB Design Using AutoCAD

by Chris Schroeder
Aug 1997 • 336pp
• pa • 0-7506-9834-9
• \$44.95

Audio Power Amplifier Design Handbook

by Douglas Self
1996 • 256pp • pa •
0-7506-2788-3 •
\$34.95

Inside PC Card

by Faisal Haque
1996 • 352pp • ha •
0-7506-9747-4 •
\$52.95

Understand Electronic Filters

by Owen Bishop
1996 • 180pp • ha •
0-7506-2628-3 •
\$26.95



High Performance Audio Power Amplifiers

by Ben Duncan
1996 • 288pp • ha •
0-7506-2629-1 •
\$59.95

Digital Storage Oscilloscopes

by Ian Hickman
1996 • 208pp • pa •
0-7506-2856-1 •
\$39.95



Please send me the book(s) listed below. (Buy more than one, and take 15% off the total order.)

Write book number(s) here:

Mail your order to: Butterworth-Heinemann, Fulfillment Center, 225 Wildwood Ave., Woburn, MA 01801 USA

Name _____

Address _____

City _____ State _____ Zip _____

Phone _____ Fax _____

E-mail _____

☐ Please send me a free Newnes catalog, item #645.

Phone: 1-800-366-BOOK

Fax: 1-800-446-6520

E-mail your order to orders@repp.com

☐ I have enclosed a check for \$ _____

☐ Please charge my:

☐ Visa ☐ MasterCard ☐ American Express

Card no. _____ Exp. date _____

Signature _____

U.S. Customers: Please add \$4.00 handling fee for the first item ordered, \$1.50 for each additional item, to all check and credit card orders. Billed orders will be charged additional shipping based on weight and destination. All U.S. orders must include your state sales tax. Prepayment or company purchase order is required for all orders. Prices subject to change without notice.

Canadian Customers: Please pay by credit card or in U.S. funds and include 7% GST on books and handling.

European Customers: Add £2.00 UK and surface postage. ☐ Check for Air Mail; extra cost will be charged.

A member of the Reed Elsevier plc group

TS232

Visit our web site: <http://www.bh.com/newnes>

PROFESSIONAL DESOLDERING with the New & Improved

More Vacuum

Lane Norman - Normans Electronics Inc. Atlanta GA 404-451-5057
A cost effective solution to desoldering equipment at less than half the price of most equipment. It's performance is ASTOUNDING.

Mike Murphy - Service Center - Van Nuys
CA 818-785-7805

The single best investment of repair equipment we've made. It outperforms all other desoldering tools we've used. Easier to use and least expensive.

Quicker Vacuum

Bob Monroe - M.A.R.C. Electronics - Virginia Beach VA 804-468-3932
Best investment we've made. Saves time, especially with multi-sided PCB's. Extremely pleased with warranty. Failed within 6 months and replaced by DEN-ON overnight.

Dick Manning - Dicks Electronics - Hartland WI 414-367-8339
The ease & speed of component removal greatly increases productive time. The SMD kit makes SMD removal a breeze, even for inexperienced Techs.

George Hefner - Hefner Electronics - Coleridge NE 402-283-4333
Being a one-men service center, I hesitated to spend the money on a desoldering tool, however all that changed when I nearly ruined a \$400 computer logic board. It has cut my desoldering time by 50%.

Higher Temperature

Don Cressin - Certified Electronics Service - Ellicott City MD 301-461-8008
We have obtained excellent results with the SC7000 including repairing high density U/V tuners. It is one of the best purchases we have made.

Doug Pettit - LuRay Electronics - LuRay VA 703-743-5400
We found that the SC7000 not only saves money vs. wick, but saves valuable time in troubleshooting. It allows you to be more accurate in removing SMD's.

Randy Whitehead - Service West - Salt Lake City UT 801-262-4069
My techs thought it would be a waste. I bought one anyway after a demo. My techs then fought over it. Now we have three. It is the Best desoldering tool we have ever used.

Same Low Price

DEN-ON SC7000Z



FREE TRIAL

Available on Request

Sale Price
\$395.00

Price includes
stand worth \$25.00
one extra filter and
two tip cleaners.

Check us out on the WEB
<http://www.heinc.com>

Timothy Kraft Monikraft, Inc.
Cherry Hill, NJ 609-751-3252
We replaced all our existing desoldering stations with the SC7000. Our technicians are very pleased with the improved performance, portability, and reliability over our previous higher priced equipment.

Bill Warren CET/CSM
Warrens Audio & Video
Knoxville TN - 234-546-1128
We have been extremely satisfied with the quality and durability of the DEN-ON SC7000 as well as with after the sale support.

Keith Sals - J & M Electronics -
Omaha NE 402-291-7100
It's a must tool for my bench. I can desolder multiple pin IC's quickly and clean. It will even take up large solder amounts on tuner and case grounds.

New Features

- ◆ Totally Self Contained diaphragm vacuum pump and AC motor for high vacuum suction or reversible hot air blow for SMD removal.
- ◆ 100Watt Ceramic heater with zero-crossover switching heater control circuit which prevents spikes and leakage currents.
- ◆ Unique patented long lasting filter cartridge design. Solder builds up on easily cleaned baffle, while air flows around the outside of baffle.
- ◆ Totally ESD Safe. The housing contains carbon and the tip is at ground potential for complete ESD Protection.
- ◆ Maximum vacuum of 650mmHg is attained in 100 milliseconds.
- ◆ Temperature adjustable from 300°C - 500°C (572°F - 932°F).
- ◆ More suction power and hotter temperature if needed.

New Specifications

- ◆ Voltage _____ AC100v, 120V, 230V, 50/60HZ
- ◆ Power Consumption _____ 120W
- ◆ Pump _____ Diaphragm Type
- ◆ Motor Output _____ 12W
- ◆ Vacuum Attained _____ 650mmHg
- ◆ Temperature Range _____ 300°C - 500°C (572°F - 932°F)
- ◆ Air Flow Rate _____ 15 Liter/Minute (Open)
- ◆ Heater _____ 100W (Ceramic)
- ◆ Control System _____ Feed Back Zero Cross-over Type
- ◆ Net Weight _____ 420Grams
- ◆ Max.Temp. of Hot Blow _____ 400°C

Visa - M/C - Discover - American Express - Terms to Qualifying Companies
30 Day Money Back Total Satisfaction Guarantee - One Year Parts and Labor Warranty

HOWARD
HEI ELECTRONIC
INSTRUMENTS INC
Your Desoldering Specialists

Toll Free U.S. and Canada
1-800-394-1984

Web Site www.heinc.com
E-Mail sales@heinc.com
International (316) 744-1993
or Fax (316) 744-1994

CIRCLE 321 ON FREE INFORMATION CARD

EARN MORE MONEY!

Be an FCC LICENSED ELECTRONIC TECHNICIAN!



Earn up to
\$60 an hour
and more!

Learn at home in spare time.
No previous experience needed!

No costly school. No commuting to class. The Original Home-Study course prepares you for the "FCC Commercial Radio-telephone License." This valuable license is your professional "ticket" to thousands of exciting jobs in Communications, Radio-TV, Microwave, Maritime, Radar, Avionics and more...even start your own business! You don't need a college degree to qualify, but you do need an FCC License.

No Need to Quit Your Job or Go To School
This proven course is easy, fast and low cost! **GUARANTEED PASS**—You get your FCC License or money refunded. **Send for FREE facts now. MAIL COUPON TODAY!**

Or, Call 1-800-932-4268 Ext. 210

COMMAND PRODUCTIONS

FCC LICENSE TRAINING, Dept. 210
P.O. Box 2824, San Francisco, CA 94126
Please rush FREE details immediately!


NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

TURN YOUR PC INTO A DIGITAL STORAGE OSCILLOSCOPE!

The all new
PC-
MultiScope
2

10Mhz
analog
bandwidth!

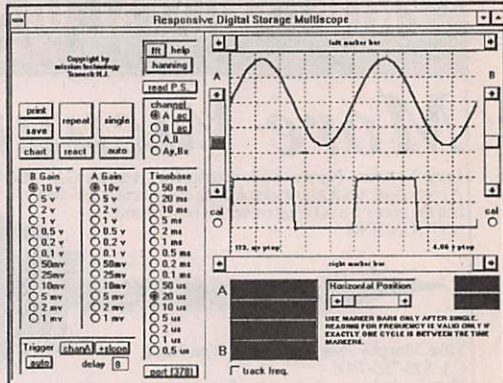At right:
Actual
scope
screen as
seen on
your PC
monitor.



For industrial, educational, hobbyist,
auto, and audio test & measurement

\$399 + S/H. Visa/MC/Check OK
Add \$99 for source code option

The top choice of corporations, universities and scientists worldwide!

FEATURES:

1. Dual channel; external triggered
2. Digital storage; Windows based
3. Connects to PC parallel port
4. 20Megasamples/sec sampling;
10Mhz max. analog bandwidth
5. 8 bit resolution/ 8K RAM buffer
6. Prog. gain: 10v/div to 1mv/div
7. Spectrum analyzer (fft) function
8. Strip chart recorder function
9. TTL output for control app's
10. Visual Basic source code available.

AMAZE ELECTRONICS CORPORATION

amaze@hooked.net www.hooked.net/users/amaze

Phone: 800-996-2008 Fax: 408-374-1737

THE HACKER'S COMPANION CD-ROM

Are you interested in using the internet in ways you never dreamed possible? Want a war-dialer program or something to crack a password? Do you want to learn how the phone company gets ripped off, or learn how to build a red box, or modify a cellular phone? Want to see what the security holes in Windows NT are? Or how to compromise a Unix machine or a BBS? Want to learn how to use the system in ways you never imagined possible? This CD is the place to look! It contains all kinds of computer, telephone and general hacking information. Even a video of dutch hackers breaking into a classified US military computer! In all, over 600 megabytes of fascinating information that's hard to get anywhere else!

PC-COMPATIBLE CD \$29.95 SHIPPING \$3

Cryptography Unlimited CD-ROM

Cryptographic software will soon be outlawed by the US government. Get this important bundle of over 200 megabytes of cryptographic software while you still can! Nobody in the US will even dare to publish a CD like this anymore and we had to import it from Africa! Includes file encryptors, disk encryptors, PGP, steganography, code cracking, PGP phone and lots more!

PC CD-ROM, \$39.95 SHIPPING \$3

Call (800) 719-4957 now!

to order (Visa/MC/COD) or call or write for **FREE CATALOG** of hard-to-get information about computer viruses, computer hacking, security and cryptography!!

American Eagle Publications, Inc.

P. O. Box 1507, Dept. E.

Show Low, AZ 85901

CIRCLE 315 ON FREE INFORMATION CARD

MCM ELECTRONICS®

Prices Effective March 5
through May 1, 1998

To take advantage of special
pricing on the items listed, you
must provide this code: ▼

SOURCE CODE: ENS45

For over 20 years, MCM has been the leading supplier to the electronics service industry. Huge inventory, rapid delivery and competitive prices have made MCM the choice for:

- Hobbyists
- Educators
- Service Technicians
- Installers

Discover the MCM difference, call today for your free catalog.

NEW

Programmable LCD Display Module

Pre-assembled circuit board provides one or two line x 16 character backlit display which is fully programmable and stores up to 14 alpha numeric messages. Messages can be individually displayed by closing specific contacts on terminal strip mounted to the board. Easy menu programming is similar to that of VCR or camcorder text. Board dimensions 3 1/2" x 2 1/2" x 1". Screen dimensions 3 3/8" x 1" (two line), 3 3/8" x 1/2" (one line). Requires 12VDC, 300mA.

Order #	Description	(ea.)
28-4766	Two line LCD display	\$140.00
28-4765	One line LCD display	115.00



VHS T-120 Video Tape

- Premium grade VHS video tape
- Recording time: EP-6 hours, LP-4 hours, SP-2 hours • Made in USA
- Suggested list \$1.99
- Limited quantities.

Order #	(1-9)	(10-29)	(30-49)	(50-up)
T-120	\$1.49	\$1.39	\$1.29	\$1.09



Panasonic AC Adaptor

Original adaptor for use with Panasonic phones and answering machines. Ideal adaptor for use with experiments and hobbies.

Input voltage 120VAC. Output voltage 12VDC, 500mA. Plug dimensions: 5.5mm (O.D.) x 2.0mm (I.D.), tip negative. **Limited quantities.** Panasonic #KX-A11.

Order #	(ea.)
58-1490	\$2.61



TENMA® Soldering Station

Perfect for all applications including SMD. Closed loop control provides precise temperature regulation and overheat protection. Temperature adjustable from 300-790°F via front panel rotary control. Digital display accurately shows tip temperature and setpoint.

Order #	Reg.	\$69.95
21-1590	\$119.00	



TENMA® 5MHz Oscilloscope

Bandwidth of DC-5MHz makes this especially ideal for audio applications. Input impedance 1Mohm. Accepts input signal up to 600V p-p. CRT display area: 75mm round, overall dimensions: 5 1/2" (W) x 11 1/2" (D) x 7 1/2" (H). Requires 110/220/240VAC, 50/60Hz.

Order #	(ea.)
72-300A	\$229.00




TENMA® Isolation Transformer

Provides isolation from AC line when servicing hot chassis equipment. Provides fused 150VA isolated outlet and fused 500VA outlet.

Order #	(ea.)
72-545	\$49.95

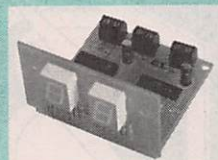Call for information on many other types of pre-assembled modules including timers, temperature controls, VOX relays, audio amplifiers and power supplies.



Two Digit LED Counter

Pre-assembled counter circuit board provides digital count from 0 to 99. Contact closure input provides one count up and reset-to-zero function. Each digit is 0.5" high. Requires 12VDC, 100mA. Dimensions 2 1/4" x 2" x 1 1/16".

Order #	(ea.)
28-4785	\$14.95



MCM AUDIO SELECT™ Square Frame Replacement Woofers

Ideal for new speaker building or existing speaker repair. Direct replacements for Curtis Mathes, JVC, Sharp, Sanyo and many other popular name brand woofers. The frame is attractively finished in flat black. All are 8ohm.

Order #	Size	Watts	Frequency Response	Voice Coil	Magnet	Weight (ea.)	(2-up)
55-945	10"	50/65	25Hz-4.5KHz	1"	10 oz.	\$17.95	\$14.95
55-950	12"	60/85	30Hz-2.5KHz	1.25"	15 oz.	21.95	18.95
55-1130	15"	100/150	20Hz-3KHz	2"	18 oz.	34.95	30.50



**FREE
Catalog!**

1-800-543-4330

www.mcmelectronics.com

Hours: M-F 7 a.m.-9 p.m., Sat. 9 a.m.-6 p.m., EST.

**Same Day
Shipping!**

In stock orders received by 5:00 p.m. (YOUR TIME), are shipped the same day.



MCM ELECTRONICS®
650 CONGRESS PARK DR.
CENTERVILLE, OH 45459
A PREMIER FARNELL Company

SOURCE CODE: ENS45



- PRODUCT ENGINEERING
- FIRMWARE DEVELOPMENT

**"QUALITY
IS OUR
CAPITAL
CONCERN."**

**Complete On Site
Electrical Engineering Lab**

- REVERSE ENGINEERING
- RF CIRCUIT DESIGN & MANUFACTURING

- MICRO CONTROLLER & EPROM HARDWARE & SOFTWARE DEVELOPMENT

From Auto-Routing to CNC Routing to Electronic Assemblies. . .
Capital Electronics is Your Best Route For Printed Circuit Boards.

DESIGN/LAYOUT

- CAD LAYOUT SERVICES
- COMPATIBLE WITH ALMOST ALL CAD SYSTEMS
- FROM SCHEMATICS OR SAMPLE PCB'S
- PHOTOPLOTTING SERVICES
- 28,800 BAUDE MODEM

PRINTED CIRCUIT BOARDS

- SINGLE & DOUBLE SIDED
- MULTI-LAYER & FLEXIBLE PCB'S
- FROM QUICK TURN PROTOTYPES TO SCHEDULED PRODUCTION RUNS
- FINE LINES, SMT
- ELECTRICAL TESTING
- PRECIOUS METAL PLATING

ASSEMBLY SERVICES

- FAST TURN BOARD STUFFING
- WIRE HARNESSSES
- WAVE SOLDERING
- ACQUISITION OF PARTS
- FINAL TESTING
- TURNKEY SERVICES
- CUSTOM ENCLOSURES

*For Quick & Competitive Pricing or More Information,
Please Call Us Today!*

303 Sherman Street • Ackley, Iowa 50601

(515) 847-3888

Fax (515) 847-3889 • Modem (515) 847-3890



Internet Access:

For Automated Info Response:
INFO@capital-elec.com

E-Mail: Quote@capital-elec.com

Web Access: <http://www.capital-elec.com>

CIRCLE 320 ON FREE INFORMATION CARD

❖ ATTENTION CABLE VIEWERS ❖

CABLE VIEWERS. . .get back to your BASIC Cable Needs

Call 800-577-8775

For information regarding all of your **BASIC** cable needs.



5 GOOD REASONS TO BUY OUR FAR SUPERIOR PRODUCT

- ❖ PRICE
- ❖ EFFICIENT SALES AND SERVICE
- ❖ WE SPECIALIZE IN 5, 10 LOT PRICING
- ❖ ALL FUNCTIONS (COMPATIBLE WITH ALL MAJOR BRANDS)
- ❖ **ANY SIZE** ORDER FILLED WITH SAME DAY SHIPPING

We handle **NEW** equipment **ONLY** - Don't trust last year's **OBSOLETE** and **UNSOLD** stock!
COMPETITIVE PRICING—DEALERS WELCOME

HOURS: Monday-Saturday 9-5 C.S.T.

It is not the intent of B.E.S.W. to defraud any pay television operator and we will not assist any company or individual in doing the same.
*Refer to sales personnel for specifications.

**BASIC
ELECTRICAL
SUPPLY &
WAREHOUSING
CORPORATION**


P.O. Box 8180 ■ Bartlett, IL 60103 ■ 800-577-8775

CIRCLE 282 ON FREE INFORMATION CARD

"Get the skills you need at a price you can afford!"

Earn up to \$45 an hour or more as a skilled Computer Programmer.

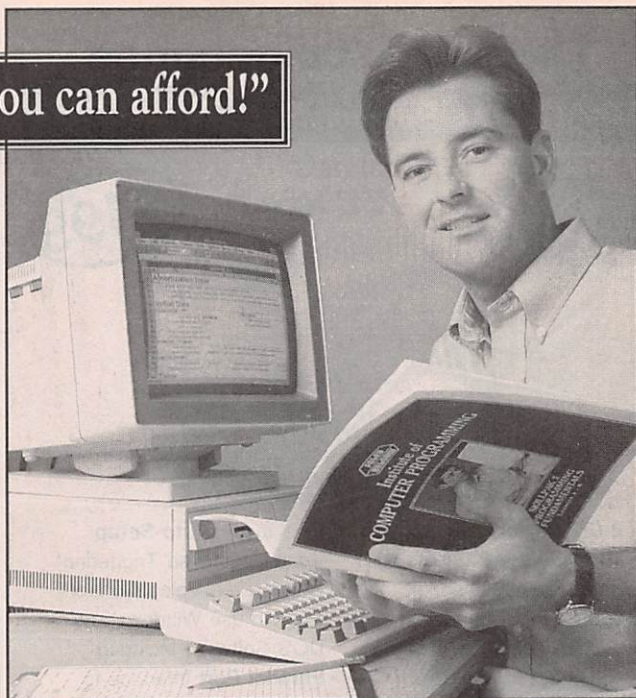Cash in on the explosion of opportunities. Start your new career or even open a business of your own as a highly-paid computer programmer.



Computer programmers today can almost write their own ticket to financial well-being and job satisfaction. Only Foley-Belsaw's unique in-home training programs can give you the skills you need at a price you can afford.

You'll learn the three hot computer languages — QBasic, C and Visual Basic. You'll even work with the hot new C++. With this easy-to-learn knowledge, you'll write your first QBasic program by the end of the first SkillPak of lessons. Soon you'll be programming sound and graphics, and even learning how to program for the Windows environment — the most popular application program today.

It's easy to cash in!

Look at some of the things professional computer programmers do. "Wrote a C program to clean up a WordPerfect file; edited the resulting file as data errors were found." This work would take a trained programmer less than five hours to complete, and they could make over \$200 for the work. That's money you could be making — and soon — with training from the Foley-Belsaw Institute of Computer Programming.

Everything is included!

We provide you with all the materials you'll need to become a professional computer programmer. You'll receive 37 lessons, designed for you by the Foley-Belsaw Professional Programmer Staff. Other valuable materials include a *Programmer's Handbook*, *Programmer's Examples* on two 3.5 inch disks, *Programmer's Flowchart Template*, and a booklet, *Selecting the Right Computer*.

Other schools force you to buy a complete computer package as part of their training program. At Foley-Belsaw we understand that your needs as a programmer may not fit into a "one size fits all" approach. Why should you pay hundreds of dollars for a computer system that you may not need?

We'll tell you what you need. When you're ready to buy your own computer, you can get the machine that fits your needs at the lowest possible price. That's the Foley-Belsaw way.

Get the free facts today.

Whether you want to change careers, have a profitable part-time job or start your own business, Foley-Belsaw Institute's new computer programming course is the first step. A profitable future in computer programming can be yours. Call or write today for a fact-filled information kit including a free copy of *Computer Programming — A Profitable Career In Your Spare Time*. See how easy it is to begin a money-making career as a sought-after computer programmer. Our free full-color information kit outlines the steps of the computer programming course and shows you everything you will receive as part of your training.

**Mail this coupon or call today
Toll Free 1-800-487-2100!**

Your free opportunity kit will be rushed to you!

If coupon is missing, write to: Foley-Belsaw Company, 6301 Equitable Road, Kansas City, MO 64120

Call or complete & return this coupon to: Foley-Belsaw Institute, 6301 Equitable Road, Kansas City, MO 64120

☐ **YES! Rush me a free information kit on Computer Programming right away. Dept. 35495**

Other career courses:

- ☐ Locksmithing, Dept. 13081
- ☐ Small Engine Repair, Dept. 52953
- ☐ Saw & Tool Sharpening, Dept. 21888
- ☐ VCR Repair, Dept. 62777
- ☐ Computer Repair, Dept. 64679
- ☐ TV/Satellite Dish Repair, Dept. 31548
- ☐ Gunsmithing, Dept. 92581
- ☐ Woodworking, Dept. 43820
- ☐ Upholstery, Dept. 81490
- ☐ Vinyl Repair, Dept. 71425
- ☐ Electrician, 95358
- ☐ Computer Specialist, Dept. 38324
- ☐ Networking Specialist, Dept. 39311


I understand that there is ABSOLUTELY NO OBLIGATION and NO SALESMAN WILL CALL.

Name _____
Address _____
City _____ State _____ Zip _____



Digital Oscilloscopes


100 MSa/s Parallel Port Based DSO

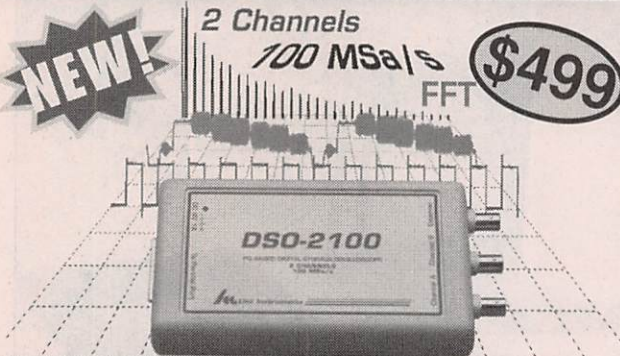


- 2 Ch. Digital Oscilloscope
- 100 MSa/s Max Single-Shot Rate on Both Channels
- 60MHz Input Bandwidth
- 32K Samples Per Channel
- Optional FFT Spectrum Analyzer*, Advanced Math* and TV Line Trigger**
- IEEE Pulse Parameter Measurements
- One touch **Auto-Setup**
- Advanced Pulse Triggering*
- Hands-Free Voice Control
- Easy to use Windows and DOS Software Included
- **Parallel Port** Interface to Laptop or Desktop PC
- Small and Lightweight (9 oz and 6.3" x 3.75" x 1.25")
- **Free Demo Software** on Web

For \$499 you get the model DSO-2102S Oscilloscope, Probes, Interface Cable, Power Adapter, and Windows and DOS Software.

*DSO-2102M \$599 **TV-Line Module \$149

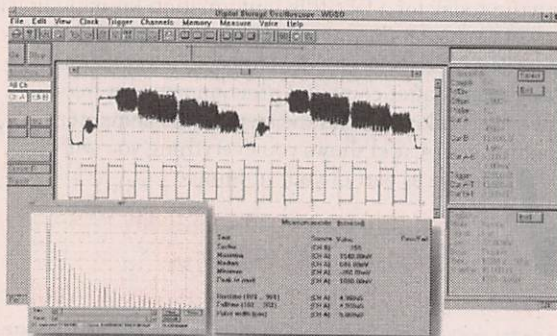

DSO w/Logic Analyzer (ISA based)

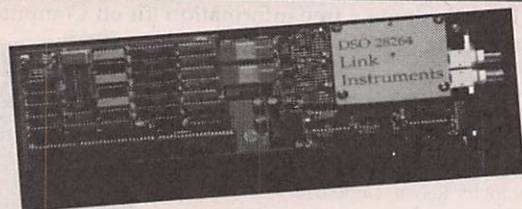

- 200 MSa/s Max Single-Shot Sample Rate
- 2 Oscilloscope Channels
- 8 Logic Analyzer Channels
- 10 Channels Simultaneously
- 125 MHz Single Shot Bandwidth
- Up to 128K Samples/Channel
- FFT Spectrum Analyzer included

DSO-28264 (10Ch, 200MSa/s, 64k) \$1999

DSO-28464 (20Ch, 200MSa/s, 64k) \$3799

All prices include Probes and Software

Link Instruments (973) 808-8990

369 Passaic Ave (Suite 100) Fairfield, NJ 07004

www.LinkInstruments.com/en4 (Email: Sales@LinkInstruments.com)

CIRCLE 335 ON FREE INFORMATION CARD

386 MINI-PC \$83

1K PRICE
EVAL \$295
8088 \$27



includes:

- 5 Serial, 3 Parallel (32bit max)
- Up to 8 meg ROM (27C080)
- 32k RAM exp. to 64Mbyte
- Battery backed RT Clock
- LCD and Keyboard ports
- IRQ x15, DMA x2, TIMER x4
- On-board LED display
- Industry Standard PC Bus

Perfect when a full-size PC is too large, expensive, or power hungry. A fully functional single board computer, needs only program and power source. Runs DOS / WINDOWS. Use Turbo C, BASIC, MASM. All utilities to do this included.

A to D D to A CONVERTERS

For PC or SBC
8,12,16 bit resolution
up to 24 channels
starting at \$21 OEM (1k)
eval kit \$75

\$95 UNIVERSAL PROGRAMMER

FLASH, EEPROM, NVRAM, EPROM up to 8 meg (27C64-080). Adapters for micros, PLCC, etc. Parallel port version for notebook. FAST AND EASY TO USE.



LOW COST... LOW POWER...

LOW RISC!

QTY 1K PRICE
\$1.99
EVAL KIT 7.00

LOWER COST, FASTER, EASIER TO PROGRAM SINGLE CHIP COMPUTER

COMPARE:	16C54	MV1200
OEM (1K) PRICE	\$2.57	\$1.99
RS232 PROGRAM DOWNLOAD	NO	YES
SINGLE CHIP OPERATION	NO	YES
BUILT-IN BASIC	NO	YES
EEPROM DATA MEMORY	NONE	64
PROGRAM MEMORY	768 OTP	1K FLASH
MATH REGISTERS	1	32
MAX INSTRUCTIONS / SEC	5M	20M
MAX COUNTER BITS	16	18
INPUT / OUTPUT BITS	12	15
A TO D COMPARATOR	NO	YES
HARDWARE INTERRUPTS	NONE	3

PINOUT:

RESET	1	20	VCC
PD0	2	19	PB7
PD1	3	18	PB6
XOUT	4	17	PB5
XIN	5	16	PB4
PD2/INT	6	15	PB3
PD3	7	14	PB2
PD4/TMR	8	13	PB1/AD1
PD5	9	12	PB0/AD0
GND	10	11	PD6

• LONG WORD INSTRUCTION • FRIENDLY SYMMETRIC ARCHITECTURE •



PC SOLID STATE DISK

\$21 OEM (1k) eval kit 75.00
FLASH / RAM / EPROM
256K-16M PCMCIA/DIPS


No More Hangups...

PC WATCHDOG!

Reboots PC OEM \$21 EVAL \$75

VGA LCD

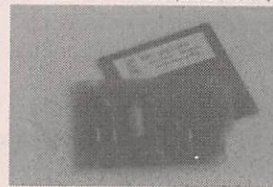640x480 controller for PC or SBC
\$27 oem \$95 eval
combo LCD/CRT
version available



visit our web site: www.star.net/people/~mvs

MVS BOX 850
MERRIMACK, NH 03054
(508) 792-9507

MVS

5yr Limited Warranty
Free Shipping
Hrs: Mon-Fri 10-6 EST

CIRCLE 323 ON FREE INFORMATION CARD

Electronic CAD for Windows

Professional Windows EDA tools at an affordable price with powerful features to make designing faster. WinBoard PCB layout delivers sophisticated interactive routing for complex designs, plus it has the tools needed for high-speed circuits, analog, RF and SMT designs.

WinDraft® Schematics


- ◆ Use True-Type fonts. Quickly copy and paste into other applications.
- ◆ Supports hierarchical designs, electrical rules checking, Annotation & Bill of Materials.
- ◆ Thousands of library parts and symbol editor included.

WinBoard™ PCB layout

- ◆ Supports 16 layers, multiple copper pours, and advanced features for RF designs.
- ◆ SMD & through hole library with on-line graphical editor.
- ◆ CAM outputs include BOM, in-circuit test, NC Drill, Gerber, Pick & Place, & Advanced Design Rule Checking (DRC).

With our unique **pin capacity** versions you only pay for what you need. You choose the base configuration to suit your needs today, and expand that configuration to handle increased pin capacity as your design requirements change.

WinDraft 2.0 Available Now

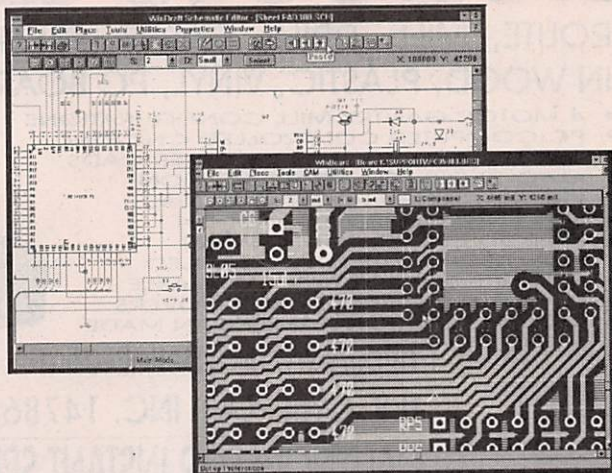

\$ 250 WinDraft or WinBoard - P650
\$ 495 WinDraft or WinBoard - unlimited

\$ 895 WinBoard P650 with CCT
 Spectra® autorouter.

Thousands of satisfied customers are using this new generation of powerful and affordable Windows EDA tools from Ivex. Your satisfaction is guaranteed!

World Wide Web: <http://www.ivex.com>

Information and free evaluation version is available on the Ivex WW Web, FTP and BBS.

Tel: (503) 531-3555
Fax: (503) 629-4907
BBS: (503) 645-0576



Ivex Design International. 15232 NW Greenbrier Parkway. Beaverton, Oregon 97006. USA.

ADV2_1

CIRCLE 319 ON FREE INFORMATION CARD


RAIN FOREST RESCUE:
TO HELP SAVE THE
BIRDS OUTSIDE
YOUR WINDOW
 Support Rain Forest
 Rescue. Help put a stop to
 the destruction of the
 planet's rain forests.
 To contribute to
 Rain Forest Rescue, call
 1-800-222-5312




The National
 Arbor Day Foundation

MEREDITH
INSTRUMENTS

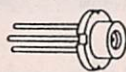5420 W. Camelback Rd #4
 Glendale, AZ 85301
 (602) 934-9387



New Visible Laser Diodes
\$10.00

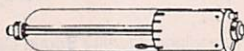

New He-Ne tubes from
\$10.00

Check out our complete line in our
Free catalog on Lasers and Optics

<http://www.mi-lasers.com>



New Green Laser Heads
\$150.00

ROBOTIC MACHINING

ROUTE, MILL, DRILL, CARVE, ENGRAVE, PAINT
IN WOOD, PLASTIC, VINYL, PC BOARD, & LIGHT METALS!

STARTING AT
\$695.00

- 4 MOTOR GANTRY MILL CONFIGURATIONS
- PC COMPUTER CONTROLLED CNC/DNC
- IMPORT/ EXPORT FILES TO OTHER CADS
- AUTO-BACKLASH COMPENSATION
- PRE-MACHINED HEAVY CASTINGS
- SIMULTANEOUS 3 AXIS MOTION
- FREE 3D CAD/CAM SOFTWARE
- AVAILABLE IN KITS OR ASSEMBLED
- EXPEDITE SERVICE ALSO AVAILABLE
- OPTIONAL ALUMINUM WAY COVERS
- .001" RESOLUTION / AMERICAN MADE



3 AXIS UNITS
FROM 12" X 12" TO
66" X 66" MACH. AREA

<http://www.uscyberlab.com>

U.S. CYBERLAB, INC. 14786 SLATE GAP RD., WEST FORK, AR 72774

CALL NOW FOR INSTANT SPECS 501-839-8293 24 HR. FAX-BACK

Since 1965, we've worked to make sure all children have the opportunity to learn valuable lessons during the years when it's easiest for them to learn. To find out how you can help, call your local Head Start.



Nurture the future
BE A HEAD START VOLUNTEER



Only You Can Prevent Forest Fires.



Filter Wiz v2.0

ACTIVE FILTER design software for Windows. Provides mastery of lowpass, highpass, bandpass and bandstop filters. Enhance critical signal components while controlling noise and other interference.


Meets the needs of both novice and professional designer. Standard (LE) version \$89, PRO version \$199.

Download: <http://www.schematica.com>
sales@schematica.com FAX:250-642-2644

Turn Your Multimedia PC into a Powerful Real-Time Audio Spectrum Analyzer

Features

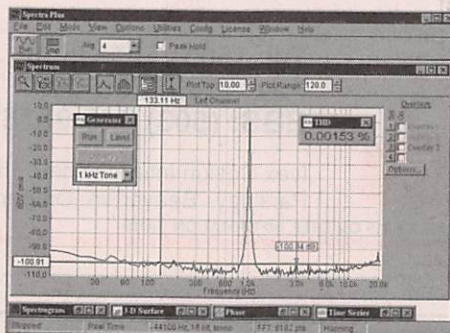- 20 kHz real-time bandwidth
- Fast 32 bit executable
- Dual channel analysis
- High Resolution FFT
- Octave Analysis
- THD, THD+N, SNR measurements
- Signal Generation
- Digital Filtering
- Triggering, Decimation
- Transfer Functions, Coherence
- Dynamic Data Exchange (DDE)
- Time Series, Spectrum Phase, Spectrogram and 3-D Surface plots
- Real-Time Recording and Post-Processing modes



Applications

- Distortion Analysis
- Frequency Response Testing
- Vibration Measurements
- Acoustic Research

System Requirements

- 486 CPU or greater
- 8 MB RAM minimum
- Win. 95, NT, or Win. 3.1 + Win.32s
- Mouse and Math coprocessor
- 16 bit sound card

Priced from \$299

(U.S. sales only - not for export/resale)

Professional Quality Sound Cards Available...Call

DOWNLOAD FREE 30 DAY TRIAL!

www.telebyte.com/pioneer

PHS

Pioneer Hill Software
24460 Mason Rd. N.W.
Poulsbo, WA 98370

Spectra Plus 4.0
Affordable Signal Processing Software

Sales: (360) 697-3472

Fax: (360) 697-7717

e-mail: pioneer@telebyte.com

PROGRAMMERS OVER 50 MODELS

ADVANTECH EETOOLS NEEDHAM'S DATA I/O ICE TECHNOLOGY HILO SYSTEM GENERAL CHROMA MODULAR CIRCUIT TECHNOLOGY XELTEK



PROMAX EMP-20 MEGAMAX MEGAMAX4 SIMM/SIP TESTER EMUPA

CALL ADVANTECH LABTOOL	599 EETOOLS SIMMAX
629 ICE TECH MICROV	795 CHROMA SIMM/SIP
650 EETOOLS ALLMAX +	359 MOD-MCT-EMUPA/R
409 EETOOLS MEGAMAX	279 MOD-MCT-EMUP/R
509 EETOOLS MEGAMAX4	49 EPROM 1G TO 512K
369 XELTEK SUPERPRO II	69 EPROM 1G TO 1MEG
409 XELTEK SUPERPRO II P	99 EPROM 4G TO 1MEG
249 XELTEK SUPERPRO L	199 EPROM 16G TO 1 MEG
165 XELTEK ROMMASTER II	89 EPROM 1G TO 8MEG
479 MOD-MCT-EMUPA	129 EPROM 4G TO 8MEG
739 STAG ORBIT-32	250 EPROM 8G TO 8MEG



LABTOOL48 MICROMASTER SUPERPRO ALLMAX PLUS ROMMASTER2

General Device Instruments

Sales 916-393-1655 Fax 916-393-4949 BBS 983-1234

Web www.generaldevice.com E-Mail icdevice@best.com

Coil Design and Construction Manual

R. E. BAKER



YOU CAN WIND YOUR OWN COILS?

There's no trick to it except knowing what you are doing. In a unique, 106-page book you can become expert in winding RF, IF, audio and power coils, chokes and transformers. Practically every type of coil is discussed and necessary calculations are given

with the mathematical data simplified for use by anyone. Get your copy today!

Mail coupon to:

Electronics Technology Today, Inc.

P.O. Box 240 • Massapequa Park, NY 11762-0240

Please send me my copy of *Coil Design and Construction Manual* (160). I enclose a check or money order for \$8.95 to cover the book's cost and shipping-and-handling expenses. NY state residents must add local sales tax.

Name _____

Address _____

City _____ State _____ ZIP _____

All orders must be paid in U.S. funds only. Sorry, no orders accepted outside of USA and Canada. Please allow 6-8 weeks for delivery.

The World's Largest Source for Home Automation

- The Best & Most Comprehensive Home Automation Catalog in the Industry.
- Best Customer Service & Technical Support

FREE

128 page full color catalog!

Thousands of hard-to-find automation, X-10 and wireless control products. Computer interfaces, software, development tools, lighting control, telephone systems, security systems, surveillance cameras, infrared audio/video control, home theater, touchscreen control, HVAC, pet care automation, wiring supplies, books and videos and much more!

World's Largest Selection!

Lowest Prices Guaranteed!



HOME AUTOMATION SYSTEMS, INC.

Questions: 714-708-0610 Fax: 714-708-0614

e-mail: catalog@smarthome.com

www.smarthome.com

Call for a **FREE** Catalog! 800-762-7846

800-SMART-HOME

Dealers/Resellers ask about our HASPRO Dealer Program 800-949-6255

Help protect our nation's soil and water.
Call for your free action packet.

1-800-THE-SOIL
WE OWE IT TO OUR CHILDREN

United States Department of Agriculture
Soil Conservation Service

EPROM+ A DEVICE PROGRAMMER FOR BENCH AND FIELD



GET MORE INFO
FROM OUR WEBSITE!
www.arlabs.com

SUPPORTS ALL
STANDARD PARTS!

USES PARALLEL
PRINTER PORT!

- FIRST GENERATION EPROMS** (24 PIN) 2708, TMS2716*, 1702*, 25XX
- SECOND GENERATION EPROMS** (24, 28, 32 PIN) 2716 - 27C080 (8 MEG)
- FLASH EPROMS** (40, 42 PIN) 27C1024 - 27C160 (16 MEG)
- 16 BIT EPROMS** (40, 42 PIN) 27C1024 - 27C160 (16 MEG)
- FLASH EPROMS** (32 PIN) 28F, 29C, 29EE, 29F FAMILIES PLUS BOOT BLOCK
- EEPROMS/NVRAMS** (24-32 PIN) 28C04 - 28C010, X2210/12, ER5901, 12XX
- SERIAL EPROMS** (ALL 8 PIN PARTS) 17, 24, 25, 35, 59, 80011, 85, 93, ER1400
- BIPOLAR PROMS** (16-24 PIN) 74SXXX AND 82SXXX FAMILIES
- MICROCONTROLLERS** (ALL FAMILIES) 874X, 875X, 87CSXX, 87C75X, 89C5X, 89CX051 68HC705, 68HC711, PIC12XXX - 16XXX, 17C4X PLUS FLASH AND 14000
- ◆ **READ, PROGRAM, COPY COMPARE, FILE LOAD/SAVE (PLUS MORE!)**
- ◆ **FULL SCREEN EDITOR W/25 COMMANDS + BYTE & WORD MODES**
- ◆ **SOFTWARE RUNS UNDER DOS, WIN3.1/95 ON ANY SPEED MACHINE**
- ◆ **MADE IN THE USA • 30 DAY MONEY BACK GUARANTEE**

SYSTEM INCLUDES: PROGRAMMING UNIT, SOFTWARE, PRINTER PORT CABLE, PRINTED MANUAL AND POWER PACK


ANDROMEDA RESEARCH
P.O. BOX 222
MILFORD, OHIO 45150
(513) 831-9708 FAX (513) 831-7562

\$289

\$5.00 SHIPPING • \$5.00 C.O.D.
VISA • MASTERCARD • AMEX

Learn MICROCONTROLLERS EMBEDDED SYSTEMS and PROGRAMMING...

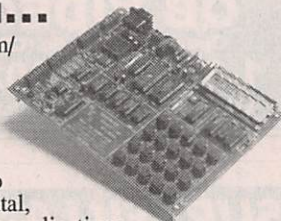...with the AES learning system/
embedded control system.
Extensive manuals guide you
through your development
project. All programming and
hardware details explained.
Complete schematics. Learn to
program the LCD, keypad digital,
analog, and serial I/O. for your applications.



**THREE MODELS AVAILABLE. Choose from an
Intel 8051, Intel 8088, or Motorola 68HC11
based system. All models come with:**

- 32K Byte ROM, 32K Byte RAM • 2 by 16 Liquid Crystal Display • 4 by 5 Keypad • Digital, Analog, and Serial I/O • Interrupts, timers, chip-selects • 26 pin expansion connector • Built-in Logic Probe • Power Supply (can also be battery operated) • Powerful ROM MONITOR to help you program • Connects to your PC for programming or data logging (cable included) • Assembly, BASIC, and C programming (varies with model) • Program disks with Cross Assembler and many, well documented, program examples • User's Manuals: cover all details (over 500 pages) • Completely assembled and ready to use • Source code for all drivers and MONITOR • Optional Text Book

Everything you need. From \$279.
Money Back Guarantee

Call for Free Info Pack, or see
WEB at <http://www.aesmicro.com>
714-550-8094, FAX 714-550-9941

AES
Advanced Educational Systems

Call 1-800-730-3232

AES 575 ANTON BLVD., SUITE 300, COSTA MESA, CA 92626, USA

Plug Power

UNIT OF MARE DESIGNS INC.

The Smallest*, Lightest*, Coolest*,
5% Regulated, 10 Watt DC
Power Supplies are here!

* 1.9 x 2.1 x 1", 2.9 oz. Tiny, aren't they?

VDC @ Amps

5.0	1.6
9.0	1.1
12.0	0.8

\$29.95

SINGLE Qty., US\$
+ NEXT DAY or 2 DAY AIR

Detailed Specs on web site!

www.plugpower.com/alpha.htm

CALL FREE in US & Canada:

1-888-PLUGPWR

(1-888-758-4797)




See the web site!

NEW! ELECTRONICS CD-ROM

The most
effective way
of learning
electronics

Two Courses on
one CD-ROM!
Only \$49⁰⁰

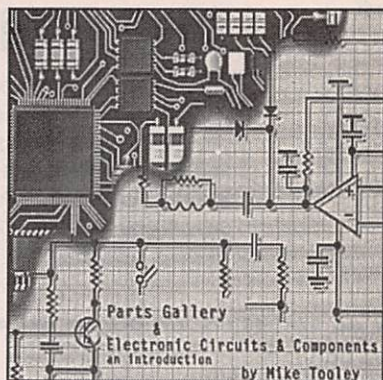

Electronic Circuits and Components

Discover the standards and application of common types of electronic components and how they are used to form complete circuits in **Electronic Circuits & Components**. Sections on the disc include: Fundamental Electronic Theory, Active Components, Passive Components, Analog Circuits, and Digital Circuits. The CD-ROM includes:

- Interactive laboratories • Supervisor notes
- Full audio commentary • Editable worksheets
- About 20 links to pre-designed Electronics Workbench circuits

The Parts Gallery

Many students have a good understanding of electronic theory but still have difficulty in recognizing the vast number of different types and makes of electronic components. **The Parts Gallery** has been designed to help overcome this problem; it will help students recognize common electronic components and their corresponding symbols in circuit diagrams. This CD ROM incorporates a quiz so that students can check their knowledge of electronic components and symbols. The CD-ROM includes:

- Over 150 component and circuit photographs • Supervisor notes
- Self-test component and symbol quizzes • Hundreds of electronic symbols

To Be Released Soon!

A series of interactive CD-ROMs provides a comprehensive and up-to-date introduction to the world of electronics. The series provides a sound understanding of the principles and behavior of electronic components and the circuits to which they are connected. Two new CD ROM discs are to be released in the very near future. They are **Analog Electronics** and **Digital Electronics**. As soon as they are released, information on their contents and availability will be published.

Cable TV Outlet



Factory
Direct!



Get the Clearest Coverage
of Sports, Movies, News,
Main Events and Adult!

- Unbeatable Wholesale Pricing-
- Converters/Descramblers-
- Filters and Accessories-
- Premium Channel Coverage-
- Full Satisfaction Guaranteed-

QB VIDEO

Open M-F 9a to 5p (CT)

1-800-249-3025

Visa, MC & C.O.D.'s Welcome

SURVEILLANCE

The Latest High Tech

Professional Electronic Devices


Our latest catalog offers a HUGE selection of surveillance, counter-surveillance/privacy devices: hidden video equipment, pinhole cameras \$149⁰⁰, telephone recording systems: 12-Hour \$139⁰⁰, 16-Hour \$199⁰⁰ touch tone decoders, scanners, bug/phone tap detectors, voice disguisers, telephone scramblers, locksmithing tools, and more.

Catalog \$5.00

SPY OUTLET

P.O. Box 337, Buffalo, NY 14226
(716) 695-8660/(716) 691-3476

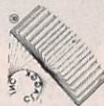Claggk Inc., PO Box 4099
Farmingdale NY 11735-0792
e-mail: claggk@poptronix.com



Name _____ Phone _____

Address _____

City _____ State _____ Zip _____

Enclosed is \$49 for each Student version (single user) of **The Parts Gallery** and **Electronic Circuits & Components** on a single CD-ROM, shipping included inside the U.S.

I am ordering (....) copies at \$49 each. NY State residents must include sales tax.

- ☐ I have enclosed my check for \$ _____
- ☐ Please charge my credit card for \$ _____
- ☐ Visa ☐ MasterCard ☐ Discover Expiration Date: ____/____/____
- Card Number _____ Signature _____

(Name on order and signature must be same as on Credit Card.)

ALL ELECTRONICS

C O R P O R A T I O N

QUALITY
PARTS

FAST
SHIPPING

DISCOUNT
PRICING

CALL, WRITE, FAX
or E-MAIL For A
Free 96 Page
CATALOG.
Outside the U.S.A.
send \$3.00 postage.

Stepper Motor Controller IC



E-Lab # EDE-1200
Controller IC for unipolar stepper motors. Designed to interface a logic-level signal to a stepper motor. Also capable of running independently (self-clocking). Allows for half-stepping and directional control. TTL/CMOS compatible inputs. TTL-level outputs. 18 pin DIP package. 5 vdc operation. Works for most unipolar stepper motors. Includes specs and hook-up diagram.

CAT# EDE-1200 **\$12.50** each

PRICE REDUCTION! SL WABER "PowerMaster" Surge/Noise Suppressor

Protect your computer, phone, VCR, TV and stereo equipment from damaging transient voltage surges. Just plug in, and you've got full 3-line protection. Visual indicator lets you know that the device is functioning.



UL, CSA listed.
CAT # PW-103
Formerly \$3.75

\$2.75 each

S-VHS Tape (Used)



Super VHS tape users! Save a bundle on name-brand S-VHS, T-120 tapes. These tapes were used for a brief period, then bulk erased. The record-protect tabs have been broken out, so you will have to cover the notch with a piece of tape, but they work great and cost a fraction of the "new" price. Try some, you'll be back for more.

CAT #S-VHS **\$3.00** each

10 for \$28.00 • 100 for \$250.00

Shielded Woofer


Designed for use in Infinity center channel video sound systems. These well constructed woofers have shielded magnets to prevent interference with picture quality.

5 1/4" 6 OHM

1" voice coil. 8 oz. magnet. 50 watts max power. 3.125" deep.

CAT # SK-7346

\$10.00 each

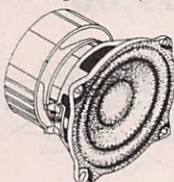

12 for \$96.00

Miniature Temperature Sensor (THERMISTOR)

Keystone (Similar to #RL0503-17-56K-96-MS) 30K ohms @ 25 degree C. (77 degree F.) Negative temperature coefficient. 0.2" long X 0.09" diameter, epoxy insulated bead. 1.13" long teflon insulated AWG#30 wire leads. Prepped with 0.75" long metal tabs.

CAT# THR-19

2 for \$1.50

box of 264
\$150.48
(57¢ each)

3 Volt Lithium Coin Cell

Panasonic # BR2330-1GU
3 volt, 255 mAh coin cell. Lithium batteries have a very long shelf life and are great for memory back-up protection. 0.9" diameter x 0.12" thick. 0.7" between positive and negative pc leads.

CAT #LBAT-16

2 for \$1.50

20 for \$12.00
100 for \$45.00
1K for \$300.00

Ferrite Bead

TDK # HF70RH 16X28X9
1.1" x 0.63" od x 0.35" id.

CAT # FB-24 \$1.00 each

10 for \$8.50 - 100 for \$70.00



RED Ultrabright LED

PAINFULLY BRIGHT RED LED
2500 to 4000 mcd @ 20 ma. These T 1 3/4 (5 mm diameter) red LEDs are significantly brighter than conventional LEDs. At close range, they are painful to look at. They are great for attention getting displays that can be seen from a distance. Water clear in off-state.

CAT # LED-42

2 for \$1.20

10 for \$5.00
100 for \$45.00
1000 for \$400.00

High Brightness FLASHER LEDs

T 1 3/4 (5mm) high brightness RED LEDs with built-in flasher unit.

3-5 Vdc operation

CAT # LED-4 2 for 90¢

100 for \$40.00 - 1000 for \$300.00

Stepper Motor

Airpax # LB82246

Unipolar, two-phase, 6 lead stepper motor. 500 ohm coil. 7.5 degrees per step. 1.4" dia. X 0.7" body. Oval mounting flange has holes on 1.65" ctrs. 0.08" (2mm) dia. shaft is 0.4" long and is fitted with a 0.31" dia. gear with 18 teeth. 15" leads.

CAT # SMT-28

\$2.00 each

"HI-8" Video Cassette

SONY Hi-8 Top quality, metal particle 120 minute video cassettes. Used for a short time, then bulk-erased. Each cassette has its own plastic storage box.



CAT # VCU-8

\$3.00 each

10 for \$28.00
100 for \$250.00

ORDER TOLL FREE

1-800-826-5432

MAIL ORDERS TO:
ALL ELECTRONICS CORP.
P.O. BOX 567
VAN NUYS, CA 91408-0567


FAX (818) 781-2653 • INFO (818) 904-0524
INTERNET <http://www.allcorp.com/>
E-MAIL allcorp@allcorp.com

NO MINIMUM ORDER • All Orders Can Be Charged to Visa, Mastercard, American Express or Discover • Checks and Money Orders Accepted by Mail • Orders Delivered in the State of California must include California State Sales Tax • NO C.O.D. • Shipping and Handling \$5.00 for the 48 Continental United States • ALL OTHERS including Alaska, Hawaii, P.R. and Canada Must Pay Full Shipping • Quantities Limited • Prices Subject to change without notice.

MANUFACTURERS - We Purchase EXCESS INVENTORIES... Call, Write, E-MAIL or Fax YOUR LIST.

New and Pre-Owned Test Equipment

Goldstar

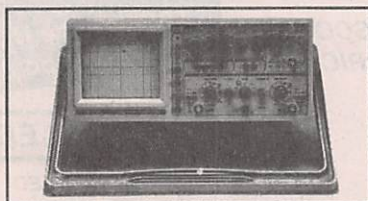

Model OS-9100P → **\$899.00**

Full 100 MHz Bandwidth!

- Dual-Channel, High Sensitivity
- TV Synchronization Trigger
- Calibrated Delayed Sweep
- Includes Two Probes, 2 Year Warranty

FREE SHIPPING!

ON GOLDSTAR EQUIPMENT
ANYWHERE IN THE U.S.
Excluding AK & HI



BK PRECISION
MAXTEC INTERNATIONAL CORP.

Model 4040 **\$499.00**
20 MHz Sweep/Function Generator

- 0.2 Hz to 20 MHz, 5 digit LED Display
- AM & FM Internal or External Modulation
- Sine, Square, Triangle, TTL, CMOS Outputs
- Burst Operation
- External 30 MHz Frequency Counter

NEW!



1-800-99-METER

Pre-Owned Oscilloscope Specials

B + K Precision 1476 10 MHz **\$229.00**
Great Starter Scope!

Tektronix 465	100 MHz	\$599.00
Tektronix 465B	100 MHz	\$699.00
Tektronix 475	200 MHz	\$799.00
Tektronix 475A	250 MHz	\$899.00

- The Industry Standard of Oscilloscopes
- Dual Channel, Calibrated Delayed Sweep
- Professionally Refurbished
- Aligned & Calibrated to Original Specifications
- 6 Month Warranty - The Longest Available!

LOWEST PRICES EVER!

NEW FLUKE MULTIMETERS & TEKTRONIX OSCILLOSCOPES

The Industry Standard in Multimeters

Fluke Model 87 ..\$285.00

TEKTRONIX TDS SERIES
ON SALE!

See us on the Web!
www.fotronic.com

1-800-996-3837

Test Equipment Depot

A FOTRONIC CORPORATION COMPANY

P.O. BOX 708 Medford, MA 02155

(617) 665-1400 • FAX (617) 665-0780

email: afoti@fotronic.com

CIRCLE 328 ON FREE INFORMATION CARD

Make Life Easy!

Program these PICs in BASIC:

12C671, 12C672, 14000,
16C554, 16C556, 16C558,
16C620, 16C621, 16C622,
16C62, 16C63, 16C64, 16C65,
16C71, 16C72, 16C73, 16C74,
16C84, 16F83, 16F84, more.



BASIC makes it easy for you to program the fast and powerful Microchip PIC microcontrollers.

- Expanded BS1/2 compatible instruction set
- True compiler provides faster program execution and longer programs than BASIC interpreters

new! PicBasic Pro Compiler - \$249.95
PicBasic Compiler - \$99.95
EPIC Pocket PIC Programmer - \$59.95
PICProto Boards - \$9.95 to \$17.95

microEngineering Labs, Inc.
Box 7532 Colorado Springs CO 80933
(719) 520-5323 fax (719) 520-1867
<http://www.melabs.com>

AC POWER CONTROL

The TC4 provides 4 triacs controlled thru the par. port of a PC. Allows fast setup of testing and production equipment. Makes those construction applications that require a "third hand" easy.

- > 4 120V triacs at 12A each & 12A total
- > Large heat sink for continuous max power
- > Controlled by PC par. port or microcntrl
- > Easy use with C, Asm, Qbasic.....
- > MSDOS driver included
- >> \$159

CYLAB
incorporated

Voc 513 271 4436
Fax 513 271 3933
5725 Dragon Way
Cincinnati OH 45227

WHOLESALE PRICES
STARTING AS LOW AS \$99.00

CABLE TV DESCRAMBLERS CONVERTERS FILTERS • VIDEO STABILIZERS

1 Year Warranty on All Products.
Affordable Extended Warranty.
FREE CATALOG!



Call the Cable Professionals 24 Hours A Day!

Orion Electronics

1-800-379-3976

[HTTP://WWW.ORION-ELECTRONICS.COM](http://WWW.ORION-ELECTRONICS.COM)



CABLE TV CONVERTERS

*Equipment & Accessories
Wholesalers Welcome*

Call C&D ELECTRONICS
1-888-615-5757 M-F 10a-6p

The Electronic Experimenter's Journal

It's part catalog, part magazine and part data book with kits, parts, plans, articles, and application notes.

Call for your **FREE**
copy today

Debo Electronics
4025 Edwards Rd.
Cincinnati, OH 45209

1 800 423-4499

BUGGED??

EAVESDROPPING is unbelievably widespread! Electronic Devices with amazing capabilities can be monitoring your telephone and room conversations **RIGHT NOW!** Are you sure you're safe? **FREE CATALOG** tells you fast! Includes Free Bonus details on fantastic opportunities now open in Counter-Surveillance field. Exciting, immensely interesting and **EXTREMELY** profitable (up to \$250/hr) full/part-time income. Call Now! **1-800-732-5000**

AMAZING PRODUCTS!



ELECTRONIC & SCIENTIFIC DEVICES



LASER WINDOW BOUNCE SCIENCE PROJECTS

USES SCATTERED AND DIRECT REFLECTIONS

Remarkable concept allows user to hear sounds within a premise over a beam of laser light reflected from a window or similar surface. Experimental device provides hours of interesting and educational use. Utilizes a visible red laser that simplifies alignment and discourages illegal use. Usable range will vary-expect about 20 to 50 meters. Optional lens will increase range 200 to 400 meters! Further range requires expensive optics. Requires a sturdy video tripod (not incl.) Caution-check local law in your state if planning to use for accessing oral communication. **REQUIRES OPTICAL ALIGNMENT**



LWB5 Plans.....\$20.00 **LWB5K KIT/PLANS**.....\$149.50
LWB50 Ready to Use With Selected Laser Pointer.....\$199.50
LWB70 Above With High Performance Laser Gun Sight, Long Range
 Extender Lens and Cushioned Headsets.....\$299.50

WIRELESS LAB KITS

ALL PARTS TO BUILD 6 EXCITING TRANSMITTER PROJECTS

- 1 Super Sensitive Ultra Clear 1 Mile+ Voice Transmitter
- 2 1 Mile+ Telephone Transmitter
- 3 Beeper Alert for Above Telephone Transmitter
- 4 Tracking/Homing Beacon "Beeper Transmitter"
- 5 Transmitter Rebroadcasts Video or Audio Outputs
- 6 Short Range TV/FM Disrupter NEAT PRANK!! Discretion Advised

All 6 Above Kits Plus FREE Info Data Pack on "HELPFUL HINTS" Building and Tuning Wireless Devices

COMBOX Kits and Plans.....\$59.50

ULTRA BRIGHT LASERS

4 to 7x brighter 650-630 nm Radiation

ALL METAL CONSTRUCTION
1 YEAR WARRANTY

BATTERIES INCLUDED
LAPN65 15mw equiv 2000 ft.....\$29.95
LAPN63 30mw equiv 3000 ft.....\$69.95

FOCUSABLE LASER POINTER

LAPN65F Focusable Above **LAPN65**...\$39.95

TRANSISTORIZED TESLA COIL

Turns a light bulb into a SPECTACULAR PLASMA DISPLAY

Transmits Wireless Energy
 Noiseless Operation
 Pyrotechnic Effect
 12 VDC/5 Amps or Battery
 115 VAC Optional Converter
 Adjustable Frequency
 Control For Effect



TCL5 Plans.....\$8.00
TCL5K Kit/Plans.....\$59.50
TCL50 Ready to Use.....\$99.50
TCLC7 12VDC/7Amps.....\$39.50

CYBERNETIC EAR!

Use For Courtesy Lowering of TV Volume Control etc. Detect Rattles and Other Mechanical Anomalies, Leaking Gases, Air, or Corona. Great Safety Aid for Shop Drivers.

Enhances Most Hearing 3 to 4 Times!
 Adjustable Volume Control, Fits Easily Into Ear. Many Many Uses!

CYBEREAR Ready to use...\$19.95

3 MI TELEPHONE TRANSMITTER

Tunable on FM Broadcast. Excellent Telephone Project. Only Transmits When Phone is Used

VWPM7 Plans Only.....\$7.00

Uses Readily Available Parts and Pieces

ELECTRIC CHARGE GUN WITH 15 FOOT RANGE!

Stuns and Immobilizes Attackers From a Distance. More Knockdown Power than a Handgun!!
 Check Your State Legality

FREE!!! 100KV Stun Gun

ECG10 With STUN100.....\$249.50

STUNGUNS SOLD SEPARATELY

STUN200 200KV StunGun.....\$49.50

STUN300 300KV StunGun.....\$69.50

JACOBS LADDER

Observe a pyrotechnical display of "traveling" fiery plasma. Starts off as 1/2" arc and expands to over 3" before evaporating into space. This is an excellent attention getting display as well as a winning science project!! With arc control.

JACK1 Plans.....\$8.00
JACK1K Kit Minus Case.....\$129.50
JACK10 Ready to Use.....\$249.50
12KVG20 Pwr Supply Only.....\$99.50
12KVG20K Kit of Pwr Supply.....\$79.50

250KV TESLA COIL

10-14" of Explosive Bolts of Lightning

Transmit Wireless Energy
 Strange and Bizarre pyrotechnical effects.
 Ion Motors Anti-Gravity
 Size 20" H x 8" Sq
 Weight - 25 Pounds
 115 Volts/2 Amps AC
 Labeled "Use Caution"



BTC3 Plans.....\$15.00
BTC3K Kit/Plans.....\$349.50
BTC30 Ready to Use.....\$449.50
BTC4 Plans, 500kv Unit.....\$20.00

HIGH CRIME AREA SECURITY!

INFINITY+ TRANSMITTER

ROOM MONITOR/ LINE GRABBER/CONTROLLER

- MONITOR YOUR PREMISES Avoid ambushes and break ins.
- ACCESS ON GOING CALLS Long distance teenagers!
- CONTROL 8 APPLIANCES Remote control your home!!!
- EXTRA ADDED FEATURE!!! Redirect those COIN HUNGRY slot coin modes from pay phones!

TELCON3 Plans.....\$10.00
TELCON3K Kit/Plans.....\$99.50
TELCON30 Ready to Use.....\$149.50
 Programmed With built in **BEEPER ALERT**

PHASOR BLAST WAVE PISTOL

130 db of Directional Sonic Shock Waves Energy
 Handheld and Battery Operated

PPP1 Plans.....\$8.00
PPP1K Kit/Plans.....\$49.50
PPP10 Ready to Use.....\$79.50

ATTENTION! HIGH VOLTAGE EXPERIMENTERS

Battery Powered Mini Sized Modules for research in: HOVERCRAFT, ION GUNS FORCE FIELDS, SHOCKERS etc

MINIMAX4 4KV@10ma.....\$19.50

BURNING LASER RAY GUN

UTILIZES LOSSLESS ENERGY CHARGING

All Parts Available

LAGUN2 Plans.....\$20.00

BURNING CO2 BENCH LASER

HOTTER THAN MOST TORCHES!

All Parts Available

LC7 Plans.....\$20.00

KINETIC ELECTRIC GUN

PIONEER A FUTURISTIC WEAPON!

500 Joules Energy Storage
 Constant Current Charging
 Triggered Spark Switch
 Ballistic Velocities
 Handheld Battery Operated
 Labeled A Dangers product

PROTOTYPED IN OUR LABS JOIN THE RESEARCH!

EGUN1 Plans with Parts List.....\$20.00

All Parts are Individually Available

3MI FM BC TRANSMITTER

Safety Product Allows Listening to Children or Invalids in Hazardous Areas, Pools, Ponds etc. Great Security Intrusion Alert! Uses FM Table Top Radio.

FMV1K Kit/Plans.....\$39.50

ION RAY GUN PROJECTS ENERGY!

Star Wars Technology
 Demonstrates Weapons Potential!

IOG7K Kit/Plans.....\$99.50

ATTENTION!! RAILGUN EXPERIMENTERS

HIGH ENERGY PULSER

RAIL GUN, COIL GUN, EXPLODING WATER, ANTIGRAVITY, MASS WARPING, LEVITATION, PLASMA PROPULSION, LATTICE SNAPPING, EMP etc

- Lossless Energy Charging
- Programmable Voltage to 2 KV and Energy Control to 3 KJ
- Triggered Spark Switch [IKJ]
- Universal 12 VDC or 115 VAC
- 7.5 X 7.5 X 7" Light weight

HEP3 Plans High Energy Pulser/Ignitor.....\$15.00

HEP3K Kit/Plans (Minus Energy Storage).....\$199.50

HEP30 Assembled (Minus Energy Storage).....\$299.50

HEPCAP 800 Joules Energy Storage.....\$199.50

GRAVITY GENERATOR

Demonstrates a unique phenomena of electrical reactions that produce the effect of "anti-gravity". You build and levitate a small mock space ship from simple materials. Excellent scientific demonstration of a fascinating method of levitation. **Levitate an Object!!**

GRA1 Plans and Book.....\$20.00

GRA1K Pwr Sup Kit/Plans.....\$99.50

GRA10 Assembled Pwr Sup.....\$149.50

ELECTRONIC HYPNOSIS AND MIND CONTROL

Generates Highly Effective Audible and Visual Stimuli With Bio-Feedback That Can Induce Hypnotic as Well as ALPHA Relaxed States of the Mind. Place Subjects "Under" Your Control. Enhances Hidden PSYCHIC Ability in Many People!

MIND Plans.....\$15.00

MIND2K Kit and Plans.....\$49.50

MIND20 Assembled.....\$79.50

TELEPHONE TAPING SYSTEM

EXTENDED X4 PLAY. Tapes Phone Conversation 20 Mins Into 21 Check Laws!

TAP30X Ready to Use.....\$84.50

BEEP10 Beeper Alert.....\$29.95

SHOCK FORCE FIELD/ VEHICLE OBJECT ELECTRIFIER

Hand Shock Balls, Wands, Electrify Objects, Great Payback for Those Who Grunt!

SHK7K Kit of Pwr Module.....\$19.50

ATTENTION!! RAILGUN EXPERIMENTERS

RAIL GUN, COIL GUN, EXPLODING WATER, ANTIGRAVITY, MASS WARPING, LEVITATION, PLASMA PROPULSION, LATTICE SNAPPING, EMP etc

- Lossless Energy Charging
- Programmable Voltage to 2 KV and Energy Control to 3 KJ
- Triggered Spark Switch [IKJ]
- Universal 12 VDC or 115 VAC
- 7.5 X 7.5 X 7" Light weight

HEP3 Plans High Energy Pulser/Ignitor.....\$15.00

HEP3K Kit/Plans (Minus Energy Storage).....\$199.50

HEP30 Assembled (Minus Energy Storage).....\$299.50

HEPCAP 800 Joules Energy Storage.....\$199.50

HOTSHOT

HEP3K Kit/Plans (Minus Energy Storage).....\$199.50

HEP30 Assembled (Minus Energy Storage).....\$299.50

HEPCAP 800 Joules Energy Storage.....\$199.50

INFORMATION

UNLIMITED DEPT EN 1097

BOX 716 AMHERST, N.H. 03031

24 Hr Toll FREE "Orders Only" Line 1-800-221-1705

Fax Your Order to 1-603-672-5406

9 to 5 pm EST Information Line 1-603-673-4730

See Our Web Site at <http://www.amazing1.com>

We Accept MC, VISA, Cash, MO, Checks. Please add \$5.00

Shipping. COD Orders Add

Additional \$4.75. REQUEST A FREE CATALOG!!

ELECTRONIX EXPRESS

WELLER SOLDERING STATION - MODEL WLC 100

- Variable power control (5 to 40 watts)
- Replaceable heating element
- Quality light-weight pencil iron

\$36⁹⁵



DUAL-TRACE OSCILLOSCOPE

W/HIGH RESOLUTION, BLUE CRT
INCLUDES PROBES, POWER CORD

2 YEAR WARRANTY
Goldstar 5020P

20MHZ **\$349⁰⁰**



SCOPE PROBE 60 MHZ

SWITCHABLE X1, X10

\$12⁹⁵

DIGITAL MULTIMETER

WITH CAP/FREQUENCY/
TRANSISTOR TESTER
Model DM645

\$34⁹⁵



PAD-234

DIGITAL/ANALOG TRAINER

Complete portable workstation. Variable and fixed power supplies, function generator, digital I/O, rugged design, high impact case.



Assembled

\$150⁰⁰

Kit

\$110⁰⁰

HIGH QUALITY TOOLS

With Cushion Grips and Return Spring

Needle Nose Pliers **\$2⁹⁵**

Wire Stripper **\$1⁵⁰**

Diagonal Cutter **\$2⁹⁵**

POWER SUPPLIES

0-30 VDC, 0-3 Amp. Built-in current limiting, overload protected, constant voltage and current operation.



01PSGP4303A

Analog Display

\$165.00

01PSGP4303D

Digital Display

189.00

SOLDERLESS BREADBOARD

830 tie points. MB102PLT model features 3 binding posts and aluminum backplate.

Part No.	1-9	10+
MB102	5.95	5.00
MB102PLT	8.95	8.00



HELPING HAND

WITH

MAGNIFIER

#060836




RESISTOR KIT

1/4W 5% film. 5 pieces each of 73 values. 365 pieces total.

\$3⁹⁵

MOTION DETECTOR

\$2 ea. - 10 For \$15

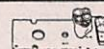

LM555 10 Min.	22¢ ea.
LM741 10 Min.	27¢ ea.
74LS00 10 Min.	18¢ ea.
7805 Regulator 10 Min.	30¢ ea.
2N3904 10 Min.	6¢ ea.
PN2222 10 Min.	6¢ ea.
Red LED T 1 1/4 10 Min.	6¢ ea.
Green LED T 1 1/4 10 Min.	7¢ ea.
Yellow LED T 1 1/4 10 Min.	8¢ ea.
Photo Cell 10 Min.	65¢ ea.
100K Pot., 1" Shaft PC Mt. 10 Min.	15¢ ea.

SOLDERING IRON 3-WIRE

HIGH PERFORMANCE

#060501

\$5²⁵

SOLDERING IRON STAND

W/SPONGE

#060842

\$3⁵⁰



1 LB. 60/40 Solder Roll .031"

\$5⁹⁵

DESOLDER PUMP

W/TIP #060820

\$3⁵⁰

15 TURN POT

69¢ ea.

7 SEG. DISPLAY

60¢ ea.

Bouras 3006P series. All standard values available.

MAN72 C.A Red 0.3"

MAN74 C.C Red 0.3"

FREE CATALOG

MORE Low-Priced Items In Our

FREE

192-Page Catalog



TERMS: Min. \$20 + shipping. School Purchase Orders, VISA/MC, Money Order, Prepaid. NO PERSONAL CHECKS, NO COD. NJ Residents: Add 6% Sales Tax.

In NJ: 732-381-8020

FAX: 732-381-1572

365 Blair Road • Avenel, NJ 07001-2293

800-972-2225

<http://www.elexp.com>

email: electron@elexp.com

CIRCLE 327 ON FREE INFORMATION CARD


"7-WAY COPY CAT \$995.00*"

NEW!

7-Way

StarTac

\$1295.*

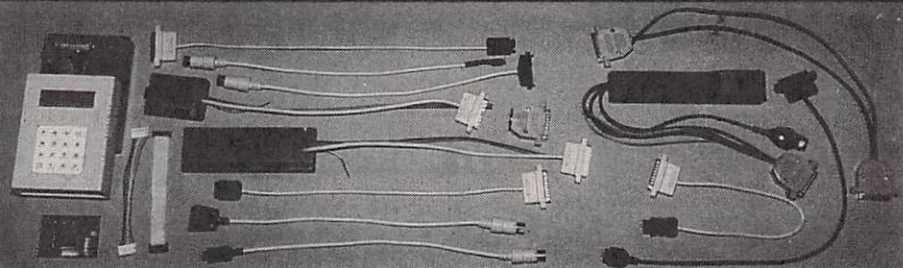

- Does.. 1. MOTOROLA (includes elite and EE3)! 2. NEC (includes P100-200-300-400-600-700)! 3. AUDIOVOX (does new 800 & 850)! 4. PANASONIC! 5. SONY (H333)! 6. MITSUBISHI-DIAMONDTE.L! 7. GE-ERICSSON (includes new version)!

We offer complete upgrade options on older units as well as new and replacement cables. We also offer used and refurbished units. For a complete catalog, visit us on the web at www.celltec.com

All units are sold for **EXPERIMENTAL AND EDUCATIONAL PURPOSES ONLY!**

Upgrade

Your Old Copy

Cat **NOW**

to a **7-Way**

with **EE3**

& **StarTac**

*cables optional

CALL US TODAY AT 770.973.8474

CIRCLE 311 ON FREE INFORMATION CARD


**FREE
244 PAGE
CATALOG**



**UNBELIEVABLE
VALUE!**

4 Way Speaker Switch

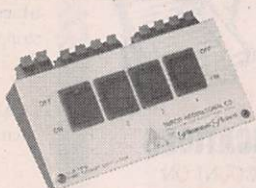Control up to 4 pairs of speakers with this compact speaker selector switch. Features circuit protector, heavy duty rocker switches, spring loaded terminals, and silver plated switch connectors. Includes one pair of amplifier inputs. Load to amplifier is minimum 4 ohms (with 8 ohm speakers) or 220 ohms with all speakers switched off. Net weight: 1 lb.



WAS \$22.50 EACH
NOW \$15.00 EACH

#EN-309-030

"The Sound Bridge" FM Stereo Wireless Transmitter

The Sound Bridge is a mini FM wireless transmitter that can be used to broadcast stereo sound from any audio source like portable CD players, TVs, electronic games, CD-ROM, even computer soundcards, to your home stereo receiver! Adjustable from 89 to 95.5 MHz.



**HOT
NEW
ITEM!**

#EN-249-220

\$14.95 EACH

Weller Professional Irons

Weller



Perfect for a variety of electronic soldering work, this top quality iron features a long life, double coated tip and a quick change, plug-in heater element. Lightweight handle includes a comfortable cushioned grip. Net weight: 1/2 lb.

#EN-372-110 (25 Watt) \$30.90 (1-3) **\$28.50** (4-UP)
#EN-372-112 (35 Watt) \$38.90 (1-3) **\$34.95** (4-UP)


Home Theatre In-Floor Subwoofer

To fully appreciate the potential of movie soundtracks, a dual voice coil subwoofer is a must! Many film special effects are extremely demanding in the low frequency range and require a subwoofer that can duplicate explosions, earthquakes, even the footsteps of Tyrannosaurus Rex! This subwoofer fits the bill by featuring a 10" dual voice coil woofer for true stereo operation and high pass filters for your main speakers. The most unique feature of this subwoofer is the fact that it is designed to be mounted in between the floor joists in new and existing home constructions. Simply mount the in-floor sub to the joists and mount a heat register grill above opening in subwoofer front enclosure. The subwoofer is now totally out of view and ready to rumble! Includes detailed installation manual.

Specifications: 10" dual voice coil treated paper cone woofer with poly foam surround ◆ Frequency response: 30-100 Hz ◆ Nominal impedance: 8 ohms per coil ◆ Power handling: 100 watts RMS channel/140 watts max ◆ SPL: 89 dB 1W/1m ◆ Dimensions: 27" D x 14-5/8" W x 9" H ◆ Net weight: 29 lbs.

#EN-300-445

\$139.95 EACH

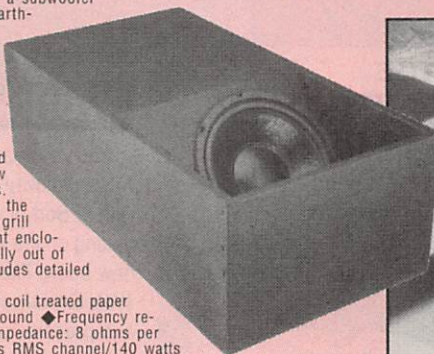

Peak Instrument Co.

"The Woofer Tester"

Peak Instrument Co. proudly introduces "The Woofer Tester". Just ask any loudspeaker engineer, and they will tell that the only way to design enclosures of the correct size and tuning is to measure the Thiele-Small parameters for the actual drivers to be used. The reason? Manufacturers published specs can be off by as much as 50%! But until now, measuring the parameters yourself required expensive test equipment and tedious calculations, or super expensive measurement systems (\$1,200 to \$20,000). The Woofer Tester changes all that. Finally, a cost effective, yet extremely accurate way to derive Thiele-Small parameters, in only minutes! The Woofer Tester is a combination hardware and software system that will run on any IBM compatible computer that has EGA or better graphics capability and an RS232 serial port. The Woofer Tester will generate the following parameters. Raw driver data: Fs, Qms, Qes, Qts, Vas, BL, Re, Le, SPL @ 1W/1m, Mmd, Cm, and Rm. Sealed box data: Fsb and system Q. Vented box data: Fsb, ha, alpha, and Q loss. The Woofer Tester system includes hardware, test leads, serial cable, AC wall adaptor, detailed instructions, and software.

**QUICKLY AND
ACCURATELY
MEASURES:
Fs, Qms, Qes, Qts,
Vas, BL, Re, Le,
SPL @ 1W/1m,
Mmd, Cm, and Rm
IN MINUTES!**

◆ 30 DAY MONEY BACK GUARANTEE
◆ 1 YEAR WARRANTY ◆ SAME DAY SHIPPING

#EN-390-800 **\$249.00** EACH

900 MHz Wireless Speaker System

- ◆ 900 MHz technology sends signal up to 180 ft., through walls, floors and ceilings.
- ◆ Ideal for use as rear surround speakers or for adding wireless sound to every room in the house!
- ◆ Full range, bass reflex design with built-in high power, low distortion amplifier.
- ◆ Weather resistant cabinet for outdoor use.
- ◆ Selectable battery (six C size for each speaker) or AC operation, adaptor included. Built-in recharging circuitry for ni-cad batteries.
- ◆ System includes: 900 MHz transmitter, wireless speaker pair, AC adaptors, and all cables necessary to hook up system.
- ◆ Limited availability. ◆ Net weight 9 lbs.
- ◆ Frequency response: 20-18KHz.



#EN-319-030 **\$169.95** EACH

Dayton Loudspeaker Co.




◆ 30 day money back guarantee ◆ \$20.00 minimum order
◆ We accept Mastercard, Visa, Discover, and company C.O.D. orders
◆ 24 hour shipping ◆ Shipping charge = UPS chart rate + \$1.90 (\$5.00 minimum charge) ◆ Hours 8:00 am - 8:00 pm ET, Monday - Friday ◆ 9:00 am - 5:00 pm Saturday. Mail order customers, please call for shipping estimate on orders exceeding 5 lbs. ◆ Foreign destination customers please send \$5.00 U.S. funds for catalog. ◆ Quantity pricing available.

1-800-338-0531

340 E. First St., Dayton, OH 45402-1257
Phone: 937-222-0173 ◆ Fax: 937-222-4644
E-Mail: sales@parts-express.com

7 SECOND IC REMOVER

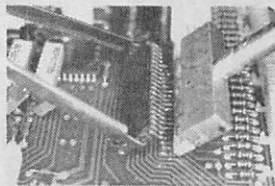Remove 100's of good IC's per hour
Won't damage IC's or circuit boards



8 Desoldering Tools
(Remove 6 thru 40 pin IC's) \$ 89.95
10 Desoldering Tools
(Remove 6 thru 64 pin IC's) \$114.95

FRANKS ELECTRONICS

P. O. BOX 357 — GLEN, MISS. 38846
Orders By Mail Only. No COD's.

THE SMART CHOICE

FOR OVER 48
YEARS THE SER-
VICEMAN'S
CHOICE FOR IN-
VOICES AND
SALES BOOKS
HAS BEEN



OELRICH PUBLICATIONS

- ⇒ QUALITY YOU CAN COUNT ON
- ⇒ PRICED AS LOW AS 4 CENTS EA.
- ⇒ COMPUTER FORMS AND CHECKS

FOR FREE CATALOG CALL

1-800-621-0105

2435 E. DEVON AVE. ELK GROVE VILLAGE, IL 60007

Make your own circuit boards at home!!

Don't project-board your electronics circuits, Afford-A-Board them!! Our complete line of circuit board manufacturing equipment lets you create professional single or double-sided circuit boards in your own home. We manufacture affordable, developing, etching and stripping tanks. Afford-A-Board is your source for 2-sided photo-sensitive copperclad board.

12x12 FR4 1 oz. DS \$15.99

Call for our low, low pricing on film, chemicals and drill bits.

Afford-A-Board

P.O. Box 32613
Kansas City, MO 64171
Tel: (913) 385-1843
Fax: (913) 895-9330
(888) 454-1017

Visa/AMEX/MC/Cash COD/MO

Printed Circuits in Minutes Direct From LaserPrint!


8 1/2" x 11"
* Or Photocopy
** Use standard
household iron
or P-n-P Press.

1. LaserPrint*
2. Press On**
3. Peel Off
4. Etch



Use Standard Copper Clad Board
20 Shts \$30/ 40 Shts \$50/ 100 Shts \$100
Visa/MC/PO/Ck/MO \$4 S&H
Techniks Inc.
P.O. Box 463
Ringoes NJ 08551
ph. 908.788.8249 fax 908.788.8837
http://chelsea.ios.com/~techniks
Retail Dealer Inquiries Invited

SC552ES CONTROLLER

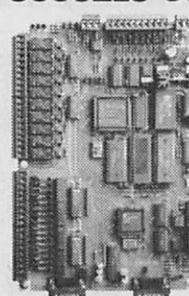

- 80C552 @ 22MHz
- Enhanced BASIC Language
- 6"x9" circuit board
- 10 5A relay outputs
- 3 LED or logic outputs
- 16 opto-isolated inputs
- 8 ch. 10 bit analog inputs
- 2 ch. 8 bit analog outputs
- Real Time clock/calendar
- 128K Static RAM
- 128K FLASH memory
- 256 byte serial EEPROM
- 3 serial ports (RS232/485)
- IIC bus expansion
- Plug-on I/O terminal blocks
- Single 12Vdc operation

APPLICATION READY ONLY




SYLVA
CONTROL SYSTEMS

519 Richard Street, Thunder Bay, Ontario, Canada P7A 1R2
Ph. 807-768-2487 fax 807-767-0587
www.sylvaccontrols.com info@sylvaccontrols.com

ADAPT-11 68HC11 Modules for Solderless Breadboards

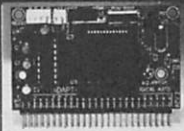- miniature 2.0" by 2.8" module
- plugs vertically into solderless breadboard for easy development
- BOOT/RUN switch for easy programming via PC serial port
- all I/O lines on dual row connector



Complete modular prototyping system!
Expansion accessories available!

For just US\$74.95, our Starter Package (AD1ISP) provides everything you need to get going fast! Now you can harness the power of the popular 68HC11 in your projects! Includes ADAPT-11 with 68HC11E2, providing 2K EEPROM (re-programmable), 8 channel 8-bit Analog-to-Digital Converter (ADC), hardware timers, counters, interrupts, Serial Peripheral Interface (SPI), Serial Communications Interface (SCI), and more! On-board RS-232 interface (cable included), 5-volt regulator, 8MHz crystal, reset circuit, and convenient program/run switch. Comes with non-commercial versions of 'HC11 Assembler, BASIC, & C, as well as handy utilities & example code. Includes Motorola 68HC11 Pocket Programming Reference Guide and manual with schematic. All you need is a PC to write & program your software, a DC power supply, and a solderless breadboard (or protoboard) to build your application circuits (or use our modular accessories).

Visa • MasterCard • American Express • Discover

TECHNOLOGICAL ARTS

309 Aragona Blvd., Suite 102, Box 418, Va. Beach, VA 23462
1644 Bayview Avenue, Box 1704, Toronto, ON M4G 3C2
voice/fax: (416) 963-8996 www.interlog.com/~techart

Slot Machines \$ 449.00

Free Shipping

Slot Machine Demo
Video \$ 5.99
40 - Minutes

33" High 20" Wide 14" Deep
Brochure \$ 1.00

Magic Box
Test Chips
Filter Kits


Buzz - Buzz
Notch Filters



Video Media www.nutnet.com
P.O. Box 93/6025
Margate, FL 33093
(954)-752-9202

FRIENDLY LITTLE MICRO CONTROLLER

\$149
(single)

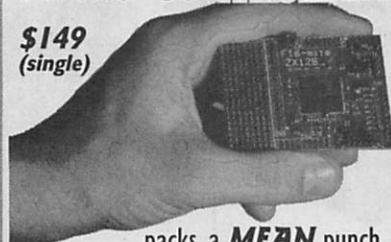

...packs a **MEAN** punch
a.k.a. "Steroid Stamp"

- 39 I/O + 8 A/D (10 bit) •
- 128K SRAM + 128K Flash •
- LCD/Keypad Interface •
- Fast 16 bit Motorola CPU •
- Affordable C Compiler •
- Comprehensive s/w Library •

* Intec Automation Inc. v: 250-721-5150
www.islandnet.com/~iil f: 250-721-4191

Timid about getting on the... World Wide Web?

You've heard about the *Information Superhighway* and all the hype that goes with it! Sort of makes you feel timid about getting on the Web. Put your fears aside! A new book, *The Internet and World Wide Web Explained*, eliminates all the mystery and presents clear, concise information to build your confidence. The jargon used is explained in simple English. Once the tech-talk is understood, and with an hour or two of Web time under your belt, your friends will believe you are an Internet guru!

To order Book #403 send \$6.95 plus \$3.00 for shipping in the U.S. and Canada only to Electronics Technology Today Inc., P.O. Box 240, Massapequa Park, NY 11762-0240. Payment in U.S. funds by U.S. bank check or International Money Order. Please allow 6-8 weeks for delivery.

Mark V Electronics, Inc.
8019 E. Slauson Ave.,
Montebello, CA 90640

Catalog 213/ 888-8988

Fax 213/ 888-6868

http://www.mark5co.com

Email: mark5co@aol.com

DIY Audio Electronic Kits
Lab Equipment kits
Audio Enclosures & more!

ORDER

1-800-521-MARK

1-800-423-FIVE

Kit skill levels

▲ Beginner
▲ Intermediate
▲ Advanced

- Fast Shipping
- Quality Kits low prices
- In business since 1985

SCHOOL PROJECT CORNER

po orders welcomed from schools

Melody Generator	▲	Kit \$ 13.85
6W Mini-Amplifier	▲	9.50
0-15V 5A Regulated DC PS	▲	17.50
36W Class A Power Amp.	▲▲	32.50
Dynamic Noise Reduction	▲	26.00
Multi-Function Control Switch	▲	10.50
20 Bar/Dot Level Display	▲▲	41.45
Microphone Mixer Mono Amp.	▲	20.79
Superior Electronic Roulette	▲	21.50
Digital Clock with Melody Alarm	▲	25.00
Stereo Pre-Amp with Mic Amp.	▲	10.78
Mini Stereo Multi-Input Amp.	▲	30.50
130-in-one Electronic Lab	▲	29.99

SEE OUR CATALOG FOR MORE KITS!

Clearance Sale

FM Wireless Microphone



Kit \$ 12.50 6.99

This is a low power real FM transmitter. Transmit frequency within 88-108 MHz. Transmit range about 200 ft. It has high sensitivity sound pickup by a capacitance microphone. May be used strictly for series purposes such as remote wireless monitoring.

20 Color LED Level Meter

Clearance Sale



Kit \$ 20.15 9.99

Use this dual LED display indicating meter with your stereo power amplifier to indicate instantaneous speaker power. Operating range is -30dB to +5dB and can be calibrated to operate with 1 to 200 W amplifiers. Not consume any amplifier power. A peak LED illuminates on overload!

Stereo Loudspeaker Protector

TY-25 ▲



Kit: \$ 16.75

Super fast acting relay protects speakers against destructive DC voltages. Can connect directly to a power amplifier or can use a separate power supply. Has a 3 second turn-on delay to avoid turn-on thumps.

Regulated DC Power Supply

TR-503 ▲



Kit: \$ 18.75

It is short circuit proof & has overload protection. Output voltage is variable over a range of 0-50 volts. Current limit trip is adjustable up to max of 3A. May use Mark V #002 transformer.


120-250W Mosfet Power Mono Amplifier AF-2 (6 lbs.) ▲▲



Kit: \$ 89.80 80.82 Asmb. \$ 114.80

Power Output: 250W into 4 ohms RMS(42VX2 6A transformer is used). 120W into 4 ohms RMS(33VX2 4A transformer is used). Frequency Response: 3Hz-22,000Hz. THD: <0.03%. Signal to Noise Ratio: 91dB. Sensitivity: 1V RMS at 47k. Load Impedance: 4 or 8 ohms. Power Requirement: ±46VDC 4A or ±60VDC 6A. May use Mark V Model 012 Transformer. Suggested Capacitor 8,200uf 100V Model 020. Suggested Metal Cabinet LG-1925.

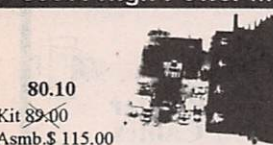300W High Power Mono Amplifier TA-3600 (5 lbs.) ▲▲▲



80.10

Kit \$ 89.00

Asmb. \$ 115.00

Power Output: 300W into 8 ohms RMS. 540W music power into 8 ohms. Frequency Response: 10Hz-20KHz. THD: < 0.05%. Sensitivity: 1V RMS at 47K. Power Requirement: 60 to 75 VDC at 8A. May use Mark V Model 007 or 009 Transformer. Suggested Capacitor: 8,200uf 100V Model 020 Capacitor. Suggested Metal Cabinet LG-1925.

120W + 120W Pre & Main Stereo Amplifier TA-800MK2 (4 lbs.) ▲▲



Kit: \$ 67.92 Asmb. \$ 86.95

Power Output: 120W into 4 ohms RMS. 72W into 8 ohms RMS. Frequency Response: 10 - 20 KHz. THD: < 0.01%. Tone Control: Bass ±12dB, Mid ±8dB, Treble ±8dB. Sensitivity: Phono Input, 3mV into 47K. Line, 0.3V into 47K. Signal to Noise Ratio: 86dB. Power Requirement: 40V DC @ 6A. May use Mark V Model 001 or 008 Transformer. Suggested Metal Cabinet Model LG-1924.

80W + 80W Pure DC Stereo Main Power Amplifier TA-802 (4 lbs.) ▲▲




Kit: \$ 49.94

Asmb. \$ 69.94

Power Output: 80W per channel into 8 ohms. THD: < 0.05%. Frequency Response: DC to 200 KHz. -0 dB, -3dB @ 1W. Power Requirement: 30V AC X 2 @ 6A. May use Mark V Model 001 or 008 Transformer. Suggested Capacitor 8,200uf 50V Model 017. Suggested Metal Cabinet LG-1924

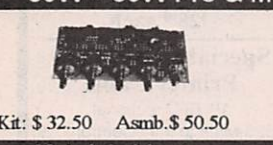30W + 30W Pre & Main Stereo Amplifier TA-323A (1 lb.) ▲



Kit: \$ 32.50 Asmb. \$ 50.50

Power Output: 30W into 8 ohms RMS per channel. THD: < 0.1% from 100 Hz to 10 KHz. Sensitivity: Phono 3mV @ 47K. Tuner, Tape 130mV @ 47K. Signal to Noise ratio: 80dB. Power Requirement: 22 to 36V AC, 3A. May use Mark V Model 002 Transformer. Suggested Cabinet LG-1684.

Metal Cabinets

Aluminum Front Panel

LG-1273	3x12x7"	(4 lbs.)	\$ 26.50
LG-1684	4x16x8"	(7 lbs.)	32.50
LG-1924	4x19x11½"	(10 lbs.)	38.25
LG-1925	5x19x11½"	(10 lbs.)	42.00
LG-1983	2½x19x8"	(7 lbs.)	35.25

Transformers (5-12 lbs.)

**Toroidal Transformers

# 001	28V/30V x2	6A	\$ 30.00
# 002	36V x2	3A	25.00
# 003	40V x2	6A	32.00
# 008**	28V/30V x2	6A	42.00
# 009**	48/53V x2	8A	68.00
# 012**	33/40/42V x2	6A	52.00

Minimum order: \$ 20.00. We accept Visa, MasterCard, Money Orders, and Checks(allow 2 weeks for clearance). We ship by UPS ground inside US (min \$6.00) and ship by US mail outside US. Please call our operator for orders over 2 lbs. or foreign orders.

Fluorescent Light Driver

TY-2 ▲ (1 lb.)



Kit: \$ 14.75

This unit drives 6-40 watts fluorescent light for portable and emergency use. Works from a 7.2 - 16 VDC battery. Includes a "Hi-Efficiency Switching Mode IC Driving Circuit" suitable for use with different lights.

30-in-one Electronic Lab Kit ▲

KA-901 \$ 15.99


12.99



No soldering is required! This simple electronics kit safely teaches the fundamentals of electronics. Build a radio, alarm, timer and more. Earphone for private listening. Uses safe battery power. Requires 4 "AA" batteries!

150MHz 8 Digit Frequency Counter


SM-100 (2 lbs.)

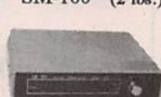

It is used for adjustment, test & repair of any kind of high frequency circuit products. It can give up to 8 digit of resolution for a wide frequency range 10Hz - 150 MHz. The last input frequency can HOLD on the display for future reference & comparison. The circuit structure is compact & reliable for the most updated A/D LSI circuitry. The input impedance is 1M ohm.

60+60W Stereo Power Amp. ▲

SM-302 (11 lbs.)

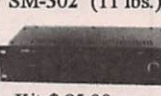

It provides 3 input jack pairs. One pair accept a high impedance microphone. The two remaining pairs are for high & low level input sources. Power Output: 60W per channel into 4 ohms RMS. 20Hz-20KHz. THD:<0.1%. Input Sensitivity: Mic /Guitar 10mV, Hi 380mV, Lo 640mV. Ready to plug in when assembled.

300-in-one Electronic Lab Kit ▲

Learn about transistors, capacitors & electronic circuits. Build electronic games, battery checker & more. It even includes a breadboard for adding your own components. Complete with easy-to-follow manual. Requires 6 "AA" batteries. (6 lbs.)

Best Buy



\$ 59.99 49.99

FEATURING

... TOOLS

Soldering

- 115 VAC 40 watt soldering iron
#TM-306 \$6⁵⁰ ea.
 Tube 60/40 electronic solder
#TM-304 \$1⁰⁰ ea.
 Soldering iron stand w/ sponge
#TM-305 \$4⁰⁰ ea.
 Portable "Helping Hands"
#TM-HLP \$5⁰⁰ ea.
 Desoldering pump-teflon tip
#TM-300 \$4⁰⁰ ea.
 Desoldering wick- Solder remover
#TM-302 \$1⁰⁰ ea.

More Tools...

- 6 pc. Mini-combo screwdriver kit
#TM-315 \$2⁰⁰ ea.

Telephone/Network Tools

- RJ11 Crimp tool w/ stripper & cutter
#TM-CR6 \$14⁰⁰ ea.
 RJ45 Crimp tool w/ stripper & cutter
#TM-CR8 \$14⁰⁰ ea.
 RJ11/RJ45 Combo tool w/ stripper
#TM-CR2 \$28⁰⁰ ea.
 Modular Handset crimp tool w/ stripper
#TM-CRH \$12⁰⁰ ea.
 Modular Offset crimp tool 6 conductor
#TM-CR-DEC \$18⁰⁰ ea.
 Impact punch tool w/ blade
 66 or 110 blade available
#TE-PUN-TOOL \$39⁰⁰ ea.

- D-sub Insert/Extract tool
#TM-303 \$2⁰⁰ ea.
 12 pc. Computer toolkit
#TM-TK1 \$10⁰⁰ ea.

Crimp It!

- IDC Connector crimping tool
#TM-IDC \$12⁵⁰ ea.
 RG 58 Teflon & PVC BNC
 Ratchet type crimper
#TM-293 \$30⁰⁰ ea.
 RG 58/59 BNC Ratchet type crimper
#TM-292 \$18⁰⁰ ea.
 Heavy Duty RG6 & RG59 crimper
#TM-392 \$16⁰⁰ ea.
 Coax strip tool for RG 58/59/6
#TM-192 \$12⁰⁰ ea.
 Pin crimper-non-insulated connectors
#TM-NIC \$8⁰⁰ ea.

Testing

- Analog volt-ohm multimeter
#TM-325 \$6⁰⁰ ea.
 Digital 3.5" multimeter
#TM-330 \$17⁰⁰ ea.

Roger's Systems Specialist

Order On-Line!

800-366-0579

Call for a
FREE catalog!

"We Have Great Connections"
 Computer - Communications
 Network - Audio - Video
www.rogerssystems.com

Specials!

Microphone

Stick-on monitor or clip on or
 stick on shirt 6 ft. cord;
 condenser mic.



#TM-MIC-2
\$2⁰⁰ each

CD Jewel Case

Replacement for original



#TM-CD1
\$1.40 each

Parallel Port

DB25 Female to 26 pin socket




#CN-702 \$5.50 each
 100/\$4.00

SVGA Shielded Cables

6 ft. HD 15 male to female

#CC-VGA-4
\$3⁰⁰ each

SCSI

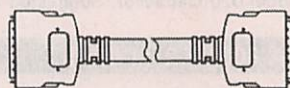

CABLES

SCSI 1 TO SCSI 1 CABLE
 50 pin Centronics
 male to male
 6 ft.

#CC-676
\$7⁰⁰ each

SCSI 2 TO SCSI 1 CABLE
 HD50 to Centronics 50
 male to male
 6 ft.

#CC-686
\$19⁰⁰ each

SCSI 3 TO SCSI 1 CABLE
 HD68 to 50 pin centronics
 male to male
 6 ft. w/ thumbscrews

#CC-687-6TS
\$37⁰⁰ each

SCSI 3 TO SCSI 3 CABLE
 HD68 to HD68
 male to male
 6 ft. w/ thumbscrews

#CC-693-6TS
\$39⁰⁰ each

SCSI 2 TO SCSI 2 CABLE
 HD50 to HD50
 male to male
 6 ft.

#CC-678-6
\$36⁰⁰ each

SCSI 2 TO SCSI 3 CABLE
 HD50 to HD68
 male to male
 6 ft. w/ thumb screws

#CC-692-6TS
\$36⁰⁰ each

DB25 TO SCSI 1 CABLE
 DB25 to 50 Centronics
 male to male
 6 ft.

#CC-670
\$4⁰⁰ each


DB25 TO SCSI 2 CABLE
 DB25 to HD50
 male to male
 6 ft.

#CC-671-6
\$20⁰⁰ each

DB25 TO SCSI 3 CABLE
 DB25 to HD68
 male to male
 6 ft.

#CC-697-6TS
\$39⁰⁰ each

All cables available in 3 ft. lengths!

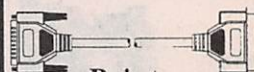

Printer Cables

DB25 to 36 Centronics
 male to male
#CC-PR6 6ft. \$3⁰⁰ ea.
#CC-PR1 10ft. \$4⁰⁰ ea.

IEEE-1284 Compliant
 printer cables

DB25 to 36 Centronics
 male to male
#CC-PR6-1284 6ft.
\$8⁰⁰ each

#CC-PR1-1284 10ft.
\$10⁰⁰ each

#CC-P15-1284 15ft.
\$15⁰⁰ each

#CC-PR2-1284 25ft.
\$28⁰⁰ each

Special IEEE 1284 Printer Cable

10' Bi-Directional
 DB25 Male to Mini Centronic 36
 A.K.A. type "A" - "C"
#CC-PR6-BIMIN
\$8.99 each

Local 805-295-5577

Remember, We Have Great Connections...For You!

FAX 805-295-8777

\$10.00 minimum order required • Add \$4.50 shipping for pre-paid orders
 California residents add 8.25% tax • eMail Sales@RogersSystems.com

Call for quantity discounts • No out of state checks accepted • Most orders shipped same day

24895 Avenue Rockefeller, Valencia, CA 91355



3 Axis Motion Control System

Complete, ready to run

\$ 255.50 + 12.00 S/H

Build or adapt CNC mills, CNC routers, Robots, Etc. Includes: 3 Stepping motors (70 oz/in 200 steps/rev). External board (connects to parallel port of a PC). Power supply. Cables, Manual and the MAXNC drive software, with linear, circular and helical interpolation, acceleration deceleration, full contouring, 'G' code programming, screen plot, code generation from CAD (CAM), and more.

For more information, phone or write to:

MAXNC


6730 West Chicago

• Suites 2 & 3

Chandler, AZ 85226

Ph (602) 940-9414

Fax (602) 940-2384

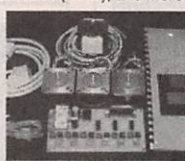

SURVEILLANCE HIDDEN CAMERAS DIRECT FROM MANUFACTURER—BEST PRICE IN THE MARKET



Ultra miniature hidden camera, in dome, smoke or motion detector. 1/3" B/W or Color. Wide view angle. Low light sensitivity + super sharp images, plus video and audio output. From \$159.00. Also 1/3" B/W board cameras w/mic, only \$99.00 USD. Wireless hidden camera, start at only \$249.00 USD. Plus \$5.95 for S/H. Wholesale/Retail Welcome. C.O.D., Check, Money Order or Visa/MC.

BOLIDE INTERNATIONAL CORPORATION

PH: (800) 355-0895 or (818) 575-8178

9660 Flair Drive #318, El Monte, CA 91731

http://www.bolideintl.com/products.html

!!!BROADCAST FARTHER!!!

The model 220 is an 80-110 MHz RF amplifier that connects to mono or stereo FM transmitters and produces a powerful 2-15 watt signal which could broadcast up to 5 miles or more! Requires 50-150 mW drive.

Step by step plans complete with part source information and antenna designs... **ONLY \$14 PLUS \$2 S&H** NO C.O.D.'s

Progressive Concepts
BOX 586 STREAMWOOD, IL 60107
(630) 736-9822 FAX: (630) 736-0353



Do You Repair Electronics?

Repair Databases for
TV, VCR, Monitor, UL
Audio, FCC, and more.

• Over 76,000 records
• Private user forums
• Live on-line chat rooms

RepairWorld.com

Electronic Corp 1 Herald Sq. Fairborn, OH 45324 (937) 878-9878



Quality Microwave TV Systems
WIRELESS CABLE - ITFS - MMDS
ATV - INTERNATIONAL - S-BAND
Amplifiers • Antennas • Books • Components
Filters • Systems • Video Products
• RF Frequency 1990 - 2700 MHz
• Cable Ready - VHF - UHF Outputs
• SASE For "FREE" Catalog or Send \$1

PHILLIPS-TECH ELECTRONICS

PO Box 8533 • Scottsdale, AZ 85252

ORDER LINE 800-880-MMDS

CATALOG/INFO 602-947-7700

FAX LINE 602-947-7799

Visa • MC • Amx • Disc • C.O.D.'s • Qty Pricing

VIDEO INVERTER Create & Restore Inverted Video

R.C. Distributing

PO Box 552 • South Bend, IN 46624
Website: www.south-bend.net/rcd



For Free Information Package
on Completed Units and Pricing
Call 219-236-5776

Interactive catalog: www.tekview.com

**TV
cable
CONVERTERS
&
EQUIPMENT**



- * 30 days money back guarantee
- * 1 yr warranty
- * Quantity Discounts
- * Dealers Welcome!

VISA MC AMEX C.O.D.

TekView Electronics

(800) 739-2253

NEW DX SERIES DMMs

3 YEAR WARRANTY

DELUXE HOLSTER INCLUDED



Bel MERIT DX Series DMMs have best values for performance, features and dependability with 3 year warranty.

DX460L, full function in a single meter

- Wide LCR Range
Inductance, up to 20H
Capacitance, up to 2000µF
Resistance, up to 20MΩ
- Logic, TTL & CMOS
- Auto Frequency, Up to 20MHz
- Diode Test, Continuity Beeper
- Data Hold, Peak Hold
- Input Warning Beeper
- Auto Power Off

Lots More Test Instruments

Oscilloscope, DC Power Supply, Function Generator, Audio Oscillator, Frequency & Universal Counter, Multimeter, Capacitance Meter, Clamp-On, Electrical Tester and More.

MODEL	DX350	DX355	DX360T	DX400	DX405	DX421	DX451	DX460L
Auto Ranging/Bargraph								
True RMS								
AC/DC Voltage (750V/1000V)								
AC/DC Current (10A)	20µA							
Resistance (20MΩ)	20Ω	20Ω	2000M			30M	2000M	
Continuity Beeper/Diode								
Temperature w/Probe, Type K								
TRHFE								
Capacitance (20µF)								2000µ
Frequency (20MHz)								
Logic (TTL & CMOS)								
Inductance (20H)								
Auto Power-Off								
Input Warning Beeper								
Data Hold								
Peak Hold								
Protective Holster								
PRICE	49.95	74.95	64.95	64.95	69.95	74.95	84.95	99.95

• See your local distributors or Call for Catalog

Bel MERIT
SOLUTIONS FOR THE TEST INSTRUMENT

1-800-532-3221

(714) 586-2310 • FAX (714) 586-3399

P.O. Box 744, Lake Forest, CA 92630

A WHOLE NEW WORLD IN SCIENCE KITS.



OWI's "Next Generation" of affordable, rugged Robot Kits challenge the enthusiast to solder circuit boards and/or mechanically assemble.

Visit our homepage
@ <http://www.owirobot.com>

Each OWIKIT also incorporates the basic principles of robotic experiments, sensing and locomotion, guaranteeing an exciting, hands-on adventure of knowledge and fun!

But remember! OWI is the recognized founder and leader in Educational Robot Kits. **ACCEPT NO IMITATIONS.**



EK
ELEKIT

ROBOTIC ARM TRAINER	OWI-007	5 Axis Control	Avail. Aug. '98	69.95
TRIPLE ACTION SOLAR CAR	OWI-685	Solar Sensor	28 pg. Book	39.95
S-CARGO	OWI-936K	Sound Sensor	47 Pg. Book	36.95
WAO II	OWI-961K	Programmable - Graphic	59 Pg. Book	69.95
SPIDER	OWI-962K	Infrared Sensor	49 Pg. Book	49.95
LINE TRACKER	OWI-963K	Infrared Sensor	48 Pg. Book	49.95
HYPER PEPPY	OWI-969K	Sound / Touch Sensor	46 Pg. Book	24.95
MOON WALKER	OWI-989K	Solar Sensor	10 Pg. Book	34.95

1160 Mahalo Place, Suite B
Rancho Dominguez, CA 90220-5443
(310) 638-7970
Fax: (310) 638-8347



Order M - F: 8 a.m. - 4 p.m. PST

CIRCLE 318 ON FREE INFORMATION CARD



To learn more about life-saving techniques,
call your Red Cross.



American
Red Cross

EZ-EP DEVICE PROGRAMMER - \$169.95

Check Web!! -- www.m2l.com

Fast - Programs 27C010 in 23 seconds

Portable - Connects to PC Parallel Port

Versatile - Programs 2716-080 plus EE and Flash (28F,29C) to 32 pins

Inexpensive - Best for less than \$200

- Correct implementation of manufacturer algorithms for fast, reliable programming.
- Easy to use menu based software has binary editor, read, verify, copy, etc. Free updates via bbs or web page.
- Full over current detection on all device power supplies protects against bad chips and reverse insertion.
- Broad support for additional devices using adapters listed below.


Available Adapters

EP-PIC (16C5x,61,62x,71,84)	\$49.95
EP-PIC64 (62-5,72-4)	\$39.95
EP-PIC12 (12C50x)	\$39.95
EP-PIC17 (17C4x)	\$49.95
EP-51 (8751,C51)	\$39.95
EP-11E (68HC11 E/A)	\$59.95
EP-11D (68HC711D3)	\$39.95
EP-16 (16bit 40pin EPROMs)	\$49.95
EP-28 (286E02,3,4,6,7,8)	\$39.95
EP-SEE2 (93x,24x,25x,85x)	\$39.95
EP-750 (87C750,1,2)	\$59.95
EP-PEEL (ICT22V10,18v8)	\$59.95
EP-1051 (89C1051,2051)	\$39.95
EP-PLCC (PLCC EPROMs)	\$49.95
EP-SOIC (SOIC EPROMs)	\$49.95

Many Other Adapters Available

M²L Electronics
310/837-7818 Fax/BBS: 310/841-6050
3526 Jasmine #4; Los Angeles, CA 90034
CA orders add 8.25% sales tax.
<http://www.m2l.com>

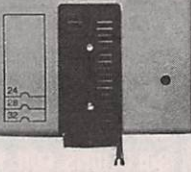EZ-EP
M²L ELECTRONICS
Los Angeles, California



MEMBRANE SWITCH KITS!

FLAT PANEL KEYPADS
ASSEMBLE IN
MINUTES WITH YOUR
LEGEND

AVAILABLE IN 4, 12,
16, 24 & 40 KEY TYPES



DSK-4
\$9.89

DSK-12
\$14.29

INDUSTRIAL TYPES AVAILABLE

MORE THAN 30 LAYOUTS
TO FIT MOST
APPLICATIONS

CALL FOR FREE
BROCHURE

SIL-WALKER

880 CALLE PLANO,
UNIT N
CAMARILLO, CA
93012

PHONE: (805) 389-8100

FAX: (805) 484-3311

VISA / MASTERCARD

NAVY

YOU AND THE NAVY.
FULL SPEED AHEAD.

1-800-USA-NAVY

Cable TV Converters

Save **\$100** Dealers
Welcome

30 Day Money Back

Call Us Last!

We will beat any advertised price

2 Pc. Combo \$95.⁰⁰


Minimum 10 Lot

1-800-842-9670

T.C.V.

KENWOOD

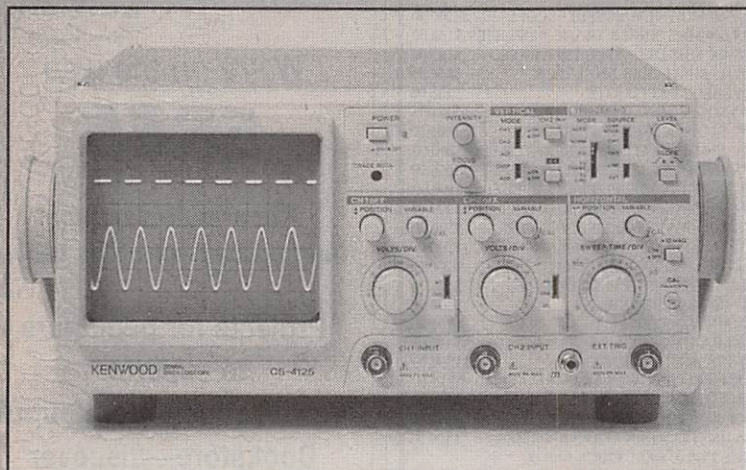*...from the company you've
been listening to for years...*




2-Channel, 20-MHz

CS-4125

Regular \$595

Sale \$389

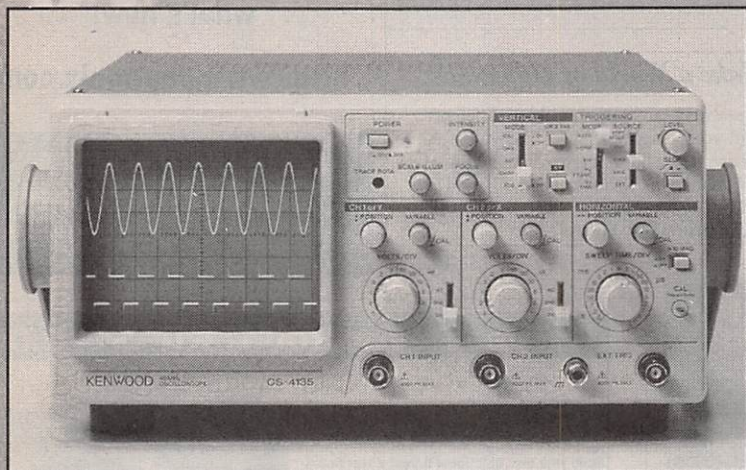

2-Channel, 40-MHz Oscilloscope

CS-4135

Regular \$855

Sale \$685

***Hybrid IC Technology is the Key to the High
Quality and High Reliability at Low Cost!***

- **FIX SYNCHRONIZATION** detects the trigger level automatically for the acquisition of stationary waveforms without complicated sync level adjustments.
- **VERT MODE TRIGGERING** enables the acquisition of stationary waveforms for both CH1 and CH2 even when the input signals to the two channels have different frequencies.
- **HIGH WITHSTAND INPUT** voltage of 400V (800Vp-p).
- **RELAY ATTENUATORS** are provided for reliable logic switchover.
- **SCALE ILLUMINATION** (CS-4135 only)
- **DIMENSIONS** (WxHxD): 300(343) x 140(150) x 415(430)mm () including protrusion.
WEIGHT: approx. 7.2kg (CS-4135) approx. 7kg (CS-4125)



PRINTTM
Products International

Call for your free 84 page test instrument catalog today!!!

8931 Brookville Road * Silver Spring, Maryland * 20910

*** Phone 800-638-2020 * Fax 800-545-0058 * email SMPRODINTL@AOL.com**

ABC ELECTRONICS 315 7TH AVE N. MPLS. MN. 55401
(612)332-2378 FAX (612)332-8481 E-MAILSURP1@VISI.COM
WE BUY TEST EQUIPMENT AND COMPONENTS.
VISIT US ON THE WEB AT WWW.ABCTEST.COM

TEK 7B15 1 GHZ DELAYING TIME BASE	\$250.00	TEK 2245 100 MHZ 4 CHANNEL O-SCOPE	\$1200.00
TEK 2465A 350 MHZ 4 CHANNEL O-SCOPE	\$3200.00	TEK 7A19 600 MHZ SINGLE TRACE AMPLIFIER	\$150.00
TEK 7A26 200 MHZ DUAL TRACE AMPLIFIER	\$75.00	TEK 7B85 400 MHZ DELAYING TIME BASE	\$125.00
TEK 7904 500 MHZ MAIN FRAME	\$250.00	HP 1630D 25 MHZ LOGIC ANALYZER	\$250.00
TEK 577/177 CURVE TRACER	\$1500.00	TEK 7S11 SAMPLING PLUG IN	\$200.00
TEK 7S12 GENERAL PURPOSE SAMPLER	\$350.00	FLUKE 95 SCOPE METER NO PROBES	\$600.00
TEK 453 50MHZ OSCILLOSCOPE	\$200.00	FLUKE 97 SCOPE METER WITH PROBES	\$1000.00
DRANETZ 626 DISTURBANCE ANALYZER	\$1500.00	HP 8182A 50 MHZ PATTERN GENERATOR	\$800.00
GENRAD 1657 RLC BRIDGE	\$750.00	PHILLIPS PM3296 400 MHZ OSCILLOSCOPE	\$1000.00
TEK 7D20 PROGRAMMABLE DIGITIZER	\$500.00	EMI SCR 7.5-300 7.5V 300A POWER SUPPLY	\$500.00
TEK 465 100 MHZ OSCILLOSCOPE	\$400.00	HP 8558B SPECTRUM ANALYZER	\$1500.00
TEK 465B 100 MHZ OSCILLOSCOPE	\$450.00	WAVE TEK 175 WAVE FORM GENERATOR	\$500.00
TEK 2335 100 MHZ OSCILLOSCOPE	\$1200.00	WAVETEK 157 PROG. WAVE FORM SYNTH.	\$500.00
TEK 2215 60 MHZ OSCILLOSCOPE	\$350.00	RACAL DANA 1901 100 MHZ COUNTER	\$200.00
TEK 496P 1KHZ-1.8GHZ SPECTRUM ANALYZER	\$5000.00	VALHALLA 2790B SYSTEM INTERFACE	\$150.00
BRADLEY 132 SCOPE CALIBRATOR	\$700.00	GENRAD 1683 RLC BRIDGE	\$300.00
PHILLIPS PM3350A 60 MHZ DIG. STORAGE SCOPE	\$1000.00	HP 3455A MULTIMETER	\$300.00
HP 8601A 110 MHZ SWEEP/SIGNAL GENERATOR	\$400.00	HP 3456A MULTIMETER	\$450.00
TEK FG504 40 MHZ FUNCTION GENERATOR	\$500.00	FLUKE 5200A AC CALIBRATOR	\$1500.00
HP 54100A 1GHZ DIGITIZING OSCILLOSCOPE	\$3000.00	TEK TM504 4 SLOT POWER FRAME	\$125.00
HP 8170A LOGIC PATTERN GENERATOR	\$150.00	HP 4955A PROTOCOL ANALYZER	\$500.00
SYSTRON DONNER DPSD 50	\$500.00	MAGTROL 4614 POLYPHASE POWER ANLZR.	\$300.00
LEADER LSG215A 125 MHZ SIGNAL GENERATOR	\$700.00	TEK CT-5 HIGH CURRENT TRANSFORMER	\$500.00
SPECIAL THIS AD ONLY TEK 475 200 MHZ OSCILLOSCOPE REGULAR PRICE \$500.00 SALE PRICE \$400.00			
SPECIAL THIS AD ONLY TEK DAS 9100 AS IS NO PROBES THESE UNITS ARE UNTESTED NOT REJECTS \$150.00			

CABLE TV CONVERTERS

Equipment & Accessories


Wholesalers Welcome

Call C&D ELECTRONICS

1-888-615-5757 M-F 10a-6p

Trees Make a World of Difference™

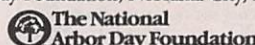Find out how trees can make a world of difference for you, and your neighborhood. For your free brochure write: Trees For America, The National Arbor Day Foundation, Nebraska City, NE 68410.



POPTRONIX®

Online Edition

We're on the web

FREE

We are starting up,
but you can watch us grow!

Projects for beginners
to experts!
New Product information!
Bookstore—discover
what's new!

<http://www.popttronix.com>

WE'RE WITH YOU EVERY DAY
24 HOURS A DAY! DROP IN!
WE'D LOVE TO HAVE YOU VISIT!

Radiotelephone - Radiotelegraph

FCC

Commercial License

Why Take Chances?

Discover how easy it is to pass the exams. Study with the most current materials available. Our Homestudy Guides, Audio, Video or PC "Q&A" disks make it so fast, easy and inexpensive. No college or experience needed. The new commercial FCC exams have been revised, covering updated Aviation, Marine, Radar, Microwave, New Rules & Regs, Digital Circuitry & more. We feature the Popular "Complete Electronic Career Guide". 1000's of satisfied customers. **Guarantee** to pass or money back. Newest Q&A pools.

Send for **FREE DETAILS** or call

1-800-800-7555

WPT Publications
4701 N.E. 47th St.
Vancouver, WA 98661

Name _____

Address _____

City _____ St. _____ Zip _____

1-800-800-7555

Carpet Rover Robot Kit \$115.00



Build your own functional Carpet Rover Robot

The kit comes complete with all hardware, structural components, 2 Hitec servos, Counterfeit Basic Stamp kit, software and an illustrated assembly manual. This robot is an excellent foundation for many experiments such as: obstacle avoidance, maze navigation, computer art and line tracking. Large 3" wheels handle rough terrain. It is a lot of fun to build and even more fun to operate. Check out our web site for more information and other robot kits.

• Line Tracker Option \$20.00 • Infrared Proximity Det \$30.00 • Mobile Robots Book \$48.00

Quantity discounts available. \$7.50 Shipping & Handling for USA, call for international and quantity shipping charges. IL residents add 6.25% sales tax to total.

Many more robot kits, ask for our free catalog!

Technical Service & Solutions
104 Partridge Road
Pekin, IL 61554-1403 USA



Tel: 309-382-1816
Fax: 309-382-1254
www.lynxmotion.com
jfrye@lynxmotion.com



Digital Entertainment GREAT VALUES ON:

USSB dish

SAVE Compare to Cable
30%-50%

MORE ENTERTAINMENT OPTIONS
ALL THE HOT ACCESSORIES
PAY LESS

Fax: 218-739-4879 1010 Frontier Dr.
Int'l: 218-739-5231 Fergus Falls, MN 56537

Call Now 800-543-3025 **Skyvision**
www.skyvision.com

Buy recycled.



It would mean
the world to them.

Recycling keeps working to protect
their future when you buy products
made from recycled materials. For
a free brochure, write Buy Recycled,
Environmental Defense Fund, 287
Park Avenue South, New York, NY
10010, or call 1-800-CALL-EDF.

8EPA 100% FSC

The Only 100% Legal, FCC approved,
DESCRAMBLER you can buy!

NAVIGATOR II

The only legal way to own your converter!

- 250 Channel Capacity
- Subscribe to two different cable systems simultaneously
- Interactive On-Screen Display
- Watch one premium channel while recording another
- Electronic program guide shows all programming over next 7 days
- One Touch Recording



NO RENTAL FEES!
Advanced Features!

**Most advanced
set-top you
can buy!**

FCC & UL Approved

**Save
Money!**

DYNAMIC Technologies • Phone: (800)-624-4258

Suite 541064 • Boystown, NE 68154

CIRCLE 312 ON FREE INFORMATION CARD



SEE WHAT TAKES SHAPE. EXERCISE.

American Heart Association

© 1992, American Heart Association

Find Bad Capacitors

In-Circuit with the Capacitor Wizard



The Capacitor Wizard is an extremely FAST and RELIABLE device designed to measure ESR (Equivalent Series Resistance) on capacitors of 1uf and larger "IN CIRCUIT", eliminating the need to remove the capacitor for accurate tests. The Capacitor Wizard finds BAD caps IN CIRCUIT that even VERY EXPENSIVE cap checkers MISS ENTIRELY, even out of the circuit!! Standard capacitor meters cannot detect any change in ESR therefore they miss bad capacitors leading to time consuming "Tough Dog" repairs. *Technicians say it is the most cost effective instrument on their workbench.*



Made in the USA

Order Today

Only \$179.95
Call 1-800-394-1984

<http://www.heinc.com>

Int. # 316-744-1993

Fax 316-744-1994

6222 N. Oliver, Kechi, KS 67067

30 day money back guarantee



CLASSIFIED

Misc. Electronics For Sale

Call for a free electronics catalog or visit our web site at www.bgmicro.com/. B.G. Micro, PO Box 280298, Dallas, TX 75228. Order line 800-276-2206

Piece parts for Delco OEM Radios Low Pricing. Factory Original. No Subs. Call today, 1-800-433-9657

Plans-Kits-Schematics

FREE CATALOG 100 Leading-Edge kits. K1, PIC. Full instructions, source code. 800-875-3214. **Science First**, 95 Botsford Place, Buffalo, NY 14216.

"I'M MAKING A BUNDLE" Reclaiming Scrap Gold From Junk Computers. Free info: 24hrs., 603-645-4767.

Electronic Project Kits. www.qkits.com 1-888-GO-4-KITS. 292 Queen St. Kingston, ON., K7K 1B8

Pocket Testbench kit. Digital analyzer, oscilloscope, counter, generator modes. RS232 interface. Handheld, inexpensive. **Oricom Technologies**, (303) 444-9776, www.sni.net/~oricom.

TUBES: "oldest", "latest". Parts and schematics. SASE for lists. **Steinmetz Electronics** 7519 Maplewood Ave., Hammond, Indiana 46324

Cable TV

Cable Descramblers and Converters 10 Lot Decoders \$38.00 ea. 10 Lot Converters \$57.00 ea. Visa and Mastercard Accepted. (304) 337-8027.

New! Jerrold and Pioneer wireless test units \$125 each, also 75DB notch filters \$19.95 each, quantity pricing available please call **KEN ERNY ELECTRONICS** 24 hour order and information hot line 516-389-3536.

Wholesale Cable Warehouse Decoders for all systems **Best Prices Guaranteed.** Helpful, friendly service and support ready to help. 30 day money back guarantee and full 1 year warranty call now 1-800-387-0349 **Dealers Welcome Call for free price quote.**

Cable Descramblers and converters. Shop no more, best prices and tech support. **Extreme Electronics** 1-888-609-4910.

CABLE TV EQUIPMENT & ACCESSORIES. Wholesalers Welcome! 30 Day Moneyback Guarantee! Free Catalog! **PROFORMANCE ELECTRONICS, INC.** 1-800-815-1512.

DESCRAMBLE CABLE WITH SIMPLE CIRCUIT ADDED TO RADIO SHACK RF MODULATOR AND USING VCR AS TUNER INSTRUCTIONS \$10.00. **TELECOM BOX 832-E3 BRUSHLY, LA. 70719**

Signal Eliminator can block severe TV interference or unwanted channels! Order by channel number - 0 thru 36 available. Only \$30 each plus \$4 S/H. Quantity discounts. Money back guarantee. Prepay, Visa or Mastercard. COD \$5 additional. Visit us on the web today at <http://starcircuits.com/tvfilter>. Star Circuits, PO Box 94917, Las Vegas, NV 89193. 1-800-433-6319.

CABLE test modules/cubes. Pioneers, S/A, Tooms, Jerrolds. Quantity discounts, Call DCR: Tel: (718) 624-8334 Fax: (718) 246-9731 No NY calls.

Free Cable Descrambler Plans. For Details Write: Sierra Publishing, 909 E. Yorba Linda Blvd., Suite H-181, Dept. ENP, Placentia, CA 92670

Cable TV Descramblers. One Piece Units. Pioneer, 6310s, Scientific Atlanta 8580's; DPV 7's and others. Lowest Prices. Money Back Guarantee. **Precision Electronics Houston, TX** 1-888-691-4610

CABLE DESCRAMBLING, New secret manual. Build your own Descramblers for Cable and Subscription TV. Instructions, schematics for SSAVI, Gated Sync, Sinewave, \$12.95, \$2 postage. **CABLETRONICS**, Box 30502R, Bethesda, MD 20824.

NEW! Cellphone E.S.N. readers \$250 each, cell phone programmers \$175 each, cell phones \$25 each, DSS satellite dish card readers and programmers \$125 each, credit card readers \$250 each, Cable T.V. notch filters 50 cents each, converter boxes \$50 each, magnetic strip card readers for ATM machines, bank cards, drivers license, and all types of data acquisitions all under \$200 each. You pay these super low prices when you deal directly with the manufacturers. When you order "Direct Connection" a 150 page directory published by Ed Treki Publications, you will receive the largest collection of names, addresses, and phone numbers of all the leading American and International manufacturers of these products never before available. Stop paying second, third and fourth hand prices and deal directly with the source!!! Order your copy of "Direct Connection" today for only \$99.95 plus \$5 shipping. All orders are sent C.O.D. Please call Ed Treki Publications 24 hour order hot line 914-544-2829.

CABLE TV major brands including Zenith St. 1600 \$249.00. New Zenith add-on \$99.00 Jerrold Model CFT2014 \$299.00 add-on TVT \$70.00 Wholesale Welcome 1-800-822-8530

CABLE BOXES-ALL MODELS-ALL CHANNELS. Jerrold Impulse DP, DPV & DPBB's, Pioneer or Scientific Atlanta-Lowest Prices in U.S. \$175.00 including remote, batteries and cable. Call for 10 lot pricing. Toll Free 888-689-0779

36 Channel Jerrold JSX manual converters. Five for \$10.00. McCullough, Box 57 Salem, AR 72576. 870-895-2528.

CABLE TV DESCRAMBLERS. ALL MAJOR BRANDS. HAVE MAKE AND MODEL NUMBER OF CONVERTER USED IN YOUR AREA WHEN CALLING. QUANTITY DISCOUNTS. K.D. VIDEO, 1-800-327-3407.

Satellite Equipment

DSS Test Card authorizes all channels. For information plus free bonus, call toll free 1-888-416-7296.

SKYVISION Your Satellite Home Entertainment Source. **Best values:** DBS and C/Ku-band equipment, including 4DTV. Most complete selection: Parts-Tools-Upgrades-Accessories! **Free Discount Buyer's Guide.** Call 800-543-3025. International 218-739-5231. www.skyvision.com.

FREE DSS TEST CARD information package. Works on new system and turns on all channels including PPV, adult and sport channels. Write **SIGNAL SOLUTIONS**, 2711 Buford Rd., Suite 180, Richmond, VA 23235.

DSS Hacking: How to construct and program smart cards, w/pic 16C84, software. Complete DSS system schematics. \$16.95 **CABLETRONICS**, Box 30502R, Bethesda, MD 20824.

VIDEOCYEPHER II descrambling manual. Schematics, video and audio. Explains DES, EPROM, CloneMaster, Pay-per-view \$16.95, \$2 postage. Schematics for Videocypher II Plus, \$20. Schematics for Videocypher II 032, \$15. Software to copy and alter EPROM codes, \$25. VCII Plus EPROM, binary and source code, \$30. **CABLETRONICS**, Box 30502R, Bethesda, MD 20824

BEST BY MAIL

Rates: Write National, Box 5, Sarasota, FL 34230

EDUCATION

HIGH SCHOOL DIPLOMA Fast, Accredited, Member Christian Schools International. 1-800-470-4723.

FINANCIAL

CASH NOW FOR FUTURE PAYMENTS! We buy payments from Insurance Settlements, Annuities, and Class Action Awards. We also buy Owner Financed Mortgage Notes. Call R&P Capital at 1-800-338-5815, Ext. 500.

"LIVE LIKE A KING" Experience Financial Freedom! Quickly and Easily Become Debt Free! Enjoy The Benefits Of Wealth! Call 1-800-968-1732. www/realnetnw.com/innovative/index.htm

Business Opportunities

ELECTRONIC BUSINESSES, Home Based. Part/Full time. 250pg Comprehensive Guidebook, insider information. \$19.95 24hr. recording (800) 326-4560 x159.

ATT: CONSUMER ELECTRONICS TECHNICIANS Rent Way, Inc. America's leader in the rental/purchase industry is rapidly expanding nationwide and needs experienced audio/video repair technicians. Openings exist in IN, OH, NY, CO, MD, SC and several other eastern states. Our compensation package includes an attractive starting salary, 401K, company vehicle and a monthly bonus program. An ability to relocate is an advantage. For more information: Fax your resume to 814-836-5008 or E-mail us at Alevelson@rentway.com.

Business Opportunities

EASY WORK! EXCELLENT PAY! Assemble Products At Home. Call Toll Free 1-800-467-5566 EXT. 5192.

Education

LEARN ELECTRONICS. HOME STUDY. OUTSTANDING CAREERS. FREE LITERATURE P.C.D.I., ATLANTA, GEORGIA. CALL 800-362-7070. DEPT. ELE342.

PIC controller course, get up and running fast with **Beginners PIC** http://www.telusplanet.net/public/rhenders. **Data Burst Software**. Box 1193, Medicine Hat, AB T1A 7H3. 1-403-526-7676.

Test Equipment

TEST Equipment pre-owned now at affordable prices. Signal generators from \$50.00, oscilloscopes from \$50.00. Other equipment including manuals available. Send \$2.00 US for catalog. Refunded on first order. **J.B. Electronics**, 3446 Dempster, Skokie, IL 60076. (847) 982-1973.

TEST EQUIPMENT SALE! VIEW COMPLETE LIST AT WEB SITE "a-mall.com" or call **NOW** to receive list by fax or mail. **AST GLOBAL ELECTRONICS**: Voice: 888-216-7159; Fax: 814-398-1176; e-mail: astmrktg@wrench.toolcity.net.

Audio-Video-Lasers

LASERS Astonishing Low Prices. Free Catalog. T.E.P. PO Box 1353 Glendale, AZ 85311 Phone # 602-487-9897

Wanted

WANTED: USED TEST EQUIPMENT. TURN IDLE OR UNWANTED EQUIPMENT INTO CASH. **AST GLOBAL ELECTRONICS**: Voice: 888-216-7159; Fax: 814-398-1176; e-mail: astmrktg@wrench.toolcity.net

Scrambling News

Best satellite TV news includes coverage of piracy. Voice/Fax 716-283-6910. www.scramblingnews.com

9 out of 10 mice prefer the Consumer Information Catalog online. Catch it at **www.pueblo.gsa.gov.**

U.S. General Services Administration



ATTENTION DEALERS: WHOLESALE ONLY!



Formerly JES, Inc.

EXCLUSIVE:



NEW!

Wavemaster 99 Channel

• Sleep Timer • Std./HRC Switch • Parental Control

10+	20 +	50+
\$57	52	45




	5+	10+	20+
Panasonic 145	\$72	65	60
Refurb. Panasonic 145	57	55	52
Panasonic 100	52	49	--
Panasonic 175	---	CALL!	---
Starcomm DQN	49	45	39
(99 ch; Refurb.)			

TOLL FREE:
800-322-9690



FAX:
516-246-5634

ELECTRONIC COMPONENTS

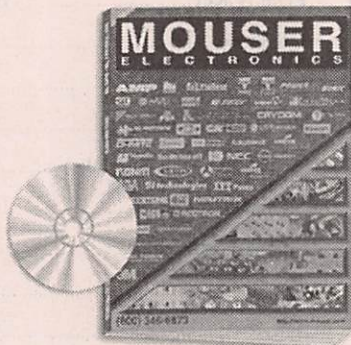

Visit our web site!
www.mouser.com

FREE catalog is available on the internet, CD-ROM, or in paper!

• 70,000+ Products • 145 Manufacturers
• Same Day Shipping • No Minimum Order

800-992-9943

817-483-6828 Fax: 817-483-0931
www.mouser.com catalog@mouser.com

958 North Main St., Mansfield, TX 76063

CIRCLE 331 ON FREE INFORMATION CARD

BEST DEALER PRICING!

CABLE DIRECT

CONVERTERS • FILTERS
DESCRAMBLERS

IMPROVE YOUR IMAGE WITH
VIDEO STABILIZERS

**FREE
CABLE TV
CATALOG!**

**100%
MONEY BACK
GUARANTEE!**



Now you can tune-in your favorite cable TV programming and **SAVE \$100'S** - **EVEN \$1000'S** on premium **CABLE TV EQUIPMENT.**



MODERN ELECTRONICS

1-800-906-6664

2609 S. 156TH CIRCLE • OMAHA, NE 68130
http://www.modernelectronics.com

ADVERTISING INDEX

Electronics Now does not assume any responsibility for errors that may appear in the index below.

Free Information Number	Page	Free Information Number	Page
— Abacom Technology	78	— James Electronics	105
— ABC Electronics	102	335 Link Instruments	86
— Adeplex Inc.	11	— Lynx Motion	102
— Aegis Research, Canada	79	— M ² L Electronics	100
— AES	89	329 Mark V Electronics	97
214 All Electronics	91	— MAT Electronics	27
— Allison Technology	76	330 MCM Electronics	83
— Amaze Electronics	82	— Meredith Instruments	87
315 American Eagle Publications	82	323 Merrimack Valley Systems	86
— Andromeda Research	89	133 MicroCode Engineering	CV2
282 Basic Electrical Supply	84	— microEngineering Labs	92
283 Bel-Merit	99	— Modern Electronics	105
326 Butterworth-Heinemann	80	331 Mouser Electronics	105
322 C&S Sales, Inc.	72-73	— NRI Schools	29
320 Capital Electronics	84	— Oelrich Publications	96
332 Circuit Specialists	77	— Orion	96
— CLAGGK, Inc.	CV3, 90	318 OWI	100
— Cleveland Inst. of Electronics	19	262 Parts Express Inc.	95
— Command Productions	82	— Pioneer Hill Software	88
226 Consumertronics	78	— Plug Power	90
311 CTG	94	— Polaris Industries	71
— Cylab	92	264 Print (Pace)	101
312 Dynamic Technology	103	— QB Video	90
— EDE - Spy Outlet	90	266 Ramsey Electronics	75
327 Electronix Express	94	— RC Distributing Co.	99
— Emac Inc.	76	333 Roger's Systems Specialist	98
336 Foley-Belsaw	85	— Sil Walker	100
328 Fotronic	92	— Square 1 Electronics	79
— General Device Instruments	88	— Tab Books	57
122 Global Specialties	5	— Tekview	99
— Grantham Col. of Engineering	4	324 Telulex	79
— Home Automation	89	— Test Equipment Sales	71
321 Howard Electronics	81	275 Timeline	74
— Howard Electronics	104	— U.S. Cyberlab	88
— Information Unlimited	93	— Visual Communications	4
126 Interactive Image Technologies	CV4	314 White Star Electronics	76
319 IVEX Design	87	— Wisch Communications	78
134 IWATSU America	25	— World College	39
— Jameco	3	— WPT Publications	102

ADVERTISING SALES OFFICES

Gernsback Publications, Inc.
500 Bi-County Blvd.
Farmingdale, NY 11735-3931
1-(516) 293-3000
Fax 1-(516) 293-3115

Larry Steckler
publisher (ext. 201)
e-mail advertising@gernsback.com

Adria Coren
vice-president (ext. 208)

Ken Coren
vice-president (ext. 267)

Christina Estrada
assistant to the publisher (ext. 209)

Arline Fishman
advertising director (ext. 206)

Marie Falcon
advertising assistant (ext. 211)

Adria Coren
credit manager (ext. 208)

For Advertising ONLY EAST/SOUTHEAST

Stanley Levitan
Eastern Advertising
1 Overlook Ave.
Great Neck, NY 11021-3750
1-516-487-9357
Fax 1-516-487-8402
slevitan26@aol.com

MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen
Midwest Advertising
One Northfield Plaza, Suite 300
Northfield, IL 60093-1214
1-847-559-0555
Fax 1-847-559-0562
bergenrj@aol.com

PACIFIC COAST

Janice Woods
Pacific Advertising
Hutch Looney & Associates, Inc.
6310 San Vicente Blvd., Suite 360
Los Angeles, CA 90048-5426
1-213-931-3444 (ext. 228)
Fax 1-213-931-7309
woodyowl@aol.com

Electronic Shopper

Joe Shere
National Representative
P.O. Box 169
Idyllwild, CA 92549-0169
1-909-659-9743
Fax 1-909-659-2469
Jshere@gernsback.com

Megan Mitchell
National Representative
9072 Lawton Pine Avenue
Las Vegas, NV 89129
Phone/Fax 702-838-6924
Lorri88@aol.com

Customer Service

1-800-999-7139
7:00 AM - 6:00 PM M-F MST

Reader Service Card

MAIL-FAX OR E-MAIL YOUR REQUEST

Now you have 3 ways to request free information on products and services featured in this issue

To insure a prompt reply, please furnish all requested information

To Receive
Information on
Products and
Services in
This Issue

Circle the numbers
corresponding to the
advertised products
or editorial items that
interest you.
Mail Card
or Fax To: (413) 637-4343
or E-Mail your request to:
BERKCOMP@AOL.COM.

For E-Mail users,
your subject is
Electronics Now 4/98
Format your message:

- Name and Address information
- Telephone and Fax numbers
- Requested item numbers separated by commas
- Responses to survey questions separated by dashes or slashes

NOTE: Submit all Free Information requests by **EITHER** Fax, mail, or E-Mail **DUPLICATE REQUESTS WILL BE DISCARDED.** Use for Free Information only. Address all editorial inquiries to Editor, Electronics Now, 500 Bi-County Blvd., Farmingdale, NY 11735-3931

BUSINESS PROFESSIONAL FREE INFORMATION CARD

**Electronics
NOW®**

4DAD9

Name _____ Title _____

Company _____

Dept. MS _____

Daytime Business Phone _____

Company Address _____

City _____ State _____ Zip +4 _____

Unclear or incomplete mailing info will prevent our processing this request.

2 ☐ Please send me 12 issues (1 year) of ELECTRONICS NOW for \$19.97 and bill me. (Canada \$27.79 — US Funds only — Includes G.S.T.)

4 ☐ Please send me 12 issues (1 year) of POPULAR ELECTRONICS for \$18.95 and bill me. (Canada \$25.63 — US Funds only — Includes G.S.T.)

Do you work in electronics to earn your Livelihood? 5 ☐ Yes 6 ☐ No

Please write in the name of the company you work for:

7 ☐ _____

Please write in your title at work: 8 ☐ _____

VOID after June 30, 1998

Allow 6-8 weeks for delivery of first issue

31	60	89	118	147	176	205	234	263	292	321	350
32	61	90	119	148	177	206	235	264	293	322	351
33	62	91	120	149	178	207	236	265	294	323	352
34	63	92	121	150	179	208	237	266	295	324	353
35	64	93	122	151	180	209	238	267	296	325	354
36	65	94	123	152	181	210	239	268	297	326	355
37	66	95	124	153	182	211	240	269	298	327	356
38	67	96	125	154	183	212	241	270	299	328	357
39	68	97	126	155	184	213	242	271	300	329	358
40	69	98	127	156	185	214	243	272	301	330	359
41	70	99	128	157	186	215	244	273	302	331	360
42	71	100	129	158	187	216	245	274	303	332	361
14	43	72	101	130	159	188	217	246	275	304	333
15	44	73	102	131	160	189	218	247	276	305	334
16	45	74	103	132	161	190	219	248	277	306	335
17	46	75	104	133	162	191	220	249	278	307	336
18	47	76	105	134	163	192	221	250	279	308	337
19	48	77	106	135	164	193	222	251	280	309	338
20	49	78	107	136	165	194	223	252	281	310	339
21	50	79	108	137	166	195	224	253	282	311	340
22	51	80	109	138	167	196	225	254	283	312	341
23	52	81	110	139	168	197	226	255	284	313	342
24	53	82	111	140	169	198	227	256	285	314	343
25	54	83	112	141	170	199	228	257	286	315	344
26	55	84	113	142	171	200	229	258	287	316	345
27	56	85	114	143	172	201	230	259	288	317	346
28	57	86	115	144	173	202	231	260	289	318	347
29	58	87	116	145	174	203	232	261	290	319	348
30	59	88	117	146	175	204	233	262	291	320	349

BUSINESS PROFESSIONAL FREE INFORMATION CARD

**Electronics
NOW®**

4DAD9

Name _____ Title _____

Company _____

Dept. MS _____

Daytime Business Phone _____

Company Address _____

City _____ State _____ Zip +4 _____

Unclear or incomplete mailing info will prevent our processing this request.

2 ☐ Please send me 12 issues (1 year) of ELECTRONICS NOW for \$19.97 and bill me. (Canada \$27.79 — US Funds only — Includes G.S.T.)

4 ☐ Please send me 12 issues (1 year) of POPULAR ELECTRONICS for \$18.95 and bill me. (Canada \$25.63 — US Funds only — Includes G.S.T.)

Do you work in electronics to earn your Livelihood? 5 ☐ Yes 6 ☐ No

Please write in the name of the company you work for:

7 ☐ _____

Please write in your title at work: 8 ☐ _____

VOID after June 30, 1998

Allow 6-8 weeks for delivery of first issue

31	60	89	118	147	176	205	234	263	292	321	350
32	61	90	119	148	177	206	235	264	293	322	351
33	62	91	120	149	178	207	236	265	294	323	352
34	63	92	121	150	179	208	237	266	295	324	353
35	64	93	122	151	180	209	238	267	296	325	354
36	65	94	123	152	181	210	239	268	297	326	355
37	66	95	124	153	182	211	240	269	298	327	356
38	67	96	125	154	183	212	241	270	299	328	357
39	68	97	126	155	184	213	242	271	300	329	358
40	69	98	127	156	185	214	243	272	301	330	359
41	70	99	128	157	186	215	244	273	302	331	360
42	71	100	129	158	187	216	245	274	303	332	361
14	43	72	101	130	159	188	217	246	275	304	333
15	44	73	102	131	160	189	218	247	276	305	334
16	45	74	103	132	161	190	219	248	277	306	335
17	46	75	104	133	162	191	220	249	278	307	336
18	47	76	105	134	163	192	221	250	279	308	337
19	48	77	106	135	164	193	222	251	280	309	338
20	49	78	107	136	165	194	223	252	281	310	339
21	50	79	108	137	166	195	224	253	282	311	340
22	51	80	109	138	167	196	225	254	283	312	341
23	52	81	110	139	168	197	226	255	284	313	342
24	53	82	111	140	169	198	227	256	285	314	343
25	54	83	112	141	170	199	228	257	286	315	344
26	55	84	113	142	171	200	229	258	287	316	345
27	56	85	114	143	172	201	230	259	288	317	346
28	57	86	115	144	173	202	231	260	289	318	347
29	58	87	116	145	174	203	232	261	290	319	348
30	59	88	117	146	175	204	233	262	291	320	349

**To Order a New Subscription or
To Renew an Existing Subscription
Call 1-800-999-7139**

.20¢ POSTAGE
REQUIRED IN
U.S.A.

**Electronics
NOW[®]**

READER SERVICE MANAGEMENT DEPT.
P.O. BOX 5192
PITTSFIELD, MA 01203-9989

.20¢ POSTAGE
REQUIRED IN
U.S.A.

**Electronics
NOW[®]**

READER SERVICE MANAGEMENT DEPT.
P.O. BOX 5192
PITTSFIELD, MA 01203-9989

The Electronics Industry is looking for a lot of good people!

Here is your chance to get in on the ground floor as an Associate CET. Is your job title "Electronics Service Technician?" Would you like to have that title? You can prove you qualify for the title with a CET Associate Certificate. It can be your career door-opener and begin your rapid advancement!

A technician or student of electronics with less than a total of four years of basic experience may take the Associate Level Exam. The exam is the basic electronics portion of the full-credit CET exam. The 75-question, multiple-choice test covers basic electronics, math, DC and AC circuits, transistors and semiconductors, instruments, measurements and troubleshooting. A successful Associate CET will receive a wall certificate valid for four years and is eligible to join ISCET as an Associate Member. ISCET is the International Society of Certified Electronics Technicians.

The ISCET Computer-Aided Associate-Level Study Guide prepares you for the Associate CET Certificate by randomly selecting sample questions with appropriate diagrams, provides multiple-choice answers, grades the test and provides a summary of your strong and weak points.

Diskette requires IBM computer or compatible with VGA color monitor, 3.5-in. drive and a hard-disk drive.

CLAGGK INC. - CET Computer-Aided Study Guide Offer
PO Box 4099, Farmingdale, New York 11735

YES, I want to step up to a career in servicing. Here is my order for the CET Computer-Aided Study Guide on a 3.5 diskette. I am enclosing \$39.95 (price includes shipping and handling charges) in U.S. funds.

Bill my ☐ VISA ☐ MasterCard Expire Date __/__/__
☐ USA Bank Check ☐ US or International Money Order

Card No. _____

Signature _____

Name (Please Print) _____


Address _____

City _____ State _____ Zip _____

New York residents add local sales taxes. Canadians add \$6.00 per order. No foreign orders. Do not send cash. Checks drawn on US Bank and International Money Orders in US funds only. Credit card users may telephone or FAX orders. Telephone 516-293-3751 or FAX 516-293-3115. Price subject to change. Allow 6 to 8 weeks for delivery.

CB06

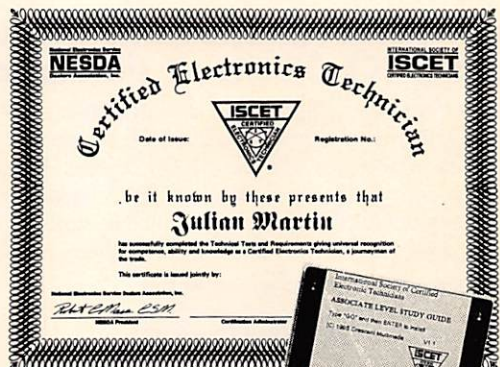Proof Positive that you are a Certified Electronics Technician



A New Computer Software Program — ISCET Computer-Aided Associate-Level Study Guide

Prepare yourself for the 75-question CET Associate Examination. Model examinations provide the technician with a study program and introduction to the actual examinations. The model examinations are automatically graded in decimal numbers and bar graphs that can be outputted on your printer. The questions for each exam are selected randomly from a loaded data base—no two exams are exactly the same. When you answer a question, the correct answer is displayed and an explanation is given. From the print-outs you will determine whether you need more practice and in which topic areas, or if you are ready to take the real test and continue to promote your electronics career today!

Better Designs - Faster


With the Personal Design Solution

The Design Solution Includes: Electronics Workbench Personal Edition + EWB Layout

**Electronics
Workbench®**
Personal Edition

Full-featured schematic capture and SPICE 3F circuit simulation!

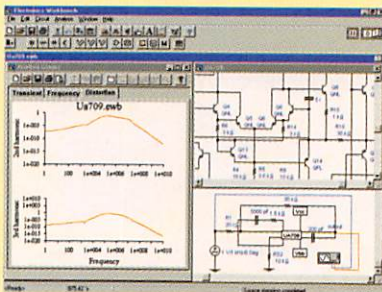The world's best selling circuit design software. With analog, digital and mixed A/D SPICE simulation, a full suite of analyses and over 4000 devices. Imports netlists. Seamlessly integrated with EWB Layout or exports to other popular PCB programs. Still the standard for power and ease of use. Still the same effective price.



\$299
Version 5

HIGH-END FEATURES


TRUE MIXED ANALOG/DIGITAL	YES
FULLY INTERACTIVE SIMULATION	YES
PRO SCHEMATIC EDITOR	YES
HIERARCHICAL CIRCUITS	YES
VIRTUAL INSTRUMENTS	YES
ON-SCREEN GRAPHS	YES
ANALOG AND DIGITAL MODELS	OVER 4,000
FREE TECHNICAL SUPPORT	YES
DC OPERATING POINT	YES
AC FREQUENCY	YES
TRANSIENT	YES
FOURIER	YES
NOISE	YES
DISTORTION	YES

**30-DAY MONEY-BACK
GUARANTEE**

**Electronics
Workbench®** **Layout**
Personal Edition

Power-packed PCB layout with autorouting and real-time DRC!

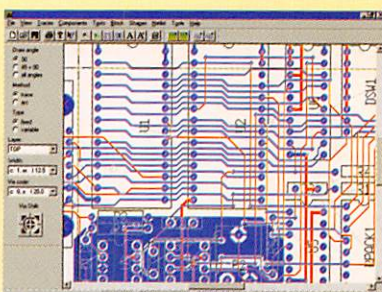EWB Layout is a powerful board layout package for producing high-quality, multi-layer printed circuit boards. Offering tight integration with our schematic capture program, you can incorporate board layout and design and quickly bring well-designed boards to production.



\$299
Version 5

POWER-PACKED FEATURES

AUTOROUTING	YES
REROUTE WHILE MOVE	YES
LAYERS	32 ROUTING LAYERS
BOARD SIZE	50" X 50"
LIBRARY SHAPES	OVER 3,500
BLIND AND BURIED VIAS	YES
EXTENSIVE OUTPUT	YES
SELECTIVE NET HIGHLIGHTING	YES
USER DEFINED PADS	YES
REAL TIME DESIGN RULE CHECK	YES
DENSITY HISTOGRAMS	YES
FREE TECHNICAL SUPPORT	YES

*Join over 85,000 customers
and find out why more circuit designers
buy Electronics Workbench than
any other circuit design tool.*

**CALL FOR INFORMATION
AND PRICING ON OUR
PROFESSIONAL EDITION.**

ELECTRONICS WORKBENCH Personal Edition \$299.00
EWB LAYOUT Personal Edition \$299.00

**BUY
BOTH
AND
SAVE**

PERSONAL DESIGN SOLUTION ~~\$598.00~~
\$548.00

CALL 800-263-5552

**For a free demo, visit our website
at <http://www.interactiv.com>**

INTERACTIVE IMAGE TECHNOLOGIES LTD., 908 Niagara Falls Boulevard,
#068, North Tonawanda, New York 14120-2060 / Telephone 416-977-5550.
TRADEMARKS ARE PROPERTY OF THEIR RESPECTIVE HOLDERS. OFFER IS IN U.S. DOLLARS AND VALID ONLY
IN THE UNITED STATES AND CANADA. ALL ORDERS SUBJECT TO \$15 SHIPPING AND HANDLING CHARGE.
Fax: 416-977-1818 E-mail: ewb@interactiv.com
CompuServe: 71333,3435 / BBS: 416-977-3540

